Wireless World

MARCH 1952 · TWO SHILLINGS

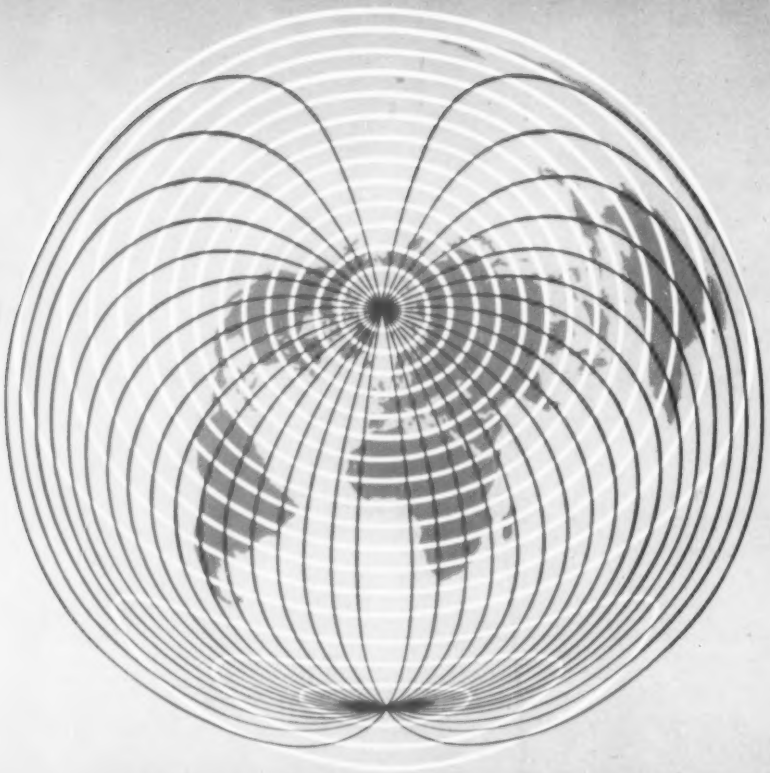

RADIO, TELEVISION AND ELECTRONICS

ERIE *Silertex*

REGD. TRADE MARK

Wirewound Resistors

SILERTEX wirewound resistors are used by all the leading manufacturers because:

* They resist moisture at extremes of temperature.
* They withstand greater overloads.
* They have high operating temperature range over high ambients.
* They are fire resistant.
* Wire connections are welded to the resistance wire.
* Low firing temperature in manufacture avoids damage to resistance winding.

Erie Silicone bonded SILERTEX wirewound resistors are made for temperatures of 200° C.

When you need power resistors which have proved their ability to stand up in these conditions at all times,

Specify SILERTEX

ERIE RESISTOR LIMITED

CARLISLE ROAD, THE HYDE, LONDON, N.W.9, ENGLAND. Telephone: COLindale 8011. Cables: Resistor, London

Factories: LONDON & GREAT YARMOUTH, ENGLAND; TORONTO, CANADA; ERIE, PA., U.S.A.

ALL-ROUND
DEPENDABILITY
AVO VALVE CHARACTERISTIC METER
AVO ELECTRONIC TESTMETER
AVO UNIVERSAL BRIDGE
AVO ELECTRONIC TEST UNIT
THE D.C. AVO MINOR
AVO WIDE RANGE SIGNAL GENERATOR
AVO
Precision ELECTRICAL
MEASURING INSTRUMENTS
Dependability is an essential quality in any good electrical testing instrument. Absolute dependability is the outcome of good design, suitability for purpose, and a high standard of accuracy. These indispensable factors are exemplified in all "Avo" Instruments, which are also noteworthy for their compact portability and robust construction.
You can depend on "Avo". When choosing instruments, consult our complete catalogue, a copy of which may be had free on application.
HEAVY DUTY AVO METER
UNIVERSAL AVO MINOR
UNIVERSAL AVO METER
THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.
WINDER HOUSE DOUGLAS STREET LONDON S.W.1
Telephone: VICtoria 3404—9

G 5

NEW WINDSOR TESTGEAR

MODEL 66A

SIGNAL GENERATOR
LIST PRICE £22·10

A newly designed A.C. mains operated R.F. Signal Generator of improved performance and reliability. Wide range and accuracy make it an ideal instrument for modern Radio and Television work.

★ **RANGES**

100-320 Kc/s.	3.2-10 Mc/s.
320-1000 Kc/s.	10-30 Mc/s.
1000-3200 Kc/s.	30-80 Mc/s.

★ **ACCURACY**
Frequency calibration accuracy is within ± 1 per cent.

★ **SCREENING**
All unwanted R.F. leakage is eliminated by scientifically designed double screening.

★ **MODULATION**
Internal modulation, of good waveform, is provided at 400 c.p.s. modulating to a depth of approx. 30 per cent.

★ **OUTPUT**
Modulated or unmodulated R.F. output up to 100 millivolts. Terminating unit provides two output levels and incorporates an artificial aerial.

VALVE TESTER
LIST PRICE £24

MODEL 45B

A comprehensive mutual conductance valve tester, suitable for most types of British, American and Continental receiving valves. Supplied with valve chart giving data for testing nearly 3,000 different valves. For use on A.C. mains only.

TESTING FACILITIES

★ **MUTUAL CONDUCTANCE.** Two ranges: 0-3 mA/V and 0-15 mA/V.

★ **CATHODE LEAKAGE.** Tests for Heater-Cathode insulation up to 10 megohms with heater at operating temperature.

★ **EMISSION.** Rectifiers and Diodes may be tested for emission.

★ **ELEMENT SHORTS.** Short circuit between electrodes are clearly indicated.

★ **GAS TEST.** Press-button test shows abnormal positive or negative grid currents

Please write for further details and information on other WINDSOR and TAYLOR products

TAYLOR ELECTRICAL INSTRUMENTS LTD

419-424 MONTROSE AVENUE, SLOUGH, BUCKS. Phone: SLOUGH 21381

Cathode Ray Tubes for Television Studio Applications

The Mullard cathode ray tubes, MW22-22 and MW13-35, have been specially designed to give high-grade pictures under the brilliant lighting conditions encountered in television studio work. They are both characterised by their exceptionally high definition and high brilliance. Halation has been reduced to an absolute minimum.

The MW22-22, which is a metallized tube with a nine-inch, white screen, is now being used extensively in television studio monitoring.

The MW13-35, being a compact tube, is finding wide application in television-camera viewfinding equipments. This tube is also metallized and has a white, flat-faced screen, five inches in diameter.

In addition to these two tubes, Mullard also have available a large selection of cathode ray tubes for use in television transmission quality monitoring systems, navigational radar equipments, and measuring and testing instruments. Full details of any of these tubes will be supplied on request.

DESCRIPTION	MW13-35	MW22-22
HEATER V_h	6.3 V	6.3 V
I_h	0.3 A	0.3 A
LIMITING VALUES	absolute ratings	design centre ratings
V_{a2} max.	11 KV	11 KV
V_{a2} min.	5.5 KV	7 KV
V_{a1} max.	450 V	400 V
V_{a1} min.	200 V	200 V
$-V_g$ max.	200 V	150 V
DIMENSIONS		
Max. bulb diameter	127.5 mm	230 mm
Max. overall length	289 mm	377 mm
Useful screen diameter	108 mm	214 mm
BASE	Octal	B12A

Mullard

MULLARD LTD., CENTURY HOUSE, COMMUNICATIONS AND INDUSTRIAL VALVE DEPT., SHAFTESBURY AVENUE, W.C.2

MVT 112

The Cone takes shape

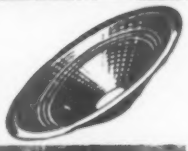

Testing at every stage. *Infinite care is taken at Goodmans to ensure and maintain the uniformly high quality of speaker cones. "Felts" are tested visually for texture as they come from the drying oven before being weighed on a delicate balance.*

Second of a series telling the story of Goodmans Loudspeakers.

It is in the processing tank that the cone first assumes a recognisable shape. Here the pulp, whose manufacture we described in the first of this series, is held in suspension in water : a suspension whose concentration is strictly controlled to ensure absolute uniformity of weight and texture of the finished cones.

The suspension is drawn through a cone-shaped gauze filter by vacuum action, and there emerges a damp, fibrous, but recognisably cone-shaped "felt". The young lady in the foreground is seen removing a "felt" as the vacuum filter head rises from the processing tank.

From the processing tank the "felts" pass through an oven where advanced techniques of infra-red drying are applied before passing to the press room for the final shaping, finishing, and testing which will be described in the next of this series. Distinct from the "Open Felting" method described above is the "Transfer" process, by which diaphragms possessing special characteristics are made to customers' specified acoustic requirements.

above: Producing a cone by the "Transfer" process.

AUDIOM 60

12" 15w. P.M. Loudspeaker

Limited supplies now available. Ask your Dealer, or write to us.

GOODMANS

GOODMANS INDUSTRIES LTD. Axiom Works, Wembley, Middx. WEM. 1200

Goodmans Industries Ltd

have pleasure in introducing
the latest in the now famous series of
AXIOM High Fidelity Loudspeakers—

The

AXIOM 150 Mark II

12-inch 15w. P.M. Loudspeaker

This high fidelity reproducer gives extremely smooth response in the middle and upper registers, ensuring minimum "scratch" from recordings. On all inputs this shows to advantage no matter what the origin.

The very low bass resonance ensures faithful reproduction down to the lowest audible frequency.

This new AXIOM is a marked advance on past models and is suitable for use with all high quality amplifiers, but is too critical for ordinary commercial receivers.

A special corner reflex cabinet has been designed with speaker aperture at optimum listening height.

SPECIFICATION

Frequency Coverage	30-15,000 c.p.s.
Overall Diameter	12.5/16" (31.3 cms)
Overall Depth	6.15/16 (17.6 cms)
Fundamental Resonance	35 c.p.s.
Voice Coil Diameter	1¾" (4.4 cms)
Voice Coil Impedance	15 ohms at 400 c.p.s.
Max. Power Capacity	15 watts peak A.C.
Flux Density	14,000 gauss

You are invited to write for details of the Axiom 150 Mk. II and the specially designed corner reflex cabinet.

GOODMANS

The Axiom 150 Mk. II will be on show at Stand 35 at the R.E.C.M.F. Exhibition, April 7-9, and will be demonstrated in a specially designed soundproof room at Stand 47 at the Northern Radio Show, April 23-May 3.

GOODMANS INDUSTRIES LIMITED, Axiom Works, Wembley, Middx. WEMbley 1200

HIRE PURCHASE SPECIALISTS

TRADE & EXPORT ORDERS ACCEPTED

RADIO & TELEVISION
ELECTRICAL APPLIANCES
ELECTRIC TOOLS
KITS

RADIO CENTRE

TEST EQUIPMENT
HI-FI REPRODUCTION
TAPE RECORDERS
AMPLIFIERS

Sole distributors for **BURGOYNE** Magnetic Recording Heads, Tape Tables, Aerial Co-axial Connectors, Instant Heat Solder Guns, etc.

Presenting the "BURGOYNE" Tape Table

£16.10 CASH, or £6.10 DEPOSIT and 12 monthly payments of £1 (10/- carr. and pkg.)

★ Precision built. ★ 3 motors with ample reserve of power. ★ Fast forward facilities to allow rapid selection of any desired portion of tape. ★ Fast re-wind facilities. ★ Tape speed 7½in. per second. ★ Heavy balanced flywheel. ★ High Fidelity Record Playback head and separate Erase Head. ★ Half track width high impedance heads. ★ Negligible "wow" and "flutter." ★ Take up spool supplied. ★ Circuit diagram included. ★ For use on A.C. mains.

The lowest priced quality tape table on the market for immediate delivery.

We are accepting orders for early delivery of the

BURGOYNE De Luxe TAPE TABLE

£25 CASH, or £9 DEPOSIT and 12 monthly payments of 30/- (10/- carr. and pkg.)

TAPE RECORDER KITS.

Complete Kit comprising Burgoyne Tape Table, Lane Oscillator Unit and MOS A4 R.P Amplifier Kit for £25.19.6 cash, or £6.19.6 deposit and 12 monthly payments of 35/-.

Complete Kit comprising Burgoyne De Luxe Tape Table, Lane Oscillator Unit and MOS A4 Record Playback Amplifier Kit (as previously advertised) for £34.10.0 cash, or £10.10.0 deposit and 12 monthly payments of 45/-.

LANE OSCILLATOR UNIT

Complete with valve 70/-

Output Variable 10/- deposit and 12 monthly payments of 8/4.

Completely enclosed except valve.

The Lane Oscillator Coil with Circuit diagram 10/-

BURGOYNE MAGNETIC RECORDING HEADS

For Superior Performance at Lower Cost—Record Playback and Erase Heads giving first-class frequency response. ★ **High Impedance.** ★ **Positive Fixing Method.** ★ **Half Track Width.** ★ **Totally enclosed with Tape Guide** ★ **Wide Frequency Range.** Record Playback or Erase **39/6** EACH, OR Set of 2 for 23/- deposit and 12 monthly payments of 8/-. OR Set of 3 for 38/6 deposit and 12 monthly payments of 10/-.

DISTRIBUTED EXCLUSIVELY BY M.O.S.

TEST TAPES.

Filling a long-felt want, we offer 600ft. reels of EMI Tape (high or low coercivity) which have been recorded with a series of steady tones and gliding tones from a sine wave audio frequency source. These tapes are ideal for testing and setting up amateur constructed tape mechanisms or playback amplifiers. When the tones are no longer required they may be erased in the normal manner.

Speed, 7½in. sec. Track, ¼ width. Direction, L. to R. **30/-** per test tape.

STANDARD MAGNETIC RECORDING TAPES.

EMITAPE (high or low coercivity)	600ft.	£1 1 0
	1,200ft.	£1 15 0
SCOTCH BOY	1,200ft.	£1 15 0
PHILIPS (homogeneous)	1,200ft.	£2 0 0
WEARITE Grade P	1,200ft.	£2 5 0

1,200ft. Spools, 4/6 each.

THE "CONNOISSEUR" DUAL SPEED MOTOR UNIT.

We are always able to deliver these short supply high quality equipments from stock.

CASH PRICE £22/18/8.
OR £7 18/8 Deposit and 12 monthly payments of 28/4.

for 33⅓ and 78 r.p.m. Non-Ferrous turntable.

THREE HEADS ARE BETTER THAN ONE.

With the well-known "Connoisseur" slogan we remind you we can supply the super lightweight Pickup and accessories on easy Hire Purchase terms.

For standard and microgroove recordings.

	Cash Price	Deposit	12 mthly pmts.
Super lightweight Pickup with one head	8 9 0	1 9 0	11 8
Head only	3 11 8	11 8	8 4
Matching transformer	15 0		
Spare armature and sapphire	14 8		
Pickup with 2 heads	10 0 8	2 0 8	16 8
Pickup with 3 heads and matching transformer	10 15 8	2 15 8	16 8
Dual speed motor unit, pickup, 3 heads and matching transformer	33 14 0	10 14 4	2 2 2

PLESSEY MULTI SPEED AUTO CHANGERS.

Cash price £33.13.0, or £7 deposit and 12 monthly payments of 31/6.

With every unit purchased for CASH we present a handsome walnut veneered playing desk (already mounted). An extensive offer by M.O.S. for a limited period.

Magnetic Recording Accessories for Cash or on easy Hire Purchase terms.

HEADPHONES for MONITOR WORK.

	Cash Price	H.P. Deposit	12 monthly payments
S. G. Brown	£ s. d.	£ s. d.	s. d.
Type A. Adjustable reed movement	3 17 6	0 17 6	8 4
Type F. Featherweight general purpose	1 10 0		
Type K. Moving coil for high fidelity	5 5 0	1 5 0	10 0

MICROPHONES.

BERLO. Ribbon type RUA with built-in transformer to 30 ohms	7	10	0	2 10 0	11	8
ACOS. MIC/22/3 on table stand. Crystal filter cell	6	6	0	1 16 0	10	10
ACOS. MIC 16/2 on table stand. Crystal sound cell	12	12	0	4 12 0	16	8
LUSTRAPHONE. Moving Coil C51 2 High Impedance	5	12	6	2 2 6	9	2
LUSTRAPHONE. Moving Coil, low impedance	5	0	0	2 0 0	8	4
LUSTRAPHONE Table Base	1	1	0	each.		
GRAMPIAN Moving Coil	5	17	6	2 0 0	9	10
Tannoy Record Playback, Playback or Erase Heads	2	19	6	each		
Quaitape Tape Table. Full track width. Two motors, fast rewind, single head, D.C. erase	13	13	0	3 13 0	20	0
M.O.S. A4 Magnetic Recording R.P. Amplifier	6	19	6	2 0 0	11	8

ALL B.S.R. GRAMOPHONE MOTORS

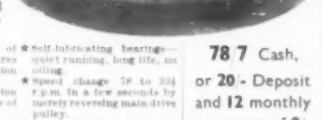

are first class, but we particularly recommend the **Dual Speed Motor Unit Type MU.10.**

★ De Luxe 4-pole motor of advanced design assures low rumble and vibration factor. ★ Self-lubricating bearings—quiet running, long life, no oiling. ★ No stray field radiation noticeable with any type of pickup. ★ Speed change 78 to 33⅓ r.p.m. in a few seconds by merely reversing main drive pulley. ★ Uniform turntable speed under widely varying record loads. ★ 10in. dia. heavy pressed steel turntable fitting on precision ground taper steel spindle. ★ Absolute minimum. Instantaneous speed variation (wow). ★ Ideal for use with any type of magnetic or crystal pickup.

78/7 Cash, or **20/-** Deposit and **12** monthly payments of **8/-**

complete with mounting plate ready for installation.

***also*: THE B.S.R. 3-SPEED GRAMOPHONE UNIT. Type GU4 with high fidelity lightweight Crystal Head.**

★ 33⅓–45–78 r.p.m. speeds by switching. ★ 4-pole induction motor. ★ Transcription quality. ★ Automatic stop. ★ 10in. heavy pressed steel turntable fitted with removable rubber mat.

£9.19.11 Cash, or DEPOSIT **£2.10.0** and **12** monthly payments of **16/-**.

All other BSR products previously advertised by the manufacturers and ourselves available for immediate delivery.

Introducing the BSR series of lightweight pickups we detail below the 3 types available from stock.

These pickups, like all BSR products, are of first-class construction, and may be relied on to give a long and useful life.

PU1	High fidelity lightweight crystal pickup, for use on 78 r.p.m. recordings.	All £3.18.7 each, or £1.1.0 deposit and 12 monthly payments of 8/-.
PU2	High fidelity lightweight crystal pickup, for use on Microgroove recordings.	
PU3	Lightweight crystal pickup, with specially designed stylus for playing both 78 r.p.m. and Microgroove recordings.	

M·O·S

MAIL ORDER SUPPLY. *The RADIO CENTRE*
Dept. WW, 33, TOTTENHAM COURT ROAD, LONDON, W.1.

MUSeum 6667

TERMS OF BUSINESS
Cash with Order or C.O.D (if goods suitable for post)
Please add sufficient to cover carriage and packing

RADIO & TELEVISION
ELECTRICAL APPLIANCES
ELECTRIC TOOLS
KITS

RADIO CENTRE

TEST EQUIPMENT
HI-FI REPRODUCTION
TAPE RECORDERS
AMPLIFIERS

HIRE PURCHASE
All H.P. facilities granted are financed solely by M.O.S. Finance Co. Terms quoted in these pages are subject to amendment to comply with the new H.P. and Credit Sale Regulations

Acclaimed by one and all – The M.O.S

QUALITY GRAND AMPLIFIER

Because of its excellent performance and thorough reliability this Amplifier is in greater demand than any other on the market. It has been designed for the connoisseur at a price within the reach of all.

★WIDE RANGE: CONTINUOUSLY VARIABLE TREBLE AND BASS CONTROLS WHICH GIVE BOTH BOOST AND CUT ABOUT A MEAN REFERENCE LEVEL AT 1,000 C.S.
★HEAVY NEG. FEEDBACK USED OVER THE STAGES AFTER THE EQUALISER CIRCUITS, ENSURING THAT ACTION OF THE TONE CONTROL IS UNIMPAIRED BY FOLLOWING AMPLIFIER STAGES.
★NO HARMONIC DISTORTION ★7 VALVES.
★TWO INPUTS ★FOR USE ON A.C. MAINS.

We specialise in issuing an instruction manual in such a form that construction of the kit is simple and straightforward. Profuse illustrations and diagrams of point to point wiring are provided and the constructor just cannot go wrong! We reproduce diagram of a stage of the wiring taken from the manual.

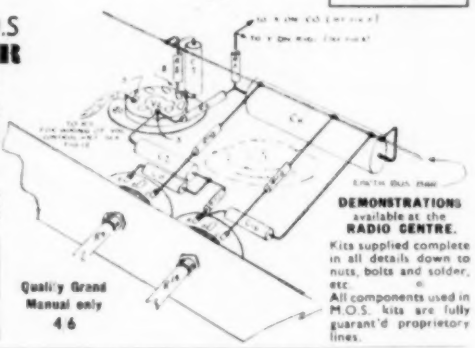

Type A Kit 6V6 6V6 Output
£9 19 6 cash, or £3 deposit and 12 monthly payments of 15/-.
Fully assembled and wired ready to use, £12 10 0 cash, or £4 deposit and 12 monthly payments of 17 6.

Type B Kit 6L6 6L6 Output
£11 5 0 cash, or £3 16 0 deposit and 12 monthly payments of 16 8.
Fully assembled and wired ready to use, £13 15 0 cash, or £4 10 0 deposit and 12 monthly payments of 18 9.

Quality Grand Manual only 4/6

DEMONSTRATIONS available at the **RADIO CENTRE.**
Kits supplied complete in all details down to nuts, bolts and solder, etc.
All components used in M.O.S. kits are fully guarant'd proprietory lines.

M.O.S. RFI RADIO FEEDER UNIT

This tuning unit uses a straight TRF circuit, tuning the Medium Wave Band only. **It provided with its own power unit,** it can be used with any amplifier. The unit is exceptionally sensitive; can be used in areas of only moderate signal strength.

By use of a TRF circuit the bandpass is such that the output fed into an amplifier is of very high fidelity, and full advantage can be taken of the transmitted quality.

The unit is provided with only two controls—Tuning and Sensitivity—and consequently is very simple to operate. No tuning scale is provided as it is thought that the great majority of constructors will prefer to fit the unit into a cabinet and so be able to choose an assembly to suit the housing. Adequate spindle length is provided in all cases.

In line with others in the "Easy-to-Build" series, kit is complete in every detail, and instruction manual fully detailed and illustrated.

Complete Kit with Valves £2 12 6
Instruction Manual only 2 0
Ready assembled and wired £3 10 0

LOUDSPEAKER SEPARATORS by WHARFEDALE

An effective device for dividing the bass and treble between two loudspeakers at low impedance, thus eliminating modulation distortion between treble and bass and permitting the most suitable mounting and placing of each speaker. The two loudspeakers should be fitted with magnets of similar flux density. The treble unit may be the same size as, or smaller than, the bass unit.
These cross-over networks are now available in eight types as follows:—

	Cross Over	Impedance	Price £ s. d.
Type A	1,000 c/s	7 to 16 ohms	3 9 6
Type B	1,000 c/s	2 to 16 ohms	3 19 6
Type C	1,000 c/s	2 to 6 ohms	4 9 6
Type D	1,000 c/s	2 to 6 ohms	3 19 6
Type E	3,000 c/s	7 to 16 ohms	2 15 0
Type F	3,000 c/s	7 to 16 ohms	3 5 0
Type G	3,000 c/s	2 to 6 ohms	3 10 0
Type H	3,000 c/s	2 to 6 ohms	3 0 0

Maximum Input 30 watts. H.P. TERMS AVAILABLE

AMPLION ALL-PURPOSE TEST METER

★ HIGHEST QUALITY MOVING COIL METER MOVEMENT.
★ SELF-CONTAINED INTERNAL BATTERY
★ 10 RANGES.

Who would have thought that all these features—and more—could be made available in a high-grade all-purpose multi-range Test Instrument for so small a cost! The outstanding sensitivity of this precision moving coil instrument makes it ideal for all who require a universal test meter for professional or amateur use.

SENSITIVITY. 1,000 ohm per volt on all D.C. and A.C. ranges.
RANGES. 10 v. 100 v. and 500 volts D.C. and A.C.
* 50 mA. and 500 mA. D.C.
* Resistance up to 200,000 ohms (3,000 ohm centre with self-contained battery.
* 5,000 volts range with a separate H.T. test prod (9 6 extra).
* Supplied with test prods.

£5 CASH or 20/- deposit and 12 monthly payments of 10/-. High-grade Leather Case if required, 15/- extra.

LOUDSPEAKERS by GOODMANS

High Fidelity, P.M. Loudspeakers.

The Axiom 150

15 watt 12in. Unit with twin Curvilinear diaphragm.

£10.5.6 CASH. or 45 6 deposit and 12 monthly payments of 16 8.

Frequency Coverage	40/15,000 c.p.s.
Overall Diameter	12⅞in.
Overall Depth	6⅜in.
Fundamental Resonance	55 c.p.s.
Voice Coil Diameter	1¼in.
Voice Coil Impedance	15 ohms at 400 c.p.s.
Max. Power Capacity	15 watts peak A.C.
Flux Density	14,000 gauss.
Nett weight	12 lb. 12 ozs.

The Audiom 60

15 watt 12in. Unit with single cone.

£8.12.6 CASH or 52 6 deposit and 12 monthly payments of 13 4.

Overall Diameter	12⅞in.
Overall Depth	6⅜in.
Voice Coil Diameter	1¼in.
Fundamental Resonance	75 c.p.s.
Voice Coil Impedance	15 ohms
Power Rating	15 watts peak A.C.
Flux Density	14,000 gauss.
Total Flux	158,000 maxwells
Nett weight	12 lbs. 13ozs.

AMPLION ACTIVETTE MODEL R.B.

Amplion has marketed one of the most important developments in the field of dry batteries. A mains unit has been specially designed to increase their life. It is only too well known that the useful life of a dry battery is limited, dependent upon the consumption and, to a great extent, on the number of successive hours of use.
With the aid of the Amplion Activette the users of dry batteries will be able to extend the usual life of a dry battery by three to six times, consumption of the Amplion Activette being approximately 3 watts. Input 200 250v. A.C. Suitable for all radio dry batteries with H.T. from 45 to 90v. and L.T. 1.4v. Fitted with three tappings to suit different H.T. batteries of 45, 67 and 69, and 90 v. Output socket a standard 4-pin (miniature). Size 4¼in. × 2¼in. × 1¼in. Weight approx. 1 lb.
£3.5.0

BURGOYNE SOLDER GUN

We regret to announce that we are now coming to the end of our stocks of these handy soldering tools. It is anticipated that we shall clear our entire stock within two months and no more will be available. The demand will be heavy, so order now!

PRICE: **79 6**, Spare bits **10** for **7/6.**
Fully guaranteed for **TWO YEARS.**

We have been appointed leading Agents for
HARTLEY-TURNER high fidelity reproduction
DELIVERY OF 215 SPEAKERS AND PRE-AMPLIFIERS FROM STOCK

M·O·S

MAIL ORDER SUPPLY. *The RADIO CENTRE*
Dept. WW, 33, TOTTENHAM COURT ROAD, LONDON, W.1.

MUSeum 6667

G.E.C.

Germanium Diodes

The photograph shows a G.E.C. germanium diode soldered between adjacent tags of an octal socket in a noise-suppression circuit. Standard half-watt and quarter-watt resistors provide an interesting comparison in size.

It is important to note that this photograph is of a G.E.C. production television sub-chassis into which the crystal is soldered without heat shunts and with the leads clipped to the required lengths.

For further information apply to Osram Valve & Electronics Dept.

THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, LONDON, W.C.

DUBILIER

MICA DIELECTRIC CAPACITORS

Eminently suitable for H.F. Transmitting and R.F. Heating Circuits.

Makers of the first and of the largest Mica Capacitors in the World, Dubilier have maintained the lead in this important branch of Capacitor Engineering.

The example shown is a high grade, oil immersed, naturally cooled mica capacitor, designed to ensure the maximum surface cooling area for the bulk, thereby occupying the minimum of floor space.

Made especially for use in the oscillatory and radio-frequency circuits of Radio-Transmitters and Radio-Frequency Heating equipment, these capacitors are available in two sizes suitable for a frequency band covering 100 to 1,600 kilo-cycles per second and with the following ratings :—

Peak Working kV	24.0	24.0
Maximum Current	70 Amps	70 Amps
Maximum kVA	350	500
Overall Height	21¼"	31¼"
Base Space	11¼" x 9¼"	11¼" x 9¼"

Full details of these and other outstanding Capacitors are available upon application.

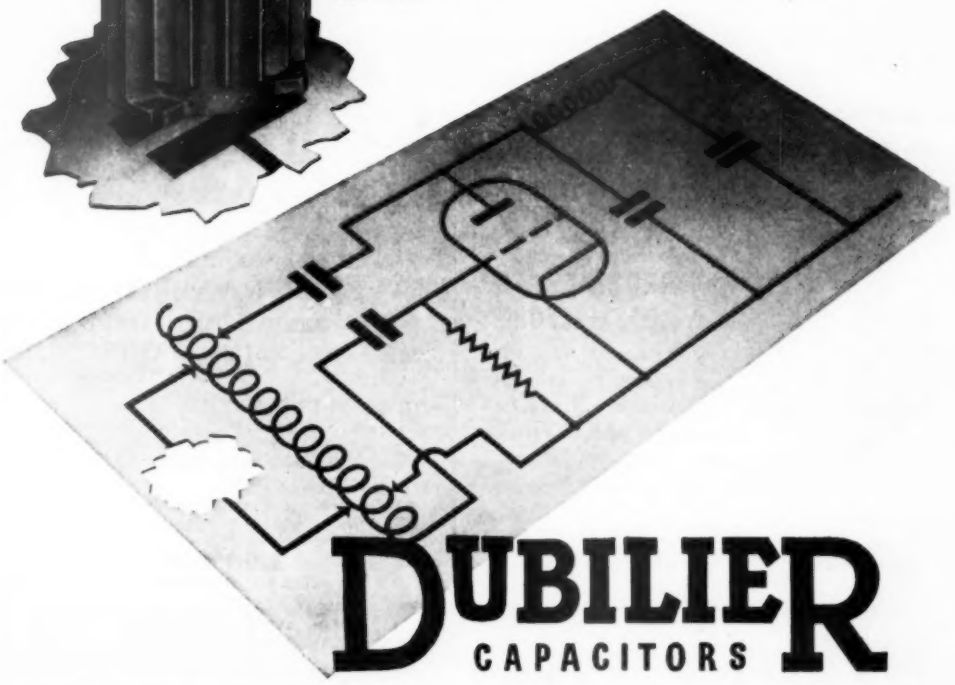

DUBILIER CAPACITORS

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA RD., N. ACTON, LONDON, W.3.
Phone: Acorn 2241 (5 lines). Grams: Hivoltcon, Wesphone, London. Cables: Hivoltcon, London, Marconi International Code

D48

VALVES!! TUBES!!

RECEIVING. TRANSMITTING. MAGNETRONS. KLYSTRONS.

CATHODE-RAY TUBES. PHOTOCELLS. ETC.

First Grade Quality - British and American Make - No Dollar Expenditure Involved

LARGE QUANTITIES & GREAT VARIETIES
IMMEDIATE DELIVERIES FROM STOCK

Write or Phone:-

S. Szymanski

(pronounced SHE-MAN-SKEE)

ELECTRONIC
ENGINEER & STOCKIST

95, STRODES CRESCENT, STAINES, MIDDLESEX

Telephone: STAINES 3971 *Telegrams: "Shemanskee" Staines*

PROBABLY THE LARGEST ACTUAL STOCKIST IN ENGLAND

WHOLESALE & EXPORT ONLY

LONG-RANGE PROJECTION T.V.

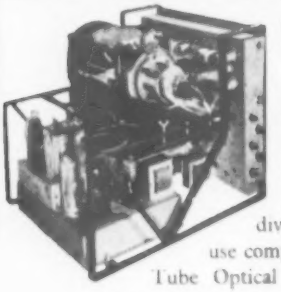

We are pleased to offer AN OUTSTANDING **RECEIVER-IN CHASSIS FORM**

Designed for the Enthusiast and Individualist. Ready for use complete with all Valves, Tube Optical Unit, Speaker, etc. Fully tested and Guaranteed.

FEATURES INCLUDE:

23 valve S.H circuit. Under 50 micro-volt input sensitivity. 18" Picture, for cabinet use, or 4' x 3' wall-projected. 5 Channel reception. Completely A.C. operated.

For full particulars apply to sole manufacturers:

TELEMECHANICS Ltd

3 NEWMAN YARD NEWMAN STREET,
LONDON, W.1. Tel.: LANGHAM 7965

A.I.D. APPROVED **"WEYRAD"** A.I.D. APPROVED

COILS
COIL PACKS
I.F. TRANSFORMERS

TELEVISION COMPONENTS
MAINS TRANSFORMERS
CRYSTAL RECEIVERS

FOR MANUFACTURERS

Capacity is available for the development and production of all types of components and sub-assemblies. FOR DEFENCE OR EXPORT.

FOR CONSTRUCTORS

We produce a wide range of standard items which can be employed in your receivers whether they be crystal or communications.

FOR SERVICE ENGINEERS

Our components will solve many of your repair and replacement problems.

ILLUSTRATED CATALOGUE . . . 6d.

WEYMOUTH RADIO MFG. CO., LTD., CRESCENT STREET, WEYMOUTH.

Efficient contact between high-speed aircraft depends on instantaneous radio communication. Aircraft radio equipment is used under arduous conditions both in peace and war and must be available instantly throughout the 24 hours of a day.

It is not surprising, therefore, that more and more G.E.C. Quartz Crystal Units are being used, for this is the most critical component and only the best is safe and good enough. *Write for list QC 5012 (R)*

SEE OUR RANGE OF INSTRUMENTS & COMPONENTS ON STAND No. 47, R.E.C.M.F. EXHIBITION, GROSVENOR HOUSE, LONDON, 7th, 8th, 9th APRIL

SALFORD ELECTRICAL INSTRUMENTS LTD · SALFORD 3 · LANCS

A SUBSIDIARY OF THE GENERAL ELECTRIC CO LTD OF ENGLAND

MAINS TRANSFORMERS

FULLY INTERLEAVED
SCREENED AND IMPREGNATED. ALL GUARANTEED.
ALL PRIMARIES ARE 200 250 v. Half Shrouded.

HSM63. (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. 18/-
HS63. Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. 18 6
HS40. Windings as above. 4 v. at 4 amps., 4 v. at 2 amps. Output 18 6
MS2. 250-0-250 v. 80 m/a. 21/-
MS3. 350-0-350 v. 80 m/a. **GS30.** 300-0-300 v. 80 m/a. 21/-
MS2X. 250-0-250 v. 100 m/a. **MS75.** 275-0-275 v. 100 m/a. 23/-
MS30X. 300-0-300 v. 100 m/a. **MS3X.** 350-0-350 v. 100 m/a. 23/-

Fully Shrouded

PSM63. (Midget). Output 250-0-250 v. 60 m/a., 6.3 v. at 3 amps., 5 v. at 2 amps. Output 18 6
PS2. 250-0-250 v. 80 m/a. 23/-
PS30. 300-0-300 v. 80 m/a. **PS3.** 350-0-350 v. 80 m/a. 23/-
PS2X. 250-0-250 v. 100 m/a. **PS75.** 275-0-275 v. 100 m/a. 25 9
PS30X. 300-0-300 v. 100 m/a. **PS3X.** 350-0-350 v. 100 m/a. 25 9
All the above have 6.3-4-0 v. at 4 amps., 5-4-0 v. at 2 amps.
PS43. Output 425-0-425 v. 200 m/a., 6.3 v. 4 amps., C.T. 6.3 v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded 51/-
PS50. Output 450-0-450 v. 250 m/a., 6.3 v. 2 amps., C.T., 6.3. v. 4 amps., C.T. 5 v. 3 amps. Fully shrouded 75/-
PS0X. Output, 300-0-300 v. 80 m/a., 6.3 v. 7 amps., 5 v. 2 amps. Framed. Flying leads 31 9
PS5X. Output, 350-0-350 v. 250 m/a., 6.3 v. 6 amps., 4 v. 8 amps., 4 v. 3 amps., 0-2-6.3 v. 2 amps. Fully shrouded 71 6
PS160X. Output, 350-0-350 v. 160 m/a., 6.3 v. 6 amps., 6.3 v. 3 amps., 5 v. 3 amps. Fully shrouded 47 6
PS43X. Output, 425-0-425 v. 250 m/a., 6.3 v. 6 amps., 6.3 v. 6 amps., 5 v. 3 amps. Fully shrouded 69/-
MS6. Output, 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. For receiver R1355. Half shrouded 29 3
MS150. Output, 350-0-350 v. 150 m/a., 6.3 v. 3 amps., C.T. 5 v. 3 amps. Half shrouded 30 9
F36. Output, 250-0-250 v. 100 m/a., 6.3 v. 6 amps., C.T. 5 v. 3 amps. Half shrouded 32 6
PS120. Output, 350-0-350 v. 120 m/a., 6.3 v. 2 amps., C.T. 6.3 v. 2 amps., C.T. 5 v. 3 amps. Fully shrouded 33/-
PS256. Output, 250-0-250 v. 80 m/a., 6.3 v. at 6 amps., 5 v. at 3 amps. Fully shrouded 30 9
PRI.1. Output 230 v. at 30 m/a., 6.3 v. at 1.5/2 amps. 23/-
PS150. 350-0-350 v. 150 m/a., 6.3 v. 4 amps., 5 v. 3 amps. 34 9
PS150X. Output, 350-0-350 v. at 150 m/a., 6.3 v. at 2 amps., C.T. 6.3 v. at 2 amps., C.T. 5 v. at 3 amps. Fully shrouded 34 9
The above have inputs of 200 250 v.

FILAMENT TRANSFORMERS

F4. Output, 4 v. 2 amps. **F6.** Output, 6.3 v. 2 amps. 9/-
F12X. Output, 12 v. at 1 amp. 9/-. **F6X.** Output, 6.3 v. 0.3 amps 6/-
F12. Output, 12.6 v. tapped 6.3 v. at 3 amps. 18 6
F24. Output, 24 v. tapped 12 v. at 3 amps. 26/-
F12 and F24 framed with Flying Leads.
FU6. Output, 0-2-4-5-6.3 v. at 2 amps. 11/-
F29. Output, 0-2-4-5-6.3 v. at 4 amps. 20 9
FU6 and F29 clamped with Flying Leads.
F5. Output, 6.3 v. at 10 amps. or 5 v. at 10 amps. or 12.6 v. at 5 amps. or 10 v. at 5 amps. 37 9
F6.4. Output, four at 6.3 v. tapped at 5 v. at 5 amps. per winding giving by suitable series and parallel connections 24 v. at 5 amps., 20 v. at 5 amps., 18 v. at 5 amps., 15 v. at 5 amps., 12.6 v. at 10 amps., 10 v. at 10 amps., 6.3 v. at 20 amps., 5 v. at 20 amps. 57/-
F5 and F6.4 framed with Flying Leads.
FU12. Output 0-4-6.3 v. 3 amps. **FU24.** Output 0-12-24 v. 1 amp. 19 6
The above have inputs of 200 250 v.

OUTPUT TRANSFORMERS

MOP1. Ratios, 26, 46, 56, 66, 90, 120-1 50 m/a. max. current. C.T. for Q.P.P. Class B, etc. Secondary 2/4 ohms. Top panel and clamped, each 6/-
OP1. Midget Power Pentode, ratios 30, 60, 90-1, 40 m/a. Secondary 2/3 ohms, each 4/-
OP2. Midget Pentode, ratios 45-1. Secondary 2/3 ohms, 40 m/a. per doz. 39 6
OP10. 10/15 watts output. 20 ratios on Full and Half primary 19 9
OP30. 30 watts output. 20 ratios on Full and Half primary 28 6
Williamson's O.P. Transformer to Author's specification £4 3 6
Chokes for Williamson's Ampl fier. 30H. at 20 m/a. 10H. at 150 m/a. 15 6 35 6
Choke C4. 60 m/a., approx. 8H. 350 ohms 5/-
Choke C5. 40 m/a., approx. 5 H., 350 ohms 4/-
Choke C6. 50 m/a., 50 H., 1,500 ohms 12/-
C8. 360 Micro henries clamped, 5/3. **C7.** 90 m/a. 180 ohms, clamped 6 3
Belling-Lee Co-Axial Plugs. Type 642/P., each 1/3
Belling-Lee Co-Axial Sockets. Type 604/S, each 1/3
Quotations, etc.—stamped addressed envelope please.
C.W.O. (add 1/3 in £ for carriage), all orders over £2 carriage paid.
Trade and also Export enquiries invited.

H. ASHWORTH (Dept. WW)
676, Gt. Horton Road, Bradford, Yorks.

Extension Loudspeakers

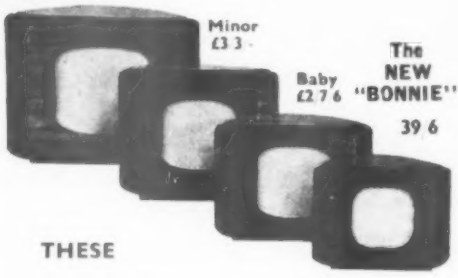

Richard Allan

"BAFFLETTES" are fitted with larger loudspeakers than any similarly priced extension speakers!

Obtainable from all Good Radio Dealers or write for details of these and other Models and Record Players to :—

Richard Allan Radio Ltd., Dept. W.D. Baffletts House Batley, Yorkshire

- Eliminates Needle Changing
- Gives better reproduction
- Filters out surface noise
- Increases life of records

Goldring "Acoustic-filtered Needles" suit any Standard Pick-ups.

Look for the Display Card at your Dealers

Goldring Needles cost 10/6, including P. Tax

The Radio Press acclaim this instruction book to build a Record Player of the highest quality. Price 2/- post free.

ERWIN SCHARF
GOLDRING PRODUCTS
49-51a De Beauvoir Road, London, N.1 Tel.: Clissold 3434/6

Outstanding in its class...

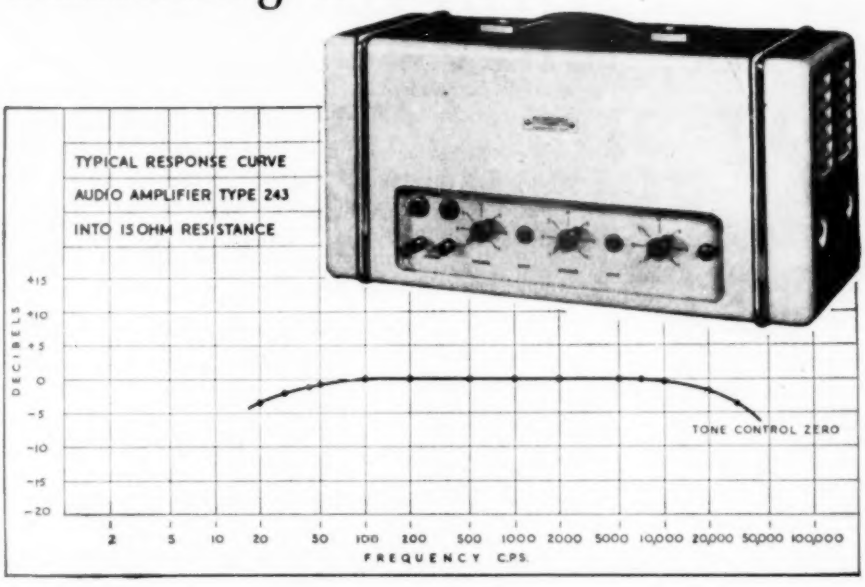

The METROVICK audio amplifier

TYPE 243

The type 243 amplifier is designed for use with high grade public address systems, for the connoisseur of quality and for industrial applications where faithful response over the audio range from 30 to 15,000 cycles is required. This Metrovick instrument is outstanding in its class and provides an output of 20 watts.

SPECIFICATION

Supply: 200/250V 50 c/s single-phase; consumption approximately 130 VA for full output.

Input: Gramophone not exceeding 0.2V for full output. Microphone not exceeding 0.02V for full output. The two circuits can be mixed as required.

Impedance: 7 ohms, 15 ohms and 45 ohms.

Output: 20 watts with negligible distortion.

Tone Control: Continuously variable.

Response: ± 1 db from 30 to 15,000 c/s at zero position of tone control.

Controls: These are recessed to avoid damage and are illuminated when in operation.

Dimensions: 18½" × 8½" × 10½".

Weight: 60lb. net.

Finish: The instrument is housed in an attractive steel case, stove enamelled in cream or blue as desired. A leather carrying handle is fitted.

METROPOLITAN-VICKERS ELECTRICAL COMPANY, LIMITED, TRAFFORD PARK, MANCHESTER, 17

Member of the A.E.I. group of companies

METROVICK *Applying Electronics to Industry*

RE/191

SIMON STYLITES* says . . .

Material shortages are restricting the output of radio components. For example, some manufacturers' current sheet steel allocations are only a fraction of their requirements.

Although we know there must be good reasons for such a cut we, at any rate, could add 25% to our output *and sell it in the export market alone* if we could get a few extra tons of sheet steel each month. No doubt others could do the same, or perhaps even better . . . and in the present economic state of the country that would seem to be highly desirable.

★ *Simon Stylites surveyed life and the world from the top of a pillar, whence somewhat wider horizons are visible.*

ISSUED BY

REPRODUCERS AND AMPLIFIERS LIMITED

WOLVERHAMPTON · ENGLAND

Telephone: Wolverhampton 22241 (5 lines). Telegrams: Audio, Wolverhampton.

ALL the A.C. power you require from your D.C. supply

with a

Valradio

D·C·/A·C· CONVERTER

Models for Electric Gramophone from **£8 16 0** *plus 10%*

Models for
- Radio-grams and Autochange Radio-grams (inc. 3-speed motors)
- Radios
- Televisions, etc., *from* **£11 16 6** *plus 10%*

Input, 6, 12, 24, 32, 50, 110 or 200/250V. D.C.
Output 230V. 50 or 60 c.s.

Valradio *Descriptive literature W.W.13 from the manufacturers:-*
NEW CHAPEL ROAD, HIGH ST., FELTHAM, MIDDX.
Tel.: FELtham 4242
Service Dept.: 57 Fortess Road, London, N.W.5. Tel.: GULliver 5165
Overseas Enquiries to nearest E.M.I. Organisation Depot.

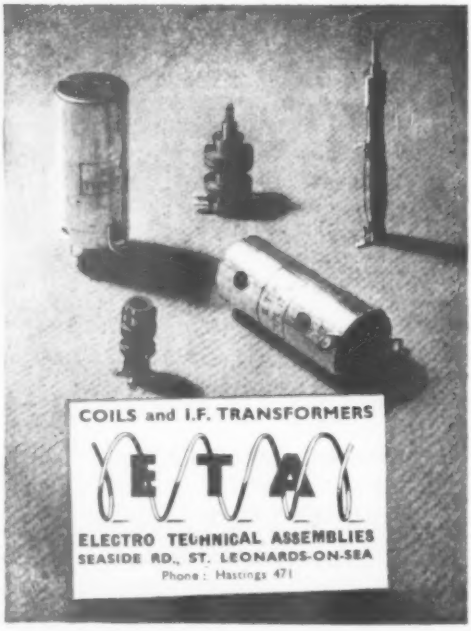

PREMIER RADIO Company

(REGD.) B. H. MORRIS & CO. (RADIO) LTD. ESTAB. 40 YRS.

RADIO *Please quote Dept. W.W.* TELEVISION

Now being Delivered!

PREMIER MAGNETIC TAPE RECORDING KIT

£29 · 8 · 0 ***Including ALL parts, Valves, Cabinet, Loudspeaker, etc., but excluding Microphone.***

(Carriage and Packing 15/-)

The kit incorporates the ***NEW MODEL*** **LANE TAPE TABLE** already assembled and ready for use, a **6 VALVE SPECIALLY DESIGNED AMPLIFIER KIT** including **Bias and Erase Oscillator for use with the** above unit, and a **WELL MADE WALNUT FINISHED TABLE CABINET** to house the complete unit. Outside dimensions when closed: Height 13½in., Length 17in., Depth 13½in.

INSTRUCTIONAL BOOKLET 2/6
This is credited if a complete Kit of the Tape Recorder is ordered.

SPECIAL FEATURES of the Amplifier include separate Bass and Treble lift controls, high and low gain Input Sockets, Record Playback indicator, etc. May be fed from Microphone, pick-up or directly from the Speaker terminals of your radio. Chassis size 14" × 9" × 2½".

The **PREMIER MAGNETIC TAPE RECORDING KIT** When completed compares favourably with all existing makes.

SPECIFICATION of the *NEW* LANE TAPE TABLE:— Made to high standards and incorporating features ensuring low level of "Wow" and "Flutter" throughout the full length of tape.

FAST REWIND Provision for fast rewind and forward run in less than 1 min. in either direction. Three motors obviating friction drive.

HIGH FIDELITY RECORD PLAY-BACK (1 hour approx. playing). The Table is fitted with high fidelity record play-back head of new design wound to high impedance and a separate A.C. Erase Head. The Heads are half track size allowing approx. 1 hr. playing from standard 1,200ft. Reel of Tape.

TAPE SPEED 7½in. sec. **For use on A.C. 200/250, 50 cycles mains only.**

The **AMPLIFIER KIT COMPLETE**

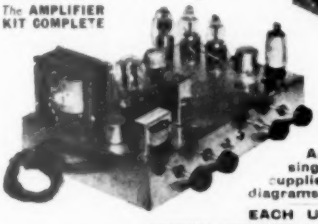

The **LANE TAPE TABLE**

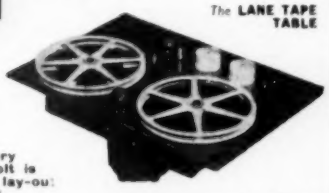

As is usual in all PREMIER KITS every single item down to the last nut and bolt is supplied. The chassis is punched and lay-out diagrams and theoretical circuits are included.

EACH UNIT MAY BE PURCHASED SEPARATELY

PREMIER AMPLIFIER KIT INCLUDING 8in. SPEAKER	PREMIER TABLE CABINET	LANE TAPE TABLE
£7 · 19 · 6	£4 · 18 · 6	£16 · 10 · 0
2/6 packing and carriage.	5/- packing and carriage.	7/6 packing and carriage.

This Recording Outfit has been designed for use with M.C.-1-111 SCOTCH BOY Magnetic Tape. With this high quality tape a frequency range of 50 c.p.s. to 9,000 c.p.s. at tape speed of 7½in./sec. can be readily achieved.

1,200ft. reels 35/-.

Moving Coil Microphones, (Stand Type) suitable for use with the above are available from stock **£5 12 6**

WE ARE EXHIBITING DAILY MAIL IDEAL HOME EXHIBITION OLYMPIA MARCH 4-29

WORKING MODELS CAN BE SEEN AT THE ADDRESS BELOW

WE CORDIALLY INVITE YOU TO VISIT OUR STAND AT THE
'DAILY MAIL' IDEAL HOME EXHIBITION
CHILDREN'S SECTION (Ground Floor) · **OLYMPIA**
Where the ***PREMIER MAGNETIC TAPE RECORDING KIT*** *and* ***BABY ALARM KIT*** *will be exhibited and demonstrated.*

STAND NO. 210

THIS IS OUR ONLY ADDRESS

207 · EDGWARE ROAD · LONDON · W·2

TERMS OF BUSINESS: *Cash with order or C.O.D. over £1. Please add 1/- for Post. Orders under 10/-; 1/6 under 40/-, unless otherwise stated*

Telephones: AMBassador 4033 PADdington 3271/2

OPEN UNTIL 6PM ON SATURDAYS

PREMIER RADIO Company

REGD. EST. 40 YRS.

C. H. MORRIS & CO. (RADIO) LTD.

Please quote Dept. W.W.

RADIO

BRAND NEW R1155 RECEIVERS

In original cases, complete with 10 valves. Frequency range 18.5 Mc/s. to 6 to 9 to 5 wave bands. **£18.10**-. 7/6 packing and carriage.

POWER SUPPLY UNIT for above incorporating output stage. Supplies an output of 250 volts at 80 Ma. which is ample for the R1155 with the output stage. Jones plugs for connecting the Power Pack to the Receiver are included. The 6V6 output stage complete with Output Transformer is built into the unit. Price **£8.19.6**. Plus 5/- packing and carriage.

BRAND NEW R1355 RECEIVERS

In original cases, as specified for the "Inexpensive Television," complete with 11 valves, **£2.15**-. 7/6 packing and carriage.

HEADPHONES

Balanced Armature Low Resistance
Type 1, 5/11 pair. Type 2, 7/11 pair.

High Resistance
12/6 pair.

Moving Coad
Type 3, 9/11 pair.

Lightweight High Resistance
14/6 pair.

CRYSTAL MICROPHONE

An entirely insulated crystal microphone which can be safely used on A.C./D.C. amplifiers. High impedance. No background noise; really natural tone. The ideal Mike for tape, wire and disc recording and sound projectors. Price **22/6**.

PREMIER BABY ALARM KIT

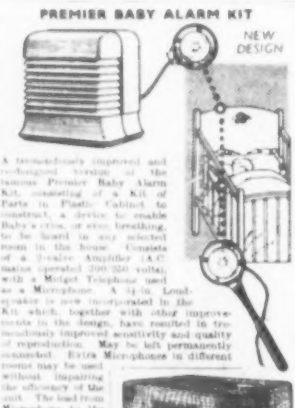

A tremendously improved and redesigned version of the famous Premier Baby Alarm Kit, consisting of a Kit of Parts in Plastic Cabinet to construct a device to enable Baby's cries, or even breathing, to be heard in any selected room in the house. Consists of a 2-valve Amplifier (A.C. mains operated 200-250 volts), with a Midget Telephone used as a Microphone. A 5-in. Loudspeaker is now incorporated in the Kit which, together with other improvements in the design, have resulted in tremendously improved sensitivity and quality of reproduction. May be left permanently connected. Extra Microphones in different rooms may be used without impairing the efficiency of the unit. The lead from Microphone to the unit may be up to 60ft. in length. Complete with valves, Circuit and Instructions. Price **69/6**.

SPECIAL OFFER
PREMIER De Luxe BABY ALARM

This is a completely wired and tested amplifier, housed in a grey wrinkle-enamel cabinet. Entirely self-contained for use on A.C. or D.C. mains supply of 200/250 volts, already assembled and ready to plug in.
Reduced price **£8.8**-, plus 7/6 p. & c.

MAINS NOISE ELIMINATOR KIT

Two specially designed chokes with three smoothing condensers with circuit diagram. Cuts out all mains noise. Can be assembled inside existing receiver, **6**/- complete.

BUILD A PROFESSIONAL LOOKING RADIO AT LESS THAN HALF TO-DAY'S PRICE

We can supply all the parts to help you:

Bakelite Cabinet (Brown or Ivory)	17/6
Packing and insurance	2/6
Punched chassis, 3-valve plus rectifier T.R.F.	3/9
Engraved Glass Dials. 180-550 and 800-2,000 m.	1/6
With station names, new wavebands	
T.R.F. Coils, 180-550, 800-2,000 metres, pair	6/6
Drum (3½in. diam.)	1/6
Driving band	1/6
Double pointer	4d.
Spring	3d.
Nylon cord (yard)	9d.
Dial Front Plate	2/6

SEND 1/6 FOR EASY TO FOLLOW POINT TO POINT DIAGRAMS AND CIRCUIT DIAGRAM which shows how YOU can build the Receiver illustrated above.

THE COMPLETE KIT

to construct a 3 valve plus rectifier TRF Receiver for use on 200/250 v. A.C. mains can be supplied at **£6 9 6** plus 7/6 packing and carriage.

Each KIt is complete in every detail, nothing has to be made or improvised. Easy to follow, point to point diagrams are supplied, making construction very simple. The Dial is illuminated and the Receiver housed in a Bakelite Cabinet size 12in. × 5in. × 8in. presents an attractive appearance. The valve lineup is:—
7/7A—H.F. Pentode. VR116—Detector.
ATP4—Output, and Metal Rectifier.
Waveband coverage is for the medium and long bands.
Choice of Walnut or Ivory coloured Cabinet.

GARRARD ELECTRIC GRAM' MOTOR

Induction motor, 100-250 volts, 50 cycles A.C. only. The GARRARD Induction Motor is totally enclosed. Entirely free from radio frequency disturbance, magnetic hum and electrostatic. Variable speed. With 12in. Turntable. Price **£5 17 6**. Plus packing and carriage 2/6.

Govt. Surplus Ex W.D. AERIALS BRAND NEW

12ft. 3 4ft. screw-in sections of copper-plated steel, highly flexible with non-stick screw fits, tapering ½in. to ¼in. *Brand new* in container, **6/9**. Packing and carriage 1/6. Insulated Base, **2/6**.

These aerials make ideal fishing rods

BATTERY CHARGER KITS

All incorporate metal rectifiers. Transformers are suitable for 200/250 v. A.C. 50 cycle MAINS.

Cat. No.		
2002	Charges 6 volt accumulator at 1 amp. Resistance supplied to charge 2 v. accumulator	£1 2 6
2003	Charges 12 volt accumulator at 1 amp.	£1 7 6

ACCUMULATORS

By world-famous maker, 2 volt 10 amp.	4/11

IMPORTANT ANNOUNCEMENT: All prices quoted in our advertisements are those ruling at the time of submitting advertisement copy, and are subject to alteration without notice.

TELEVISION

M.T. ELIMINATOR AND TRICKLE CHARGER KIT

All parts to construct an eliminator to give an output of 120 volts at 20 m.A. and 2 volts to charge an accumulator. Uses metal rectifier, **£2**.

LUSTRAPHONE HIGH FIDELITY HAND MICROPHONE.

Moving Coil Microphone, HIGH IMPEDANCE. The case has been "tailored" to follow the form of the user's hand and is ruggedly constructed as a pressure die casting in order to withstand the rough treatment to which hand microphones are usually subjected. The ideal microphone for use with Tape Recorders. Price **£6 6**-.

EX-U.S.A. U.H.F. AERIAL

with untuned detector stage, consisting of V.R.92 valve, etc. Brand new, in carton **5**/-.

ADJUSTABLE BENCH LAMP

Complete with flex, lampholder and reflector, **25**/-. Post and insurance 2/-.

BURGOYNE SOLDER GUNS, 75/-.

TUNING CONDENSERS

3-Gang .0005 mfd. Ceramic insulation, ¼in. spindle, **5**/-; 3-Gang .005 mfd. ¼in. spindle, **7/6**.

GERMANIUM CRYSTAL DIODES

Wire ends, midget size. The ideal Crystal Detector, G.E.C. or R.T.H., **4/6**.

PREMIER SUPERHET COILS

16-50, 180-550, 800-2,000 metres, set with circuit, **10/6**.

METAL RECTIFIERS FULL WAVE

6 v. 1 amp., **4**/-; 12 v. 1 amp., **8**/-.

E.H.T. Pencil Type:
Output 650 v. 1 m.A., **4/7** each. 1,000 v. 1 m.A. **6**/- each.

CAR BATTERIES—*BRAND NEW*

6 v. 11 plate WALKER. Hght. 9¼in., Lgth. 7¼in., Dpth. 6¼in. Price **77/6**.

6 v. 15 plate READING. Hght. 7¼in., Lgth. 9¾in., Dpth. 7¼in. Price **85**/-.

6 v. 15 plate DELCO-REMY. Hght. 7¼in., Lgth. 9¾in., Dpth. 7¼in. Price **97/6**.

6 v. 23 plate DELCO-REMY. Hght. 8¼in., Lgth. 13¾in., Dpth. 7¼in. Price **110**/-.

12 v. 9 plate WALKER. Hght. 8¼in., Lgth. 12¾in., Dpth. 8¼in. Price **110**/-.

ALL PRICES PLUS 7/6 CARR. & PACKING.

FRACTIONAL H.P. MOTOR

A 50 v. 2 phase A.C. motor, 1 40th h.p. by famous maker. Supplied complete with resistor, condenser and circuit diagram to convert the motor to ¼ h.p. for use on 240 v. single phase A.C. mains. Brand new **25**/-, plus 2/6 carriage and packing.

SPECIAL OFFER of
ADMIRALTY REFLEX-RE-ENTRANT P.A. LOUDSPEAKERS

Visual Tubine. Matching transformers 4-1 and 6-1 ratios with volume control at mot. Very sensitive and directional. Twin Units, **75**/-. Plus 5/- carriage and packing.

SUPER QUALITY TELEVISION MAGNIFYING LENS

To suit 5in., 6in. or 7in. Tubes. Increase picture size considerably. **25**/- each.

WHITE RUBBER MASK

For 5in. Tube, **9/6**.

CORRECT ASPECT WHITE RUBBER MASK

For 12in. Round or Flat-faced Tube 16/11

SORBO RUBBER MASKS

Grey Felt Finish (New Aspect Ratio). 9in., **5**/-; 12in., **5/6**.

THIS IS OUR ONLY ADDRESS

207 · EDGWARE ROAD · LONDON · W·2

TERMS OF BUSINESS: Cash with order or C.O.D. over £1. Please add 1/- for Post. Orders under £20, 5% under £5. Business otherwise stated.

Telephones: AMBassador 4033, PADdington 3271/2

OPEN UNTIL 6PM ON SATURDAYS

IMPORTANT ANNOUNCEMENT: WE CANNOT ACCEPT RESPONSIBILITY FOR, NOR CAN WE GUARANTEE ANY-

PREMIER RADIO Company

(REGD.) ESTAB. 40 YRS.

E. H. MORRIS & CO. (RADIO) LTD.

Please quote Dept. W.W

RADIO

TRANSMITTER RECEIVER TYPE TR9H

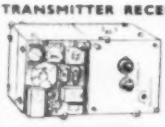

Consists of Transmitter type T1396 and Receiver R1139 in one case. This is a 9-valve Battery operated Unit covering 4.3 Mc.s. to 6.6 Mc.s. Crystal controlled, complete with valves. **50 -**, plus 7/6 packing and postage.

PX25 AMPLIFIERS

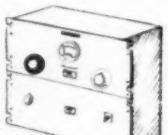

A superb push-pull 15-watt model with all the latest refinements, extended tone control range, 3in. moving coil panel meter for current and distortion checks, oil filled condensers, fuses in circuits, two smoothing chokes and although in a steel case the front panel extends to fit on a 19in. standard rack. The high gain circuit of latest design will give full volume from the smallest input. 500 ohm output. Less valves. **£5 5 -**, plus £1.1.- carriage, packing and insurance.

UNREPEATABLE OFFER SUPER QUALITY CARBON MICROPHONE

Limited number only. High grade super quality carbon Microphone, spring suspension mounted, complete with heavy duty Telescopic floor stand. **79 6**, plus 5 - p&g., carriage and insur.

CARBON HAND MICROPHONE

super quality, with switch in handle. Type 3A. **4 11.**

MOVING COIL MICROPHONE INSERTS

A moving coil loudspeaker or microphone unit, 1¼in. dia. **3 -**.

7-VALVE SUPERHET CHASSIS

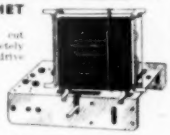

All control mountings cut out, fitted with completely assembled full vision drive scale, long, medium and short wavebands and band spread. Heavy flywheel tuning. **19 6**, plus 2/6 p&g. and carr.

4-WATT 'GRAM AMPLIFIER

This is a converted ex-Govt. unit, incorporating a 6V6 OUTPUT STAGE giving excellent reproduction on Gram. Complete in a metal case finished in grey enamel. Outside dimensions (approx.) 9in. long, 6¼in. high, 8in. deep. Price **£6 10 -**. Plus 5/- packing and carriage.

RADIO CABINET (WALNUT FINISH)

Outside dimensions: 12¼in. high, 10¼in. deep, 20in. wide.

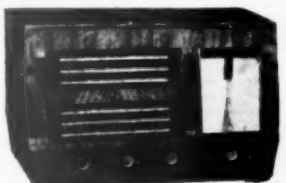

Price **£2 2 6**, plus 7/6 carr. p&g.

GRAMOPHONE UNITS

Collaro RC500 Autochanger Unit, single speed, 78 r.p.m., already mounted on metal frame, ready to drop into cabinet	£16 10 0
Collaro Autochanger 3-speed Unit, including Crystal Head for long playing and standard recordings	£18 14 1
Connoisseur 2-speed Gramophone Unit, LESS Pick-up	£22 18 8
Pick-up and 2 heads for above	£10 0 8
Conrad Rim Drive Gramophone Unit, Less Pick-up arm, 78 r.p.m.	£4 3 10
Ditto, 33 r.p.m.	£4 7 5
Decca 3-speed Rim Drive Gramophone Unit, LESS Pick-up	£7 3 4
Decca Single-speed Rim Drive. LESS Pick-up, 78 r.p.m.	£3 14 4
Ditto, 33 r.p.m.	£3 14 4
Decca Pick-up with 2 heads, one long playing and one standard	£7 0 0
Plessey Autochanger 3-speed magnetic head, plays mixed records	£23 13 0
Collaro Rim Drive Magnetic Unit, 78 r.p.m.	£6 11 4

Plus Packing and Carriage 5/-.

ALL THE ABOVE ARE FOR USE ON A.C. MAINS ONLY

P.M. MOVING COIL LOUDSPEAKERS

(3 ohm voice coils)

2in. Goodmans	15 -	6in. Truvox	12 6
3in. Plessey	15 -	8in. Plessey	16 6
5in. Plessey	12 6	8in. Rola	17 6
5in. Truvox	12 6	10in. P.M.C.	27 6
5in. Rola	13 6	12in. Truvox	70 -

PREMIER 3-BAND COIL PACK

Consists of a wired and aligned Coil Pack of the most Modern Type incorporating such features as Air Dielectric Trimmers, Litz wound medium wave coils. Tuned R.F. stage, covers 13-14, 40-129, 200-557 metres. Dimensions of pack: 6in. x 4¼in. × 2¼in. Complete circuit is supplied. Price **29 6**.

PREMIER 4-BAND COIL PACK

Consists of a fully wired and calibrated Coil Pack of the latest type. 5 Position Switch includes a Gram. position. Wavebands covered: 12-6.52 metres (22-5.8 Mc.s.), 51-190 metres (5.9-1.57 Mc.s.), 190-540 metres and 900-2100 metres. Air Dielectric Trimmers on all Short-wave Coils. Unit consists of 3 Screened Sections, Aerial, R.F. and Oscillator. Dimensions of Pack: 6in. × 4¼in. × 2¼in. Price with circuit diagram. **£4 11 6**.

PREMIER TELEVISOR CABINET FOR 12in. TUBE TELEVISOR

A handsome walnut finished cabinet. Primarily designed for our own Kits. They are quite suitable for most of the kits published in the various Radio periodicals. For this reason the holes for control knobs have not been drilled. A baffleboard suitable for a 10in. Loudspeaker is provided. Outside dimensions 33¼in. high, 20½in. deep 16in. wide **£9 9 -**, plus 7/6 packing and carriage.

IMPORTANT ANNOUNCEMENT: All prices quoted in our advertisements are those ruling at the time of submitting advertisement copy and are subject to alteration without notice.

TELEVISION

RADIO CABINET (WALNUT FINISH)

Outside dimensions: 16¼in. high, 9in. deep, 17in. wide

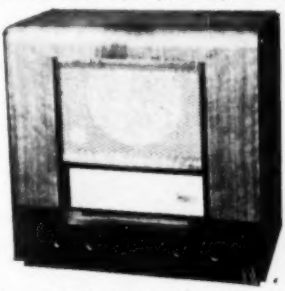

A beautifully made cabinet. **£3 10 -** plus 7/6 carr. p&g.

5-VALVE SUPERHET RADIO CHASSIS

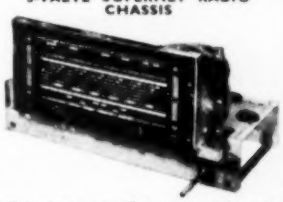

Drilled and cut out for all necessary control mountings and Mains Transformer, fitted with 5 Amphenol Octal Valveholders, Aerial, Earth and Gramophone Sockets. 500 pf Tuning Gang Condenser, full vision drive Tuning Assembly consisting of unbreakable perspex 3-coloured scale for long, medium and short wavebands. Calibrated in metres, kilocycles and station names, price **39 6**.

AS A SPECIAL OFFER—CABINET ILLUSTRATED ABOVE AND CHASSIS, TOGETHER £5. 5. 0. Plus 7/6 Carr. Pkg. & Insurance.

RADIO CABINET (WALNUT FINISH)

Outside dimensions: 17in. high, 11in. deep 16in. wide

Price **£2 2 6**, plus 7/6 carr. / p&g.

THIS IS OUR ONLY ADDRESS

207 · EDGWARE ROAD · LONDON · W·2

TERMS OF BUSINESS: Cash with order or C.O.D. over £1. Please add 1/- for Post Orders under 10/-, 1/6 under 40/- unless otherwise stated

Telephones: AMBassador 4033, PADdington 3211/2

OPEN UNTIL 6PM ON SATURDAYS

—KIT OR COMPONENT SOLD AS A PREMIER PRODUCT BY FIRMS OTHER THAN OURSELVES

In April

Visitors to the Northern Radio Exhibition at the City Hall, Manchester, are cordially invited to visit our Showrooms (opposite the City Hall on Deansgate) to see a comprehensive working display of the latest television and radio test equipment. Expert Consultants will be in attendance.

●

THE LARGEST STOCKISTS OF ELECTRONIC INSTRUMENTS IN THE NORTH OF ENGLAND

●

ADVANCE—AVO—BALDWIN—
CINTEL—COSSOR—ELECTRO METHODS
—ELECTRONIC INSTRUMENTS—HIVOLT
—LEAK—METVICK—MULLARD—
SARGROVE—TAYLOR—
WAYNE KERR—WAVEFORMS—
ETC., ETC., ETC.

●

F. C. Robinson & Partners Ltd.,
287 Deansgate, Manchester, 3
(Tel.: DEA 6601)

BAKERS 'Selhurst' RADIO

PIONEERS OF MOVING COIL SPEAKERS SINCE 1925

NEW "HIGH FLUX" 1952 MODELS

HIGH FIDELITY SPEAKERS

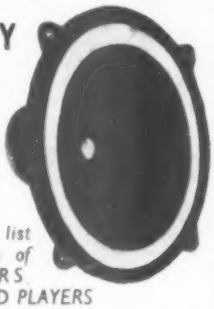

The World Famous
12" Triple Cone.
12" Single Cone Model.
18 "Duplex".

Write for illustrated list and technical details of SPEAKERS, TUNERS AMPLIFIERS & RECORD PLAYERS

BAKERS 'SELHURST' RADIO
Quitable House, Dingwall Road, Croydon
Telephone CROydon 2371/2

Variable Coils...
-and wizard performance

NEW OSMOR "Q" RANGE COILS charm away all doubts, difficulties and complications—thanks to their super-selectivity and sensitivity

Consider these five star features:

★ **Only 1in. high.**
★ **Variable iron dust cores.**
★ **Low-loss Polystyrene formers.**
★ **Packed in dampproof containers.**
★ **Fitted tags for easy connection.**

—and they're backed by the OSMOR quality guarantee! Supplied with leaflet giving data, circuits, etc., 4/- each.

COILPACKS. A full range is available for Superhet and T.R.F., Mains or Battery. Size only 1⅞in. high × 3¼in. wide × 2¼in. Ideal for the reliable construction of new sets, also for conversion of the 21 RECEIVER, TR., 1196, TYPE 18, WARTIME UTILITY and other receivers. Aligned and tested, with full circuits, etc. Fully descriptive leaflets available. **WARNING! Avoid inferior imitations. Genuine OSMOR Coilpacks are sold only under the name OSMOR.**

MATCHED COMPONENTS. Various types of OSMOR Dials, Chassis, I.F.'s, Speakers, Transformers, etc., etc., to match our coils and coilpacks are all listed.

Send 5d. (stamps) for *FREE CIRCUITS and full lists of coils, coilpacks and radio components.*

OSMOR RADIO PRODUCTS LTD. (Dept. W.28)
BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON, SURREY
Telephone: Croydon 5148.

Fit..

the same make and type the setmaker uses

When a valve or cathode ray tube replacement is needed you can't do better than fit the same make and type the Setmaker uses. This is particularly important in television, when many of the special circuits used require for their proper operation the exact type of valve round which they were designed. That is why so many Setmakers use Ediswan Mazda valves and tubes and that is why you should replace with Ediswan Mazda. They're the right valves for the job.

EDISWAN
MAZDA

Valves and Television Tubes

The Edison Swan Electric Company, Ltd. 155 Charing Cross Road, W.C.2.
Member of the A.E.I. Group of Companies.

BV84

Three heads are better than one!

For Standard and Microgroove Recordings

Green Spot with .001" radius sapphire for microgroove recordings.

Red Spot with .0025" radius sapphire for modern standard recordings.

Yellow Spot with .003" radius sapphire for older standard recordings.

These pickup heads are fitted with an easily replaceable armature system complete with a semi-permanent sapphire. Armature mass 20 mg.

Extremely low mass at needle point (4·5 mg. only), allowing for reduction in downward pressure to 10/12 grams for standard recordings and 7/9 grams for microgroove recordings.

Prices: With one head £4 10 0 plus £1 19 0 Purchase Tax. Extra heads each £2 10 0 plus £1 1 8 Purchase Tax. Spare armature system with sapphire 14/8 including tax.

Licensed under Letters Patent No. 586900 and/or 615424.

a **Connoisseur** product

Tel.: HALIFAX 69169.

Manufactured by A. R. SUGDEN & CO. (ENGINEERS) LTD., Well Green Lane, Brighouse, Yorks.

SHORTAGE OF ELECTRONIC TECHNOLOGISTS

The demand of Industry and the Ministries for our trained students is still far greater than we can supply. For top-grade technologists we offer:

THREE-YEAR COURSE IN TELE-COMMUNICATION ENGINEERING (including one year's Factory attachment)

Next Course commences 25th August

Write for FREE BROCHURES giving details of the above and other day-time attendance courses

E.M.I. INSTITUTES — the only college which is part of a great industry

E.M.I. INSTITUTES
(DEPT. 16E), 10 PEMBRIDGE SQUARE, LONDON, W.2. Tel.: BAYSWATER 5131-2.

Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC

The new HYDE

foot operated

WIRE STRIPPER

These two machines will, between them, strip with speed and accuracy practically all types of Insulated Wires and Cables from Small Wires and Flexes up to Cables of 1" diameter. HYDE Stripping Machines are cutting the costs and speeding the production of many world famous manufacturers.

SEND SAMPLES OF WIRES AND CABLES USED, FOR FULL REPORT.

. . . *and the* **BENCH MODEL**

Telephone Wythenshawe 2850

I. B. HYDE & CO. LTD., Wythenshawe, Manchester

For Mutual and Self Inductance measurement...

. . . . in the range 0.001μH to 30mH, the 'CINTEL' Mutual and Self Inductance Bridge will be found unequalled for accuracy and simplicity of use. Also measuring resistance in the range 100μΩ to 3000Ω, this bridge is an essential piece of laboratory equipment, full details of which are available on request.

CINEMA-TELEVISION LIMITED

A Company within the J. Arthur Rank Organisation

WORSLEY BRIDGE ROAD · LONDON · SE 26

Telephone: HITher Green 4600

SALES AND SERVICING AGENTS

F. C. Robinson & Partners Ltd., 287 Deansgate, Manchester, 3 — H. Hawnt & Co., Ltd., 59 Moor St., Birmingham, 4 — Atkins, Robertson & Whiteford Ltd., 100 Torrisdale Street, Glasgow, S.2

CINTEL

REGISTERED TRADE MARK

Here is your area and here is your

Aerialite
AERIAL

FRINGE

UP TO 15 MILES

MODEL 65 "Aeradoor." Designed for indoor skirting board mounting. Fitted with one telescopic and one flexible arm. Can be adjusted to any channel. Complete with 5 yards of coaxial lead-in. **PRICE 32/-**

MODEL 65A with 5 yards of Twin feeder. **PRICE 32/-**

Also **MODEL 66**, which has two flexible arms. Complete **PRICE 25/9**

MODEL 66A, with 5 yards twin feeder. **PRICE 25/9**

15 TO 25 MILES

MODEL 74. Has three fully flexible elements. High pickup properties. Trouble-free performance. Centre element has a spring tensioning device and neat connector box. All Channels. **PRICE 13/6**

MODEL 53 (similar to 74). Three rigid metal elements. Installed in variety of positions. All Channels. (Coaxial lead-in extra.) **PRICE 32/6**

25 TO 40 MILES

MODEL 57. Single dipole for chimney stack mounting. Complete with chimney bracket, mast, lashings, etc., ready for installation. Excellent performance. **PRICE 62/6**

MODEL 58. A dipole designed for wall mounting. Cranked stand-off mast similar to Model 57. **PRICE 52/6.** (58A with straight stand-off arm, 47/-.) All Channels.

40 TO 60 MILES

MODEL 55. An H-aerial with dipole and reflector. Forward gain 3.8 dB. Front/back ratio 11.0 dB. Acceptance angle 180 deg. All Channels. Complete with a 10ft. x 2in. dural mast, brackets, lashings, etc. **PRICE £7 19 0.** Various styles of this model available.

60 MILES & OVER

MODEL 63A. For fringe and difficult reception areas. Folded dipole three element aerial. High gain 8.1 dB. Front/back ratio 29 dB. Acceptance angle 90 deg. All Channels. Complete with 10ft. x 2in. dural mast, brackets, lashings, etc. **PRICE £13 5 0** With 14ft. mast, **£14 2 0.** Various styles of this model available.

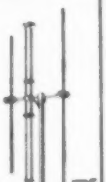

A NEW INDOOR AERIAL
MODEL 71. A directional double folded dipole with four fully flexible elements. Easily erected in loft, attic or upper room. Highly directional characteristics. Forward gain 3.75 dB. Excellent reception at considerable distances from transmitters. Complete ready for erection to any channel specified. **PRICE 25/-**
Send 3d. stamps for FREE Illustrated Catalogue.

AERIALITE LTD., Stalybridge, Ches.

A NEW SERVICE FOR T.V. DEALERS & ENGINEERS

This Pool has been formed to supply direct manufacturers' replacements of special components by return post. *Send S.A.E. For List*

COSSOR - DECCA - EKCO - FERGUSON - G.E.C. - K.B. - PYE - ULTRA

PYE	Line Output Transformer	LV20	27/6
	EHT Line Output Transformer	FV1	53/6
	Frame Osc. Transformer	FV1	10/6
	Frame Output Transformer	FV1	15/6
	Deflector Coils	B18T	24/3
	R.M.4. Rectifiers	LV21C	22/6
	Line Output Transformer	LV21C	32/6
G.E.C.	Germanium Crystal Diode	T/V	6/6
BAIRD	EHT Transformer	Townsman	46/6
EKCO	EHT Transformer	TSC30	87/-
	EHT Osc. Coil	TS46	19/6
FERGUSON	Line Output Transformer	943T	46/6
	Line Osc. Transformer	943T	11/6
	Line Output Transformer	968T	46/6
	Deflector Coils	968T	32/-
H.M.V.	Line Osc. Transformer	1811	12/6
	Frame Osc. Transformer	1807	15/6
	Line Output Transformer	1807	41/6
K.B.	Line Output Transformer	EV30 or FV30	91/6

Controls for all above makes in stock.

T.V. Engineers Lab. Resistor Kit 180 ½ watt 15 standard values in free cabinet **£6 0 0**

T.V. Servicing Manual including 7 service sheets **4 9**

Prices include packing and postage. Cash with order.

DIRECT T.V. REPLACEMENTS

A. ROSE

134-136 LEWISHAM WAY, NEW CROSS, S.E.14
TIDEWAY 3696

RECENTLY PUBLISHED

TELEVISION RECEIVER PRACTICE
by Roy Holland
(*Chief Development Engineer, Scophony-Baird*)

Demy 8vo. 80 pages. 5/-

This book is devoted to practical descriptions of the circuit techniques in current use, and covers the following: Power Supplies; Cathode Ray Tubes and Associated Circuits; Timebase Oscillators; Electromagnetic Deflection; Signal Amplifier Circuits; Detectors and Video Amplifiers; and Separation of the Synchronising Pulses. The majority of the 80 figures are circuit diagrams with explanatory waveforms and typical component values. Operation is explained in non-mathematical terms easily followed by any reader familiar with the elementary principles of radio.

AUDIO HANDBOOK No. 2: FEEDBACK
By N. H. Crowhurst, A.M.I.E.E.

Demy 8vo. 64 pages. 3/6

An essentially practical work, explaining clearly what feedback can do, where and how, and what its limitations are. The theory of closed loops is presented in a simple form, progressively developed without involved mathematics. There are design charts, specially developed for this book, which use a new and simplified approach to the problem. Examples are given illustrating the practical application to actual circuits, and showing how the methods can be applied to a wide range of problems and circuits. With 40 figures drawn by the Author.

List of publications available on request.

NORMAN PRICE (PUBLISHERS) LTD.,
283, CITY ROAD, LONDON, E.C.1.
LONdon Wall 9292

The Impress of Quality

The craftsmanship of the toolmaker, genesis of genius, creates in steel the intricate dies from which are produced porcelains omnigenous to meet the multiplexity of needs demanded by the electrical, electronic, and radio industries of this modern age.

The dexterity of the operators connaturalise their pattern in precise repetition, and machinery of the latest kind weds quality to quantity—until at last, much travelled through the kiln, emerge fine Porcelains—Porcelains die-made by Taylor Tunnicliff, bearing that impress of Quality by which they will be recognised the world over.

Taylor Tunnicliff & Co Ltd.

Low Loss Ceramics

Head Office EASTWOOD · HANLEY · STAFFS
Telephone : Stoke-on-Trent 5272-4
London Office : 125 HIGH HOLBORN W.C.1 *Telephone : HOLborn 1951/2*

ROLA SPEAKERS
DESIGNERS USE THEM . . .
DEALERS CHOOSE THEM . . .
Because the CUSTOMER Wants the Best!
ROLA CELESTION LTD.
FERRY WORKS, SUMMER ROAD, THAMES DITTON, SURREY
(Emberbrook 3402-6)
Wholesale enquiries to —
TRUVOX LTD.,
Exhibition Grounds, Wembley, Middlesex. Wembley 1212
ROLA

HANNEY OF BATH

"VIEWMASTER" Wrantie units for London 22/-, Birmingham, Holme Moss AND KIRK O'SHOTT4 30/-; Constructors envelopes L, B, H M, 5/6 post free. WB100 18/6, WB101 6/-, WB102 18/6, WB103 37/6, WB103A 52/6, WB104 15/6, WB105 32/6. TCC tone-corrector set £7/7/- (all channels). Morganite resistors 15/3 set. Harmonic type 9 pots 5/- each. Westinghouse rectifiers MEH1100 29/5, 1400 11/7, 14A86 20/4, WX3 a WX6 3/6 each. Colvern pots. CLR9013/3 each, CLR1000 22/6/4. Bulgin set 11/6. Pre-amp. coils 5/- pair pre-amp. chassis 17/6. Line transf. 27/9. Frame transf. 22/6. With control 10/-. Boost choke 6/-. Valve supports 1/6. Focus ring WB109/1. Marshall 29/6. Focus ring Pioneer 23/6. Mullard 22/6. Also pre-amp. kits, remote conversion kits etc., any item sold separately from our resistor upwards.

CATHODE RAY TUBES. Mullard MW22-14C, MW22-16, MW22-17, MW22-18. Mazda CRM92, £13 13/8. 12in. Mullard MW31-14C, MW31-16, 17 and 18. Mazda CRM121A and 121B, £18 4/1. Mazda CRM123 £20 10/4. Brimar C12B £19/7/4. We pay carriage on all tubes and guarantee safe delivery per passenger train.

WILLIAMSON AMPLIFIER. PARTRIDGE output transformers (1.7 ohm sec.) limited number only £6/7/-. Woden 12H 150 ma. potted choke, limited number only 36/6. Matic transformer to specification (Elstone) 57/6. 10H 150 ma. choke £1/10/-, 20 ma. choke 10/-. KT66 valves, matched pair 50/2/-, KT61 valves 25/1, gold rectifiers (indirectly heated 3 v., 2 amp., 500 v. 250 ma.) 21/6. EF37 (5 mil) metal packs 2/10. 10 mfd/mfd/mfd 2/1 each, 8 mfd/mfd/mfd/mfd 1/5 each. 3 bank 5 position switch 9/6. RESISTOR and CONDENSER sets are available for all Williamson units—and are made up with the finest quality components ONLY. The condensers are TCC and Dubilier, resistors Erie and Morganite and the pots either Reliance or Colvern. There are no surprises in our quotations. Full details are given in our current catalogue and all items are EX STOCK.

EDDYSTONE 740 RECEIVERS are still available at £38/15/-, we pay carriage per passenger train.

ACOS GP-20 pickups, standards or LP £3/11/5, heads only £2/3/4 either type. SUNDRIES. All gram motors, WB and Celestion speakers, coils and coil-packs are still available as per our Feb. advert. 12 E.K. germanium crystals 4/-. Brimar metal rectifiers RM1 4/6, RM2 5/-, RM3 6/-, SR3 10/6. Polystyrene 6 varnish 1/10. Simon soldering iron, model 22/6, pencil for 23/6. Brownlea 10 watt iron, a super job at 17/3. Valve manuals, GEC, Mullard and Brimar 5/6 each inc. postage. Wireless World reprints Williamson Amplifier 2/9, supertest TV Unit 2/9, High Quality Radio Loudspeakers 2/9, Radio Valve Data 3/9, all inc. postage. Sound Reproduction by Briggs 11/-. Nuts, bolts, washers, soldering tags, copper wire, tie on tags, group boards, etc., etc., etc., long & Hambro's CRT masks 3in. screen, new aspect ratio 11/-.

Send 6d. stamp for our new list which covers all TV designs and general components.

L. F. HANNEY
77 LOWER BRISTOL ROAD, BATH
Tel. 3811

ICS

HOME STUDY
backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an ICS Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of instruction covering radio and, if necessary, television, include the following: **Complete Radio Engineering . Radio Service Engineers . Radio Service and Sales . Advanced Short-Wave Radio . Elementary Electronics, Radar and Radio . Television Technology**

And the following Radio Examinations

British Institution of Radio Engineers . P.M.G. Certificates for Wireless Operators . City and Guilds Telecommunications . Wireless Operators and Wireless Mechanics, R.A.F.

Students intending to sit for the above Examinations should enrol NOW for preparatory Courses.

Using a specially prepared study programme, students study at their own pace, in their spare time and, with time for revision, sit with full confidence of success. (*I.C.S. Students are coached until successful.*)

Moderate fees include ALL books required.

GENEROUS DISCOUNT TO H.M. FORCES.

Write today for our FREE **"RADIO"** booklet which fully describes the above ICS Courses and the facilities for the complete study of Radio and/or Television technology. The ICS Advisory Department will also give free and impartial advice on the need for and the means of instruction.

International
CORRESPONDENCE SCHOOLS

Dept. 213A, International Buildings, Kingsway, London, W.C.2

CAPACITANCE

FIXED CONDENSERS: You see them every day in electronic equipment and take them at their face value. The condenser manufacturer can't — he must determine their capacitance, power factor and other important characteristics with the aid of high grade test equipment. When *you* want to make measurements of this type, remember that a range of Marconi instruments is available specially designed for the job.

MARCONI instruments

MARCONI INSTRUMENTS LTD · ST. ALBANS · HERTS · Telephone: St. Albans 6161/7

Midland Office: 19 The Parade, Leamington Spa. Northern Office: 30 Albion Street, Hull.
Export Office: Marconi House, Strand, London, W.C.2.

EXACT EFFORTLESS TUNING

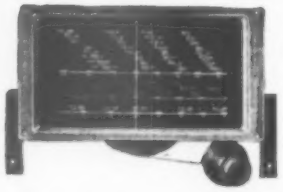

The S.L.8 Spin wheel drive gives easy control through a ratio 24-1. Fitted with constant velocity coupling, it eliminates strain on the Condenser, providing mechanical and electrical isolation from vibration and noise.

Complete with 3-band glass scale 9in. × 4½in. Printed short, medium and long wavebands with station names. Scale length 7in. Supplied with florentine bronze escutcheon.

PRICE 27/6.

S.L.5, similar but fitted with reverse vernier drive, gives ratios of 18-1 search and 50-1 reverse vernier.

PRICE 26/6.

Replacement Scales calibrated to Copenhagen Plan now available for :

Airplane Drive **2/3** retail — Full Vision Drive **2/9** retail
Squareplane Drive **2/6** retail — S.L.8 or S.L.5 Drive **4/6** retail

PRECISION COMPONENTS BY

JACKSON

BROS. (LONDON) LIMITED

KINGSWAY · WADDON · SURREY

Telephone Croydon 2754
Telegrams: Walfilco, Souphone, London

YOUR TELEVISION SET'S *Spectacles!*

Just as your reading glasses are optically correct, each MAGNAVISTA Filtachrome Television Lens is scientifically computed to suit its particular set. That's why with a MAGNAVISTA you get clearer as well as bigger pictures, no eye-strain, and daylight viewing without overworking the tube.

The New MAGNAVISTA *Filtachromatic Television Lens*

THE ONLY OPTICALLY COMPUTED TELEVISION LENS

A product of

METRO-PEX LTD.,

42a Denmark Hill, London, S.E.5

GRAM MOTORS PICK-UPS

for MICROGROOVE & STANDARD RECORDS

"X-ray" view of MU-10

B.S.R. MU-10 motors for 33 & 78 r.p.m. Speed change by reversing drive pulley. 10in. turntable. 100/250v. **£3.15s.**

MU-14

MU-14 de luxe model with ROTACAM instant speed change for 33 45 & 78 r.p.m. **£6. 10s.**

ACOS GP-20 pickups, standard **£3.11.5**
GP-19 LP microgroove head only **£3.3.6**

MARCONI Type 14, with matching transformer **£3.8.6**

GOLDRING Type 130 standard lightweight **£1.15.10**
Type 137 De-luxe lightweight **£1.19.5**
ditto with AUTO STOP **£2.6.7**
Type 150 with adjustable counterweight for 33 45 or 78 r.p.m. records. Complete with two sapphires. **£3.11.8**

DECCA Twin head 'turnover' **£3.19.4**

CONNOISSEUR Standard **£6.11.8**
Super de luxe, with two heads **£10.0.6**

All post free in U.K.!

GU-4A Three-speed **RADIOGRAM UNIT**

Now available for the home market, this new combined unit uses the popular MU-14 motor on a unit plate with pickup and AUTO-STOP.

The pickup is of the Acos dual purpose type fitted with a sapphire needle.

Beautifully finished in mottle enamel. **£10.**

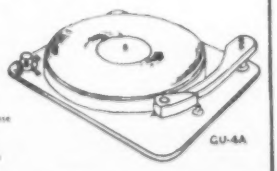

GU-4A

Full list including Auto changers on request!

RADIOCRAFT Ltd

ENGINEERS 2A977
CHURCH GATE LEICESTER

MANNING BRITAIN'S RADAR DEFENCES

There's a place for YOU..

in the PART-TIME R·A·F

In building up Britain's air defences the Royal Air Force needs a large, fully trained reserve of men and women on whom it can rely in any emergency. On their skill the whole fighting efficiency of the R.A.F. hinges — and there's a place for you among them. In the cheerful atmosphere of the part-time R.A.F. you will find yourself doing work that is vital and fascinating, among people you will be proud to call your friends. You can get full particulars by posting the coupon now.

TO : ROYAL AIR FORCE (W.D.71.A.), VICTORY HOUSE, LONDON, W.C.2

Please send particulars of part-time service with the R.A.F. (*Applicants from British Isles only*)

NAME _____ ADDRESS _____

(*If ex-R.A.F. or ex-W.A.A.F. give rank, trade and No.*)

★ IF YOU ARE BETWEEN 14 AND 17 — AND KEEN — JOIN THE A.T.C. ★

SELECTIVE TRANSMISSION MEASURING SET

B.C.C. introduce another outstanding success in their development of Measuring Instruments.

This instrument is a direct reading, selective, gain and loss measuring set to be used with an external signal generator.

Four terminal networks, active and passive, balanced or unbalanced, can be measured.

Facilities are provided for use as a high impedance Selective Detector Amplifier.

Frequency Coverage : 1—68 Kc/s in 4 ranges.
Range of Measurements : Gain 0-60 db. Loss 0-60 db.
Accuracy : ± 0.5 db.
Impedance range : 75, 150 and 600 ohms., balanced or unbalanced.
Det.-Amp Sensitivity : 10-12 μV.
Power Supplies : 100-150-200-250v. 50 c.s.

Based on Signals Research and Development Establishment design.

Manufactured for Ministry of Supply and G.P.O.

BRITISH COMMUNICATIONS CORPORATION LIMITED
31 GORDON AVENUE, STANMORE, MIDDX. GRIMSDYKE 2266 Cables : BEECEECEE, STANMORE

Power increased but price reduced

—in the new

GRAMPIAN
Pressure Unit
(S.P.1.)

Pressure Unit only £6 - 6 - 0
Complete Speaker £14 - 14 - 0

New design and improvements in production methods offer you many advantages in this new unit.

Data.	
Frequency response (useful working range)	90-8000 c/s
Power handling, with 42" horn	15 watts
Impedance	15 ohms
Flux density	11,000 lines per sq. cm.
Weight	7 lb. 6 oz.
Throat thread	1.362" dia. × 18 T.P.I.
Dimensions	4¼" dia. × 4⅛" overall

GRAMPIAN REPRODUCERS LTD
9, HANWORTH TRADING ESTATE, FELTHAM, MIDDX.
Telephone: Feltham 2657 Telegrams: Reamp, Feltham

21281

DESIGN ENGINEERS!
Seamless one-piece METAL BELLOWS

Combining the properties of :

1. A compression spring capable of repeated flexing.
2. A container which can be hermetically sealed.
3. A packless gland.

HYDRAULICALLY FORMED BY A PROCESS UNIQUE IN THIS COUNTRY

FOR Automatic coolant regulation. Movement for pressure change. Packless gland to seal spindle in high vacua. Reservoir to accept liquid expansion. Dashpot or delay device. Barometric measurement or control. Pressurised couplings where vibration or movement is present. Dust seal to prevent ingress of dirt. Pressure reducing valves. Hydraulic transmission. Distance thermostatic control. Low torque flexible coupling. Pressure sealed rocking movement. Pressurised rotating shaft seals. Aircraft pressurised cabin control. Refrigeration expansion valves. Thermostatic Steam Traps. Pressure amplifiers. Differential pressure measurements. Thermostatic operation of louvre or damper.

Write for List No. N.800-1

Drayton METAL BELLOWS
Drayton Regulator and Instrument Co. Ltd., West Drayton, Middlesex

An Announcement . . .

DUREX ABRASIVES LTD. wish to announce that as from June 14th, 1951, the name of the Company has been changed, and is now the MINNESOTA MINING & MANUFACTURING COMPANY LTD. Identification will be as before, except that the words "Scotch Boy" will be used instead of "Durex" as a prefix to the name of the material, e.g., "Scotch Boy" Magnetic Recording Tape instead of "Durex" Magnetic Recording Tape.

Existing high standards in the quality of the products will be maintained, the change is in name only.

'SCOTCH BOY'

Magnetic Recording TAPE

ANOTHER 3M COMPANY PRODUCT

Manufactured by:—

MINNESOTA MINING & MANUFACTURING COMPANY LTD

167, STRAND - LONDON - W.C.2 - AND SLOUGH

SUPREME AT ANY DISTANCE!

Telecraft T.V. Aerials give the utmost in service and satisfaction and provide the most popular range on the market today. There is a *reliable* TELECRAFT Aerial for every district—for any distance.

to the extreme fringe

FA22

Guaranteed for 2 years, the famous FA22 Long Distance Aerial is unsurpassed. First class construction and high sensitivity. Built to stand up to all weather conditions. Seamless Steel Spreader, adjustable Steel Mast-head Clamp to fit masts from 1¼in. to 3in. dia. Shock Absorber Reflector Mountings. The FA22 still leads for value, durability and reliability. £5 17 6.

"Telestrip" room Aerial ...	15 0
Loft Aerial	£1 5 0
Type TS.50 "H" chimney mounting, 7ft. mast	£5 5 0
Type TS.55 "H" chimney mounting, 10ft. mast	£6 5 0
Type TS.25 "H" mast mounting to fit 1¼in. to 3in. dia. ...	£3 10 0
Type FA.22 Long Distance to fit 1¼in. to 3in. dia. mast ...	£5 17 6
Matching transformer 6 6 extra.	

There is a TELECRAFT AERIAL for every contingency—indoors or out.

BETTER THAN ANY—CHEAPER THAN MOST

Send for illustrated brochure and price lists

TELECRAFT LIMITED

THORNTON HEATH, SURREY

Tel.: THOrnton Heath 1191-2-3

Depots:—BIRMINGHAM, BRISTOL, MANCHESTER, WORTHING.

SCOTTISH ENQUIRIES: LOUIS GRACE, 38 Langside Place, Glasgow, S.12. Giffnock 2992

PHIDELITY

MAGNETIC PRODUCTS LTD

—Sole U.K. Agents for Messrs. Jorgen Schou, Denmark, manufacturers of

TRANSFORMERS

★

Full particulars of the extensive range of standard-type JS-Transformers, and Mu-metal shielded-type JS-Transformers will be forwarded on request.

★

All types now available for

EARLY DELIVERY

Special-type Transformers made to customer's specification.

Trade enquiries invited.

PHIDELITY MAGNETIC PRODUCTS LTD.
65-66 Chancery Lane, London, W.C.2. (CHA 4342)

CITY SALE & EXCHANGE Ltd.

OF

93-94 FLEET STREET

LONDON, E.C.4 (Ludgate Circus) Phone: Central 9391

Can supply the following from stock:—

Leak TL/12 amplifier with pre-amp	36 gns.
Rogers Baby de Luxe amplifier	£17 10 0
Acoustical Q.U.A.D. amplifier	£35 0 0
Decca corner horn speaker ...	£21 10 0
Goodmans 12in. Audiom speaker	£8 12 6
Decca 347/M 3 speed record player	£19 19 0
Decca 348/M walnut case ...	21 gns.
Connoisseur 2 speed gram motor	£22 18 8
Connoisseur superlight weight P.U.	£10 0 8
Decca XMS twin head P.U. ...	£7 0 0

Send 25% of price with order. Balance over 12 months.

Let us quote you our part exchange offer for your present equipment.

"Frequentite" is the most suitable insulating material for all high frequency applications. Seventeen years ago we introduced the first British-made low-loss ceramic, and consultation with us before finalising the design of new components is a wise precaution.

STEATITE & PORCELAIN PRODUCTS LTD.

Head Office: Stourport-on-Severn, Worcestershire. Telephone: Stourport 111. Telegrams: Steatain, Stourport

S.P.77

THE "Q-MAX" B4 40 TRANSMITTER

- A complete 40 watt, Four Band Transmitter for Phone or C.W.
- Four Bands 80-40-20-10 metres at the turn of a single switch.
- 40 watts C.W., 35 watts Phone to KT8C Final.
- Built-in Modulator and Power Pack.
- Provision for low impedance input from a V.F.O.
- The whole completely housed in attractive black crackle-finished steel cabinet, 19in. x 10in. x 9½in.

PRICE : **£75** complete.

IN STOCK

AMPLIFIERS

LEAK "Point One"	£28 7 0
Pre-amplifier	£9 9 0
Tuner Unit	£37 4 6
ACOUSTICAL "QUAD"	£35 0 0
Tuner Unit	£26 0 0
BERRY'S 10 w S-valve	£15 15 0
WILLIAMSON. All components including precision resistors and capacitors	

RECORD CHANGERS, Etc.

PLESSEY Three Speed	£23 13 0
CONNOISSEUR Twin-speed motor	£22 18 8
Pick-up with two heads	£10 0 5

SPEAKERS

BARKER Natural Sound Reproducers : 148A	£15 15 0
150	£18 18 0
GOODMAN'S "Audiom 150"	£10 5 6
15in.	£18 10 0
W.B. Con. Duplex 10in.	£7 15 0
WHARFEDALE : Super SCS/AL	£4 12 6
Super 8CS/AL	£4 12 6
"Golden" 10in.	£5 2 6
Super 12/CS/AL	£15 0 0

"Q-MAX" CHASSIS CUTTERS in 13 sizes from ⅛in. to 3⅛in. (round) and 1in. (square). Prices from 10/6 to 32/6 each.

THE "LINCOLN" OSCILLATOR COIL

Completely enclosed in "Neosid" former ensuring minimum external field. Unusually good waveform with maximum amplitude at 45 kc/s. Numbered tag panel connections and one-hole fixing. Overall size 1⅝in. x 1⅝in. x 1in. only. PRICE 12/6. Post, packing 6d.

MAGNETIC TAPE RECORDING

We have carried out considerable development work on this project, and the benefit of our experience may be had on request. Send for List MTR1 (3d. in stamps, please), which contains full details of amplifier kits, tape decks, accessories, etc., but, better still, call in for a demonstration and a chat on this absorbing subject.

"Q-MAX" MODEL G.D.O.I. GRID DIP OSCILLATOR is an ideal instrument for the determination of tuned circuit resonant frequency, tuning transmitters without application of power, for the determination of coil mutual and stray inductances and both fixed by stray capacitances. Covers 1.5 to 300 Mc/s in eight ranges. PRICE : 9½ gns. with one coil. Extra coils 3/6 each.

BERRY'S

(SHORT WAVE) LTD.

25 HIGH HOLBORN, LONDON, W.C.1

TEL.: HOLBORN 6231

PRICES

Nos. 1—4 ..... 7/- plus 3/1 P.T. post 6d.

No. 5 ..... 9/3 plus 4/1 P.T. post 6d.

(Subject to full Trade Discount)

No. 1 "Miniature" jewel-tipped needle for light-weight pick-ups.

No. 2 "Straight" jewel-tipped needle for crystal pick-ups.

No. 3 "Trailer" jewel-tipped needle for medium-weight pick-ups.

No. 4 "Knee Bend Trailer" jewel-tipped needle for older heavy-weight pick-ups.

No. 5 "Miniature Solid Sapphire" needle for light-weight pick-ups.

All S. G. Brown Precision Sapphire Needles are protectively mounted on a useful double-sided stroboscope (78 and 33⅓ r.p.m.). An instructive and interesting Brochure with many useful hints on obtaining better reproduction, gladly sent on request. Write to Dept. W.

S. G. Brown Ltd. SHAKESPEARE ST., WATFORD, HERTS

BUILDING THE

"WILLIAMSON"?

if so, we have in stock all the specified components to make this superlative amplifier

Partridge Mains Output Transformers
Partridge Chokes
T.C.C. Condensers
High Stability Resistors, 1% & 5%
Precision Condensers, 1%, 2% & 5%
Matched valves
in fact "the works"

DETAILED PRICE LIST OF ALL COMPONENTS AVAILABLE ON REQUEST

TELE-RADIO (1943) LTD.

177 EDGWARE ROAD, LONDON, W.2

Phone : PAD. 5606
PAD. 6116

Shop Hours :
Mon.-Sat. 9 a.m. — 6 p.m.
Thursday 9 a.m. — 1 p.m.

Type FSK.2 for frequency shift keying and is designed for conversion of any stable conventional communications transmitter for frequency shift operation.

Frequency Shift Equipment

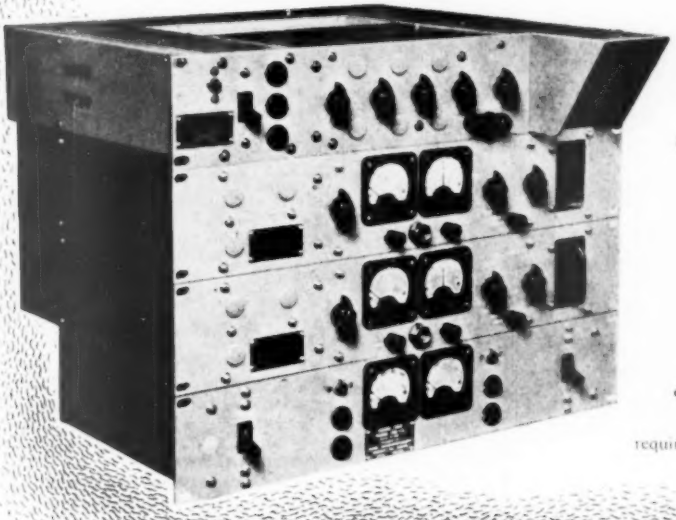

Type FSY.7 is for dual diversity frequency shift reception, and provides a visual indication on a cathode ray tube of the correct tuning point of the receivers when the transmission is being keyed. Other models are available for single receiver reception.

Both these units can be fitted on site by station engineers, any modification of radio equipment required being only of a minor nature.

AUTOMATIC TELEPHONE & ELECTRIC CO. LTD.

RADIO AND TRANSMISSION DIVISION

STROWGER HOUSE, ARUNDEL STREET, LONDON, W.C.2

Telephone: TEMple Bar 9262. Cablegrams: Strowgerex, London

AT. 14221-BX.107

For
IMMEDIATE DELIVERY
From
OUR LARGE STOCKS

RESISTORS
VITREOUS WIRE WOUND and HIGH STABILITY, close tolerances ¼, ½, 1 and 2 watt. All values up to 2 meg. also 8, 13 and 30 meg.
CARBON—¼ watt to 5 watt. Standard Car Suppressors 15,000 ohms.

CAPACITORS
Block Paper, Silvered Mica, Mica, Tubular and Ceramic.

SWITCHES
TOGGLE, YAXLEY, OAK, ETC.

VARNISHED COTTON SLEEVING
Various colours ½ mm.—20 mm.

GLASS CARTRIDGE FUSES
1¼" in all popular sizes. From 150 mA. to 10 amps.

LAMINATIONS
RADIOMETAL 31, 39 and 40. Also many other types.

VOLUME CONTROLS
MORGANITE "H" type, "M" type and WIRE WOUND. Most popular values in stock.

PLUGS AND SOCKETS
CINCH, PYE, JONES, BELLING & LEE, BULGIN, ETC.

TRIMMERS
Variable CERAMIC TRIMMERS. Capacities from 5 to 100 pf. Spindle and pre-set types.

WIRES
ENAMELLED, SILK COVERED, REGENERATED CELLULOSE and PUSH-BACK.

VALVE HOLDERS
Paxolin, Moulded and Ceramic. Large selection including all latest types.

NUTS, BOLTS, WASHERS, P.K. SCREWS, RIVETS, EYELETS, SOLDER TAGS, GROMMETS, ETC.

Many other lines including ex-government components in stock. All enquiries dealt with individually, but regret no lists are issued.

TRADE COUNTER OPEN
9.30 TO 5.30 MONDAY TO FRIDAY

WHOLESALE, MANUFACTURERS' AND EXPORT ENQUIRIES ONLY

RADIO TRADERS LTD.
23, WARDOUR ST.,
LONDON, W.1.
Phone: GERrard 3977/8 *Grams: "Radiotrade"*

SHORTAGE OF RADIO & T/V ENGINEERS

The demand of Industry for our trained students is still greater than we can supply —and is likely to remain so for many years.

We offer:

FULL TIME DAY COURSE
1 year course in Principles and Practice of Radio and Television.

Next Course commences 15th April

Write for FREE BROCHURES giving details of the above, of our 3-year course, and of others.

E.M.I. INSTITUTES—the only college which is part of a great industry.

E.M.I. INSTITUTES
(DEPT. 10A), 10, PEMBRIDGE SQUARE, LONDON, W.2. TEL.: BAYSWATER 5131 2

Associated with "H.M.V." MARCONIPHONE COLUMBIA ETC

EA1

ARTHURS HAVE IT!
LARGE STOCKS OF NEW VALVES

TEST METERS IN STOCK
"AVO," "TAYLOR" TEST METERS AND SIGNAL GENERATORS

Leak Point One Amplifiers	£28 7 0
Leak Pre-amplifiers	9 9 0
Leak Tuning Unit	36 17 4
Chapman Tuning Units	17 6 8
Crystal and Moving Coil Microphones.	
Decca Replacement Heads and Pickups.	
Goodman's Axiom 150 Speakers	£10 5 6
Partridge Output Transformers for Williamson Amplifiers	6 12 0
Cossor Double Beam Oscilloscope 1035	85 0 0
Cossor Double Beam Oscilloscope 1049	120 0 0

LATEST VALVE MANUALS

MULLARD, OSRAM & BRIMAR No. 4. 5/- each.
MAZDA 2/- each.

TELEVISION SETS, WIRE AND TAPE RECORDERS ALWAYS IN STOCK.

Goods offered subject to price alterations and being unsold.

Arthurs EST. 1919
PROPS: ARTHUR GRAY, LTD. **first**

OUR ONLY ADDRESS: **Gray House,**
150-152 Charing Cross Road, London, W.C.2

TEMple Bar 5833/4 and 4765 *WRITE FOR LISTS*
TELEGRAMS—"TELEGRAY, WESTCENT, LONDON"
CABLES—"TELEGRAY, LONDON"

PAINTON

By Appointment to the Professional Engineer...

ATTENUATORS · FADERS · SWITCHES · WIREWOUND POTENTIOMETERS · PLUGS AND SOCKETS · WIREWOUND RESISTORS · HIGH STABILITY CARBON RESISTORS KNOBS DIALS AND POINTERS · TERMINALS

PAINTON

Northampton England

For critical analysis

or routine production

The 1684D/2 Cathode Ray Oscilloscope has been designed to meet these diverse requirements of laboratory, field and production units. Symmetrical d.c. circuiting is employed throughout, the amplifiers having a high and uniform sensitivity from zero frequency up to 3 Mc/s

Furzehill

FURZEHILL LABORATORIES LIMITED
BOREHAM WOOD, HERTS. TEL : ELStree 3940

A *workshop* in your *pocket!*

THE TELEVISION AND RADIO SERVICE ENGINEER'S **MASTER** TRIMMER KIT

Contains:

1 End Trimmer.
1 Side Trimmer.
1 Yaxley Switch Contact Adjustor.
1 Low Capacity Trimmer.
1 Screwdriver.
1 Set of Feeler Gauges.
1 Set of six Box Spanners from 1 to 8 B.A.
1 Set of four Spanners from 0 to 8 B.A.

A durable black crackle finish metal case.

Export enquiries invited

SEND YOUR ORDER TO
J. & S. NEWMAN LTD.
100 HAMPSTEAD RD., N.W.1
Tel: EUSton 5176-7

Widney-DORLEC
REGISTERED TRADE MARKS
CABINETS

We are now able to accept ORDERS for small or large quantities to any specified design

We are pleased to announce the opening of our new Office and Showrooms, and shall be pleased to welcome our trade customers.
Owing to the limited supply of raw material, we regret that we cannot supply private individuals.

If you do not already know about this unique Cabinet system, write for details to our new TECHNICAL SALES OFFICE, 290, NEW KING'S RD., LONDON, S.W.6

Manufacturers

Widney
ESTABLISHED 1898
HALLAM SLEIGH & CHESTON LTD
WIDNEY WORKS · BIRMINGHAM · 4

be played
absolutely new condi
playings even vintag
view of frequency range an
tracing distortion benefit from
derate filter slope above 8 kc/s.
With a separate low-pass filter to deal with deficiencies
the input signal, the conventional bass and treble
control can be applied to the correction of room
acoustics or loudspeaker deficiencies and once set need
no further adjustment. This is a distinct advantage, as
was proved by a comparative test in which a programme
with over-emphasized sibilants was subdued by the two
alternatives available, the variable-slope filter went
straight to the heart of the trouble, whereas the conven-
tional top-cut control alone made appreciable incursions
to middle frequencies before satisfactory suppression
achieved.
QUAD amplifier and control unit can be co
recommended to those who have discovered
of the simpler tone controls, the wider
useful life of records, and the settings
can be used as a criterion of the
in the basic amplifier
12 watts output th
per cent
With acknowledgements to "Wireless World."

Straight to the heart of the trouble

Now that there are some very good loud-speakers about (especially on Corner Ribbon), mere frequency range in an amplifier can be more of a liability than an asset. The achievement of great bandwidth is quite easy with modern techniques, but it does seem a shame (and very unscientific) that all except the strongest willed must reach for the top cut knob to escape the nasty noises which intrude. Hence the switched frequency, variable slope filter which is one of the UNIQUE features of our QUAD amplifier : an arrangement which permits one to go " straight to the heart of the trouble " (" Wireless World " page 372, October 1950), without removing all trace of treble response and producing the well known and professionally despised " mellow tone."

IF YOU would like to know how to get " more of the music and less of the noise " as one of our customers put it, write for the QUAD booklet now.

ACOUSTICAL
MANUFACTURING CO LTD
HUNTINGDON · HUNTS · TEL. 361

B.A. SCREWS, NUTS, WASHERS, ETC.

Prices per gross.

Assd. Screws	2 6	Brass Nuts			Brass Washers		
Assd. Nuts	2 6	OBA Full & 1	Lock 5 6	Assd. 1 6, OBA 2 -			
Screws and Nuts		2BA " 5 -	" 4 6	1BA 2 -, 2BA 1 10			
¼ gr. each	2 6	4BA " 4 6	" 4 -	3BA 1 9	4BA 1 8		
Brass Screws		5BA " 4 -	" 3 9	5BA 1 6, 6BA 1 6			
Assorted		6BA " 4 -	" 3 6	8BA 1 6			
2BA 5 6, 4BA 5 -		7BA " 4 6					
6BA 4 -, 8BA 4 6		8BA " 4 -	" 3 6				

Soldering Tags. Assd 2 -. 2BA 2 3, 4BA 2 -, 6BA 1 10, 8BA 1 10. Eyelets and Rivets, assd. 1 6. Aluminium Rivets, assd. 1 6. Br. Knurled Terminal Nuts. 6BA 8d., 4BA 1 -, 2BA 1 6 dozen. Br. Terminals, w/nuts, heavy type, NP, 6d. each, 5 6 dozen. Br. Terminals, w/nuts, very heavy, NP, OBA, 9d. ea., 8 - doz.

A SELECTION FROM OUR HUGE STOCK OF SCREWS.

PRICES PER **HALF-GROSS.**

ABBREV.: Heads. CH., Cheese. RH., Round. CS., Countersunk. NP., Nickel Plated. CP., Cadmium Pl. SC., Self-colour.

6BA	BRASS		STEEL	
¼" CH NP	1 6	¼" RH NP	1 5	¼" CH NP 1 -
¼ " SC	1 5	¼ " "	1 6	¼" RH SC 1 -
¼" " NP	1 7	⅜" "	1 7	¼" CS CP 1 -
⅜ " "	1 9	⅜ " "	1 9	⅜" RH SC 1 2
⅜ " "	1 10	½ " "	1 11	⅜" CS CP 1 1
½ " "	1 11	½ " "	2 -	⅜ " " 1 2
½ " "	2 -	⅝ " SC	2 1	½" RH SC 1 2
⅝ " SC	1 11	⅝ " NP	2 3	½" CS CP 1 4
⅝ " NP	2 1	¼ CS SC	1 4	½ " " 1 5
¾ " "	2 3	¾ " NP	1 6	⅝" RH SC 1 5
1" "	2 6	¾ " "	1 7	1" CS CP 1 7
¼" Inst H	1 9	⅞ " "	1 8	1" CH " 1 9
¼ " NP	1 9	1" "	1 9	1 1/16" " 2 6
1" CS "	2 -	1" "	1 10	1 1/16" H H 2 9

4BA	BRASS		STEEL	
¼" CH SC	2 -	¼" RH NP	1 10	¼" CS CP 1 2
¼ " NP	2 1	⅜ " "	2 3	⅜ " " 1 3
⅜ " "	2 1	⅜ " "	2 9	⅜" RH " 1 4
⅜ " "	2 2	⅜ " "	3 -	⅜ " SC 1 2
½ " "	2 6	½" CS "	1 8	½ " " 1 4
½ " "	3 3	½ " "	2 -	½" CS CP 1 4
⅝" Hex H "	2 6	½ " "	2 3	½" RH SC 1 6
¾ " "	3 6	¾ " "	1 10	½ " CP 1 9

2BA	BRASS		STEEL	
¼" RH NP	2 10	¼" CH NP	4 3	⅛" RH SC 1 6
¼ " "	3 -	¼ " SC	3 -	¼" LgeRH 2 -
¼ " "	3 3	¼ " "	5 -	¼" RH SC 2 -
⅛" " SC	3 3	¼" RH "	4 9	¼" CH 2 6
¼ " NP	4 3	⅜" CS NP	4 -	¼" RH CP 2 9
¼ Hex H SC	10 -	½" " SC	4 9	

8BA	BRASS		STEEL	
⅛" CH NP	2 -	¼" RH SC	1 9	⅛" CS CP 2 -
⅛ " "	2 6	¼ " NP	2 2	⅛" CH " 2 2
⅛" CS "	1 8	¼ " "	2 6	⅛" RH " 2 2
⅛" CH "	2 3	¼ " "	2 9	¼" CH NP 2 3
⅛" CS "	1 9	¼" Hex "	2 9	¼" RH CP 2 3
¼ " "	2 6	¼ " "	2 10	

ALL ABOVE POSTAGE EXTRA

Manufacturers enquiries invited, abundant stocks of most items

Large stocks of Copper and RESISTANCE WIRES; Paxolin type TUBING; Laminated Bakelite and Ebonite PANELS; TUFNOL and EBONITE TUBES and ROD; ERIE and DUBILIER RESISTORS; GERMANIUM and SILICON DIODES.

POST ORDERS ONLY PLEASE.

Send stamp for comprehensive lists. Trade supplied.

POST RADIO SUPPLIES
33, BOURNE GARDENS,
LONDON, E.4
Telephone: CLIssold 4688 & 2021

CONSOLES

For Major Film Mixer Suites to Individual requirements

"VIEWMASTER" CONSOLES

AS SHOWN

Beautifully designed and finished in Walnut, Oak, Mahogany and Teak, to customers' requirements.

Standard "VIEWMASTER" model as shown **£12.10.0**
With Full Length Doors **£13.10.0**
Carriage and Packing **15 - extra**

Fitted with shelf for easy mounting. These are **NOT** mass produced and dimensions can be altered to suit personal requirements.

Individual and Trade Enquiries to —

H. ASHDOWN
CABINET MAKER
98, HERTFORD ROAD,
EDMONTON, N.9.
Phone: TOT. 2621

SENSITIVE PANEL MOUNTING METERS

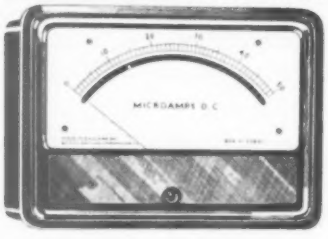

SIZE	2½"	3½"	5"
RANGE	25μA to 50A	10μA to 50A	10μA to 50A

(Prices on application.)

S.50 type microammeters are stocked by M.R. Supplies Ltd. at New Oxford Street, W.C.1

All sizes available with MIRROR SCALE 1st Grade Accuracy.

BRITISH PHYSICAL LABORATORIES
HOUSEBOAT WORKS · RADLETT · HERTS
Telephone · RADLETT 5674-5-6

STRICTLY EXPORT ONLY

HALTRON

Leading Exporters of all types of Radio Receiving and Transmitting Tubes. Current Production and Ex-Government Surplus Special Purpose Tubes. Over 500 types in large quantities, available Ex-Stock. Suppliers to Foreign Governments, Airlines, etc.

SOME OF THE TYPES CARRIED IN STOCK

1A5GT	6AM6	6SF7	12K8	78	836	BL63	NT63A
1C5GT	6AQ5	6SG7	12K8GT	80	837	CCH35	NU3/U14
1E7G	6AT6	6SH7	12SA7	81	838	CL33	QP21
1G6GT	6AU6	6SH7GT	12SA7GT	82	841	CMG25	QZ4
1G7GT	6A8G	6SJ7Y	12SC7	83	843	CV1501	QZ4A
1LD5	6A8GT	6SK7	12SG7	83V	860	CY32	PEN46
1LN5	6BA6	6SK7GT	12SH7	84	864	D63	PM4DX
1P5GT	6BE6	6SL7GT	12SJ7	89	865	DA60	PM202
1P31	6B7	6SN7GT	12SK7	100TH	866A	DET5	PT15
1R4/1294	6B8	6SQ7	12SK7GT	117L7GT	866JR	DET19	PX4
1R5	6B8G	6SQ7GT	12SL7	210VPT	869B	E1148/CV6	PX25
1S4	6C4	6SS7	12SL7GT	211 (VT4C)	872	E1190	R2
1S5	6C5	6ST7	12SN7GT	220B	872A	E1231	R3
1T4	6C5GT	6U7G	12SQ7	262B	874	E1248	RI2
2A3	6C6	6V6	12SQ7GT	304TH	878	E1271	RK28A
2A5	6C8G	6V6G	12SR7	282A	884	E1273	RK34
2A6	6C21	6V6GT	12Y4	304TH	902	E1320	RK59
2C26	6D6	6X4	15E	304TI	923	E1323	RKR73
2C34	6E5	6X5G	25A6G	307A	931A	E1415	RL7
2J21A	6F5	6X5GT	25L6GT	311A	954	E1436	RL37
2X2	6F5G	6Y6G	25Y5	313C	955	E1468	RT20A
2X2A	6F5GT	6Y7G	25Z4G	327A	956	E1516	S27A
3A4	6F6G	6Z5	25Z5	328A/4328A	957	EA50	SI30
3AP1	6F7	7A7	25Z6G	357A	958A	EBC33	SO12
3B7/1291	6F8G	7B6	25Z6GT	388A	959	ECH22	SP2
3BP1	6G6G	7B7	28D7	394A	991	EF22	SP4
3D6	6H6	7BP7	30	510A	1297	EF39	SP41
3Q4	6H6G	7C4	32	703A	1613	EF50	SP210
3Q5GT	6H6GT	7C5	35L6GT	705A	1616	EK32	SP15297
3S4	6J5	7C6	35T	708A	1619	EL32	STV280/40
3V4	6J5G	7C7	35TG	713A	1622	EL33	STV280/80
4D1	6J5GT	7B5	35W4	715A	1624	GTIC	TT4/NR57
5BP1	6J7	7E6	35Z3	715B	1625	GU20	TZ20
5BP4	6J7G	7E7	35Z4GT	717A	1626	HK54	TZ40
5CP1	6K6G	7L7A	35Z5GT	724A	1629	HP210	UI2/U14
5FP7	6K6GT	7N7	36	725A	1633	HP4101	UI8
5R4GY	6K7	7Q7	37	726A	1642	HR210	UI9
5U4G	6K7G	7R7	38	747	1960	KT24	U23
5V4G	6K8	7S7	39/44	800	2051	KT44	VCU "C"
5X4G	6K8GT	7Y4	40	801	4033A	KT61	VP23
5Y3G	6L5G	8D3	41	801A	4074B	KT66	VR53
5Y3GT	6L6G	9D2	41MXP	802	5763	KTW61	VR90
5Y4G	6L7	10	42	803	7193	KTW62	VR105/30
5Z3	6L7G	10Y	43	805	7475	KTW63	VR150/30
5Z4	6N7	12A6	45	807	8011	KTZ63	VT90
5Z4G	6N7G	12A6GT	45SPEL	808	8012	KTZ73	VT224/RW4
5Z4GT	6N7GT	12AH7	46	810	8013A	L2	VT501
6A6	6P7G-2	12AH7GT	50L6GT	813	9001	LD210	VT505
6A7	6Q7G	12AT6	50Y6GT	814	9002	LS5	VU39A
6AB7	6Q7GT	12AX7	54	815	9003	M1254	VUI20A
6AC7	6R7	12AU7	57	826	9004	MH4	VUI33A
6AG5	6R7G	12BE6	58	828	9005	ML6	VU508
6AG7	6SA7	12C8	72/RX235	830B	9006	MSP4/NR65	X24
6AK6	6SA7GT	12H6	75	832	AR300	MS/PEN	X63
6AL5	6SC7	12J5GT	76	832A	ATP4	NCI3	X65
6AM5	6SF5	12K7GT	77	833/833A	AUS(VUIII)	NGT5	X66

HALTRON

HALL ELECTRIC LTD

89, CHARLOTTE ST., LONDON, W.1. Phones: MUSEUM 9661 (5 lines) Cables: HALLECTRIC LONDON

HALTRON

SIFAM ENGLAND

Precision **INSTRUMENTS**

Type M35
4½" Square

The choice of leading electronic equipment designers

A first grade B.S.I. moving coil panel mounting instrument, supplied as D.C. Microammeter, Milliammeter, Ammeter, Millivoltmeter, or Voltmeter. Also available as A.C. Voltmeter for frequencies up to 50,000 c/s, A.C. Ammeter with internal transformer, or R.F. instument with internal thermo-couple.

Thermaster

New Temperature Indicator

The most versatile instrument for temperature measurement in the range —80° to +200°C. Easy detection of changes to within 1°, instant response; self contained with small dry battery; readings unaffected by voltage change. Pencil type "Detector" for surface contact, immersion, air or liquid temperatures supplied with any length of leads without affecting accuracy. Accuracy ±1%. Scale 8" long, can be scaled for any intermediate range, minimum 20°C.

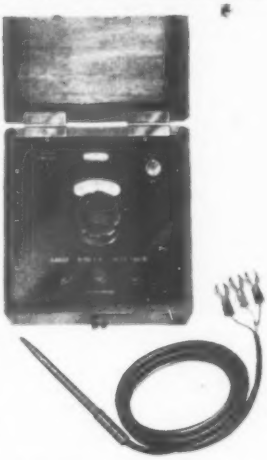

● *Write for Catalogue giving full details of the complete SIFAM range.*

SIFAM ELECTRICAL INSTRUMENT CO. LTD., Leigh Court, Torquay. *Telephone 4547 8.*

MODERN ELECTRICS LTD.,
164, Charing Cross Road,
London, W.C.2 'phone TEMple Bar 7587

Immediate delivery from stock

Export enquiries welcomed. Prompt attention to post orders.

TAPE RECORDERS

SOUNDMIRROR
Table Model £69 10 0
Portable Model £79 10 0

SIMPHONIC
1A (now booking early delivery) £76 0 0

SCOPHONY BAIRD
Mk. I £58 5 6
Mk. II (new model) £68 5 0

Magnetic Recording by S. J. Begun. Post free £1 6 0

PICK-UPS AND MOTORS

ACOS G.P.20 £3 11 9
L.P. and Std. Heads £2 3 4

DECCA Pick-up Std. £3 15 4
XL. Pick-up, T.O. Head for L.P. and Std. £3 19 2
Mag. XMS for L.P. and Std. Hds. £7 0 0

DECCA MOTORS
33⅓ and 78 spds. £3 14 4
33⅓, 45 and 78 £7 3 4

PLESSEY 3-speed Auto-changer unit £33 13 0

RECORDING TAPE

Soundmirror	£1 5 0
E.M.I. (Hi-Co)	£1 15 0
(Med-Co)	£1 15 0
Type 57 3250ft.	£6 0 0
600ft. 5in. spool	£1 1 0
Durex (Scotch Boy)	£1 15 0
Philitape	£2 0 0
Empty spools	4 0 & 6 6

TEST GEAR

AVO

Models 7 and 8	£19 10 0
D.C. Minor	£5 5 0
Universal Minor	£10 10 0
Univ. Bridge	£26 0 0
Wide Band Signal Generator	£30 0 0
Valve Tester	£50 0 0
Electronic Testmeter	£40 0 0

PIFCO Radiometer £1 7 6

TAYLOR
ALL THE NEW TAYLOR TEST-GEAR IN STOCK AND AVAILABLE ON H.P. TERMS.
Send S.A.E. for catalogue and terms.

Only with **CO-AX** *R.F.* **CABLES**

AIR-SPACED • ARTICULATED

THE LOWEST EVER CAPACITANCE OR ATTENUATION

IMMEDIATE DELIVERIES

SPECIALISTS IN AIR SPACED ARTICULATED CABLES SINCE 1929

TRANSRADIO LTD
CONSULTING TO THE GOVERNMENT
138A CROMWELL ROAD LONDON SW7
ENGLAND

LOW ATTEN TYPES	IMPED OHMS	ATTEN dB/100ft at 30 Mc/s	LOADING for 30 Mc/s	O.D."	
A 1	74	1.7	0.11	0.36	
A 2	74	1.3	0.26	0.44	HIGH POWER FLEXIBLE
A34	73	0.6	1.5	0.88	
LOW CAPAC TYPES	CAPAC mmf/ft	IMPED OHMS	ATTEN dB/100ft at 30 Mc/s	O.D."	
C 1	7.3	150	2.5	0.36	
PC1	10.2	132	3.1	0.36	PHOTOCELL CABLE
C11	6.3	173	3.2	0.36	
C 2	6.3	171	2.15	0.44	
C22	8.5	184	2.8	0.44	
C 3	5.4	197	1.9	0.64	
C33	4.8	220	2.4	0.64	VERY LOW CAPACITANCE
C44	4.1	252	2.1	1.03	

INTRODUCE

LEDEX

ROTARY SOLENOIDS & CIRCUIT SELECTORS

THE N.S.F.-LEDEX ROTARY SOLENOID is a compact, robust and efficient electro-mechanical device which provides a powerful snap-action rotary movement of substantially constant torque over the whole of the angular stroke.

The Rotary Solenoid was originally developed in the United States during World War II as the result of an urgent demand for a dependable bomb release with a high speed action. In the course of long and extensive use in many types of American fighter and bomber aircraft, it proved itself capable of standing up to all the arduous working conditions imposed upon it.

Evolution of the Rotary Solenoid was soon afterwards followed by the development of the LEDEX CIRCUIT SELECTOR, which employs the Rotary Solenoid in conjunction with OAK Switch sections. Many thousands of these units have since been embodied in a wide range of equipment using remote control switching.

In arriving at the decision to manufacture LEDEX ROTARY SOLENOIDS and CIRCUIT SELECTORS in Great Britain, N.S.F. were inspired by the fact that the large quantities that have been produced in the United States have been giving reliable and efficient service over an extensive period.

Besides achieving success in bomb release mechanisms, the LEDEX ROTARY SOLENOID has subsequently been employed with great success in aircraft and automobile radio equipment; sports-

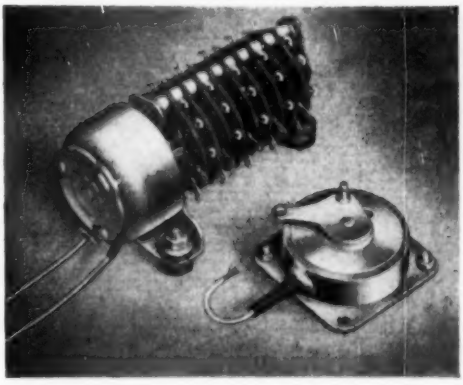

ground scoreboards; totalisators; accounting machines; machine tool controls; co-axial switch drives for television, tele-communications and radar; hydraulic valve operation; and auxiliary fuel tank release apparatus on jet fighter planes.

We at N.S.F. are confident that these and all present applications of LEDEX ROTARY SOLENOIDS and CIRCUIT SELECTORS represent a very small percentage of the total potential uses in both the mechanical and electronic fields. We therefore earnestly invite all Engineers who feel they could make use of these devices in any project they may have under development to contact us, in order that they may have full benefit of our accumulated experience.

Sole Licensees of G. H. Leland, Inc., Dayton, Ohio, U.S.A.

N.S.F. LIMITED · KEIGHLEY · YORKS

Phone: KEIGHLEY 4221/5. Grams: ENESEF, Keighley

London Office: 9 Stratford Place, W.1. Phone: Mayfair 4234

'Let's have "THE GONDOLIERS" AGAIN!'

Whatever your favourite piece of music, the Soundmirror will record it and play it back for you again and again. There is no end to the thrills which this new magic entertainer can bring. It will record the humorous patter of your favourite comedian, the art of the orator, the fun of a party or important family occasions like weddings. It will play them back with perfect fidelity immediately it is recorded and as often as you wish. Unwanted recordings are automatically erased as new ones are made and the magnetic tape used time and time again.

MODELS FROM £69.10.0 exclusive of microphone.

Manufactured under agreement with the Brush Development Co., of the U.S.A. Licensed under the Brush Development Co., the Brush Crystal Co., Magnetone Inc., and Thermionic Products Ltd. Patent No. 454595 and others; and patents pending in all the principal countries of the world.

THE **Soundmirror**

MAGNETIC TAPE RECORDER

Now available in England—the book "Magnetic Recording" by Dr. S. J. Begun. A comprehensive treatise. Price 25/- postage 9d. extra.

Call on your local radio dealer and hear your own voice recorded or write for literature or a demonstration by appointment to the manufacturers.

THERMIONIC PRODUCTS LTD.

(Division TM WW), Hythe, Southampton. 'Phone: Hythe 3265

London Showrooms: **Morris House, Jermyn Street, S.W.1**

Telephone: Whitehall 6422 (5 lines). Sales and Service Centres: Manchester, Birmingham, Bristol, Leeds, Newcastle, Glasgow, etc.

THE

Wharfedale

10" BRONZE Speaker

TODAY'S PRICE **69/6**

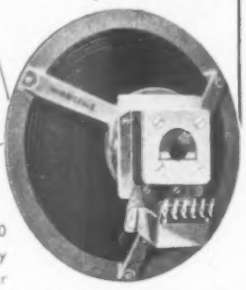

With a flux density of 10,000 lines the speaker is in every respect equal to the pre-war GOLDEN unit. It is fitted with a wide response cone with bakelised apex: maximum input 6 watts on baffle, 8 watts in reflex cabinet. Speech coil 2-3 ohms or 12-15 ohms. Fitted with heavy die-cast chassis. Transformer extra.

Made and guaranteed by

WHARFEDALE WIRELESS WORKS

BRADFORD ROAD, IDLE, BRADFORD, YORKS

'Phone: Idle 461

BRIERLEY DIAMOND MICROARMATURE PICK-UP

This new pick-up has many noteworthy characteristics, some of which are listed below:—

1. The mass of the moving parts is less, we believe, than in any other pick-up of any type—other than our own Ribbon, which is, of course, unique.
2. The output voltage—about 1·25th v.—is high enough to cause no trouble.
3. It is sufficiently robust to be used by any reasonably intelligent and careful family.
4. The use of a diamond point has, *inter alia*, the enormous advantages that a very large number of records may be played with negligible point wear. This results in a sustained "new" performance together with the elimination of that mental irritation at the gradual and perceptible "falling off" unavoidable with less wear-resistant points.
5. Organised production on a reasonable scale should give us a satisfactory "spares" and repair service and has enabled us to produce this pick-up at a price which many may at first have believed to be either a mistake or a printer's error.

Photograph of A. Standard Needle, B. Miniature Needle and C. Brierley Microarmature.

Pick-ups, types JB.P.A.ID (78) and JB.P.A.IMD (LP), £6.6.0. Purchase Tax, £2.12.-.

Mumetal Coupling Transformer, type JB.T.A, £1.5.-.

Full details sent on request.

J. H. BRIERLEY Gramophones and Recordings LTD.

KIRKBY TRADING ESTATE LIVERPOOL

Measurement of Magnetic properties of Radiometal Stator Laminations by A.C. Potentiometer.

Routine Factory testing of Mumetal toroidal cores.

Precision measurement of magnetic characteristics of toroidal Mumetal cores by the Ferrometer.

Technical Control

The key to the consistent excellence of TELCON Magnetic and Special-purpose Alloys.

Projection Microscope in use in Metallographic laboratory.

Precision measurement of X-Ray difraction pattern.

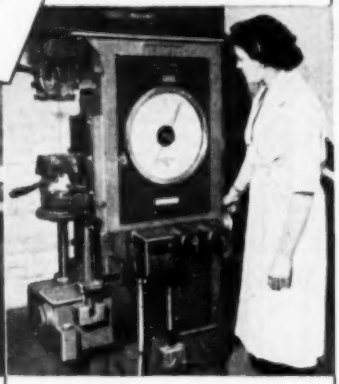

Automatic testing of physical characteristics of Telcon wire specimens.

Close technical control of production is an all-important factor in the manufacture of Telcon Metals. Accurate tests and measurements are made at various stages in the course of production and the above illustrations show a few of the many routine examinations conducted in our well-equipped laboratories.

MAGNETIC ALLOYS—Mumetal, Radiometal, Rhometal, H.C.R., Permendur, R2799, 36/64, Dust.
RESISTANCE ALLOYS—Pyromic, Calomic, Telcuman, Telconstan, Telconal
SPECIAL ALLOYS—Thermostatic Bimetals 140, 400, 15, Telcoseal, Invar, Beryllium-Copper.

TELCON METALS

THE TELEGRAPH CONSTRUCTION & MAINTENANCE CO LTD

HEAD OFFICE: 22 OLD BROAD STREET, LONDON, E.C.2. *TELEPHONE:* LONdon Wall 7104
ENQUIRIES TO: TELCON WORKS, GREENWICH, LONDON, S.E.10. *TELEPHONE:* GREenwich 3291

TELCON

Model 1200 B Oscilloscope with model 1400 B Alignment Signal Generator

Weight 18 lbs. Size 7" x 8" x 9"

D. C. OSCILLOSCOPES

Model 1200 B	Model 2000
Tube dia. . . . . 2¾"	Tube dia. . . . . 6"
Frequency Response . . . . . D.C-100 Kc/s	Frequency Response . . . . . D.C-100 Kc/s
Deflection Sensitivity . . . . . 7 mV/mm.	. . . . . 1 mV/mm.
Time Base 5c/s-20 Kc/s in 5 ranges	. . . 30 secs. 100 Kc/s

Write for specifications to

INDUSTRIAL ELECTRONICS

Makers of
Industrial Controls and Precision Instruments

99, GRAYS INN RD., LONDON, W.C.1

Telephone : Holborn 9873/4

Masteradio

'VIBRATORPACK'

EARTH FREE

& Silent as the Stars

FOR
RADIO RECEIVERS
TRANSMITTERS
AMPLIFIERS
PUBLIC ADDRESS SYSTEMS
SCIENTIFIC APPARATUS
EMERGENCY POWER SYSTEMS

Masteradio Vibratorpacks convert low voltage DC to H.T. with minimum loss of power.

Please write for full details.

MASTERADIO LTD.

FITZROY PLACE - - LONDON, N.W.1

The

"RD BABY DE-LUXE" Amplifier

Accepted as the most outstanding low priced amplifier available in this Country, the "Baby" provides the answer for the man of modest means who requires High Fidelity Reproduction.

Within its power limitations, which are entirely adequate for normal domestic use, its performance matches the majority of high priced amplifiers on the market.

In keeping with all "RD" products the "Baby" is individually built by craftsmen, and represents the best in British Workmanship.
Price, complete with pre-amplifier and engraved control panel, **£17 10 -.**

A detailed specification will gladly be forwarded on request, and a demonstration may be heard at any time. Also obtainable in London from : Webb's Radio, The Gramophone Exchange, Tele-Radio, City Sale and Exchange and Holley's Radio Stores.

Trade and Export enquiries invited.

ROGERS DEVELOPMENTS Co.

"Rodevco House," 116 Blackheath Road,
GREENWICH, S.E.10.

Telephone : TIDeway 1723

GOVERNMENT SURPLUS

LONDON CENTRAL RADIO STORES

DELIVERY FROM STOCK

FLUXMETERS Model WY0023

Calibrated in three ranges, 500-1,000, 1,000-2,000, and 2,000-4,000 Gauss. Direct reading. Complete with polarity indicator and probe for minimum gap of 1¼in. Brand new in portable wood case with carrying handle. 12in. × 9in. × 5½in. Less battery.

£4.5.0 Carr. and pkg., 5/-.

TELE F. DESK TELEPHONE complete with Amplifier

New condition. In two separate units. Suitable for office and many other purposes. Battery operated. Complete in transit case. Carr. and pkg. 3/6 **£5.17.6**

VIBRATORS

2-volt, Type R70C. 7-pin self-rectifying. Output 200 v. at 60 mA. Made by Electronic Laboratories Inc. **7/6.**

Mallory, Type 650, 6-volt 4-pin American base. **7/6.**

Mallory, Type G629C. 12-volt, 4-pin American base. **7/6.**

Owing to our large contract we are still able to supply

PHILCO 6-VALVE Reconditioned SETS

— UNIVERSAL MAINS

These superhet receivers have all been thoroughly overhauled at our works. Ready for immediate use and GUARANTEED. We have sold over 3,000 of these sets all over the country. If in London call and see them for yourself.

184/- **ALL-WAVE TABLE MODEL,** incorporating two-speed tuning and provision for normal aerial or dipole. Medium or dark walnut cabinet, size 18½ × 20 × 9½in. Really excellent performance.

115/- **LARGE TABLE MODEL,** in light walnut cabinet only, size 19 × 16 × 10½in., large dial in metres and frequency. Exceptional high gain using high "Q" IF transformers and special aerial circuit. Normal or dipole aerials may be used.

110/- **MEDIUM TABLE MODEL,** known as the "Cathedral Model," receiving all British and European stations with great clarity and freedom from interference. Normal or dipole aerial input. Available in light or dark oak. Cabinet size, 19 × 14 × 10in.

Plus **10/6** per set carriage and packing.

NEW TRANSMITTING AND S.P. VALVES

ATP4 .. **9/6** VT136 .. **9/6** 1299A .. **7/6** 954 Acorn **4/6**

WALKIE-TALKIE Transmitter and Receiver CHASSIS, Type 38 Mk. II. Range 7.4-9 Mcs.

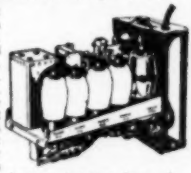

We have purchased a limited number of these sets all in new condition. Requires 3 v. L.T., 120/150 v. H.T. Complete with four APR12 one ATP4 valves, one pair throat mikes, pair headphones and aerial, also battery junction box. In metal case. Free wiring diagram. Batteries supplied. **£4.10.0**

Carr. and packing 2/6.

MARCONI *De Luxe* 8 VALVE

MOTOR TUNING PRESS-BUTTON ALL-WAVE TABLE RADIO SUPERHET

Output 8 watts from 61.6 and High-gain Pick-up input. In use with the latest high-fidelity types. Together with a host of Push-button stations this makes a most useful receiver. You can cruise round the dial on the motor tuning. This type of set is not available on the home market, and we are fortunate in being able to offer it to readers. Thoroughly overhauled. Complete with maker's Instruction Book. For callers only. Price **£23.10.0**

WANTED URGENTLY

GOOD USED or NEW EQUIPMENT

AR88s · D.B. 'SCOPES · METERS and all kinds of TEST GEAR · CONVERTERS, etc.

UNISELECTOR SWITCHES

Full Wipers

3-bank **19/6**
4-bank **35/-**
6-bank **35/-**
8-bank **47/6**

Half Wipers

4-bank, **27/6**; 6-bank, **27/6**; 8-bank, **42/6**

Have various applications, including automatic tuning circuit selection, etc. Operates on 25-50 v.

TELESONIC 4-VALVE BATTERY PORTABLE

(Fixed Range.) Type YA4915

Includes three XH and one XP Hivac midget valves. Can be adapted for Deaf Aid or Midget Receiver, but we do not supply information on this point. Batteries equired, 3 v. L.T., 97 v. H.T. In metal case, size 5½ × 7 × 2in. Weight 4 lb., less batteries. Carr. and pkg., 2/6. **45/-**

(Illustration shows chassis partly removed from cabinet.)

SIMPSON MOVING COIL OHM-METER

Two-range 0-2,000 ohms, 0-200,000 ohms. Size 3in. × 5in. P.and Pkg. 2/6 **42/6**

D.C. Motors, 24 v. approx. 3in. square. Carr. pd. **10/6.**
A.C. Unshrouded Motors 220 v., 3in. square, spindle ⅜in. × ⅜in. long. Useful for electric signs, fans, etc. **15/6,** post free.
New Blower Motors, 24 v. **22/6,** post and pkg. 1/6.
Self-energising Headphones, less headbands. **6/6** pr., post and pkg. 1/-.
Milliammeters. Centre zero 0-30, 3in. dia. **10/-,** post and pkg. 1/-.
Voltmeters. Centre zero 0-3 and 0-30, with testing point attached, 3in. dia. **22/6,** p. & p. 1/-.
Tannoy Hand Microphones, with switch. **8/6,** p. & p. 1/-.

Midget Volume Controls, 30 ohm, wirewound. **2/6,** p. & p. 6d.
Volume Controls, 8,000 ohm wirewound. **2/3,** p. & p. 6d.
New Morse Keys. 3/6, p. & p. 9d.
Moving Coil Inserts, 30 ohm. Suitable for miniature speakers and microphones. 2in. dia., 1½in. deep. **4/6.**
Rotary Converters, 12 v. D.C. output, 275-500 v. D.C. Size 7½ × 4½ × 5in. Weight approx. 10 lbs. **21/6,** carr. & pkg. 2/6.
Ex-G.P.O. Plug and Jack. 2/9, p. & p. 6d.

NEW INERT CELLS

No acid or charging required. Suitable for battery sets, electric bells, etc. 1.5 v. **2/10.** Post 9d.

Phosphor Bronze Stranded Aerial. Ex-Admiralty. 100ft. coils. **6/6,** p. & p. 1/-.
Garrard Motor, 12in. Turntable and Magnetic Pick-up. 95/-, carr. and pkg. 7/6.

ELECTRO-MAGNETIC COUNTERS FRESH CONSIGNMENT JUST ARRIVED

Ex-G.P.O., every one perfect, electro-magnetic, 500 ohm coil, counting to 9,999, operated from 25 v. 50 v. D.C., many industrial and domestic applications. **ALL EQUAL TO NEW.** Post and pkg. 9d. **15/-**

NEW NIFE ACCUMULATORS. 2.5 v. 2½ amp./hours for 8 hours. Size 3 × 4¼ × 1¼in. (Flat) **6/6.** Post and packing 9d.

WALKIE-TALKIE (Transmitter-Receiver), Type 48 (Mk.1*). Brand new

Made by Emerson.

Frequency coverage 6-9 Mc/s. Comprises transmitter/receiver with 10 valves and one 1-Mc/s crystal, in metal case with waterproof cover, sectional rod aerial in satchel. Spare valve case, complete with 10 spare valves, key assembly, hand microphone, two headsets, one hand generator (10 watts) with tripod as illustrated in April issue, two battery boxes, all essential connecting cables. The complete equipment, together with comprehensive instruction manual (inland only). Carr. and pkg. 15/6 **£21.10**

N.B. All carriage charges relate to Inland Orders only. ● We do not issue list or catalogues.

LONDON CENTRAL RADIO STORES, 23 LISLE ST. (GERrard 2969) LONDON, W.C.2

Closed Thursday 1 p.m. Open all day Saturday and weekdays 9 a.m. — 6 p.m.

FERROXCUBE

FERROMAGNETIC FERRITE

FOR TELEVISION

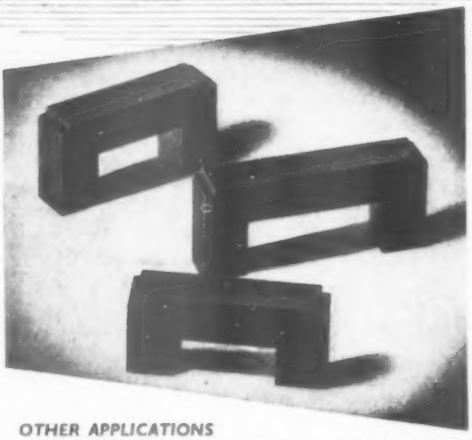

THE improvement in television components, with their smaller size and greater efficiency, is largely due to Ferroxcube, the new Mullard magnetic core material.

The uses of Mullard Ferroxcube in the production of TV components fall into these three main groups:

LINE OUTPUT TRANSFORMER CORES

Since the advent of wide-angle television tubes, with the accompanying demand for increased E.H.T. supplies, the need for line output transformers of the highest possible efficiency has been greater than ever. Mullard Ferroxcube, with its low iron losses, completely fulfils this need — also facilitating the assembly of small, compact transformer units by means of solid, non-laminated U-shape cores.

DEFLECTION COIL YOKES

Mullard Ferroxcube cores in ring form are ideal for producing the magnetic circuit around deflection coils. Used in this way, Mullard Ferroxcube makes possible the construction of efficient deflector coils with a high Q factor. In order to simplify assembly problems, these ring cores are supplied either in the form of a complete circle, as two semi-circles, or as castellated yokes.

LINEARITY AND PICTURE WIDTH CONTROLS

Mullard Ferroxcube can very conveniently be extruded into rods and tubes. In this form it is ideal for use in linearity and picture width controls, providing a smooth control in a compact assembly.

OTHER APPLICATIONS

In addition to its uses in television receivers, Mullard Ferroxcube is also being widely employed in line communications, radar, and other specialised electronic equipments. The purposes for which it is already being most successfully applied in such equipments include filter networks, wide band transformers, magnetic amplifiers, and pulse transformers.

PLEASE WRITE FOR FULL DETAILS

Mullard **Mullard FERROXCUBE**

FERROMAGNETIC FERRITE

MULLARD LIMITED CENTURY HOUSE SHAFTESBURY AVENUE LONDON W.C.2.

MR376

M. R. SUPPLIES Ltd.

Offer from stock the following brand new (or otherwise perfect) material. All prices nett. Immediate despatch.

FRACTIONAL H.P. MOTORS, brand new by B.T.H. 230/250 v. A.C./D.C., 1/20th h.p. Continuously rated. 5,000 r.p.m. Here is a fine F.H.P. Motor which will do a good job of work: sewing machines, projectors, small lathes, pumps, grindstones, small drills, mixers, agitators, useful to everybody. Approx. size 3½in. × 3½in. with shaft projecting approx. 1½in. Real opportunity. **47 6** (despatch 1/6). It is important to note that these are the genuine product of B.T.H. and not conversions.

MAINS GEARED MOTORS. 200/240 v. A.C./D.C. 1/100th H.P. 80in. long, 4½in. dia. Final speed 700 r.p.m. Double-ended final shaft, sturdy construction. New, ex-Admiralty. **£4 17 6** (despatch 4/6). **HOOVER SHADED POLE INDUCTION MOTORS**, 200/250 v. A.C. Model SP 302. Body 2¾in. × 3¼in. with ¼in. shaft proj. 1in. 900 r.p.m., very good. **26**/- (des. 1/-).

MINIATURE MOTORS, for models, etc., 12 v. D.C. (up to 20 v. A.C.). Note the small size, 2½in. long, 1¼in. dia., fitted removable pulley, with internal adjustable governor, approx. 3,000 r.p.m., good power. **12 6** (des. 9d.).

CAMBRIDGE THERMO-COUPLES (Vacuo Junction). Useful range: 2.5 mA., 5 mA., 10 mA., 20 mA., 25 mA. and 50 mA. Full data on each container. Brand new: Uncapped **7 6**, capped with 4-pin base **9 6** (des. 6d.).

TUBULAR HEATERS, 230/240 volts, 240 watts. Length 4ft. Very efficient for the low construction and ideal for laboratories, workshops, greenhouses, lofts, garages, etc. A good buy, free issue. **27 6** (des. 2/6 each). Also **PANEL HEATERS**, 220/240 v. 1,250 watts, 24in. × 13in. **35**/- (des. 5/6 each).

DAMP-PROOF PLUGS AND SOCKETS, with screw-on 2-pin 5-amp. plug and "out of use" cover. Ideal for use in open air lamp situations. **2 9** (des. 6d.).

HIGH DUTY BOOSTER TRANSFORMERS (G.E.C.). 190/250 volts in 10 v. taps. Loading continuous 4 KVA. In steel housing 16in. high overall, 9½in. × 12in. with handwheel selector. A few, in new condition, at **£11 10**/- (despatch England 10/-).

HIGH DUTY STEP-DOWN TRANSFORMERS, prim. 250 v. 50 c. 1 ph. Sec. 50 volts 50 amps. (cont.) in steel housing 18in. × 13in. × 14in. with bracket. **£7 10**/- (des. England 8/6).

SANGAMO TIME SWITCHES, synchronous 200/250 v. 50 c. Capacity 20 amps. Min. period between operations 15 mins. Model A provides one on-off sequence per 24 hours and has day-omitting device. Model B is the same style but has three on-off sequences in 24 hours but no day-omitting device. Both in black plastic housing, 6½in. × 5½in. with window. Either **£5 5**/- (des. 1/6). Also **SANGAMO SHORT INTERVAL PROCESS TIMERS**, synchronous 200/250 v. 50 c. Single-pole switch capacity 5 amps. Operation sequence periods adjustable for 5, 10, 15, 20, 30 and 60 mins. and timed circuit period continuously adjustable from 2 to 75 secs. for any of the sequence periods. In same style as above. Very valuable instruments of almost unlimited application. **£7 5 6** (des. 1/6).

KNIFE SWITCHES. S.P.C.O. quick M. & B., 10 amps., on base 7in. × 1¼in. **7 6** (des. 6d.).

THERMOSTATS, ex A.M. frost protection, set at 40 deg. F., cut at 49 deg. F., capacity 1.5 amp. 1/50 v. **4 6** (des. 6d.). Capillary type, tube 7ft. long, with 9in. phial, range 25-90 deg. F., cap. 5 amps. for air or immersion **17 6** (des. 1/-). Room type, and for greenhouse, by British Thermostat Co., range 40-80 deg. F., 10 amps., differential 4 deg. **45**/- (des. 2/-).

HIGH DUTY RECTIFIER UNITS (S.T.C.). Input 220/240 v. 50 c. 1 ph. D.C. Output 36 v. 30 amps. Rigid spec., ambient 50 deg. C. Metal rectified, fitted switch and fuses and thermostatic control. Size 40in. high, 21in. × 18in., weight approx. 3 cwt. **£28** (des. England 20/-).

Details on request. Kingshed Bridge Meggers, Ohm meters, Lighting Dimmers, Stuart Electric Pumps, Pressure Speaker Units.

M. R. SUPPLIES Ltd., 68 New Oxford Street, London, W.C.1

Telephone: Museum 2958

to-day there is no better television than

AMBASSADOR

ILLUSTRATED LITERATURE FROM

AMBASSADOR RADIO & TELEVISION

BRIGHOUSE YORKSHIRE

P.P.A.

The BPL UNIVERSAL TEST SET

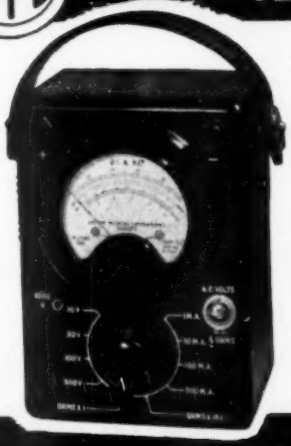

★ Leather carrying handle.

★ Easy to read 2-colour dial.

★ 1,000 ohms per volt for D.C. and A.C.

★ Two ohms ranges operated from large internal battery. Zero setting holds over long periods.

★ Captive head terminal connectors for all ranges.

★ Readings accurate to 2%.

★ Rotary switch selects ranges clearly marked.

★ Solid bakelite moulded case.

FOR EASY SERVICING

The B.P.L. Universal Test Set is designed for the easy servicing of all electrical appliances, and radio sets. The ranges have been selected to cover all values to be expected in such work. Radio engineers will appreciate the provision of two ohms ranges. This enables the accurate measurement of low resistance as experienced in motors, windings of transformers, switches, fuses or radio tuning coils, speakers, filaments of valves etc., as well as the higher values of resistors.

For the measurement of A.C. current a 3-range current transformer is available which fits directly on to the terminals of the instrument. Ranges 0.1, 1 and 10 amps. List price 39/6.

LIST PRICE

£8.17.6 including test leads. Subject to Trade Discount.

Also supplied:

B.P.L. Super Rangers and D.C. Test Sets.

LONDON STOCKIST:

M.R. SUPPLIES LTD., 68, New Oxford Street, W.C.1.

BRITISH PHYSICAL LABORATORIES

HOUSEBOAT WORKS · RADLETT · HERTS · Telephone: RADlett 5674-5-6

Recognised as the Most Reliable Valveholders

McMURDO Moulded Valveholders

POLYTHENE PUSH-ON COVER

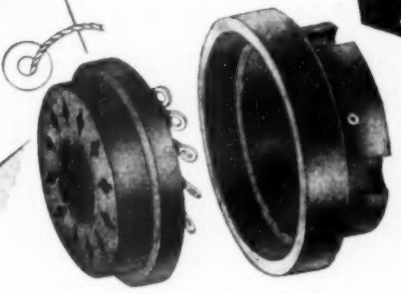

B12A—Duodecal

FOR CATHODE RAY TUBES

Ref. No. **B.12 U**—moulded in **Phenol-Formaldehyde with Polythene Cover**

" " **B.12 U.1**— " " " " " without cover

Wholesale Enquiries:—CYRIL FRENCH LTD., HIGH STREET, HAMPTON WICK, MIDDLESEX · KIN. 2240

Manufacturers' Enquiries:—THE McMURDO INSTRUMENT CO. LTD., VICTORIA WORKS, ASHTEAD, SURREY ASHTEAD 3401

SALWAY MORGAN & CO LTD
SM
WEST QUAY ROAD, POOLE, DORSET

EXCEPTIONAL OFFER !

(EXPORT ONLY)

UNUSED U.S.A. RADAR EQUIPMENT

TYPE S.Q.	All equipment is tropical packed.
TYPE S.G.A.	Complete range of Equipment, Stock and
TYPE S.G.I.	Tender Spares ; large stocks available.

A.M. RADAR EQUIPMENT

TYPE H2S.	Reconditioned, with A.I.D. Certificates.

INSTALLATION AND MAINTENANCE SERVICE AVAILABLE

SALWAY MORGAN & CO. LTD.

'PHONE 840, 841, 842.
'GRAMS 'SERVICES, POOLE' POOLE DORSET

ETA TOOL CO

(LEICESTER) LTD

MANUFACTURERS OF

AUTOMATIC AND HAND COIL WINDING MACHINES

We invite enquiries for an entirely NEW MACHINE for LAYER WINDING for coils up to 12" long and 10" diameter.

Wire gauges from 14 S.W.G. to 30 S.W.G.

29A WELFORD ROAD LEICESTER

Phone 5186

-towards perfection-

LOWTHER :-

TUNERS

AMPLIFIERS

WHISTLE FILTERS

CORRECTORS

etc., etc.

Latest list now available, copy gladly sent upon request.

THE LOWTHER MANUFACTURING CO.

(The Laboratory Production Unit)

Lowther House, St. Mark's Road, Bromley, Kent. RAV. 5225.

This MARKS THE SPOT...
FOR AERIAL NEWS AND VIEWS

Why the 'X' . . . ?

THE design and development of the "Antex" aerial by our Research Department constituted a notable advance in aerial technique. The targets aimed at in our continuous aerial research programme are, better performance, simplicity of construction, lightness in weight and reasonable cost. The "Antex" proved greatly superior in all these qualities to the "H" aerial and in fact has other incidental advantages which were at the time unforeseen, including exceptional ease from the installation point of view. Since the "Antex" aerial was released to the trade, some two and a half years ago, the response has been overwhelming. Ever since that time we have been doing our best to fulfill the demand but regret that material restrictions have made it impossible for us to satisfy everyone. Nevertheless our efforts have resulted in some 200,000 "Antex" aerials being delivered in this comparatively short space of time, and throughout the country dealers have now confirmed that the "Antex" is a great step forward in aerial technique. We would thank all those who have troubled to write to us. Their reports add to the store of practical knowledge which we can share with other users. Among letters recently received are some giving details of remarkably good reception with the "Antex" in fringe areas, such as Southampton, Middlesbrough, Carlisle, etc.

There is a model suitable for every location. Full details in leaflet No. E/50/W sent on request.

Other Antiference Aerials

Single Dipole, Dipole and Reflector, Three Element arrays, etc.; also Radio aerials including "Exstat" Anti-static Aerials; "Silmount" for the flat dweller, and the "Autoaerial" for the car.

ANTIFERENCE *Aerials*

ANTIFERENCE LIMITED 67 BRYANSTON ST LONDON W.1

Beam Tetrode Subminiature Amplifier

XFW30

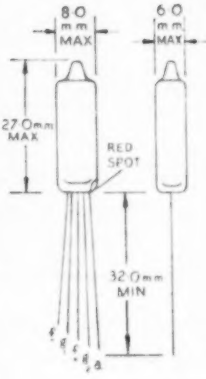

The XFW30 is the first of a new series of very small, flat subminiature valves of Beam Tetrode construction.

The maximum cross-section is only 8mm. by 6mm. and the normal filament current is 12½ mA.

These features in conjunction with the high efficiency of the XFW30 permit still greater scope to the designer of the most modern hearing aids and other small electronic equipment.

TYPICAL OPERATION

Filament Voltage . .	0.625v
Filament Current . .	12½mA
H.T. Supply Voltage	22½v
Anode Load	1 to 2MΩ
Screen Resistance . .	3MΩ
Stage Gain . .	32

HIVAC
THE SCIENTIFIC VALVE
BRITISH MADE

GREENHILL CRESCENT,
HARROW-ON-THE-HILL, MIDDLESEX

Telephone: HARrow 2655

RADIO SUPPLY CO

Post Terms C.W.O. or C.O.D. No C.O.D. under £1

15 WELLINGTON ST., LEEDS 1

Postage 1/3 charged on orders under £3. Open to callers 9a.m. to 5.30p.m. Saturdays until 1p.m.

R.S.C. MAINS TRANSFORMERS

Fully Guaranteed, Interleaved, and Impregnated. Primaries 200-230-250v. 50c/s. Screened.

TOP SHROUDED, DROP THROUGH

260-0-260 v. 70 ma., 6.3 v. 3 a., 5 v. 2 a. 14/11
260-0-260 v. 80 ma., 6.3 v. 2 a., 5 v. 2a. 14/11
350-0-350 v. 80 ma., 6.3 v. 2 a., 5 v. 2 a. 16/11
350-0-350 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a. 19/9
250-0-250 v. 100 ma., 6.3 v. 4 a., 5 v. 3 a. 21/9
250-0-250 v. 100 ma., 6.3 v. 6 a., 4 v. 3 a., for R.1355 conversion 25/9
150-0-350 v. 100 ma., 6.3 v.-4 v. 4 a., C.T. 0-4-5 v. 3 a. 21/11
350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a. 25/9
350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a. 27/11

CLAMPED UPRIGHT MOUNTING

250-0-250 v. 100 ma., 6.3 v.-4 v. 4 a. C.T. 0-4-5 v. 3 a. 21/11
250-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., for R1355 conversion 21/11
300-0-300 v. 100 ma., 6.3 v.-4 v. 4a., C.T. 0-4-5 v. 3 a. 21/11
350-0-350 v. 100 ma., 6.3 v. 3 a., 5 v. 3 a. 21/11
350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a. 27/9

FULLY SHROUDED, UPRIGHT

250-0-250 v. 60 ma., 6.3 v. 2 a., 5 v. 2 a. Midget type 2½-3-3in. 16/9
250-0-250 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a. 18/9
350-0-350 v. 100 ma., 6.3 v.-4 v. 4 a., 0-4-5 v. 3 a. 24/9
350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a. 28/9
350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a. 31/-
350-0-350 v. 250 ma., 6.3 v. 6 a., 4 v. 8 a. 0-2-4 v. 2 a., 4 v. 3 a., for Electronic Eng. Televisor 65/-
425-0-425 v. 200 ma., 6.3 v.-4 v. 4 a. C.T. 6.3 v.-4 v. 4 a., C.T. 0-4-5 v. 3 a., suitable Williamson Amplifier 48/9
325-0-325 v. 20 ma., 6.3 v. 0-5 a., 6.3 v. 1.5 a. for Williamson Preamplifier 17/6

FILAMENT TRANSFORMERS

All with 00-250 v. 50 c/s., primaries: 6.3 v. 2 a., 7/6; 0-4-6.3 v. 2 a., 7/9; 12 v. 1 a., 7/11; 6.3 v. 3 a., 10/11; 6.3 v. 6 a., 16/9; 0-2-4-5-6.3 v. 4 a., 16/9; 12 v. 3 a., or 24 v. 1.5 a. 16/9

CHARGER TRANSFORMERS

All with 200-230-250 v. 50 c/s. Primaries: 0-9-15 v. 1.5 a., 12/9; 0-0-15 v. 3 a., 15/9; 0-9-15 v. 6 a., 21/9; 0-4-9-15-24 v. 3 a., 21/9; 0-9-15-30 v. 3 a. 22/9

SMOOTHING CHOKES

250 ma., 8-10 h., weight 12lb. 17/6
200 ma. 5 h. 100 ohms 7/6
100 ma. 10 h. 100 ohms 7/6
80 ma. 10 h. 350 ohms 5/6

50 ma. 50 h. 1,500 ohms (Williamson pre-amp.) 8/9

AUTO TRANSFORMERS

100 watts 100-200-230-250 v. 19/9

ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c/s 120 v. 40 ma. 7/11
1 0-0-1 0 v. 30 ma., 4 v. 1 a. 12/9

OUTPUT TRANSFORMERS

Midget Battery, Pentode 66 : 1 for 3S4, etc. 3/6
Small Pentode, 5,000 ohms to 3 ohms 3/9
Standard Pentode 8,000 ohms to 3 ohms 4/9
Multi ratio 40 ma.: 30 : 1, 45 : 1, 60 : 1, 90 : 1 Class B Push-Pull 5/3
Push-pull 8 watts 6V6 to 3 ohms 8/9
Push-pull 10-12 watts 6V6 to 3 or 15 ohms 15/11
Push-pull 10-12 watts to match 6L6, PX4, 6V6, etc., to 3-5-8 or 15 ohms speaker 16/11
Push-pull 15-18 watts to match 6L6, etc., to 3 or 15 ohms speaker 21/9

P.M. SPEAKERS. All 2-3 ohms: 5in. 11/9; 6in. 14/11; 8in. 14/11; 10in. 25/9.

M.E. SPEAKERS: 8in., 3 ohms, field 600 ohms, 12/9.

BATTERY CHARGER KITS

To charge a 6 v. or 12 v. acc. at 1.5 amps. Input 200-250 v., consists of mains trans., bridge, rectifier, ammeter, fuseholder, fuse, adjustable resistor and circuit, 35/-. Suitable black enamelled case, 10/6.

SPECIAL OFFERS

Fil. trans. (small), 220/240 v. input, 6.3 v. 1.5 a. output 5/9
Auto Trans. 0-200-230-320 v. 70 ma., with separate L.T. 6.3 v. 3 a. 7/6
Standard Output Trans. 5,000 to 3 ohms 3/9
25 mfd. 25 v. cans with clip 10d.
2,000 mfd. 15 v. Can Electrolytics 7/6
Accumulators, dry charged, 2 v. 10 a. H. 4/9
.0005 mfd. 2-gang variables (ex. E.M.I.) 5/9

RECEIVER CHASSIS, 16 s.w.g. aluminium (undrilled) 10-5½-2in., 3/6; 11-6-2½in., 3/11; 12-8-2½in., 4/11; 16-8-2½in., 6/9; 20-8-2½in., 7/11.

AMPLIFIER CHASSIS, 16 s.w.g. aluminium, (undrilled) 12-8-2½in., 7/11; 16-8-2½in., 10/11; 20-8-2½in., 13/6

MISC. ITEMS. Philips chokes 90 ma. 8 h. 100 ohms 3/11; Vol. Controls, 200 k., long spindle, 1/3 ea., 12/6 doz.; Ex-Govt. R1124 Units, less valves 10/9

SELENIUM RECTIFIERS. Ex-new equipment. 120-0-120 v. 60 ma., 4/6; 230 v. 50 ma. H.W., 4/9; 250/500 v. 60 ma. H.W., 6/9; 680 v. 30 ma., 6/9.

ELECTROLYTICS. Tubular 8 mfd. 350 v. 1/11; 8 mfd. 450 v. 2/3; Can 16 mfd. 450 v. 2/11; 24 mfd. 350 v. 2/11; 8-16 mfd. 450 v. 4/6; 12-12 mfd., 350 v., 3/3; 16-16 mfd. 450 v., 5/3; 32 mfd. 350 v. 4/3; 32 mfd. 450 v. 5/3; 32-32 mfd. 350 v., 6/6; 32-32 mfd. 450 v., 6/11.

FULL RANGE OF STANDARD COMPONENTS AVAILABLE AT KEEN PRICES, ALL GOODS GUARANTEED AND NEW, UNLESS OTHERWISE STATED. QUANTITY QUOTATIONS GIVEN FOR STANDARD TYPES OR SPECIAL MAINS TRANS. S.A.E. PLEASE WITH ALL ENQUIRIES. FULL STOCK LIST 4d. SPECIAL LIST FOR TRADE, 4d.

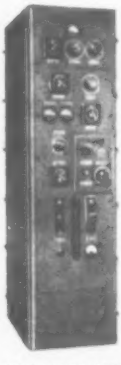

R.C.A. TRANSMITTER ET4336. Unused and reconditioned. This magnificent transmitter is complete in one totally enclosed rack and includes aerial tuning panel.

TUBE LINE UP: 807 CO/Buffer. Two 813 P.A. Two 805 P.P. Class B modulator. Four 866A rectifiers. Controls: Manual or remote. Power output, 350 watts. Frequency coverage normal. Normal 2-20 Mcs continuous. Frequency control. The transmitter has a detachable front panel for insertion of Wilcox Gay V.F.O. or Crystal Multiplier. 20-page manual and circuit diagram with each equipment. Every instrument is air tested and guaranteed perfect. Also available Wilcox Gay V.F.O., Crystal Multiplier, speech amplifier (British made) with 500 ohm output suitable for use with ET4336. Valves available for ET4336 in large quantities, 813, 805, 866, 807.

ET4336 SPARES: We carry very large stocks of essential maintenance spares and invite enquiries.

RECEIVERS AR88D and L.F. Available with A.I.D. certificate, £75 each.

COMPLETE SETS CRYSTALS AND COILS for BC611 and BC711 handie talkies, SCR640, etc.

TELESCOPIC CAR AERIAL, 7ft. with 10ft. shielded, lead coax connector. 15/- each.

EVERSHED AND VIGNOLL BRIDGE MEGGERS, 250 volt. £21 each.

BC610 P.A. COILS, in complete sets. 7 Coils bulk quantities only supplied.

McELROY-ADAMS MFG. GROUP LTD.

Sole concessionaire: U.K. for Hallicrafter Communication Equipment

46, GREYHOUND ROAD, LONDON, W.6

Cables: Hallicraft, London Phone: Fulham 1138

Dept. W.W.

ALEC Davis SUPPLIES Ltd.

18 TOTTENHAM COURT ROAD, LONDON, W.1.

Tel.: MUSeum 2453/4539

Shop Hours: Monday-Friday 9 — 5.30 Saturday 9 — 1

RELAYS

D.C. COIL RESISTANCE

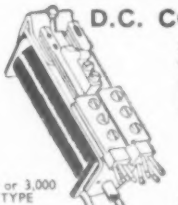

600 or 3,000 TYPE

3,000 TYPES: 1.9Ω to 80,000Ω
600 TYPES: 0.4Ω to 9,200Ω.

ALSO LARGE STOCKS OF DOUBLE & TRIPLEWOUND AND SLUGGED COILS.

CONTACTS

3,000 TYPES: up to 8 sets.
600 TYPES: up to 4 sets.

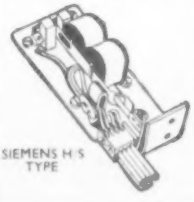

SIEMENS H.S. TYPE

3,000 TYPES: Make (M), Break (B), in Twin-silver, Twin-platinum, Dome-silver (2 amp.), Tungsten (5 amp.), and Flat-silver (8 amp.). Change-Over (C), in all but Tungsten: Make-Before-Break (K), in Twin-silver and Twin-platinum.

600 TYPES: (M), (B) and (C), in Twin-silver and Twin-platinum.

SPECIAL

High resistance slugged coils (up to 10,000 OHMS with 1" slug) now available.

FOR HIGH-FREQUENCY INSULATION

specify

'FREQUELEX'

The Tuning Coil shown is supported by our "FREQUELEX" Ceramic Rods, and forms part of a 200 K.W. Radio Transmitter. This is only one of many applications where Rods made to close limits are required.

We specialise in the manufacture of Ceramic Rods and Tubes of various sections in several classes of materials over wide dimensional ranges.

The Principal Materials are :—

1. Porcelain for general insulation.
2. Frequelex for High Frequency insulation.
3. Permalex and Templex for Capacitors.

The degree of accuracy depends on the size of the Rod or Tube, but the standard degree of accuracy is outlined in the Inter Service Component Manufacturer's Council—Panel R Specification embodied in our Catalogue of Radio Frequency Ceramics, copy of which will be sent on request.

Large Rods up to 44" long and 1¼" square are used as supports for Tuning Coils, etc.

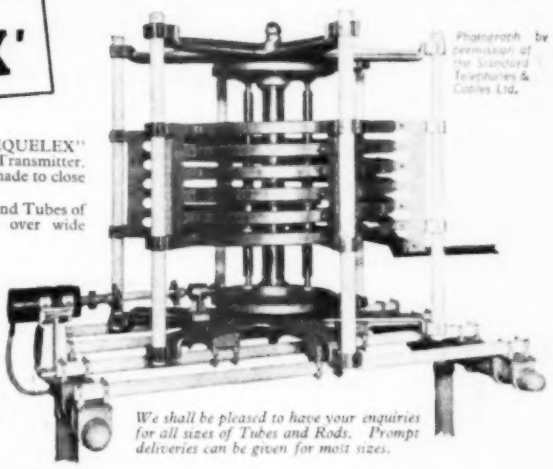

Photograph by permission of the Standard Telephones & Cables Ltd.

We shall be pleased to have your enquiries for all sizes of Tubes and Rods. Prompt deliveries can be given for most sizes.

Bullers LOW LOSS CERAMICS

BULLERS LIMITED, 6 Laurence Pountney Hill, E.C.4. Phone: MANsion House 9971 (3 lines) Grams: Bullers, Cannon, London

81.48

REFLECTOGRAPH

MAGNETIC TAPE RECORDER DECK

—for easiest operation and truest reproduction!

Robust mechanical construction keeps the unit vibration-free. Entire absence of "wow" and "flutter". No background hum. Choice of two or three heads. Two recording tracks—side by side. Three motors. Tape speeds: 3¾" and 7½" per second. Playing time 60 mins. per track at 3¾" per second; 30 mins. per track at 7½" per second. Rewind time: 1½ minutes.

TAPE THREADING NOW TAKES LESS THAN ONE SECOND!

TO CHANGE TAPE LIFT THROUGH SLOT —*what could be simpler?*

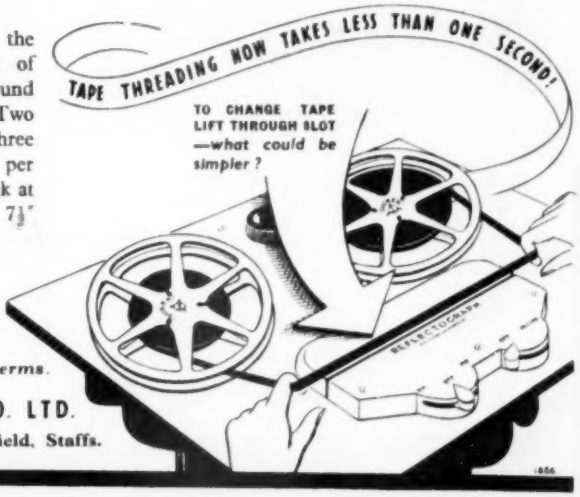

Price **£36** RETAIL

Trade Enquiries Invited

Write today for full details and trade terms.

RUDMAN, DARLINGTON & CO. LTD.

Clyde Works, Litchfield Road, Wednesfield, Staffs.

856

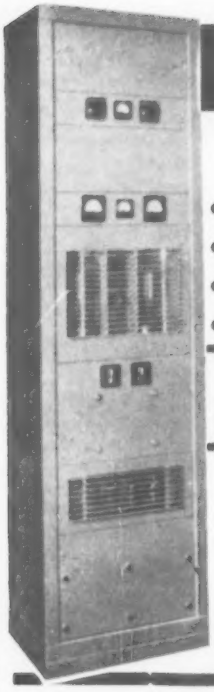

POWER AT AUDIO FREQUENCY FOR INDUSTRY & RESEARCH

THE SAVAGE MARK II KILOWATT AMPLIFIER

FACTS TO IMPRESS:

- The Savage Amplifier was used recently for echo-sounding to the bed of the deepest ocean.
- Used by aircraft manufacturers as a source of power for vibration tests.
- Used as variable frequency power source for machine tools.
- This Amplifier may have a direct application to your problems. Ask us for full details.
- Amplifiers used in Broadcast Relay networks throughout the country each feed several thousand loudspeakers.
- Invaluable for instrument calibration, transformer testing, transmitter modulation, etc.

FEATURES

NEGATIVE FEEDBACK OVER 3-STAGES
NO ELECTROLYTIC CONDENSERS ARE USED
ALL VALVES ACCESSIBLE FROM FRONT OF RACK
UNIQUE CONSTRUCTION ENSURES QUICK ACCESS TO ALL WIRING

SPECIFICATION

OUTPUT : 1,000 watts, A F
DISTORTION : 0.6%, at 1,000 c s
NOISE LEVEL : —70 dB
OUTPUT REGULATION : 0.0 (0.8 dB)
SENSITIVITY : 0.09 V at 600 ohms

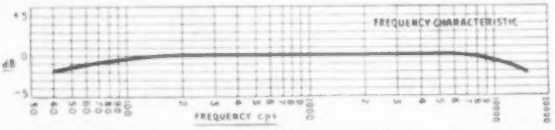

W. BRYAN SAVAGE LIMITED

WESTMORELAND ROAD, LONDON, N.W.9 COLINDALE 7131 'GRAMS: DECIBEL, PHONE, LONDON

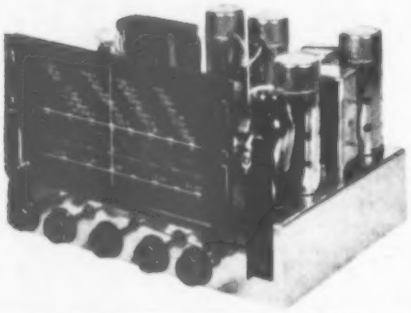

BUILD WITH OUR HANDSOME HOME CONSTRUCTION UNITS!

ANYONE can build this magnificent "SUPERHET"!

Using our new and improved unique point-to-point Construction Sheets for this famous 6 v. A.C. Super, with the latest 40 Tuning Unit you can, for an evening's entertaining construction, compete with a radio set (without ANY test gear) whose range and performance will at least equal that of commercially built receivers at double the cost!

As our delighted friends already know the secret lies in our pre-aligned 40 R.L. TUNING UNIT comprising our famous 3 band 40 Coil pack, "MM" I.F.T.s, new slim, 3 gang — READY ALIGNED, MATCHED and SEALED! Price 12/6 — direct or £7 11 6 with J.B. 8 S.L.F. spin wheel Tuner. NOTE for Conversions — Our 40 Tuner using above Tuning Unit with HI-FI switching for local stations (and Grams.) with Low push-pull Quality Amplifier and variable negative feedback is the TOPS! (Also Ideal with Williamson, P.J.M., of 8 E.14. styles) — it does all you claim — I had the surprise of my life when it went perfectly first time — it is the best set I've ever heard." For constructional details, illustrations, TWELVE circuits, data, etc., send 2/6 NOW for LATEST 1952 EDITION of "Home Constructor's Hand-book."

ALL items supplied by Mail DIRECT ONLY from

RODING LABORATORIES (Dept. WWM)

694 LEA BRIDGE ROAD, LONDON, E.10.

PULLIN

MINIATURE INSTRUMENTS

MOVING COIL
THERMO-COUPLE
RECTIFIER

Small round, square or rectangular pattern instruments for flush mounting or as round projecting types.

Available as Micro-ammeters, Milli-ammeters, Ammeters, Millivoltmeters and Voltmeters.

Supplied in four sizes 2", 2½", 3½" and 3¼".

Our catalogue giving scale ranges and prices will be sent on request.

MIP

MEASURING INSTRUMENTS (PULLIN) LTD.
Electrin Works, Winchester St., Acton, London, W.3. Phone: ACOrn 4651

GOODSELL SOUND

A NEW

WILLIAMSON AMPLIFIER - - TYPE GW.12
to Goodsell's full quality specification:—

★ 12 watts output at 0.1% distortion.
★ Paper Condensers on H.T. supply line.
★ Double Power Supply.
★ Impregnated grid coupling condensers.

PRICE £29 - 0 - 0

• • • • •

SERIES S.P. 'PRE-SELECTIVE' TUNER UNITS with or without R.F. stage, panel illustrated.

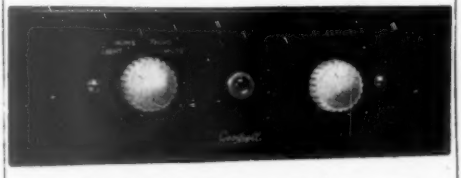

★ VARIABLE SELECTIVITY ★ 3 STATION CONTROL
PRICE from £10 - 10 - 0 plus tax

• • • • • • •

WIDE RANGE 4 STAGE CONTROL UNIT WITH OR WITHOUT PRE-AMPLIFIER FROM £7 - 10 - 0

• • • • • • • •

OTHER AMPLIFIERS FROM £15 - 15 - 0 UPWARDS

• • • • • • • •

MILNES

enter the high fidelity L.S. field with their TRUPRODUCERS. New and sensational features include:-

★ Hexagonal speech coil used on a new claw principle.
★ Speech coil ¼ the normal weight.
★ No spider, as such, suspension and centring by six glass cords.
★ Flux density 17,000 lines per sq. cm.
★ Frequency response from 25 to 16,000 c.p.s.

PRICE 12" UNITS £15 - 15 - 0
10" UNITS £14 - 14 - 0

All Enquiries to:—

B.K. PARTNERS LTD., 229 REGENT ST., LONDON, W.1. Telephone REGENT 1267

DISTRIBUTORS FOR GOODSELL SOUND & MILNES TRUPRODUCER

WE ARE APPOINTING AGENTS THROUGHOUT GT. BRITAIN AND WELCOME TRADE ENQUIRIES

THE MAN THE MACHINE AND PARMEKO

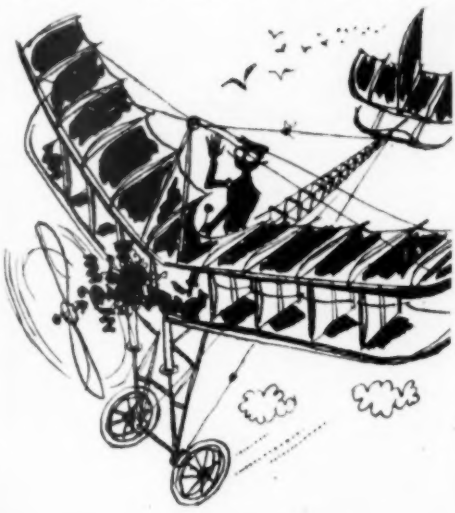

Flying Machine!

It looked like nothing on earth, so perhaps it was natural that it should rise, if a little uncertainly, into the skies. Remember those early days of aircraft - when men had little more than faith...and an idea? Parmeko, young then, have grown too, in faith, ideas, and experience. Parmeko transformers in control systems and instruments have strengthened pilots' hands for nearly three decades.

PARMEKO *of* **LEICESTER**

Makers of Transformers for the Electronic and Electrical Industries

Send for our fully illustrated Catalogue

WODEN

THE HEART OF EVERY CIRCUIT

is to be found in its Transformer, which, like the human heart must keep the lifeblood flowing evenly and constantly under both normal and abnormal conditions.

POTTED COMPOUND FILLED TRANSFORMERS AND CHOKES

manufactured by WODEN have been designed to fulfil such a purpose, and for this reason they have been standardized by many leading Radio, Television and Electronic manufacturers and also Government Research Departments. Their choice is only made after exhaustive tests for accuracy and reliability. To merit this confidence, there is a constant need to provide components of the highest quality and our ample research and testing facilities ensure continued progress in this direction.

WODEN TRANSFORMER CO. LTD.

MOXLEY ROAD · BILSTON · STAFFS.

TELEPHONE: BILSTON · 41959

J.T.L.

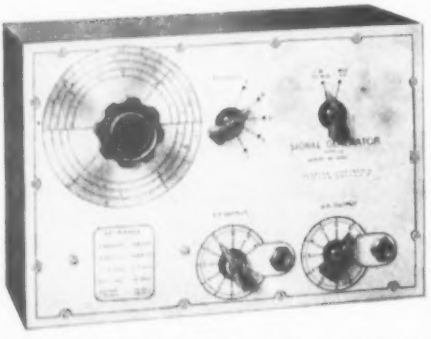

SIGNAL GENERATOR TYPE 10. 100 Kc/s-100 Mc/s

Price £7 . 10 . 0

The accuracy, reliability and comprehensive specification, are some of the reasons why the TYPE 10 has achieved such outstanding success.

● 100 Kc/s to 100 Mc/s ● Modulated or unmodulated carrier ● Direct calibration ● Adjustable 400 c.p.s. AF signal ● Stable RF oscillator Large, easily read scale ● AC mains operation.

New instruments now available include the HOMELAB CHECKTEST price 37/6d., and a range of accurately calibrated variable condensers, 100pf., 500pf., and 1000pf., price 42/- each.

Obtainable only direct from the manufacturers. Send for full technical details or call at address below.

HOMELAB INSTRUMENTS LTD.,
68a, COBDEN ROAD, LONDON, E.11
Telephone: LEY 5651

TELEVISION

for "Fringe" and "Long distance" viewers is vastly improved with the SPENCER-WEST type AC/3 Pre-Amplifier. The specification includes a first stage neutralised triode cathode coupled to a grounded grid triode. The optimum arrangement for best "noise factor." Self-contained power supply unit complete with correctly adjusted interference filter. Price complete, **10 gns.**, from your Dealer or direct. Leaflets, etc., on request.

Conversion units type AC/4 for Holme Moss/London, or Sutton Coldfield or Sutton Coldfield/London, etc. Double oscillator mixer stage and R.F. stage for correct reception with absence of mixer noise and radiation to other receivers. Price complete with 5 valves and self-contained power supply unit, **15 gns.** Leaflets on request.

SPENCER - WEST
QUAY WORKS, GT. YARMOUTH
Phone: Gt. Yarmouth 3009

RELAYS AND KEY SWITCHES

LARGEST EX-GOVT. STOCK IN GT. BRITAIN

Types 600-3000 Relays—Siemens High Speed
Also A.C. 400 volts 50 cycles

Uniselector Switches, Telephone Switch-boards, Telephone Components Plugs, Jacks, Handsets — **Government Contractors.**

JACK DAVIS (RELAYS) LTD. (DEPT. W.)
36 PERCY STREET, LONDON, W.1
Phones: MUSeum 7960 LANgham 4821

FREE! for YOU

The opportunity of a personal demonstration of the Simphonic Tape Recorder! . . . . .

As a result of increasing requests from "Wireless World" readers for a personal demonstration of the Simon Simphonic Tape Recorder, we today institute a scheme to give YOU the opportunity of seeing and hearing for yourself the outstanding merits of this equipment FREE—wherever you are in Great Britain.

There is no obligation on your part. Simply fill in the coupon alongside and post to us TODAY. We will do the rest. Act NOW as requests must be taken in order of receipt.

To:—SIMON SOUND SERVICE (Dept. W.1)
48-50 George Street, London, W.1.

Please arrange for me to have a personal demonstration of the Simphonic Tape Recorder as advertised.

Name .....

Address .....

★ Offer applies to Great Britain only.

AN ULTRASONIC SOLDERING IRON

Can be used for soldering aluminium, and other metals that form refractory oxides

THE problem of soldering metals that form refractory oxides has now been overcome.

A new soldering iron, developed by Mullard Ltd., destroys oxide film by ultrasonic stimulation and provides a "clean" metallic surface.

This means that perfect soldering of aluminium, and other metals, can now be achieved without scraping or brushing molten metals. Standard soft solders can be used. And no flux is needed.

A small electronic amplifier supplies the ultrasonic power. Two controls, a mains and a trigger switch, ensure simplicity of operation. Unskilled workers can use the apparatus without discomfort, since the ultrasonic frequency used is inaudible to the human ear. Full information about the Mullard Ultrasonic Soldering Iron—the only commercial model in the world — is available on request.

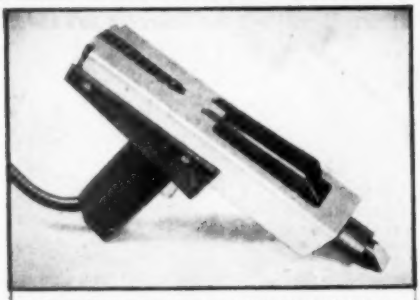

The soldering iron has a nickel silver bit driven by a magnetostriction transducer. The transducer is arranged to run at its natural resonant frequency by a feed-back system. A conventional low voltage winding heats the soldering bit.

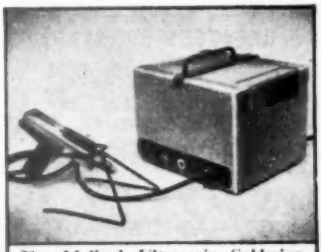

The Mullard Ultrasonic Soldering Iron and Amplifier. The unit operates from A.C. mains and is robustly made to suit workshop conditions.

Mullard CONDUCTIVITY EQUIPMENT · POTENTIOMETRIC TITRATION APPARATUS · ELECTRONIC POLAROGRAPHS · TEMPERATURE CONTROLLERS · UNIVERSAL MEASURING BRIDGES · VALVE VOLTMETERS · F.M. SIGNAL GENERATORS · OSCILLOSCOPES

NORTHERN AGENT: F. C. Robinson & Partners, Ltd., 287, Deansgate, Manchester, 3
MIDLAND AGENT: Hadley Sound Equipments Ltd., 72, Cape Hill Smethwick. *Tel: Smethwick 0977.*
SCOTTISH AGENT: Land, Speight & Co. Ltd., 73 Robertson Street, Glasgow, C.2.

Mullard Ltd., Equipment Division, Century House, Shaftesbury Avenue, London, W.C.2. Telephone: GERrard 7777

Mullard

(ME.340)

FIRST AGAIN! ★★★★★★★★★★★★★★★★★★★★★★★★★★

Here is Your Two-Valve Translator

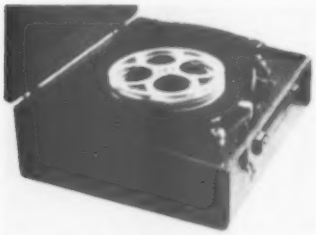

You can magnetically record, using your gramophone motor as a drive and the amplifier within your radio as the tape amplifier. Conversion Kit (readily detachable) containing all necessary parts and instructions, £7, includes postage, etc.

★ 1948 We gave you wire recording utilising a gramophone motor
★ 1949 We gave you talking books for the blind
★ 1950 We gave you tape recording utilising a gramophone motor
★ 1952 We give you now for the FIRST TIME in MAGNETIC RECORDING

A Two-Valve Translator

By clever circuitry we have produced for you a 2-valve translator which supersedes costly amplifiers and saves you needless expense. This unique translator will magnetically record from any microphone or pick-up. This unique translator will playback from any make of recorder. It will (without electrical connection to telephones) record 2-way conversations. It will playback into business intercom systems. It will playback into cinema or wireless relay systems.

The translator has both audio and a radio frequency outlet so that any radio receiver tunable to say 900 metres can boost the output to greater volume if desired. This wonderful new TWO-VALVE TRANSLATOR CHASSIS costs only **£12 10 -** ready for use on 230 A.C. Other voltages to order.

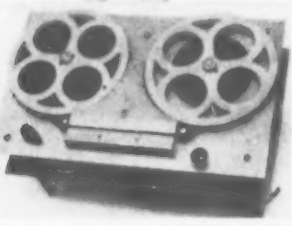

The Diamond Tape Recorder. Two speeds (Diction 2 hours Music 1 hour). Twin tracks. Fast forward wind and fast rewind. Strongly built for hard work. Can be used with any conventional amplifier or the translator. **£25**, including choice of tape. Diamond, Scotch Boy, E.M.I., G.E.C.

Recording playback and erase heads for home assembly.
Bandoau Type 7 6 pair. Record playback and erase. Kit contains all parts and instructions.
Cassette Type 30 -. Contains both record playback and erase heads in one housing. The heads can be changed about according to tape direction (erase should preceed record head). Gaps are adjustable. Cores are stacked mumetal half width for 2-way tracking. Bobbins ready wound Hi or Lo impedance to choice.

Oscillator coils 6 6. For generating 45Kc supersonic bias current and erase current. Primary and secondary windings for Hi or Lo impedance heads.

PARK RADIO OF MANOR PARK DISTRIBUTORS FOR JUDGE INDUSTRIES 783 ROMFORD ROAD, LONDON, E.12 Phone **ILF 2066** for demonstrations by appointment only

Instruments for Research and Industry

The TWENTY MILLION MEGOHMMETER

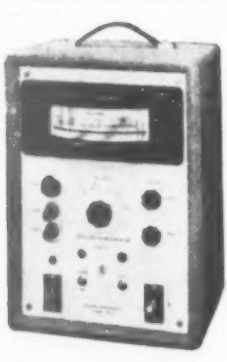

The modern instrument for the measurement of resistance. Covers the range from 0.1 to 20,000,000 megohms in six decades. Two test voltages, 81v and 500v are provided and a six-inch mirror scale meter enables readings to be taken accurately and quickly. The instrument is especially useful for testing cables, resistors, condensers, and all insulating materials.

ELECTRONIC INSTRUMENTS LTD
27 PARADISE ROAD RICHMOND SURREY ENGLAND

NEON TEST PROD

Suitable for testing up to 250 V. supplies. Will indicate polarity and detect leakage. Housed in moulded rubber black case. Totally shockproof and safe.

Tests on A.C. & D.C.

FOR EVERY SERVICEMAN

PRICE 10/- RETAIL

NEW

A.F. BULGIN & CO., LTD.
BYEPASS RD., BARKING, ESSEX

THE WORLD'S GREATEST BOOKSHOP

FOYLES
FOR BOOKS!

Stock of over 3 million volumes

New, secondhand and rare Books on every subject. Large Technical department.

Subscriptions taken for magazines.

119-125 CHARING CROSS ROAD LONDON W.C.2
Gerrard 5660 (16 lines) ★ Open 9-6 (inc. Sats.)

VITAVOX

LOUDSPEAKERS AND MICROPHONES

. . . for solving sound problems

The VITAVOX range of microphones, loudspeakers and reproducers is sufficiently wide in its scope to meet all practical requirements in the field of sound reproduction. Thus the solution to your sound problem is primarily the selection of the right Vitavox model to meet your specific needs and the manufacturers will be pleased to assist you by sending full details of Vitavox products on request.

Specify **VITAVOX**

VITAVOX LIMITED, WESTMORELAND ROAD, LONDON, N.W.9

Telephone: COLindale 8671-3

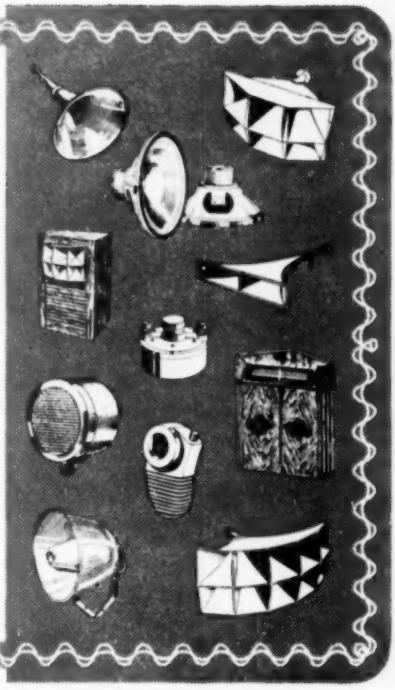

The **BROADCASTER** *Gliding*

SAPPHIRE PICK-UP **NEEDLE**

Plays for Months without replacement

No. 1

TRAILER for use with heavy magnetic pick-up

No. 2

STRAIGHT for use with standard or crystal pick-up

No. 3

LIGHTWEIGHT for use with miniature pick-up

AS USED FOR BROADCASTING

OBTAINABLE FROM ALL MUSIC & RADIO DEALERS

PRICE 6/6 TAX PAID

or direct from

BROADCASTER RADIO SUPPLIES LTD., 112-114-116 Old Street, London, E.C.1

Telephone: CLErkenwell 2133-7 Telegrams: Plusagram, Cent, London

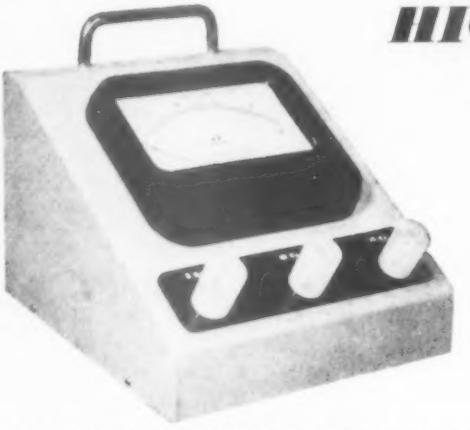

HIGH VOLTAGE METER

0-15. KV
Model P.015

SPECIFICATIONS

Voltage Range :	0-5, 0-10, 0-15 KV. D.C.
Polarity :	Positive
Loading :	50 Micro-amps. F.S.D.
Scale :	5 inches
Dimensions :	8" wide. 8½" deep. 6" high
Insulation :	25 KV
Finish :	Grey enamel and chromium

PRICE 18 GUINEAS
High Voltage Probe — 10 6 extra

Also available.—Model PN.1030. The range of this instrument is 0-30 KV. D.C. in three steps, with polarity reversing switch. Permits measuring of positive or negative voltages from ground. OFF position of switch locks meter movement

Price 26½ Guineas

Both instruments available direct from Manufacturers only

TELEONICS (COMMUNICATIONS) LTD.

181 EARLS COURT ROAD, LONDON, S.W.5

Telephone : FRObisher 0387

URGENTLY REQUIRED

THE FOLLOWING EQUIPMENT IN ANY CONDITION :—

FREQUENCY METERS Type BC.221, BC.221AK, TS.174/U, TS.175, TS.69/AP. Also LR2 (Naval Version) by General Radio Co., and other types.

AMERICAN TEST SETS Type TS.13AP, TS.12AP, TS.34AP, TS.47AP, TS.10, TS.16APN, TS.33, TS.35, TS.36, TS.45, TS.59, TS.110, TS.118, and others.

RECEIVERS Type APR1, APR4 and APR5 also Tuning Units types TN1 APR4, TN17 APR4, TN18 APR4 and others.

AR88D spare parts, particularly wave change switches.

ALSO :—IMPEDANCE OR UNIVERSAL BRIDGES, OSCILLOSCOPES, "Q" METERS, VALIACS, OUTPUT METERS, ETC.

Please write, call or phone, giving price, condition, etc.

ELM ELECTRIC CO.,
175, UXBRIDGE RD., HANWELL, W.7
EALing 0779

POLYTHENE
H. F. EQUIPMENT
(AMBYTHENE BRAND)

COIL FORMERS
CHOKES
STAND-OFFS
FEED-THROUGHS

Send for Particulars and Samples

AMPLEX APPLIANCES (KENT) LTD.
19 DARTMOUTH ROAD, HAYES, BROMLEY, KENT
(RAVensbourne 5531)

PRATTS RADIO
1070 Harrow Road, London, N.W.10
(Nr. SCRUBBS LANE)
Tel.: LADbroke 1734

MODEL AC10E £10 7 6

AMPLIFIERS. College general purpose units. MODEL AC10E. 4 valve 10 watts. Neg. feedback. £10 7 6. MODEL AC12E. 4 valve. 12½ watt P.P output. Feedback over 3 stages. £15 5 -. MODEL AC22E. 22 watts P.P. output. Feedback over 3 stages. £18 18 -. MODEL U10E. for D.C./A.C mains. 6 valve 10 watt P.P output. Feedback over 3 stages. £12 19 6. All are complete with cases and chrome handles. They have a separate microphone stage. Separate inputs for mike and gram., allowing individual mixing, etc. Outputs match 3, 8 or 15 ohms speakers. Max. input volts required for full stated output average Mike .003, Gram. .3 v. MODEL AC8C. 4 valve P.P 8-10 watt unit for records, radio, etc. Feedback over 3 stages. Output to 3, 8, 15 ohms £10 10 -. MODEL AC6C. 3 valve record/radio amplifier, 4 watts to 3 ohms. £5 15 -. Ditto U/C for D.C./A.C mains £5 15 -. Stamp for list. Full range of accessories available including Rothermel Crystal Mikes. 105 -. Goodmans 12in. P.M. speakers. £8 12 6. Collaro A.C. Record Players, rim drive, magnetic model. £6 0 -. Crystal. £6 15 -. Jack plugs 2/- each extra.
All amplifiers are complete and ready for use.

CAPACITANCE STABILITY MEANS

Our Silvered Mica Capacitors are mass produced to precision standards. Electrical characteristics which have previously been specified for laboratory standards are now a feature of a component which we produce by the million.

Reliability is the key word of our inspection methods which are based on statistical control in addition to the comprehensive application of modern electronic instruments. Quality control of this nature can only be performed by a specialist manufacturer who has carefully collected and analysed the production results of many millions of units over a period of years.

SRC

STABILITY RADIO COMPONENTS LTD

COMMERCE ESTATE · WOODFORD AVENUE
LONDON · E.18
TELEPHONE · BUCKHURST 6501/2

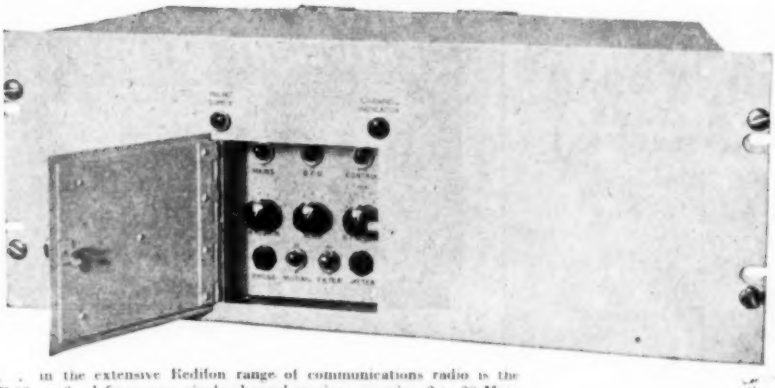

An Important Receiver...

. . . in the extensive Redifon range of communications radio is the R.93—a fixed frequency, single channel receiver covering 2 to 20 Mc/s. Its crystal controlled oscillator and other special features make this the ideal unattended receiver for point-to-point and ground-to-air channels and it has full remote control facilities. Specialised applications of the R.93 include monitoring, diversity reception or frequency shift working.

The Redifon range includes MF, HF and VHF transmitters, receivers, radio telephones, navigational aids, AF amplifying systems and other electronic equipment. Enquiries for single units or complete networks including aerials, masts, power supply, land line amplifiers, remote controls and other apparatus are welcome.

AIRPORT Redifon Radio

Radio Communication Division

The R.93 is designed to the specification of International Aeradio Limited

REDIFON LIMITED, BROOMHILL ROAD, WANDSWORTH, S.W.18

DESIGNERS & MANUFACTURERS OF RADIO COMMUNICATION & INDUSTRIAL ELECTRONIC EQUIPMENT

Phone: VANdyke 7281

PANREK

for Tape and Wire Recorders

Tape Machines for Domestic Use
Simphonic TR 2b · Clifton
M.S.S. · Excel · Magnegraph

Wire Recorders for Domestic Use
Wirek B 1 · Wirek B 2 · Wirek A

Office Machines
Retalker · Dictabel

Tapes
G.E.C. · Scotch Boy
E.M.I. · Gevart

Wires
Boosey & Hawkes
Tophet M High Quality

Microphones
Reslo Ribbon · Reslo Dynamic
Lustraphone · Cosmocord
Vitavox

Magnetophon B.A.S.F. Recording Tape. Finest quality available. 400 yard spools 45/-d.

PANREK, 28 NEW BOND STREET, LONDON, W.1 • MAY 3903
CABLES: PANREK LONDON GRAMS: PANREK WESDO LONDON

The Latest
"CLIFTON" 1952
MAGNETIC TAPE RECORDING MACHINE
Incorporating
- Magic Eye Volume Indicator
- Improved Capstan Drive
- Speeds: 15 in.–7½ in.–3¾ in. per sec
- Playing Time 17–34–68 mins
- Response–50 to 10,000 cycles

PRICE
£55-10-0
EXCLUSIVE OF TAPE OR MICROPHONE

Export Enquiries to:
PANREK
28, NEW BOND STREET, LONDON, W.1
Telephone MAY 3903
Manufacturers
BRISTOL MAGNETIC TAPE RECORDERS LTD.
11, ALMA VALE ROAD, BRISTOL Telephone 36085

A MINIATURE MAGNETIC LIGHTWEIGHT EARPHONE

The new Amplivox E.4 Earphone has been primarily developed for use with office dictating machines, industrial equipments and hearing aids where a highly sensitive, lightweight, miniature receiver is needed.
Available in D.C. resistances 2-2000 ohms; frequency 100-4000 c.p.s.; diameter .835", depth .420"; weight ½ oz.

AMPLIVOX LTD.
2 Bentinck Street, London, W.1

TRANSFORMERS
COILS
CHOKES
TRADE ENQUIRIES INVITED
SPECIALISTS IN
FINE WIRE WINDINGS
MINIATURE DEAF AID TRANSFORMERS, PICK-UP
CLOCK AND INSTRUMENT COILS ETC.
RADIOMENDERS LTD.
123-5-7 PARCHMORE ROAD, THORNTON HEATH, SURREY
LIVINGSTONE 2261 EST. 1933

ULTRA GEN
No. 1

USING 1·4v VALVES—PROPERLY

The Ultra "Twin" is a portable for use on AC/DC mains, or on batteries. The four valves (plus metal rectifier) are 1.4v miniatures whose filament voltage is obtained from the smoothed HT supply. An important design requirement is that the filament voltage must be maintained substantially constant in the interest of the life of the valves. This is much easier said than done.

This difficulty could arise when the mains input to a normal rectifier circuit is changed from, say, 230v A.C. to 230v D.C. The HT voltage would decrease on the D.C. supply by as much as 25%. This change —added to the normal mains variation that has to be allowed for—is more than could be tolerated. To avoid the necessity for complicated switching to equalise the HT between A.C. and D.C. mains, the Ultra engineers have designed a circuit such that the rectifier efficiency on A.C. mains is adjusted to a value which compensates for the voltage drop which occurs when the set is used on D.C. mains. See resistance R in the diagram. In this way, the HT voltage and filament voltage is maintained substantially constant at the correct value when changing over from A.C. to D.C. mains without the need for switching.

This is just one of the outstanding features of the Ultra "Twin" portable that has made it about the most popular receiver for many years past.

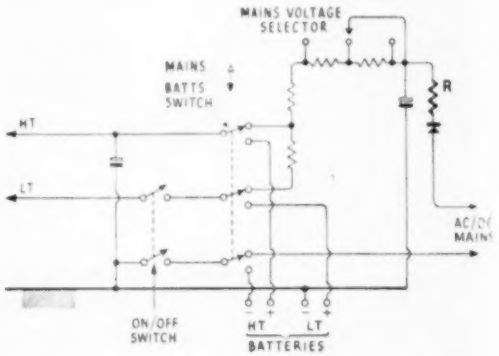

ULTRA ELECTRIC LIMITED
WESTERN AVENUE · ACTON · W.3

Ceramic Hermetic Seals & Bushes
by
U.I.C

UNITED INSULATOR CO. LTD. OAKCROFT RD. · TOLWORTH · SURBITON · SURREY
TELEPHONE ELMBRIDGE 5281 CABLES CALANEL, SURBITON

E·L·A·C
MANUFACTURERS OF LOUDSPEAKERS • CHOKES
TRANSFORMERS • TELEVISION FOCUS UNITS • ION TRAPS
ELECTRO ACOUSTIC INDUSTRIES LTD
STAMFORD WORKS, BROAD LANE, TOTTENHAM, N.15 TEL: STAmford Hill 5606-8

Cut this out. You may need something at the last moment!

Pamphonic

in St. Paul's Cathedral

Articles appearing in the "Wireless World" describe the

D.S.R. EQUIPMENT AND LINE SOURCE LOUDSPEAKERS

recently demonstrated in St. Paul's Cathedral. We are pleased to announce that this equipment is

NOW AVAILABLE FOR GENERAL DISTRIBUTION

Pamphonic Reproducers Ltd.,
Westmoreland Rd., Queensbury, London, N.W.9.

NEW

COLLOIDAL SILVER PREPARATIONS

for

Mica and Ceramic Condensers

Full details and samples from :-

FACTICE & CHEMICAL SUPPLIES LTD.

4 Lloyds Avenue, London, E.C.3

Grams : Factice *Phone* : ROYal 1762

Qualtape Magnetic Tape Recorder

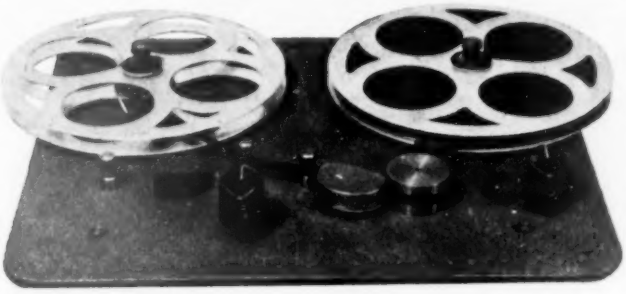

- ★ IMPROVED DESIGN
- ★ NEW FEATURES
- ★ PRECISION MADE
- ★ PERFECTLY BALANCED CAPSTAN DRIVE BY SEPARATE MOTOR
- ★ UP - TO - THE - MINUTE DESIGN. RECORD HEAD, PLAYBACK HEAD, TAPES STOCKED.

Complete Kit of Parts **£13-13s.**

FULL PARTICULARS ON REQUEST TO—

ELECTRONIC SERVICE
(HALLAMSHIRE) LTD.
93-95, BUTTON LANE, SHEFFIELD
Telephone: Sheffield 21690

The Ideal Tape Recorder for home, office, board meetings. Make your own party records. Use it to improve musical and voice talent. Provide synchronised music and speech for home cine. All these and many more with "Qualtape." Only tools required—
PLIERS, SCREWDRIVER

They are the most Reliable

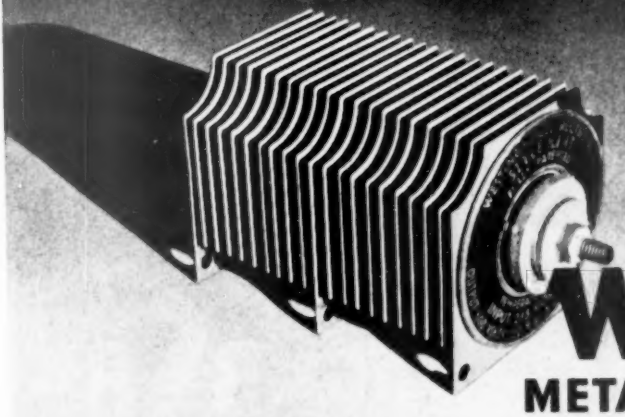

WESTINGHOUSE
WESTALITE
METAL RECTIFIERS

WESTINGHOUSE BRAKE & SIGNAL CO., LTD., 82, York Way, King's Cross, London, N.1.

FOR RECORD PERFORMANCE..

GU4

A beautifully styled three speed gramophone. Complete with ingenious automatic stop and light weight crystal pickup fitted with two permanent sapphire styli.

MU14

A de luxe three speed turntable unit which can be used with the buyer's own choice of crystal or magnetic pickup

MU10

A high performance two speed turntable unit designed for easy conversion from 78 r.p.m. to 33⅓ r.p.m.

These units set a new high standard of design and quality. They are backed by extensive research and the latest production methods.

BIRMINGHAM SOUND REPRODUCERS LTD BSR

Old Hill, Staffs. Tel. Cradley Heath 6212/3, Grams: 'Electronic Old Hill, Cradley Heath.'

Wireless World

RADIO, TELEVISION AND ELECTRONICS

41st YEAR OF PUBLICATION

Managing Editor: HUGH S. POCOCK, M.I.E.E.
Editor: H. F. SMITH

MARCH 1952

In This Issue

EDITORIAL COMMENT 83

TELEVISION GHOSTS. By *J. A. Hutton* 84

VALVE VOLTMETER. By *M. G. Scroggie* 89

ORIGINS OF RADAR 95

AWARDS TO RADAR PIONEERS 99

WORLD OF WIRELESS 101

LETTERS TO THE EDITOR 103

LOCATING TELEVISION PIRATES 104

"TRUSTWORTHY" VALVES. By *E. G. Rowe* 105

SPEECH REINFORCEMENT IN ST. PAUL'S CATHEDRAL. By *P. H. Parkin and P. H. Taylor* 109

ECONOMICAL METERING. By *H. B. Dent* 112

DECADE MULTIVIBRATOR DESIGN. By *J. E. Attew* .. 114

BUSINESS RADIO 116

TOTAL POWER. By "*Cathode Ray*" 117

IONOSPHERE REVIEW—1951. By *T. W. Bennington* .. 121

MANUFACTURERS' PRODUCTS 123

RANDOM RADIATIONS. By "*Diallist*" 124

UNBIASED. By "*Free Grid*" 126

PUBLISHED MONTHLY (last Tuesday of preceding month) by ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1. *Telephone*: Waterloo 3333 (60 lines). *Telegrams*: "Ethaworld, Sedist, London." *Annual Subscription*: Home and Overseas, £1 7s. 0d. U.S.A. $4.50. Canada $4.00. BRANCH OFFICES: *Birmingham*: King Edward House, New Street, 2. *Coventry*: 8-10, Corporation Street. *Glasgow*: 26B, Renfield Street, C.2. *Manchester*: 260, Deansgate, 3.

VALVES...and their Applications

INDIRECTLY-HEATED VALVES FOR BROADCAST RECEIVERS

Double-Diode Pentodes

The popular mains superhet receiver, commonly known as the "4+1" valve receiver, i.e. one having four receiving valves and a rectifier, has a valve complement performing the following functions:—

V1 Frequency changer.
V2 I.F. amplifier.
V3 Combined detector, A.G.C. rectifier and A.F. voltage amplifier.
V4 Power amplifier.
V5 Rectifier.

It is possible, however, to design a somewhat less expensive receiver, at some sacrifice of overall sensitivity, by dispensing with the A.F. voltage amplifying stage. This can be achieved by employing a double diode pentode as combined I.F. amplifier, detector and A.G.C. rectifier for V2, and omitting the double diode triode (V3 in the 4 + 1 receiver). Such a set is often termed a "$3\frac{1}{2}$ + 1" valve receiver.

The valve complements for such sets employing Mullard mains valves are then:—

	A.C. Mains or Car Radio	D.C./A.C. Mains
V1 Frequency Changer	ECH42	UCH42
V2 I.F. amplifier, detector and A.G.C. rectifier	EBF80	UBF80
V3 Power amplifier	EL41 (EL42 for car radio)	UL41
V4 Rectifier	EZ40 (EZ41 for car radio)	UY41

All the above valves have already been described in this series of advertisements with the exception of the double diode pentodes types EBF80 and UBF80.

As will be seen from the table, the pentode sections of these valves have characteristics substantially the same as those of the EF41 and UF41. The diode characteristics, while somewhat different from those of the diode sections of the EBC41 and UBC41, are well within the wide range of values suitable for their applications, for which the characteristics are not critical. Although primarily intended for use in R.F or I.F. stages, the pentode sections of these valves are quite suitable for audio frequency voltage amplification.

DOUBLE-DIODE PENTODES

Type EBF80 for A.C. Mains & Car Radio Sets

Type UBF80 for D.C./A.C. Mains Radio Sets

Heater	EBF80	UBF80	
V_h	6.3	17	V
I_h	0.3	0.1	A

Mounting Position Any

Capacitances

$C_{a'd-g1}$	<0.0008	<0.0008	μμF
$C_{a''d-g1}$	<0.001	<0.001	μμF
C_{a-a}	<0.2	<0.2	μμF
$C_{a'd-a}$	<0.05	<0.05	μμF
Pentode Section			
C_{a-g1}	<0.0025	<0.0025	μμF
C_{out}	4.6	4.6	μμF
C_{in}	4.0	4.0	μμF
C_{g1-h}	<0.07	<0.07	μμF
Diode Sections			
$C_{a'd-k}$	2.15	2.15	μμF
$C_{a''d-k}$	2.35	2.35	μμF
$C_{a'd-a''d}$	<0.35	<0.35	μμF

Limiting Values

Pentode Section			
$V_{a(b)}$ max.	550	550	V
V_a max.	300	250	V
p_a max.	1.5	1.5	W
$V_{g2(b)}$ max.	550	550	V
V_{g2} max. (I_a<2.5 mA)	300	250	V
V_{g2} max. (I_a=5 mA)	125	125	V
p_{g2} max.	0.3	0.3	W
I_k max.	10	10	mA
V_{g1} max. (I_{g1} = +0.3 μA)	−1.3	−1.3	V
*R_{g1-k} max.	3	3	MΩ
R_{h-k} max.	20	20	KΩ
V_{h-k} max.	100	150	V

*R_{g1-k} max. = 2.2 MΩ if grid current biasing is employed.

Diode Sections			
$v_{ad(pk)}$ max.	200	200	V
I_{ad} max.	0.8	1.3	V
V_{ad} max. (I_{ad} = +0.3 μA)	−1.3	0.8	mA
R_{h-k} max.	20	20	KΩ
V_{h-k} max.	100	150	V

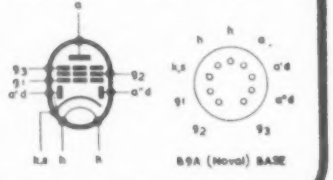

B9A (Noval) BASE

THE COMPLETE SERIES

	FREQUENCY CHANGER	I.F. AMP., DET. & A.V.C. DIODE	R.F. OR I.F. AMPLIFIER	DET., A.F. AMP. & A.V.C. DIODE	OUTPUT PENTODES	RECTIFIER
6.3V Heater	ECH42	EBF80	EF41	EBC41	EL41; EL42	EZ40; EZ41
0.1A Heater	UCH42	UBF80	UF41	UBC41	UL41	UY41

Reprints of this article together with additional data may be obtained free of charge from the address below.

Mullard

MULLARD LTD., Technical Publications Department, Century House, Shaftesbury Avenue, W.C.2.

MVM 190

Wireless World

MARCH 1952 VOL. LVIII. No. 3

For Services Rendered

THERE will be general satisfaction among our readers that substantial monetary recognition has been accorded by the Royal Commission on Awards to Inventors to those who entered claims for their contributions to the initiation and development of radar. The findings were announced as we were going to press with our last issue, and elsewhere in the present number we record the awards made both to the team headed by Sir Robert Watson-Watt and to a number of workers who made claims independent of the team.

The awards will generally be taken as recognition of the foresight, ingenuity and technological competence of those who found means of putting to practical use a by-product of radio-wave propagation that had hitherto been usefully employed only for ionosphere sounding. They started with a very simple idea, but in a surprisingly short time developed it into an instrument that proved of incalculable value in war and is now proving of great value in peace. Indeed, the speed of radar development is one of its most remarkable features. Within three or four short years—and without the stimulus of self-preservation brought about by actual war—an effective weapon was evolved from the brand-new idea of using radio reflections for location of distant objects. Within ten years the same principle was in use in highly complex and refined equipment readily adaptable to peacetime use. *Wireless World* offers its congratulations to all those—whether they figured in the Commission's award list or not—who produced such spectacular results in so short a time.

One useful by-product comes from the Commission's lengthy and searching investigations. They will go some way to establish priority of "invention" in many fields of radar. Unfortunately the findings do not go all the way. The Commission did not concern itself solely, or even mainly, with "invention" in the strict and limited technical sense of that word. Equally, the published findings did not disclose the bases on which all the awards were made; it cannot be said categorically how many of the multiple claims made by some successful claimants were accepted. However, the voluminous evidence that is on record should help to settle some of the controversies that are bound to arise.

The Commission's awards do not represent the total sum received by those who contributed to the development of radar. There were, of course, similar awards to the originators of the magnetron. In addition, it has been stated that some £200,000 has been paid by the Ministry of Supply and the Admiralty. It is believed, however, that this sum is mainly accounted for by payments to industry for the use of patents as a matter of legal right and not as *ex gratia* awards.

More Reliable Valves

IN the early days nobody claimed that radio valves were reliable. They were regarded as expendable accessories, and their holders were usually mounted in accessible positions so that replacements could easily be inserted when needed. Then manufacture on more scientific lines got into its stride, and soon the pendulum swung in the other direction; valve makers began to urge that the valve was no longer an accessory but a component no more liable to failure than other components; as such, it might well be permanently wired in position, thus doing away with the (sometimes) troublesome holder. Though this line of argument has been adduced with some show of reason, it has not yet been accepted to any great extent except where sub-miniatures are concerned. In the meanwhile, we find occasional outbreaks of inconclusive recrimination as to the true reliability of valves. Inconclusive, because, as an article on another page will show, the apparently simple word "reliable" must be carefully defined when applied to such things as valves.

The present concentration of attention on valve reliability is very much to the good, especially in the sphere of industrial applications. Users of valves for such purposes naturally regard with suspicion any device with a reputation for unreliability. Valve manufacturers are alive to this, and, in the process of increasing the robustness of special-purpose types, are improving their general production.

TELEVISION GHOSTS

Effect of Multi-path Propagation in Hilly Country

By J. A. HUTTON, B.Sc.*

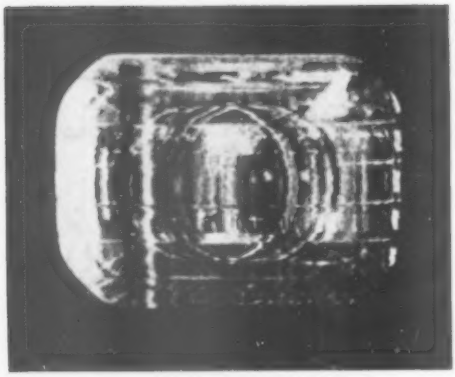

Fig. 1. A picture received with a commercial aerial at Hebden Bridge.

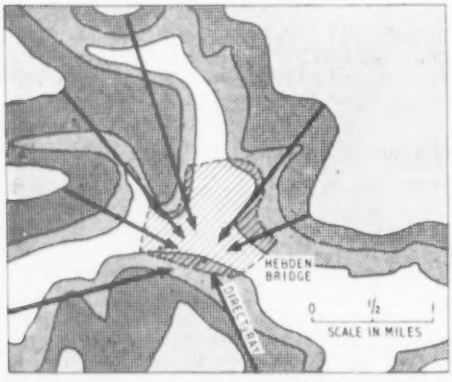

Above: *Fig. 2*

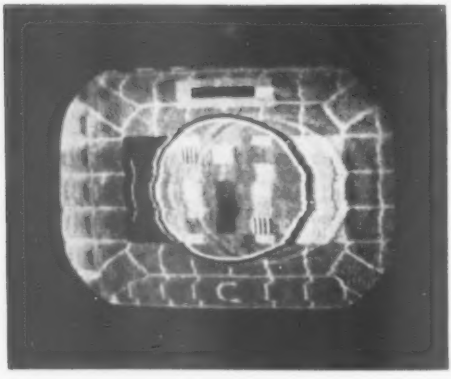

Below: *Fig. 3*

WHEN the television station at Holme Moss was opened, many viewers, although they were within twenty or thirty miles of the transmitter, found that signals reflected from the hills were causing very unsatisfactory reception, Fig. 1 being a typical example. On previous occasions when multi-path propagation has affected television reception the reflecting objects have usually been small—such as buildings or gasholders—and the reflected signals have been of considerably lower field strength than the direct signal. It has been possible in these cases to clear the trouble with simple directional aerials, but in hilly country like that of the Pennines this is not the case, for the reasons explained in this article.

Affected Districts:—The worst conditions in the Holme Moss area occur in the valleys which lie at right angles to the direction of propagation such as the valleys of the Calder, Don, Loxley and Rivelin. Probably the most badly affected town is Hebden Bridge, although in some places, notably parts of Sheffield, the situation is aggravated by low field strength.

The topography of the districts where the effect is most serious follows a distinct pattern in which the receiver is situated on the lee side of a hill, and where neighbouring hills are fairly high and close to the receiver. In such localities the reflected ray is frequently stronger than the direct ray. This is because the direct ray is attenuated by the obstructing hill, while the incident signal on the reflecting hill is so large that, despite the poor reflection efficiency, a considerable signal is reflected. Hebden Bridge is just such a place (see Fig. 2).

It has been shown theoretically by D. I. Lawson[1] that reflecting objects which are on the side of the receiving site away from the transmitter subscribe more energy to the receiver than similar reflectors on the other side. This was checked experimentally at Luddenden, where the hills are suitably placed for such a test, using a broadside array to measure the signal reflected by each hill, and it was found here that hills to the side and rear produced fairly strong reflections, while those to the front, although much nearer to the receiver contributed very poor signals.

Throughout three weeks of intensive investigation it was noticed that strong ghost images with time

* Murphy Radio, Ltd.

[1] D. I. Lawson: *Journal I.E.E.*, Vol. 92, Part III, No. 19, September 1945.

Fig. 2. A sketch map of Hebden Bridge showing the directions from which strong reflected signals were arriving.

Fig. 3. A picture received in a radio shop at Sowerby Bridge after considerable trouble had been taken with the installation.

delays greater than 40 μsec were very unusual. This corresponds to hills roughly 3½ miles to the rear or seven miles to the side, and it was decided that hills which are more than five miles away can be neglected as reflectors of seriously interfering signals. A typical example of ghost images is shown in Fig. 3, in which two strong images can be seen delayed by approximately 11 μsec and 17 μsec respectively. These delays correspond to path differences of roughly two and three miles, the path difference being given by (Time Delay) × (Velocity of Propagation) where velocity = 0.186 mile per μsec.

Experiments with Different Aerials.—For the series of experiments there were used twelve aerials, of which nine were commercial types and three were constructed in the laboratory. So that we could estimate the required directivity of an aerial for the elimination of ghost images, the polar diagram of each aerial was measured under the same conditions on a stretch of open moor.

The first practical comparison of aerials took place at Hebden Bridge. All the commercial aerials gave poor pictures, the worst being illustrated in Fig. 1 and the best in Fig. 4 (a). Fig. 4 (b), (c) and (d) show the results obtained at the same place, using a slot aerial,[2] slot aerial with a reflector, and a double-H aerial respectively. The slot aerial was too large to be mounted on the mast, and was tested on the ground, whereas all the other aerials were raised 40 feet. Details of the slot aerial are given in Fig. 5.

This led naturally to an experiment from which it was concluded that no significant change occurred as the height of an aerial was altered. Although this may appear surprising at first sight, it merely means that the *relative* strengths of the direct and indirect

[2] H. Page: *Wireless World*, May 1951, page 168.

Fig. 4. Pictures received at the same site as Fig. 1 using (a) the best of the commercial aerials available, (b) a slot aerial, (c) a slot aerial with reflector, and (d) a double-H aerial.

Fig. 5. The experimental slot aerial with reflector.

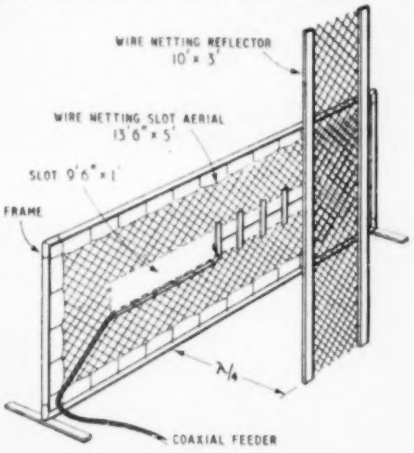

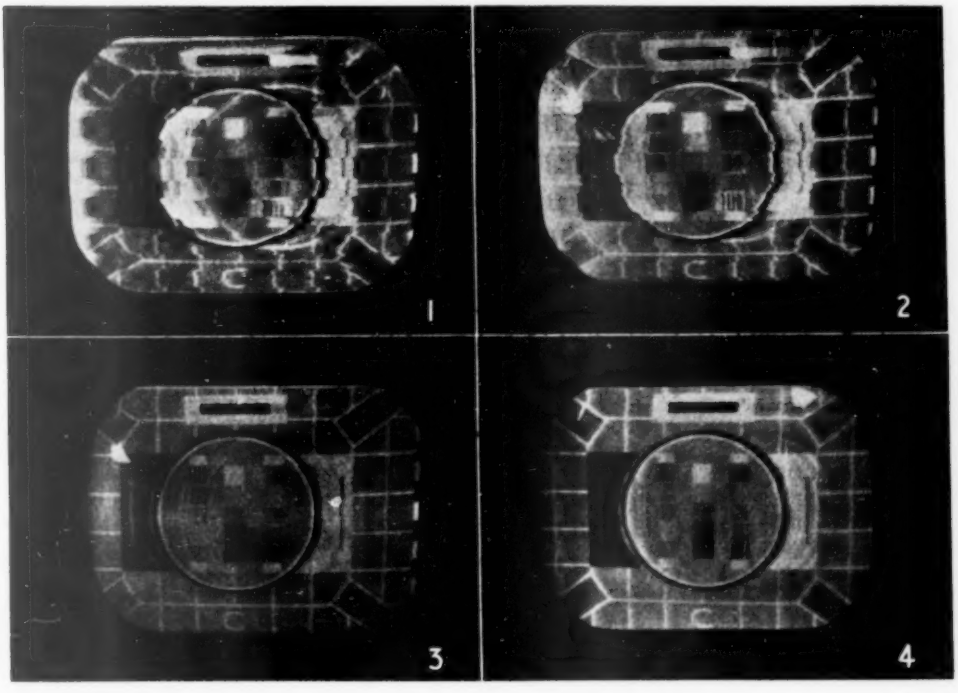

(a)

(b)

Above: Fig. 6. Pictures received at Oughtibridge using (a) the best of the commercial aerials available, and (b) the double-H aerial.

Fig. 7. Broadside array of λ 4-spaced H aerials.

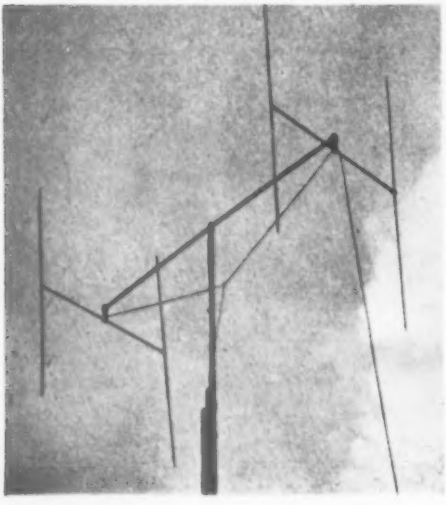

signals do not change appreciably over the limited range of height which is practicably possible.

Some of the aerials were now discarded as useless under multi-path conditions, namely, those with poor front/back ratios and large side pick-up, and tests were continued at Oughtibridge in the valley of the Don, at Rivelin (west of Sheffield) and in Sheffield itself. It became clear that the double-H type was the best of the aerials available for dealing with the situation. An example of the performance of this aerial in comparison with the best of the commercial aerials tested is given by Fig. 6.

The double-H aerial (Fig. 7) consisted of a broadside array of two $\lambda/4$-spaced H aerials mounted $\lambda/2$ apart and connected (by equal lengths of feeder) in parallel. The noteworthy feature of the polar diagram of this aerial is the small sensitivity at the sides. The front/back ratio was not so large as that of some of the commercial aerials. The polar diagram requirement for an aerial which is to have general application is minimum total pick-up from back and sides.

Use of the Reflected Ray.—At two of the sites where tests were made, a reflected signal existed which was stronger than the direct signal. With an aerial directed towards the reflecting hillside the resulting picture was of poor quality, even though the direct signal was adequately attenuated. The explanation of this is that the variation of signal path caused by the immense size of the reflecting hill gave rise to very poor definition.

It was then decided to rotate the plane of the aerial in order to learn something of the form of polarization of reflected and direct signals, and to see whether any difference might form a basis for separation. The direct ray appeared to have maintained its vertical form fairly well, but the indirect signal tended towards random polarization. This implies that rotating the plane of an aerial can reject only the direct signal, leaving the reflected one. There seemed, therefore, little to be gained by using the reflected signal, although on one occasion a picture obtained in this way was considered to be superior to the one from the direct signal which was spoiled with ghost images.

Television Standing-Wave Field:—During the Hebden Bridge experiments the necessity to maintain the position of the mast with precision was discovered, otherwise the results were inconsistent. When the mobile laboratory, on which the mast was fixed in the manner of a fire-engine ladder, was moved a yard or so, the resulting picture changed considerably in character. This was clearly due to the fact that a

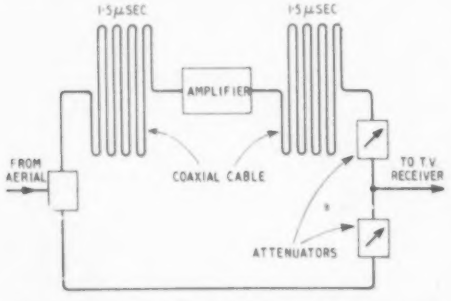

Fig. 8. A circuit for producing an artificial ghost image.

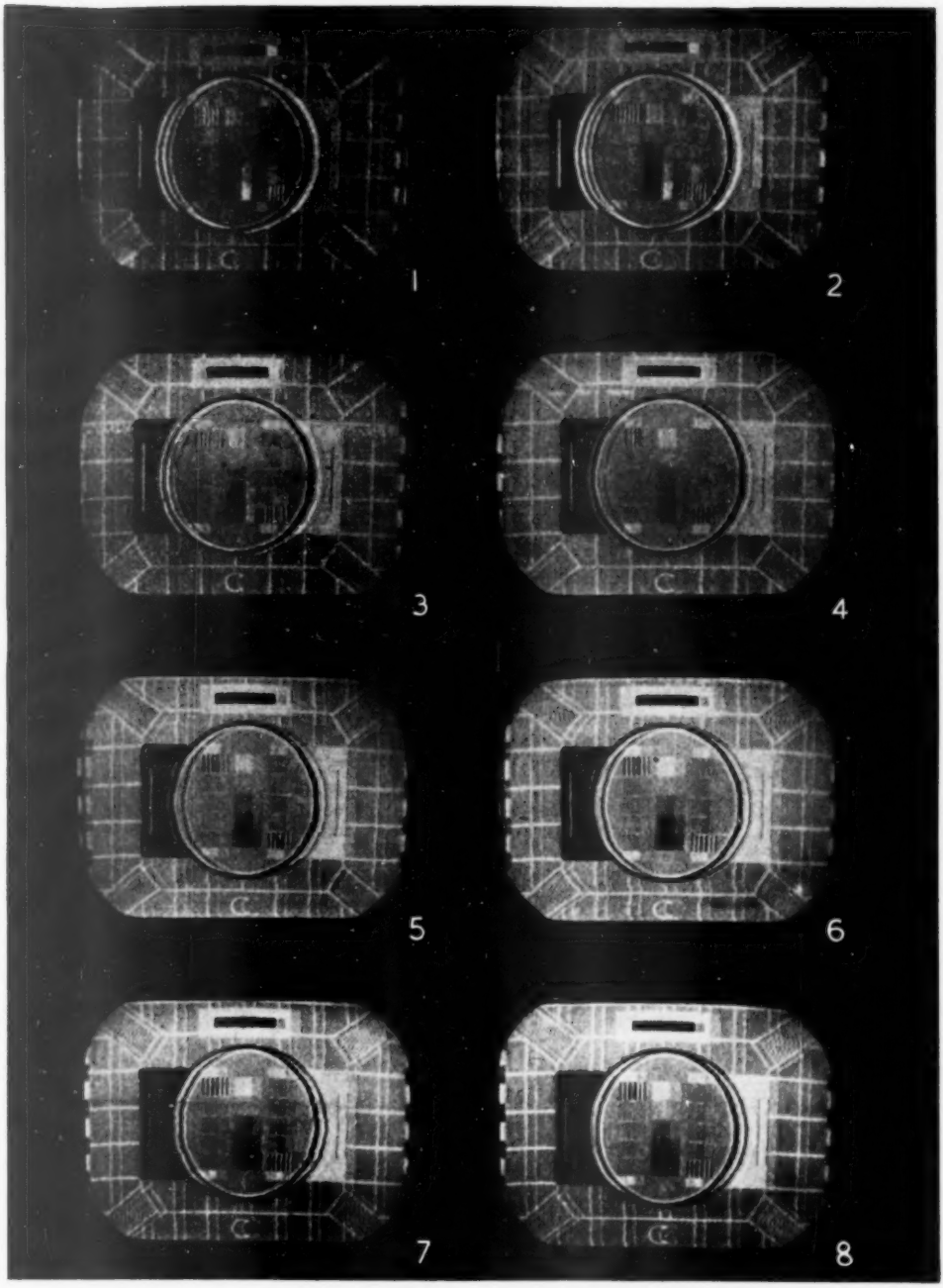

Fig. 9. The effect on the picture with variations of phase between direct and indirect signals. Photograph 1—180 deg., 2—154 deg., 3—129 deg., 4—103 deg., 5—77 deg., 6—51 deg., 7—26 deg., 8—0 deg.

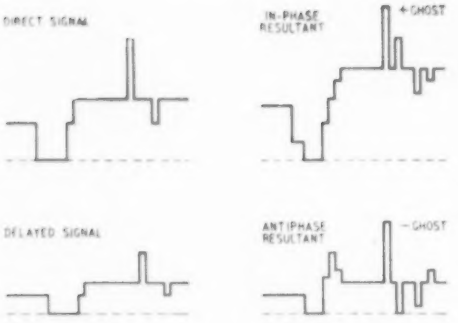

Fig. 10. Waveform of line synchronizing pulse followed by white and black bars when subject to an interfering signal which is half the direct signal amplitude and delayed 4 μsec.

Right : Fig. 11. A useful type of aerial mounting.

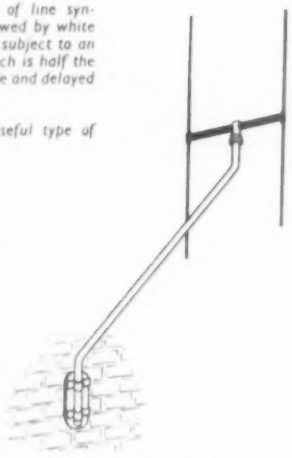

standing-wave field existed. The nature of this field is worthy of consideration, for it is rather different from the normal standing-wave field due to sound-modulated signals where the only factors governing the state of the field at a point are the relative phase and amplitude, and the only apparent effect is variation of signal strength between a node and antinode of the field. In a television standing-wave field, the path difference between the two signals also has an effect.

Since the reflected signal has followed a longer path than the direct signal, a particular element of picture information carried along the indirect route reaches the receiver after the same element which has arrived by the direct route. This delay means that, even though the mean amplitude of the reflected signal is less than that of the direct signal, the instantaneous amplitude may be considerably greater. For example, during a synchronizing pulse of the direct signal there is no carrier, while the reflected signal may be at maximum amplitude, conveying peak white information. A ghost image is thus formed, and its nature depends upon the phase and amplitude of the reflected signal.

If the modulus of the vector sum of the two signals exceeds the direct signal amplitude the ghost image will be positive, that is, white picture elements will be white in the ghost image. Should the modulus of the vector sum of the signals be smaller than the direct signal (e.g., at a node of the standing-wave field), a negative ghost will be obtained; i.e., white picture elements will be black in the ghost image. Stated mathematically, the condition for a positive ghost is that the phase difference, θ, is less than

$$\cos^{-1}(-e_2/2e_1)$$

where e_1 is the direct signal amplitude, and e_2 is the reflected signal amplitude, at the same instant.

Thus, when θ is less than 90 deg, or greater than 270 deg, the ghost images are always positive, but when θ is between 90 deg and 270 deg, the type of ghost image depends upon e_1 and e_2. If $e_1 = e_2$, then, statistically, one-third of the ghost images will be negative; i.e., when θ lies between 120 deg and 240 deg. With very small indirect signals roughly half the ghost images will be negative.

The form of a television signal standing-wave field, therefore, depends upon the time delay and the modulation.

In order to examine the appearance of ghost images as θ is varied, a circuit was set up as shown in Fig. 8. The delayed signal amplitude was arranged to be roughly half the direct signal amplitude, but even so an amplifier was necessary to overcome the attenuation of the delaying cable. Short lengths were removed from one of the cables in order to vary the phase difference between the signals, the resulting pictures being shown in Fig. 9. Exactly the same effect was obtained when aerials were moved in the standing-wave fields in the Pennine valleys.

It had been noticed also that when strong negative ghost images were obtained, the synchronization of the picture was poor. The explanation of this will be clear from Fig. 10. Under antiphase conditions a large white picture signal will cause a black ghost image, which may reduce the level of the resultant to below black level. This level will pass through the synchronizing pulse separator and may cause the timebase to fire at the wrong time. Modifications to the shape of the synchronizing pulses can occur with positive ghost images, but this effect was found to be much less serious.

One might expect that when an aerial is moved from a node to an antinode of the standing-wave field the appropriate adjustment would be receiver gain (contrast or sensitivity), whereas, as is indicated in Fig. 10, the preferable adjustment is picture brightness.

Aerial Installation:—Using the apparatus illustrated by Fig. 8, it was found necessary to attenuate all indirect signals to a level 26 db below that of the direct signals to reduce ghost images to a negligible level. Since increasing the height of the aerial did not seem to make any significant difference, it would seem to be a good idea to use the building on which the aerial is mounted as an attenuator of unwanted signals. In other words, mount the aerial on the side of the building which faces the transmitter, rather than on the chimney if no obstructions exist.

Judging from Fig. 9, a point between a node and antinode of the standing-wave field is the most desirable position for an aerial, since here the ghost image is least apparent, but the possibility of negative ghost images must be avoided, first because of the effect on synchronization, and secondly, because the resulting pictures are unpleasant.

A useful method of mounting an aerial is illustrated in Fig. 11. This form is commercially available, and enables an aerial to be fixed to a wall and then moved a few feet to avoid any negative ghost images that may appear.

The writer would like to thank Mr. R. Cook, who helped with the experiments under most trying weather conditions.

VALVE VOLTMETER

The Rectifier Section

By M. G. SCROGGIE, B.Sc., M.I.E.E.

Design of Input Circuits for Alternating Voltage Measurement

THE following article is a sequel to the one published in January describing a highly stable valve voltmeter for direct voltages only. The special feature of that instrument, it may be remembered, was that the addition of the valve circuitry to the moving-coil voltmeter did not necessitate any recalibration, since the output voltage of the valve unit was the same as its input, within a fraction of 1 per cent. But although this feature may not be common to valve voltmeters in general, most of them are similar in so far that the rectifier that fits them for measuring alternating voltages is organically distinct from the "d.c. amplifier" (really a resistance converter), so the principles now to be discussed have a much wider application than the particular system already described. The subject, in other words, is the left-hand unit in Fig. 1. This does not, of course, necessarily take the form of a completely detachable unit, though it is often made up as a flexibly connected probe.

Because the circuitry of this part is so very simple, consisting of a diode and one or two resistors and capacitors, it may be supposed that it calls for little consideration. But it is a good rule that anything with a rectifier in it calls for plenty of consideration. What follows does not claim to cover anything like the whole subject of how to rectify with a diode, but it may help to remove some common misunderstandings.

The first thing to consider is the "value" of the alternating voltages to be measured—peak, mean, or r.m.s.? Sometimes one is required and sometimes another, but for most purposes the r.m.s. value is the most appropriate, because it is the one from which the power can be calculated, regardless of waveform. Unless the contrary is specified, alternating voltages and currents are generally assumed to be r.m.s. Unfortunately the types of meter that respond on principle to r.m.s. values generally consume an excessive amount of power for the purposes chiefly in view, or have other limitations and inconveniences. Direct voltages can be measured, using the Fig. 1 technique, with very little disturbance of their source, so for corresponding alternating-voltage (a.v.) measurements the usual practice is to add a rectifier. If a suitable rectifier could be obtained with a natural square-law, the resulting readings would be r.m.s.; but the best that can be found is an approximation to a square-law over a very limited range. So for wide ranges of measurement the r.m.s. ideal is generally abandoned.

Instead, the aim is a "perfect" rectifier—one with zero (or at least negligible) forward resistance and infinite back resistance, like a switch. With such a rectifier connected in series with a high resistance, the average direct voltage across the resistance is equal to the average alternating voltage of the active half-cycles. If the waveform is sinusoidal, the average of a half-cycle reckoned over the period of half a

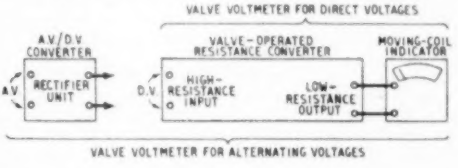

Fig. 1. Functional arrangement of the general class of valve voltmeters considered, showing inputs for direct voltage (d.v.) and alternating voltage (a.v.).

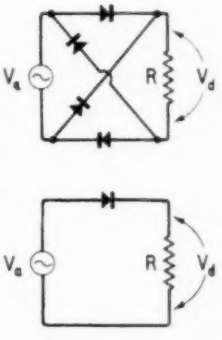

Fig. 2. Comparison of input and output voltages with (a) full-wave and (b) half-wave non-cumulative rectifier. The symbols V_a and V_d, here and in the text, do not imply any particular value—instantaneous, peak, r.m.s., or average.

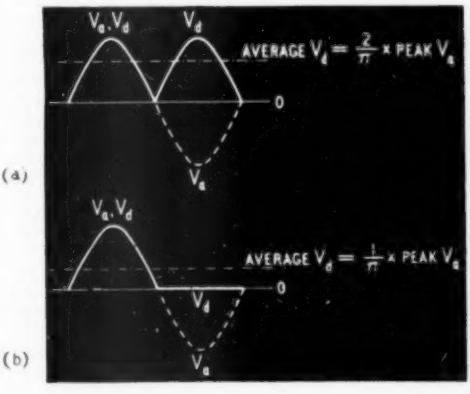

cycle is $2/\pi$ or 0.637 of the peak value, so is 0.637 0.707 or nine tenths of the r.m.s. value. With full-wave rectification this ratio holds over the whole cycle (Fig. 2(a)) so if the whole voltage across the resistor is applied to a d.v. valve voltmeter and the reading multiplied by 10/9 the result should be the r.m.s. value of the alternating voltage. But if there are harmonics in the waveform the resulting errors are likely to be of the same order as the percentage of harmonics.

Using half-wave rectification (Fig. 2(b)) each half-cycle is averaged over a whole cycle, so the readings are half as much—with sine waves, less than one third of the peak value.

Not only is the reading with a simple half-wave rectifier rather low, but at very high frequencies the stray capacitance across the load resistance (R) retains sufficient charge to be appreciable during the inactive half-cycle, so causing the reading to be higher at high frequencies than at low. The way out of these difficulties is to add so much capacitance (C) across R that the charge is almost fully retained at *all* working frequencies, down to the lowest. The result is the familiar "cumulative" diode rectifier, used in most radio receivers as well as valve voltmeters. If the rectifier really were ideal and had no forward resistance, C would charge up to the full peak value during the first half-cycle. From then until the next half-cycle it would leak through R, but provided that R and C are so large that their time-constant RC is very long compared with the period of a cycle the loss is small and the reading is very nearly equal to the peak value, which with sine waves is $\sqrt{2}$ or 1.414 times the r.m.s. value.

It might seem, then, that all that need be done is to connect a suitable rectifier in series with R and C (Fig. 3) and apply 70.7 per cent. of the voltage across R to the direct-voltage instrument described in the January issue, which would then read r.m.s. values (so long as the voltages being measured were sinusoidal).

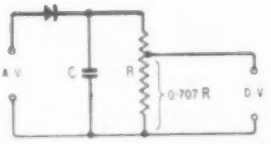

Fig. 3. Theoretical circuit of cumulative rectifier giving r.m.s. readings of sinusoidal voltages.

Fig. 4. Input output diagram for cumulative rectifier, when the charging resistance (r) is much less than the discharging resistance (R).

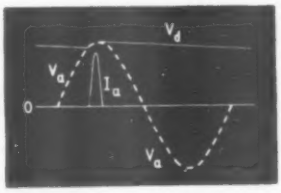

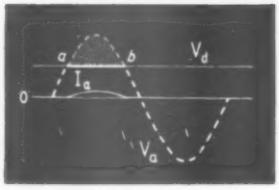

Fig. 5. If r is adjusted to reduce the output to one half, the diagram (compare Fig. 4) is altered to this.

Effective Input Resistance

In practice it is not quite so simple, however. The requirement from which all the complications spring is that the measuring system must present a very high impedance to the a.v. source. A perfect rectifier is at all times either conducting completely or not at all. Nearly all the time the charge on C biases it back so that it is not conducting, and except for any stray capacitance in parallel with the rectifier the input impedance is infinite. But at the very peak of the active half-cycle the input voltage momentarily exceeds the voltage to which C is charged (because since the last peak there has been a slight leakage through R), so the rectifier conducts and restores the charge to full peak voltage. If the forward resistance of the rectifier really were nil, the charging process would be instantaneous and the charging current infinite; in reality, of course, charging takes an appreciable time, but as it is small compared with the whole cycle the current is correspondingly large compared with that which discharges through R (Fig. 4). For example, if the peak V_a were 10V, and R were 100kΩ, the leakage current would be nearly 0.1mA; and if charging occupied one twentieth of the cycle the charging current would have to average $20 \times 0.1 = 2$mA over that period. So although most of the time the input impedance would be infinite, during 0.05 of each cycle it would be about $10/2 = 5$kΩ.

If one insists on a single figure for input resistance, the most reasonable reckoning is on a basis of power dissipation. The forward resistance of the rectifier being neglected, the only dissipating component is R, and the wattage is V^2_d/R. V_d being practically equal to the peak V_a, or (with sinusoidal input) $\sqrt{2}$ times the r.m.s. V_a, V^2_d/R can be taken as equal to $2V^2_{a(r.m.s.)}/R$. If the effective a.c. input resistance is denoted by R′, it must by definition be such that the dissipation is $V^2_{a(r.m.s.)}/R'$. By equating the dissipation expressed in these two different ways, R′ is seen to be equal to R/2, subject to the approximation assumed.

When the source of V_a is a sharply resonant circuit, the flywheel effect of the circuit keeps the input waveform reasonably sinusoidal, and although the damping due to the voltmeter is concentrated into a small fraction of each cycle, its effect is practically the same as that of a resistor of value R/2. In the example considered, $R' \sim 50$kΩ, and if the dynamic resistance of the tuned circuit were also 50kΩ the effect of connecting the rectifier circuit would be to reduce V_a by one half, without causing much change of waveform. The tuned circuit is analogous to the pendulum or balance-wheel of a clock, which, though it bears a very uneven load during its cycle, has enough stored energy to maintain a smooth, regular swing.

But when the source is a non-resonant generator with internal resistance, such as the output of a valve with resistance coupling, the effect is quite different. During the active part of the cycle the source resistance (say 50kΩ) limits the charging current to an amount which clearly cannot be many times the discharge current through 100kΩ, so must spread over a considerable proportion of the cycle. Consequently the simplifying assumptions break down and calculation becomes much more difficult. At the same time practically the whole of the enlarged active peak is cut off by the voltage drop in the 50kΩ, so the

waveform at the voltmeter input is highly distorted.

Fig. 5 shows in thick line this waveform when the source resistance (call it r) is adjusted to reduce the rectified voltage to one half, CR being assumed sufficiently large to maintain it very nearly steady. Current is flowing from the source during the period a to b, and since a sine wave reaches half its peak at 30° and 150° this period is 120° or one third of the whole cycle. The voltage driving this current through r is represented by the shaded area, and can be averaged over the whole cycle by measuring this area and dividing it by the length representing the cycle period. It is about 0.11 times the sine peak. The mean rectified voltage (driving the discharge current through R) having been adjusted to half the sine peak, the mean charging voltage is 0.22 times the discharging voltage. Since the mean charging and discharging currents must be equal, the ratio of r to R must be 0.22—not 0.5 as with the resonant source.*

Alternative Circuits

Experiments with an oscilloscope confirmed all the foregoing statements, and brought out very clearly that with a non-resonant source the distortion and the drop in output voltage are considerable even when r is less than 1% of R. This fact is of great importance in valve voltmeters, but before following it up the reader might note input resistance as an example of how this apparently simple circuit is commonly misunderstood. In one textbook it is stated that the input resistance (at 60 c/s) is equal to the value of series resistance required to drop the full-scale deflection to one half. Without any guidance to the contrary the reader might easily assume that input resistance found in this way (presumably with a non-resonant source) meant the same thing as input resistance calculated on a power-dissipation basis, or measured with a resonant source. If so he would be seriously misled.

This is not the end of confusion about input resistance as will soon be seen; but in the meantime it should be noted that with the Fig. 3 type of rectifier connection the source resistance r includes the forward resistance of the rectifier. So even if the source itself has no resistance, or it is allowed for by regarding the voltage to be measured as the voltage at the terminals of the instrument, there is still a loss or error due to this forward resistance. Fig. 6, which is a generalization of the half-drop example considered with Fig. 5, shows that to get the rectified voltage within 1% of the peak input it is necessary for R to be something like 2,000 times the rectifier forward resistance. Now although the forward resistance of a thermionic or a germanium diode with inputs of at least several volts may be of the order of 100Ω, so that for the high ranges this source of error could be kept negligible by making the load resistance R no more than one megohm, at low voltages the rectifier resistance rises to thousands of ohms, so that the values of output and peak input rapidly diverge as the input is reduced, causing the well-known bend at the foot of the calibration curve. Even if one were content to put up with considerable curvature by using a 1-MΩ load resistance, one would have to face the fact that connecting the valve voltmeter would cause an appreciable drop in the voltage to be measured, even when the resistance of the source was only the hundreds of ohms! So the oft-repeated claim for valve voltmeters in general, that they can confidently be used for measurements on high-impedance circuits, can hardly be accepted without reserve—even before starting to consider disturbance due to input capacitance. Taking this together with the fact, emphasized in the previous article, that only exceptional amplifier valves will allow more than a megohm or two in their grid circuits without appreciable drop therein due to leakage current, one sees that valve voltmeters demand a good deal of care in design if they are to come anywhere near their popular reputation.

Connecting the rectifier as in Fig. 3 has one important advantage: the output voltage is almost perfectly smooth. It is taken for granted that in order to avoid low-frequency error the time constant CR must be many times the period of one cycle; for example, if the lowest frequency to be measured is 20 c/s, the period is 1/20, and the choice of CR would be at least 0.5 and probably 1—say 10MΩ and 0.1 μF. The ripple on the output would then be so small as hardly to need additional smoothing. Fig. 3 is not unusual if the rectifier is a germanium diode, which has many advantages. But unfortunately the backward resistance of germanium diodes obtainable up till now is far too low if the load resistance is required to be of the ten-megohm order, for it is

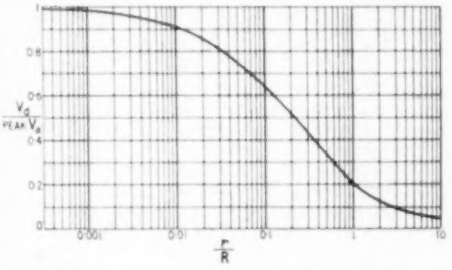

Fig. 6. Effect of the ratio r/R on rectification. (Data by D. A. Bell).

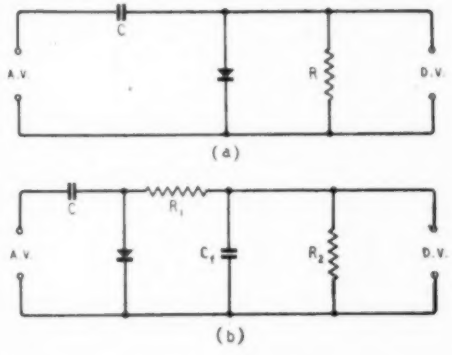

Fig. 7. Series-C modification needed when the voltage source includes a direct voltage or an open circuit. Owing to the large a.v. component passed on, a filter is desirable (b).

* This subject is discussed in greater detail by D. A. Bell in "Diode as Rectifier and Frequency-Changer," *Wireless Engineer*, Oct. 1941, pp. 395–404.

effectively in parallel. For high-impedance instruments the only kind of rectifier is the thermionic diode, hereafter to be called the diode. If it is connected as in Fig. 3, and R is many megohms, there may be undesirable effects from the heater circuit. With a carefully insulated heater winding, however, it should not be impossible to exclude such effects. Stray capacitance is harmless, for it comes across C. But with any type of rectifier the Fig. 3 arrangement is restricted to uses in which there is a highly conductive path through the source, and no direct voltage. To avoid these restrictions the circuit is usually rearranged as in Fig. 7(a). Here the d.v. output is accompanied by the full alternating component. This ought to be removed, because even if one does not measure voltages of sufficiently low frequency to make the pointer vibrate there is risk of overloading the amplifier. So some sort of filter is required. Seeing that there is (as Fig. 3 indicates) some output voltage in hand, there is the obvious possibility of using the series part of R as a filter element (Fig. 7(b)). If rectification were 100 per cent, the ratio of R_1 to R_2 to make the output equal the r.m.s. value of sinusoidal input would be $(\sqrt{2}-1):1$. With rectification less than 100 per cent (as it must be), R_1 could be reduced to compensate—if the rectification percentage would oblige by remaining constant.

Although the Fig. 7 arrangement is broadly equivalent to Fig. 3 the fact that the approximate effective input resistance (to resonant sources) is no longer R/2 is often overlooked. This can be seen in Fig. 7(a) by noting that in addition to providing the same d.c. through R as in Fig. 3, the source also has to provide an a.c. through R (the impedance of C being negligible). By the theorem of superposition these can be reckoned as if they flowed separately. So the effective input resistance is the original R/2 in parallel with R, making R/3.

But when the circuit is complicated by filtering, the input resistance is modified accordingly. Fig. 7(b) is one that might be used to fit the amplifier already described. As before, input resistance is half d.c. resistance in parallel with an a.c. resistance. The d.c. resistance is $R_1 + R_2$, and a.c. resistance (C_r being large enough for its impedance to be neglected) is R_1. Input resistance is therefore $\frac{R_1(R_1+R_2)}{3R_1+R_2}$; if $R_1 = (\sqrt{2}-1)R_2$ it is roughly one quarter of R_2.

Some more usual arrangements are shown in Fig. 8. If it is desired to pass the whole rectified voltage to the amplifier, it can be said for (a) that the filter is not appreciably loaded, so the effectiveness of R_1 can be increased by using a higher value. But in (b), where R_1 and R_2 form a potential divider as in Fig. 7, R_3 seems to serve no useful purpose and only reduces the input resistance.

Zero Displacement

Besides having an almost infinite backward resistance and a reasonably low forward resistance (given at least several volts input), the thermionic diode has the advantage of not being easily destroyed by excessive input voltage. The usual maximum rating for suitable diodes is 420V peak inverse, which in practice means $420/2\sqrt{2}$ or 150V r.m.s. input. It is rather useful if the a.v. ranges go up to 250 to include mains voltages, and some makers of valve voltmeters apparently run the risk of exceeding the diode's rating. If the instrument is mainly for high voltages, at not more than about 10Mc/s, the type of diode used for flyback e.h.t. (such as the EY51) is very suitable, as it is quite safe up to at least 8kV peak input.

But it is the low-voltage end that is usually most important, and most difficult to arrange. For not only is there the awkward "bottom bend" but thermionic diodes have the unfortunate complication of "zero current." This is the current that flows in the anode circuit when there is no applied voltage. What matters most is the voltage, negative at the anode, that this current sets up across the load resistance. The current itself varies a good deal from one sample to another of even the same type of diode, but in any given sample depends mainly on the heater voltage. Over a considerable range it is roughly proportional to it, as shown in Fig. 9, which refers to a typical diode. Both current and voltage obviously depend also on the resistance in the anode circuit, and it is an interesting experimental fact that over a very wide range of resistance the voltage is very nearly proportional to the logarithm of the resistance, as shown in Fig. 10 for the same diode. Note that the slope of these nearly straight curves is only very slightly affected by heater voltage.

Now the zero displacement resulting from this effect must obviously be corrected in some way. And since the required correction drifts so steeply with heater voltage,

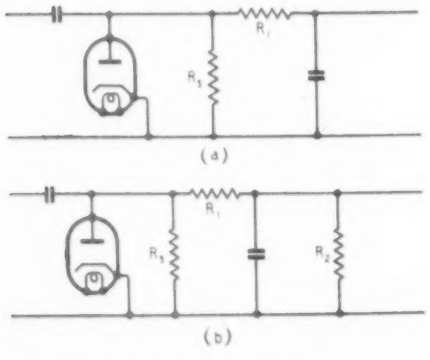

Fig. 8. Alternative load and filter circuits.

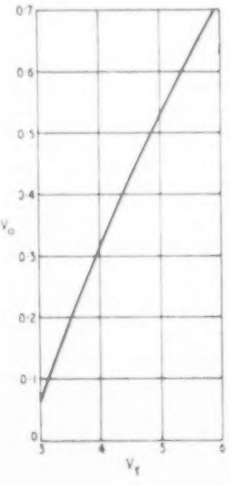

Fig. 9. Variation of "zero voltage" (Vo) with heater voltage (Vf) of typical diode, with a load resistance of 20MΩ.

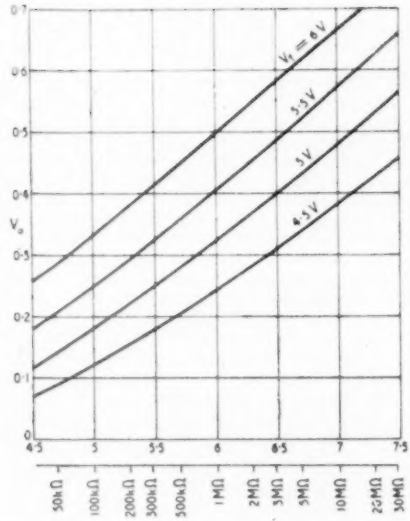

Left : Fig. 10. Variation of V_o with load resistance (R), for several values of heater voltage.

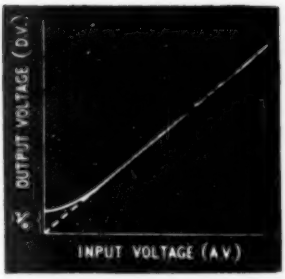

Right : Fig. 11. Method of arranging for the greater part of an a.v. calibration curve to fit the d.v. scale.

the usual method is to balance it out with another diode of the same type, in conjunction with a preset adjustment to take up any initial difference between the two. This method fits very well into the instrument already described, which is symmetrical. The second diode, which can conveniently be one of the same pair as the first in a double diode, can be connected to the input of the balancing amplifier valve. Fig. 9 shows that the zero displacement voltage can be much reduced by running the heater at, say 4.5V instead of the rated 6.3V, and experiment shows that, with this type of diode at least, and with 10-20MΩ load resistance, the calibration curve is displaced bodily with hardly any change of shape ; but Fig. 9 also shows that *variation* of displacement (which is what matters) is not reduced, so there is really nothing to be gained by underrunning the heater.

Non-linearity at Low Voltages

And now at last it is necessary to deal with the most troublesome feature of all—the bottom bend. This, as we have seen, exists because at low input voltages the forward resistance of the diode cannot be neglected in comparison with the load resistance (in parallel with the backward resistance, if that is not infinite). One result is that even with the highest practical load resistance it is not possible to measure voltages below about 0.1 at all. Another is that up to at least several volts the curvature prevents one from using the same linear scale for all ranges. The only effective remedy is pre-diode amplification, and that calls for very skilful design to avoid drastic reduction in accuracy or frequency range or both. Even with the most modern wide-band amplifier technique one could hardly hope to cover 20c/s to 200Mc/s with good accuracy, or even at all. In any case it is a subject in itself.

An attractive way of dealing with the matter is that proposed by R. Kitai*, who deliberately arranges for a certain amount of zero displacement, v_0 in Fig. 11, so that when the curve does straighten out it will coincide with a straight line through the origin, and by suitable adjustment of the slope can be made to fit the common linear scale, at least from the point where the curve joins the straight line. Mr. Kitai places this point at 0.2V, but this seems over-optimistic, for neither the type of diode specified by him nor any other tried by the present writer has been found to approximate reasonably closely to a straight line down to such a low voltage, even with 20MΩ load resistance. Not only so, but when an accurately-drawn input output voltage curve is examined it can be seen that there are appreciable differences in slope and zero displacement between the straight lines that best represent even the upper ranges of it. Except for rough work, then, a single preset adjustment of slope and zero displacement for all ranges is not good enough.

Scale Fitting

There are two alternatives. One is to abandon the idea of using the same linear scale for direct-reading a.v. as well as d.v., and to use a calibration curve. If you agree that almost anything is worth while to escape from a calibration curve, you will prefer the second alternative, which is so to contrive the range switching as to fit the curve as nearly as possible to the existing linear scale on all ranges. This will cause the pointer, set to zero for d.v., to move up from zero on a.v. The only range on which this matters is the lowest, because on all the others the first 30 per cent or so of the scale is better served by a lower range. The top readings on the d.v. ranges in the meter already described are 1.5, 5, 15, and 50 ; so the required extent of the ranges is 0–1.5, 1.5–5, 5–15, and 15–50. The rectification characteristic of a normal diode can be fitted with satisfactory accuracy to all except the first, which must be treated as if there were a still lower range by disregarding all below about 0.5 V. For these lower voltages one must either use a calibration curve or embody it in the meter by marking an extra scale.

The first step is to make as accurate calibration curves as possible for at least the first three ranges, using the Fig. 7(b) circuit with R_2 equal to what has already been chosen for the amplifier (15MΩ in the instrument already described) and R_1 equal to $\sqrt{2}-1$ times as much (6.2MΩ in that example). If the diode were a perfect rectifier, and the input were perfectly sinusoidal, all the curves would be straight lines with a 1 : 1 slope, and all the readings would be the correct r.m.s. values of the input voltage. In reality, of course,

* *Electronic Engineering*, Oct. 1950, p. 420.

the slope gradually approaches 1, and the best straight lines representing the curves over the effective parts of the ranges cut the vertical axis at different points above zero. The following are the results of a test on an EB91 :

Range, V	Slope	v_o (Fig. 11)	Suitable value of R_1 (MΩ)
0.5—1.5	0.92	0.13	4.5
1.5—5	0.97	0.18	5.6
5—15	0.98	0.22	6.0
15—50	0.99	0.31	6.1

The slopes can be brought up to 1.00 by making the range switch reduce R_1 to the values shown in the last column. This, incidentally, varies the zero setting in two opposite ways : by varying the total zero voltage from anode to cathode (see Fig. 10) and by altering the proportion of that voltage passed to the amplifier. The net effect is small, and in any case can be taken care of by the second range-setting adjustment—that needed to provide the appropriate v_o. To do this, and at the same time retain the full compensating effect of the balancing diode, one would have to provide a complete duplicate of the first diode circuit with its range switching, plus a switched preset v_o from some d.c. source. But fortunately a much simpler system can be devised to give results that are practically indistinguishable even with high-grade equipment.

The slope is adjusted by varying R_1, as suggested ; and the appropriate v_o for each range is derived by making the balancing diode yield just that much less than the zero voltage of the signal diode. This is done by reducing its coupling resistance, in accordance with Fig. 10. It is reduced sufficiently to meet this requirement even though (with the object of making a single untapped resistor do for each range) the whole of the voltage is passed on to the amplifier, and not only about 70 per cent of it as with the signal diode. If the curves in Fig. 10 were perfectly parallel the result would be that the balancing voltage would vary with heater voltage at a rate 40 per cent higher than the zero voltage to be balanced, but it conveniently happens that the converging of the curves towards the left just about offsets this effect over the range of resistance needed to provide v_o.

The circuitry for both diodes, designed on these lines, is shown in Fig. 12, with the adjacent parts of the direct-voltage unit sketched in lightly. Of course there are other ways of arranging the range-adjusting resistors. The values found correct in a particular case are specified as a guide. The procedure for final adjustment is rather like that for tracking a superhet. With a rheostat to provide the balancing diode load (R_b), and another for the variable part of R_1, R_b is set to the estimated value for the range, and R_1 adjusted, if necessary, to make the instrument read correctly at full scale. Then the reading at about one-third scale is checked. If it is high, the slope is not enough, and R_1 must be reduced. It is adjusted until the difference in reading at full and one-third scale is correct ; R_b is then readjusted to take up any equal displacement of these points. On the lowest range the best tracking is actually obtained if the instrument reads very slightly high at these points and a similar amount low at about two-thirds scale. When the best settings have been obtained for all ranges the rheostats can be replaced by suitable fixed resistors, unless one prefers the refinement of preset components and can tolerate their bulk and expense. They need not be adjusted very precisely, especially on the upper ranges.

To check the adequacy of heater-voltage compensation with this simplified circuit, calibration was carried out very carefully over the range 0–1.5V, with the heater voltage of the EB91 double diode adjusted first to 6.0V and then to 4.5V. The difference caused by even this 25 per cent drop varied from imperceptible at the ends of the scale to barely perceptible (0.003V) at the middle. This of course is well below the probable error from other causes.

The need for the source of calibrating voltage to have a low resistance is emphasized by the fact that a perceptible drop in reading on the 50-V range occurs when 2kΩ is inserted in series, and 1 per cent with 10kΩ. Errors of several per cent can be caused by waveform distortion in a source transformer, particularly if controlled by a series primary resistance.

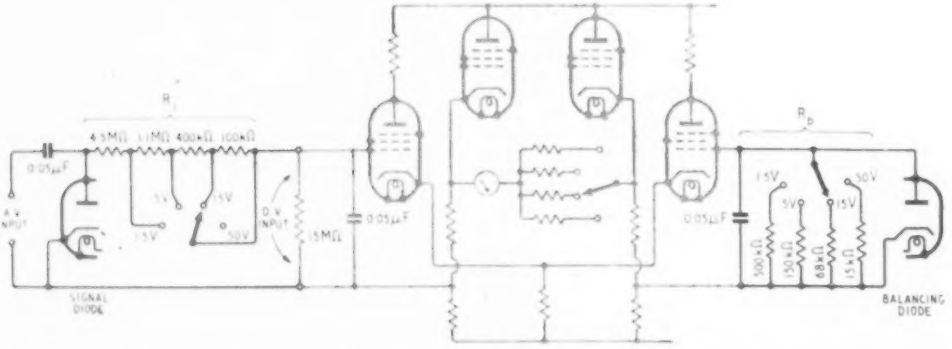

Fig. 12. Complete circuit diagram of a.v. adaptor, showing connections to the partly drawn d.v. voltmeter previously described (Jan. issue). Typical resistor values are shown for the EB91 double diode.

Ready NOW!

APPLICATION REPORTS

and circuit data on

BRIMAR VALVES

STIFF, LEATHERETTE, LOOSE-LEAF RING BINDER WITH GOLD-BLOCKED LETTERING Size 9" × 8"

IN order to meet the demands of engineers engaged in the electronic and allied industries for more complete information on Brimar Valves, a loose-leaf volume of Application Reports has been prepared. In addition to the usual technical information, these reports will contain measured performance data in typical circuits, together with comprehensive curves of the various valve parameters so necessary for the convenience of the circuit designer.

Current equipment Brimar Valves will be included in this service; new types as they appear will be covered by data sheets whilst the application data is being prepared.

The volume will also include circuit reports and other information which is issued from time to time by the Valve Applications Department.

The complete service will be available on an annual subscription of 20/- (including the issue of binders). Additional copies of individual reports can be obtained at 2/6 or 5/- each, depending on the type.

We anticipate a heavy demand for this service and, therefore, advise all who are interested to reserve their copy without delay. Send your enquiries to:

Publicity Department, (Application Reports),

Standard Telephones and Cables Limited

Radio Receiver Valve Division, Footscray, Kent *FOOtscray 3333*

acos

high fidelity

MICROPHONES

FOR PUBLIC ADDRESS
RECORDING
AMATEUR RADIO

TYPE MIC 22

TYPE MIC 22 incorporates the famous Acos "Filtercel" insert giving extreme sensitivity and high fidelity. Response is substantially flat from 40-6,000 cps. The microphone is vibration and shock-proof and is not affected by low frequency wind noises. Two alternative mountings are available for the MIC 22 head:

MIC 22-1 is for fitting to any British or American type standard floor stand or for use as a hand microphone.

MIC 22-2 is a complete desk stand unit with cable side entry.

Price £6.6.0 (Either Model)

Brief Specification

Output impedance	*Equivalent to approximately .002 Mfd (.8 megohm at 100 cycles)*
Omni-directional	
Frequency response	*Substantially flat from 40 to 6,000 cps.*
Recommended load resistance	*Not less than 5 megohms*
Output level	*Minus 50 db below 1 volt bar*

TYPE MIC 16

Brief Specification

Recommended load resistance	*Not less than 1 megohm*
Output level	*68 db ref 1 volt/dyne/cm².*
Frequency response	*Substantially flat from 30 to 10,000 cps.*
Directivity	*Non-directional*

TYPE MIC 16 incorporates the Acos Floating Crystal Sound Cell giving a response substantially flat from 30-10,000 cps. Performance is unaffected by vibration or shock and low frequency wind noises. As in the case of the MIC 22, two alternative mountings for the MIC 16 head are available:

MIC 16-1 is for fixing to either British or American type floor stands.

MIC 16-2 is a complete desk stand unit with side cable entry.

Price £12.12.0 (Either Model)

COSMOCORD LIMITED - ENFIELD - MIDDLESEX

ORIGINS OF RADAR

Background to the Awards of the Royal Commission

This article deals only with those principles and devices that formed the subject of successful claims before the Royal Commission on Awards to Inventors for services rendered to the Nation: it is largely based on evidence given to the Commission. No attempt is made here to ascribe particular developments to individual claimants, but a list of the claimants, their claims, awards and short biographical notes is given at the end of this article.

THE speed with which Sir Robert Watson-Watt's suggestions for radio-detection of aircraft were given practical effect was probably due to the fact that he and his colleagues were familiar with cathode-ray tube techniques and with the application of these techniques to ionosphere sounding. Still earlier, they had used the techniques for the study of the waveforms of atmospherics and then for a twin-channel cathode-ray direction finder (CRDF).

Those who to-day see oscilloscopes left "on" for hours at a stretch (possibly even during a lunch-hour interval) may be interested to know that some of these early tubes cost £30 (1920 prices) and lasted for 10 hours. The trace of a transient was so faint that the observer had to stay ten minutes in pitch darkness before he could see it.

An excellent opportunity for an extension of the use of c.r.ts was given when the team studying the nature of the ionosphere under the direction of Sir Edward Appleton came to work at the Radio Research Station. At first, the frequency-change method (due to Appleton and Barnett) of measuring the equivalent height of the ionosphere was used. Later, a change was made to the "pulse" method of the Americans, Breit and Tuve, which gave much more easily interpreted indications, especially when more than one echo was present. The "display" (to use the modern term) was a Duddell oscillograph, observed on a rotating mirror and photographed on a film whose movement provided the time-scale. Watson-Watt provided a c.r.t. with a time-base, synchronized to the pulse-recurrence (the first of its kind) for monitoring the indications of the Duddell oscillograph. It was soon obvious that the monitor provided all the necessary indications and was much easier to handle than the mechanical oscillograph.

The first transmitters used in ionosphere research were based on the "squegger" circuit—now regarded as a type of blocking oscillator. Later, this was superseded by the much more efficient low-power modulation of a c.w. transmitter based on the developments of co-workers at Cambridge.

Concurrently with the development of a better transmitter, much work was done on receiver design; the characteristics required being high gain, minimum distortion of the received pulse and quick recovery from the paralysis caused by the pulse received direct from the transmitter. The development of the receiver and the display arrangements are described at length in "The C.R.O. in Radio Research" (H.M.S.O., 1933).

This was the state of knowledge at the Radio Research Station when the Government's advisers were becoming very worried about the problem of sufficient warning of air raids.

In 1934, the Director of Scientific Research, Air Ministry, wrote to Watson-Watt asking him to give his opinion on the possibility of developing a technique of destruction by radio (popularly called "death rays"). Watson-Watt replied (after making some calculations) that *radio-destruction* appeared to be quite impossible, but *radio detection* might be worth investigating.

The Defence Committee then asked Watson-Watt to expand the latter theme. In a memorandum dated February 27th, 1935, and headed "Detection and Location of Aircraft by Radio Methods" he set out in detail and with remarkable foresight the conditions necessary for an effective radar system. Among the topics discussed were: measurement of three co-ordinates (range, bearing and elevation) to give location: need for "radar frontiers" formed by a chain of stations: advantages of shorter wavelengths: IFF (Identification, friend or foe?). The need for high-power transmitters was stressed, and the possibility of radars which automatically follow a target was mentioned.

This report was written *before a single echo had been seen* by the workers at Slough. After a simple demonstration that aircraft did in fact reflect radio waves authority was given for a small team of workers to start experiments at Orfordness in Suffolk. Radar had started.

Early Days

The move was made on May 15th, 1935. The transmitter (built on steel scaffolding for flexibility) used a large Naval silica valve directly coupled to the aerial (a horizontal dipole on a 70ft mast) modulated by a transformer-coupled low-power valve. The wavelength was about 50 metres. The receiver (fed from a similar aerial) was one of the Radio Research Station's "ionosphere" receivers but with the acceptance band widened. The pulse duration was about 10 microseconds, but its shape was not particularly good. On June 16th, aircraft were being followed out to 17 miles—good progress for one month's work. A month later, the range of detection was over 40 miles.

RDF.—At about this time, the technique became officially known as RDF. The origin and intended meaning of these letters has been the subject of much speculation. The fact seems to be that the letters DF were intended to suggest that the technique was a form of direction finding. This was done to confuse a potential enemy: at that time the workers saw no

solution to the problem of direction-finding pulses, and were modest enough to think that the solution would be long in coming. The first letter, R, was chosen "out of the bag." As mentioned later, the DF technique was thought of soon after RDF was so named. The (wrong) explanation followed that they stood for "Reflection Direction Finding" or "Range and Direction Finding."

An unexpected difficulty soon arose through the discovery of a reflecting layer (christened the "Z" layer) at a height of between 10 and 20 km. This set an upper limit to the detection range when using wavelengths susceptible to reflection from the layer, with aerials radiating a substantial upwards component. Accordingly, a change was made to 25 metres and, later (in 1936), at Bawdsey, wavelength was again halved to 12½ metres to avoid jamming. This became the nominal wavelength of the "Chain" stations.

DF.—Until the direction-finding problem was solved, the only possible way of locating an aircraft was to use two radar stations, measure the range from each and plot the position by triangulation. This was simple when only one aircraft was present, but two aircraft gave four possible positions and N gave N^2 positions. The system would therefore be operationally useless.

The solution came unexpectedly soon, and rather embarrassingly so in view of the would-be confusing name of "RDF." This was the use of a vertical array of crossed pairs of horizontal half-wave dipoles connected to a radio-goniometer. Success was immediate and in January, 1936, good bearings were obtained on an aircraft 25 miles away flying at 7,000ft. The first radio-goniometers, designed at Slough, were of the two-section type with two search coils, one moving in each field coil. Later, it was shown that they suffered from an inherent octantal error, and the more conventional type (with a single search coil) superseded them.

Sense.—An accompanying problem to that of d.f. was the determination of "sense" (i.e., an echo is on a North-South line: is it North or South?). In normal d.f. on vertically polarized waves, this is determined by using a vertical (all-round) aerial and comparing the phases of the signal received on it with that in the d.f. aerials. This was not possible at Orford as the polarization was horizontal. The difficulty was solved by placing dipole reflectors behind the crossed dipoles, equipped with relay-operated switches which closed and opened gaps at the centre of the reflectors.

Height-finding.—In the Watson-Watt memorandum of February, 1935, three co-ordinates were stipulated for complete location, i.e., finding the position of an aircraft in space. Height-finding (or, more correctly, angle-of-elevation finding which, in conjunction with range finding, gave the height of an aircraft) was actually achieved before direction finding. The technique was copied from that used at Slough for finding the angle of arrival of waves from transatlantic transmitters which had suffered one or more reflections from the ionosphere and the sea. A probable direction for air raids was assumed, and two horizontal dipoles were erected at right angles to this direction and spaced by a convenient distance. Echoes reached one dipole before they reached the other, and there was therefore a phase-difference between the received signals. The echoes received on one aerial were fed to the field coils of a radio-goniometer in such a way that a rotating field was produced.

The search coil picked up a voltage whose phase depended on its position, the instrument acting as a phase-shifting transformer. The signal in the search coil was compared with the echo from the second aerial, and the phase-difference thus determined.

This method of height-finding suffered from several disadvantages. (1) It gave increasingly inaccurate readings as the angle of elevation decreased; (2) it required a knowledge of the direction of the aircraft, and failed to give any reading as the direction of the aircraft approached the "end-on" direction of the dipole.

A greatly improved method, which was tried in 1936 at Bawdsey, was universally adopted on metre-wave land stations. Consider the signals received from an aircraft on two horizontal dipoles fixed at different heights on the same vertical mast. The *strength* of signals will depend on the different vertical radiation diagrams of the two aerials—different because of differing heights above the earth or sea. It can be shown that the *phase difference* between the signals is zero—a fact not recognized at the time by American workers. Because of this co-phasal property, if the amplitudes of the signals are applied directly to the field coils of a radio-goniometer, the search coil can be set to a minimum, and the position of the search coil will give an indication of the angle of elevation of the downcoming waves. Under certain circumstances there will be an ambiguity of indication: the angle of the search coil will correspond to more than one angle of elevation. This ambiguity is resolved by changing from one of the dipoles to another at yet a third height.

Transmitters.—The two main requirements for radar transmitters—shorter pulses and higher power—were first tackled.

The problem of higher power was attacked by obtaining large (1-kW) silica valves whose design was a speciality of the Navy's Signal School at Portsmouth. As these valves would only be conducting for a short time (10 microseconds), followed by a rest period of 1990 microseconds (corresponding to a recurrence rate of 50 pulses per second), thermal effects were negligible. It was therefore possible to overrun them considerably, and peak powers of sixty times the rated figure were obtained. By using silica valves specially designed for radar much higher power was subsequently obtained. In 1939 silica tetrodes were developed.

Transmitter Monitor.—During the early days much effort was expended in getting "lots of power" into the aerial. The problems of frequency variation during the pulse and of reasonably square pulse shape were of secondary importance. The need for a pulsed-transmitter monitor was recognized, and provided. It allowed observation of the pulse shape, and, in conjunction with a variable-frequency oscillator, showed up any signs of frequency variation during the pulse. This device cast so much light on the design of the early pulse transmitters, and taught the workers so much, that it was not needed in later models.

Coupling to the Aerial.—During the early experiments, working into a single dipole with fairly short transmission lines, the problem of matching the transmitter to the lines was not too difficult. With increasing lengths of lines and more elaborate arrays, this direct coupling became impracticable, and an

isolating or "buffer" stage had to be interposed between the oscillator and the open-wire lines.

Transmitting Aerials.—The first transmitting aerial was a single horizontal half-wave dipole slung between two 70ft masts. Later, metal-covered hollow wooden spars, threaded through the structure of 240ft wooden towers, were used. In the final CH (Chain) stations curtain arrays, suspended from cantilevers fixed to 360ft steel towers took their place. Owing to the effect of the ground, the vertical radiation pattern consisted of several lobes. An aircraft would be lost to the radar observer if it flew into the minimum region between two lobes. The technique called gap filling, which consisted of using alternative aerial arrays at different heights, overcame this difficulty.

Receiving Aerials.—The first receiving aerial was exactly like the transmitting aerial. The next design, using the hollow wooden spars, was used subsequently for all CH aerials. The receiver aerials were necessarily more complicated, as they had to give direction-finding facilities (crossed dipoles), height finding and gap filling (sets of dipoles) at different heights.

Lines.—For satisfactory d.f. it was essential that there should be no coupling between the lines from the aerials to the receivers. As no suitable low-loss concentric lines were available at the time, these were made locally by threading copper wire, carrying triangular ceramic spacers, into copper tube.

Receivers.—In the early days the ideal receiver characteristics were not obvious, and so it was decided to make an i.f. amplifier lavishly equipped with adjustments. The assistance of the Radio Department of the N.P.L. at Teddington was called in. Later, a receiver was developed with ganged adjustments for gain and for bandwidth. This became the prototype for the CH receivers made by a commercial firm. The r.f. amplifier used two stages of push-pull amplification and was followed by (usually) five stages of i.f. amplification at 2 Mc/s. All possible precautions known at that time were taken to ensure stability, such as separate screened boxes for each stage, "binocular" intervalve transformers and filtered heater supplies to each stage. Grid bias was supplied from tappings on a dry battery, as any voltage-dividing circuit (necessarily associated with r.f. bypass capacitors) seriously delayed recovery from the effect of the very powerful transmitted pulse.

Display.—This consisted at first of a c.r. tube with a sine-wave time base fed through a bridge-type phase-changing network from the 50-c/s mains which also controlled the timing of the pulse. The sufficiently linear part of the sine wave around zero volts was used, the range scale derived from a 15-kc/s oscillator being marked on the surface of the c.r. tube. Later, conventional time-base circuits were employed.

Anti-jamming.—Any new military device is likely to be confronted by a corresponding new "anti-device." In 1937 steps were therefore taken to explore the possibilities of and protection against jamming. The former were brought forcibly to the notice of Bawdsey, when someone turned on a metre-wave radio-therapy device using a spark generator and brought all the radar development work to a standstill. It was thought that c.w. interference should be guarded against, and attention was given to rejector circuits with their "Q" artificially increased by positive-feedback valves. It seemed natural to put these circuits in the r.f. amplifier, as early as possible, to prevent overloading the early stages. Success was only reached when the circuit was inserted in the i.f. amplifier, and the IFRU (intermediate-frequency rejection unit) came into being.

Another suggestion for combating jamming (of the "noise" type) was the use of a long-persistence c.r.t. screen.

Permanent Echo Suppressor.—An example of the application of a little science to an unusual problem is given in the way in which trouble due to radar echoes from an important balloon barrage were overcome. It was at first thought that it would be necessary to move a complete radar station, as these echoes put it completely out of operation. One of the Bawdsey team who was consulted installed in the direction of the barrage an aerial fed with a suitably phased fraction of the transmitter output. The cure was completely successful and the station once more became operational.

Identification : Friend or Foe ?

Watson-Watt, in his 1935 memorandum, had recognized the need for some form of identification of the sources of echoes. The satisfaction of this need was called IFF (Identification: Friend or Foe?). He suggested the use of keyed radiators, on friendly craft, which would cause the echoes to change abruptly in time in accordance with a prearranged code. In order to increase the difference of radiation caused by keying the radiator, tests were also made with dipoles whose Q was reduced by valve circuits using positive feedback. Success was obtained when experiments were carried out on these lines, but the results were too dependent on the attitude of the craft. A remarkably successful experimental flight was carried out to test the following principle.

A super-regenerative receiver was fed from a dipole. When the r.f. pulse impinged on the dipole, the receiver greatly amplified the effect, and the amplified oscillations were re-radiated from the dipole and received at the ground station. This principle, with modifications, has been since used in many IFF systems. It was necessary that the receiver be tuned to the radar frequency in order that it should respond to a number of different radar frequencies; and to allow for drift in its own tuning and in that of the radar transmitter, a slow frequency sweep was applied by a motor-driven capacitor. The frequency sweep, which caused the "blip" to appear intermittently on the radar, permitted a simple form of coding.

PPI.—The Plan Position Indicator has been described so often that details will not be given here. The principle was suggested at Orfordness as early as October, 1935, but radar technique was hardly ready for it. The PPI for its proper development needed a more-or-less directional aerial system; the comparatively long wavelengths (50 and 25 metres) in use at that time prevented the use of the requisite directional array. PPI, though used with "metre" radar (3m and 1½m), did not come fully into its own until centimetre radar became possible with the invention of the magnetron. Without PPI the positions of aircraft had to be plotted manually by reading the range on an "A" (range-amplitude display) and the bearing on the goniometer scale. At a later date, a mechanical computor was designed, but was superseded by a very effective electrical computor (named

the "fruit machine") based on automatic telephone practice.

Increased Accuracy.—The team at Orfordness were, at first, not concerned with accuracy of range or bearing: they were only interested in extending the range of detection and in plotting the positions of raiders sufficiently accurately to enable fighters to be directed towards them. When radar was being developed for directing guns, there was a need for greater accuracy in range and bearing. Two developments, dealing respectively with these two problems, will now be mentioned.

Bearing Accuracy.—Whereas the CH stations used a goniometer to obtain bearings, the shorter wavelength used in the gun-laying (GL) sets made this technique less easy: further, there was the ultimate aim of making the GL sets follow the target automatically, a condition for which goniometer operation is not suitable. The simplest way of obtaining a bearing was to rotate an array until the signal was a minimum. This has two grave disadvantages, the "minimum" direction is vague and, if the target bearing alters, the direction of change is not at once obvious.

To overcome these two difficulties, the system known as "split" was devised. In this, the axis of the beam could be switched rapidly from one direction to another a few degrees away. If the size of the echo remained constant, the target lay on the bisector of the angle between these two directions. If the direction of the target altered, the two echoes became different in size. It was necessary to distinguish which echo was produced with which direction. In one scheme a rotating disc synchronized with the aerial switch with red and green sectors moved in front of the c.r. tube, the echoes there were distinguished by colour. Another scheme (which gave the technique its name) was based on applying a small horizontal shift to the time base: the echoes appeared to have "split" into two echoes side-by-side—hence the name. (Confusion was later caused by the transfer of the term "split" from the echo to the beam, and the term "split beam" gained currency. As the two beams exist in succession and not simultaneously this usage is clearly wrong, and the term "switched beam" is now recommended.)

Range Accuracy.—The early radar displays used a range scale marked on the face of the c.r. tube. The accuracy of reading was low, as the whole range (perhaps 20 miles) was included in a length of about four inches, and parallax errors (due to the thickness of the glass envelope) were in evidence. Further, if the voltages applied to the c.r. tube changed, serious "zero" errors could occur. Two solutions to the problem were produced: (a) the potentiometer method, and (b) the "goniometer" method.

Potentiometer.—In the first of these, a time base was expanded to many times the diameter of the c.r. tube screen, only a small portion, therefore, being visible. The range was read by applying a horizontal shift to the trace until the echo was brought to coincidence with a line marked on the screen. The shift voltage was supplied from an accurate potential divider (potentiometer) connected across the h.t. supply to the c.r. tube. This artifice compensated for variations in the h.t. since an increase of h.t. voltage both *reduced* the c.r. tube deflectional sensitivity and *increased* the shift voltage available in the same ratio.

"Goniometer" Method.—The second method is usually referred to as the "goniometer" method because in some cases it made use of a radio-goniometer (part of a Naval Bellini-Tosi d.f. set) as a phase-shifting transformer. In this system there appear two traces on the screen. The upper one is a normal "A" display, the lower consists of calibrating pips from an accurate oscillator. If these pips correspond to ranges of thousands of yards, the range can be estimated by eye by noting the relative positions of the echo and the nearest two pips. If, now, a phase-shifting transformer is inserted between the oscillator and the pip-generating device, and the spindle of the transformer is turned steadily through 360 degrees, the pips will all move along the trace until each takes the place of its neighbour, i.e., moves 1,000 yards on the range scale, so that 1 degree on the phase-shifting transformer corresponds to 1,000/360 or 1.8 yards. If the phase-shifting transformer is adjusted so that the echo coincides with one of the pips, the range can now be measured to a high degree of accuracy.

Airborne Radar

Metre-Wave AI.—We now turn to another branch of radar—the use of radar in the air. In 1935 it was suggested that a half-way solution to the problem of airborne radar might be found: an airborne receiver only, receiving echoes from an aircraft as the result of transmissions from a *ground* transmitter. (This was called RDF 1½, RDF 1 being all ground radar and RDF 2 the future all-airborne radar—but the name soon disappeared.) In comparison with CH the requirements for the all-airborne set were: reduction in size and weight; reduction in wavelength (this would reduce aerial size) to 1 or 2 metres; reduction of pulse duration one or two microseconds to give sufficient range discrimination at short ranges; development of a suitable display of beaming, range and elevation to be indicated directly without turning knobs.

It was rightly anticipated that severe difficulty would be caused by the closeness of the transmitter to the receiver. A start was made on a receiver on 6.7 metres; this was completed in six months. At the end of 1936 trials of RDF 1½ were carried out, resulting in detection ranges of 8 miles. The co-operation of a powerful ground transmitter was responsible for a greater range being attained than on all other AI radar during the war. In early 1937 an airborne transmitter was designed and tested with negative results against aircraft. Ground objects and ships were detected. This was the start of ASV (Air to Surface Vessel), described later.

By December, 1937, a complete airborne set was in existence working on 1½ metres. The peak power was 100 watts. The maximum range of detection was 5,000 feet. The set could only measure range. In mid-1939 it was possible to judge bearing and elevation; for this purpose two c.r. tubes were used. This set became AI (Air Interception) Marks 1, 2 and 3. AI Mark 4 followed in the winter 1940/41. This was the last of the metre AI sets.

ASV (Metre).—As mentioned above the 6.7 metre trials showed that echoes could be received from objects on the ground and from ships. In the autumn of 1937, a range of 5 miles was obtained at 1½ metres. This led to the development of ASV Marks 1 and 2. The problems were easier than that of AI because the minimum range need not be so short and there is no need to measure elevation.

In 1940 large numbers of these sets were fitted by the Navy in escort vessels under the designation Type 286. Part of this apparatus was also used on the searchlight patrol set (SLC or "Elsie").

AI (Centimetre).—Suggestions for the use of much shorter waves which would allow narrow beams to be employed were made in 1940, but development had to wait for the magnetron and centimetre waves. The first centimetre AI sets were flown in early 1941 as AI Mark 7.

ASV (Centimetre).—As in the "metre" sets, the AI technique was applied to ASV. Here it had an important operational success. The Germans were beginning to fit their submarines with listening sets for detecting the approach of aircraft fitted with metre ASV. When we changed to centimetre waves they were puzzled and lost confidence in their sets.

H_2S.—The discovery (mentioned above) that objects on the ground could be distinguished by their echoes led to the development of H_2S—there are so many explanations of the reason for the name that it is inadvisable to mention any—for blind bombing. The development was held up because it was for a long time considered inadvisable to risk a magnetron falling into German hands, but in July, 1942, permission was given. The display is a plan position indicator.

AWARDS TO RADAR PIONEERS

Successful Claimants and Their Claims

AFTER A LONG and highly detailed investigation of claims, the Royal Commission on Awards to Inventors recommended that an *ex gratia* award be paid to Sir Robert Watson-Watt "in respect of his initiation of radar and his contribution to the development of radar installations." Sir Robert made a joint claim on behalf of a team of ten but the Commission has recommended individual awards to each member and also to eleven other claimants for their "contribution to the development of radar installations."

We give below a list of the successful claimants—twenty-one in all—with their claims and awards.

Sir Robert Watson-Watt (£50,000): RADAR.

At the time when Sir Robert Watson-Watt began his *magnum opus* as leader of the team that developed the means of using radio reflections for aircraft location, he was Superintendent of the Radio Dept. of the National Physical Laboratory (incorporating the Radio Research Station at Slough, where the initial experiments were made). In 1938 he became Director of Communications Development, Air Ministry, and from 1942-46 was Vice-Controller of Communications Equipment, Ministry of Aircraft Production. He received his knighthood (C.B.) in 1942. In 1946 Sir Robert left M.A.P. to set up a private company of technical consultants but continued as scientific adviser on telecommunications to a number of Ministries. He is a Fellow of the Royal Society.

Dr. E. G. Bowen* (£12,000): Development of single-station radar systems; metre-wave and centimetre-wave AI; metre-wave and centimetre-wave ASV; PPI; GCI; discrimination of ground targets (as used in H_2S); radar blind bombing (as used in H_2S); h.f. engine-driven alternators.

Dr. Bowen went to the Radio Dept., N.P.L., in 1935 as a junior scientific officer. He worked under Sir Robert Watson-Watt on the first airborne radar equipment. In 1940 he was a member of the Tizard Mission sent to the United States to disclose details of radar techniques to the American Chiefs of Staff. For nearly two years from 1942 (when he received the O.B.E.) he was British Liaison Officer at the Radiation Laboratory, Massachusetts Institute of Technology. In 1944 he went to the Australian Commonwealth Scientific and Industrial Research Organization as Deputy Chief of the Radiophysics Division of which he is now Chief.

A. F. Wilkins* (£12,000): Method of height measurement in single-station radar; gap-filling in single-station radar; sense-finding device for use with crossed-aerial d.f. system; IFF apparatus and aircraft aerials for use with IFF; device for reduction of effect of permanent echoes at CH stations.

Mr. Wilkins, who undertook research in radio at both the Manchester College of Technology and Cambridge University, was engaged in work on v.h.f. propagation and direction finding during most of his service (1930-36) at the D.S.I.R. radio research station. In May, 1935, he went to Orfordness as one of the Watson-Watt team, being mainly concerned with the design of transmitting and receiving aerials. From 1936-41 he was successively scientific officer and senior scientific officer at the Bawdsey research station where he was concerned with the design of the original CH stations. During 1942-45 Mr. Wilkins was officer-in-charge of the Operational Research Sections at Fighter Command and later at Air Command Headquarters in Ceylon. He returned to the radio research station (Slough) in 1946 as senior principal scientific officer (which position he still holds) and is concerned with the propagation of h.f. at oblique incidence and the maintenance of the overseas ionospheric observatories of D.S.I.R.

L. H. Bainbridge-Bell* (£2,400): Radar transmitter and receivers; optical converter.

Mr. Bainbridge-Bell, whose absorbing personal interest is the presentation of technical information (on which he has contributed to *Wireless World*), has been at the Admiralty Signal and Radar Establishment since 1939. From 1927 to 1936 he was at the Slough radio station developing the c.r. direction finder for atmospherics and ionosphere-sounding apparatus. During this period he was co-author with Watson-Watt and Herd of "The Cathode-Ray Oscillograph in Radio Research." Prior to joining the research staff at Slough he was for six years with the Radio Communication Company developing the Robinson system of d.f. for ships.

H. Larnder* (£2,400): Radar countermeasures; afterglow of c.r. tubes; pulse analysis and monitoring; measurement of transmitter power; measuring standing waves on transmission lines.

Before joining the Watson-Watt team at Bawdsey in 1936, Mr. Larnder was for some months in the transmitter laboratory of the Plessey Co. He is now superintendent of Weapons Assessment, Armament Development Establishment, Ministry of Supply.

Geoffrey A. Roberts* (£2,400): Electrical calculators.

Prior to joining the Bawdsey research station in 1937 Mr. Roberts was for seven years with Standard Telephones and Cables, where his experience in automatic telephony contributed largely towards his designing the electrical calculator for which he received the award. He became a M.B.E. in 1946.

Dr. Denis Taylor* (£2,400): GCI.

After graduation in 1931 Dr. Taylor became a research assistant at University College, Hull. For two years prior

* Members of the Watson-Watt team.

to joining T.R.E. in 1939 he was senior lecturer in physics and radio engineering at the Polytechnic, Croydon. During his five years at T.R.E., first at Bawdsey and later at Dundee, Swanage and finally Malvern, he was concerned with ground radar. He was subsequently on counter-measures against "flying bombs" and V2s. From 1944-46 Dr. Taylor was Superintendent, T.R.E. (Far East), and has, since then, been head of the Electronics and Instrumentation Division, Atomic Energy Research Establishment (Harwell). He is author of "Principles of Radar" and "Measurement of Radio Isotopes."

Dr. A. G. Touch* **(£2,400)**: Metre-wave AI and ASV.

Dr. Touch, who, since 1947, has been Superintendent of the Blind Landing Experimental Unit, joined the Civil Service in 1936 as a junior scientific officer at the Air Ministry research station, where he worked with Dr. Bowen on the development of AI and ASV. In 1940 he went to the Royal Aircraft Establishment, Farnborough, on the development of airborne radar, and in the following year was appointed to the British Air Commission, Washington, where he assisted in the development and production of airborne radar and navigational aids in N. America.

R. Hanbury Brown* **(£1,200)**: Metre-wave AI and ASV.

Mr. Brown, who has, since 1949, been at the Jodrell Bank research station of Manchester University as I.C.I. Research Fellow, working on radio noise from the galaxy, joined the Bawdsey research station in 1936, where he participated in the early experimental flying with night-fighter equipment (AI) and ship and submarine-detection equipment. With Dr. Bowen he detected the first submarine by radar in 1939. From 1942-45 he was in the Naval Research Laboratory, Washington, D.C., as assistant head of the combined research group working on the development of radar equipment. For two years from 1945 he was principal scientific officer at the T.R.E., Malvern, after which he undertook radar consulting until going to Manchester University.

W. A. S. Butement (£1,200): "Split" method of d.f.; developments leading to CHL, CD/CHL, CDU and GCI sets; fire control system using echoes from shell splashes.

Mr. Butement, who for the past few years has been chief scientist in the Australian Government's Department of Supply, was assistant director of scientific research in the British Ministry of Supply during the latter part of the war. He was appointed an O.B.E. in 1946.

P. E. Pollard (£1,200): Radar ranging systems; radar beacons.

The whole of Mr. Pollard's working career has been in the Scientific Civil Service, and he is at present chief superintendent, Radar Research and Development Establishment of the Ministry of Supply. His technical training as a physicist was at King's College, London, under Sir Edward Appleton. He was appointed an O.B.E. for his part in the development of radar.

R. H. A. Carter* **(£750)**: IFF.

Mr. Carter, who was at the Slough radio research station in the early '30s, was one of the team at Orfordness and Bawdsey and later went to Malvern, where he is now senior experimental officer at T.R.E.

H. Dewhurst (£750): 4-metre receivers; gap-filling arrays; sense-finding array; PPI type display; phasing dipole array; transmission line feeds; mobile receiver RM1; intermediate CH chain.

Mr. Dewhurst is now head of the Photographic Division and Film Unit, T.R.E. His researches while in the Research Pools of the Ministries of Air, Aircraft Production and Supply include work on h.f. filters, mobile radar, a supersonic impedance bridge and aircraft microphones.

S. Jefferson (£750): Intermediate frequency rejector unit; frequency measurement using IFRU.

Before joining the radio research station, Slough, in 1936, Mr. Jefferson spent five years in industry (Siemens, Murphy and the Gramophone Co.). From Slough he went to Orfordness and Bawdsey. In 1947 he was a technical adviser to Sir Stanley Angwin at the Atlantic City Conference. He went to T.R.E. the same year and was engaged on industrial applications of electronics, and since 1951 has been at A.E.R.E. (Harwell) working on the industrial applications of radio isotopes.

Dr. J. H. Mitchell (£750): Beam techniques; use of spark gaps, etc.; Yagi aerials.

Dr. Mitchell, now controller of research at Ericsson Telephones, Ltd., joined the Air Ministry Scientific Pool in 1936 and after a few months went to Bawdsey research station for work on radar. He returned to the Royal Aircraft Establishment, Farnborough, in 1937 to take part in research on v.h.f. communication and in 1939 took charge of radio aids to navigation. After working on general electronic problems he joined Ericsson Telephones in 1947.

B. Newsam (£750): Crystal-controlled calibrator used on GL1, GL2, GL3 and CD; controlled squegg modulator used on GL1, GL2, CHL and CD; improvements on Pollard's time-base used on GL1 and GL2; "strobe" circuits and gating circuits; "spiral" time-base used on CD; "fine" and "coarse" time-bases used on GL3.

After graduation in 1932, Mr. Newsam was with E.M.I. and Standard Telephones and Cables before joining the staff at the Bawdsey research station in 1938. While with S.T.C. he worked on cathode-ray oscillography, particularly on the time-base circuit now known by its American name of "Bootstrap Circuit" (British Patent No. 493,843). At Bawdsey he developed the equipment which is the subject of the Award, and applied it to army radar during the early years of the war. Later he was in charge of the Group responsible for microwave test gear. Since the war Mr. Newsam has been working on the fundamental Theory of Information.

E. J. Dickie and Dr. B. J. O'Kane (£500 jointly): North-seeking PPI.

As liaison officer between T.R.E. and Bomber Command R.A.F., Wing Commander Dickie participated in the early flight trials of H2S with Dr. O'Kane in 1941. He also assisted in operational trials of "Gee." Since 1946 he has been operations officer at the Ministry of Civil Aviation where he has been associated with the introduction of the "Airways" system.

Dr. O'Kane, who is at present chief engineer of International Aeradio, was in the G.E.C. Research Laboratory, Wembley (1935-40), before transferring to T.R.E., Malvern. He returned to G.E.C in 1945 and joined International Aeradio in 1947.

P. A. Marchant (£250): Aerial switching equipment; computors 60a and 60b.

Although a telecommunications engineer, Mr. Marchant became associated with radar in 1938 as a member of the Post Office sub-committee for air defence communications. From 1939 onwards he was in charge of a small group of design engineers responsible for the provision of telecommunications for radar; control devices for switching power into radar transmitting aerials; plotting, recording and sending equipment; and computors. He is at present a senior executive engineer in the E-in-C's office, G.P.O.

D. A. Weir and P. A. Marchant (£250 jointly): Electrical calculator.

For nine years prior to joining T.R.E. in 1939, Mr. Weir was with the Automatic Telephone & Electric Co. At T.R.E. he was concerned with the development of the electrical calculator, colloquially called the "Fruit Machine." He was also associated with the development of GCI and OBOE. In 1946 he joined Standard Telecommunication Laboratories.

R. V. Whelpton (£250): High-power multi-stage transmitters; mobile radar sets; hand-made CHL stations.

Mr. Whelpton joined the Research Dept. of Metropolitan-Vickers in 1928. While there he worked on the development of the high-voltage c.r. oscillograph and the high-voltage electron microscope. He went to the Air Ministry research station at Orfordness in May, 1936, and to Bawdsey later that year. In 1940 he went to R.A.E., Farnborough, and became deputy head of the Radio Dept. in 1946. He has been assistant director in charge of research and development of airborne and ground radar and radar aids to navigation at the Ministry of Supply's Directorate of Communications Development since 1949.

WORLD OF WIRELESS

Organizational, Industrial and Personal Notes and News

News in Morse

IT is many months since we published a schedule of transmissions of news in Morse in the London Press Service and, as a new timetable was introduced early in February, we give below the revised details. The bulletins, which are radiated by the Post Office stations, are transmitted at 20-27 w.p.m. In addition to the bulletins scheduled there are a large number of Hellschreiber transmissions.

G.M.T.	Call	Freq. (Mc/s)	Area
0015—0230 w*	GAC	6.945	1
0030—0230 *M*	GAC	6.945	1
0030—0230 *M*	GAD6	7.355	2
0130—0220 w*	GAD6	7.355	2
0130—0300 w	GDC	4.125	3
	GDI	7.780	4
0130—0300 *d*	GCX	8.920	5
0945—1045 w	GPF	16.190	6
1100—1200 w	GPF	16.190	6
1215—1315 w	GPA	20.100	5
	GIA	19.640	7
1600—1700 w	GPA	20.100	5
	GDT	8.925	6
1600—1800 w	GPT	9.270	7
1815—1930 *d*	GAH	8.065	6
	MLJ	7.447	7
1845—1945 w	GDG	6.912	3
	GCX	8.920	4
1945—2215 w	GAH	8.065	6
	GDB2	6.795	7
2000—0015 w	GIH	10.650	2
2045—2200 *S*	GAH	8.065	6
	GDB2	6.795	7
2100—2200 w	GAN	10.805	5
2245—0015 w	GAC	6.945	1
2330—0030 *S*	GAN	10.805	5

d daily. *S* Sundays.
M Mondays. w weekdays.
w* weekdays except Mondays.

The number in the fourth column of the table denotes the area to which the transmission is beamed: 1, N. America; 2, S. America; 3, Distant Europe; 4, Middle East; 5, Africa; 6, N.E. Asia, Australia and New Zealand; 7, S.E. Asia.

There is no restriction on the reception and use of these bulletins outside the United Kingdom.

Hospital Radio

"FREE Grid's reference to the deplorable state of the radio installation in many hospitals has prompted a reader to draw our attention to the recent appeal by the *Cambridge Daily News* for funds for new radio equipment for Addenbrooke's Hospital, Cambridge. The scheme, for which £7,000 was subscribed within three weeks, provides for a selection of three or four programmes at each bed, with volume control, selection switch and Pillophone for each patient. The technical adviser to the Appeal Committee is G. E. Middleton, Secretary of the Cambridge Radio Group, I.E.E.

Standard Frequencies

STARTING with the March issue, our associated journal *Wireless Engineer* is publishing regularly the results of measurements made daily by the National Physical Laboratory on the standard frequency transmissions of MSF Rugby on 60 kc/s. Figures for Droitwich, 200 kc/s, are also given. The results are presented in the form of the deviations in "parts in 10⁸" from the nominal frequency; the results for January appear in the March issue and so on regularly.

Television Convention

DETAILS of the convention on "The British Contribution to Television," which the I.E.E. is organizing for April 28th to May 3rd, are now available, together with registration forms, from the Institution. The registration fee for non-members is 30s. Sessions covering various aspects of television—from the studio to the viewer—will be held at Savoy Place. In addition, there are to be visits to research and industrial establishments.

Solar Eclipse

TWO ionospherists have been sent by the D.S.I.R. to sounding stations in the tropics in order to carry out continuous observations over a period including that of the solar eclipse (February 25th). They will use equipment installed by the D.S.I.R. at the University Colleges at Ibadan (Nigeria) and Khartoum (Sudan) for regularly sounding the ionosphere. W. R. Piggott, who is principal scientific officer at Slough, has gone to Ibadan, and C. M. Minnis, a scientific officer at Slough, is in Khartoum.

PERSONALITIES

Sir Edward Appleton, F.R.S., has been elected an Honorary Member of the I.E.E. "for his distinguished work in the field of pure and applied physics and his researches into the characteristics of the ionosphere." Sir Edward, who has been Principal and Vice-Chancellor of Edinburgh University since 1948, was for ten years Secretary (Administrative Head) of D.S.I.R. He was awarded the Nobel physics prize in 1947.

Sir Arthur Fleming, D.Eng., has also been elected an Hon. M.I.E.E. "for his distinguished work in electrical engineering, in particular in the field of technical education." Sir Arthur, who has been with Metropolitan-Vickers and its associated companies since 1902, is a member of the Government Technical Personnel Committee.

J. D. McGee, Ph.D., M.Sc., A.M.I.E.E., a senior scientist with E.M.I. Research Laboratories, has been appointed an Officer of the Order of the British Empire (O.B.E.). Australian born, he graduated B.Sc. in mathematics and physics from Sydney University, where, continuing with physics research, he took his M.Sc. degree (1928) and was awarded the University Medal in Physics. He was also awarded a research scholarship to Clare College, Cambridge, where he worked from 1928-1931 on atomic physics in the Cavendish Laboratory under the late Lord Rutherford. In 1932 he joined

SCOTTISH TELEVISION. Engineers testing the 5-kW Marconi vision transmitter at Kirk O'Shotts preparatory to the opening of the Scottish television service using initially this stand-by equipment on March 14th. Test Card C will be transmitted from 10-12 on weekdays and the London programme at normal times.

E.M.I., where he has worked mainly on the development of Emitron camera tubes.

H. L. Kirke, C.B.E., M.I.E.E., Asst. Chief Engineer, B.B.C., has been elected vice-president of the American Institute of Radio Engineers for 1952. Before joining the B.B.C. in 1924 he was for four years with Marconi's at their experimental station at Writtle, near Chelmsford. Unfortunately, owing to ill health, he has been absent from the B.B.C. for some months.

E. G. Rowe, M.Sc., M.I.E.E., contributor of the article "'Trustworthy' Valves," studied at the City & Guilds Engineering College, where he obtained his degree in engineering. He joined the M.O. Valve Co. in 1933, where, for fifteen years, he was engaged in the design and development of valves, being successively superintendent of receiving valve staff and chief design engineer. In 1948 he went to the Brimar valve division of Standard Telephones & Cables and is now chief engineer.

J. Alan Hutton, who contributes the article "Television Ghosts," graduated from Sheffield University. He subsequently worked in Pye's Research Dept., where he was in charge of the e.h.f. and aerial section. He left in 1949 to join Murphy's Research Dept.

IN BRIEF

Receiving Licences.—Approximately 12,547,700 broadcast receiving licences, including 1,181,200 for television, were current in Great Britain and Northern Ireland at the end of 1951. The increase in television licences during December was 67,300.

R.S.G.B. Officers.—The new president of the R.S.G.B. is F. Charman (G6CJ) and L. Cooper (G5LC) is acting vice-president. Jack Hum (G5UM), editor of *Murphy News*, was elected Hon. Editor. The following were elected members of the committee: C. H. L. Edwards (G8TL), H. A. Bartlett (G5QA), T. L. Herdman (G6HD), P. W. Winsford (G4DC), H. McConnell (GM2ACQ), F. G. Lambeth (G2AIW) and R. Walker (G6QI).

R.C.E.E.A. Council.—At the annual general meeting of the Radio Communication and Electronic Engineering Association the following member firms were re-elected to form the Council. The representative's name is in brackets. B.T.H. (V. M. Roberts), E.M.I. (J. S. Carr), G.E.C. (M. M. Macqueen), Kelvin & Hughes (C. G. White, vice-chairman), Marconi's (F. S. Mockford), Metro-Vick (L. H. J. Phillips), Mullard (T. E. Goldup), Murphy (K. S. Davies, chairman), Plessey (P. D. Canning), Pye (C. O. Stanley), Redifon (B. St. J. Sadler), and S.T.C. (L. T. Hinton).

Scottish Section of the Brit. I.R.E. is holding a conference and exhibition in Glasgow on March 14th and 15th to mark the opening of the Kirk O' Shotts television transmitter. Papers on many aspects of television will be presented at the conference and a display of receivers, aerials, test gear and other items of television equipment will be provided by manufacturers. Full details of the conference, attendance at which is not limited to members of the Institution, are obtainable from R. H. Garner, 66, Buchanan Drive, Cambuslang, Lanarkshire. Registration fee is 7s 6d.

Technical Writing.—A series of ten lectures on "The Technique of Technical Writing" will be given at Norwood Technical College, Knight's Hill, West Norwood, London, S.E.27, on Tuesday evenings at 7.0, commencing March 18th. The fee for the complete course, which will be given by Geoffrey Parr, former editor of *Electronic Engineering*, is 15s.

Dr. J. D. McGEE
(See "*Personalities*")

"Microphones."—The price of this new *Wireless World* book by the staff of the Engineering Training Dept., B.B.C., was misquoted in our note in last month's issue. It costs 15s (postage 5d).

MEETINGS

Institution of Electrical Engineers

London Meeting.—"Electronic Telephone Exchanges" by T. H. Flowers, M.B.E., B.Sc., at 5.30 on March 13th.

Radio Section.—"The Slot Aerial and its Application to Aircraft" and "A Survey of External and Suppressed Aircraft Aerials for Use in the High-Frequency Band" by R. H. J. Cary at 5.30 on March 12th.

"Radio-controlled Models" by P. A. Cummins at 5.30 on March 24th.

London Students' Section.—"Industrial Electronics" by R. A. Jones at 7.0 on March 19th.

The above meetings will be held at the I.E.E., Savoy Place, London, W.C.2.

Cambridge Radio Group.—"An Investigation into the Mechanism of Magnetic-Tape Recording" by P. E. Axon, O.B.E., M.Sc., at 8.15 on March 11th at the Cavendish Laboratory, Cambridge.

Mersey & North Wales Centre.—Faraday Lecture on "Sound Recording—Home, Professional, Industrial and Scientific Applications" by G. F. Dutton, Ph.D., B.Sc.(Eng.), at 6.45 on March 17th at the Philharmonic Hall, Liverpool.

North-Eastern Centre.—Faraday Lecture (see above) at 7.0 on March 11th at the City Hall, Newcastle-upon-Tyne.

North Midland Centre.—Faraday Lecture (see above) at 7.0 on March 13th at the Town Hall, Leeds.

Northern Ireland Centre.—Faraday Lecture (see above) at 6.45 on March 20th at the Sir William Whitla Hall, Belfast.

Scottish Centre.—"Instruments for use in the Microwave Band" by A. F. Harvey, D.Phil., B.Sc.(Eng.), at 7.0 on March 5th at the Heriot-Watt College, Edinburgh.

South Midland Radio Group.—"Stereophonic Sound Reproduction" by J. Moir and J. A. Leslie, B.Sc., at 6.0 on March 24th at the James Watt Memorial Institute, Great Charles Street, Birmingham.

Irish Branch.—"Modulation—Some Fundamental Considerations" by T. P. Allen, M.Sc., at 6.0 on March 20th at Trinity College, Dublin.

Norwich District.—"The Nervous System as a Communication Network" by J. A. V. Bates, M.A., M.B., B.Chir., at 7.30 on March 31st at the Royal Hotel, Norwich.

British Institution of Radio Engineers

London Section.—"The Application of Magnetic Amplifiers to Industrial Measurement and Control" by H. M. Gale, B.Sc., at 6.30 on March 27th at the London School of Hygiene and Tropical Medicine, Keppel Street, Gower Street, London, W.C.1.

South Midlands Section.—Above paper, by H. M. Gale, B.Sc., at 7.15 on March 19th at the Exhibition Gallery, Public Library, Rugby.

Scottish Section.—"Radar as an Aid to Navigation" by N. J. Donald, B.Sc., at 7.0 on March 13th at the Natural Philosophy Department, The University, Edinburgh.

"The Future of Broadcasting," by Paul Adorian, at 7.0 on March 14th at the Institute of Engineers and Shipbuilders, Glasgow.

British Sound Recording Association

London.—"Recording Characteristics" by P. E. A. R. Terry at 7.0 on March 14th at the Royal Society of Arts, John Adam Street, Adelphi, London, W.C.2.

Portsmouth Centre.—"Crystal Pick-up Devices" by S. Kelly at 7.30 on March 6th at the Central Library, Guildhall Square, Portsmouth.

Television Society

London.—Fleming Memorial Lecture by Prof. H. M. Barlow, Ph.D. (University College) at 6.30 on March 20th at University College, Gower Street, London, W.C.1.

"Some Mechanisms of Signal Generation in Stage-type Television Camera Tubes," by Dr. R. Theile (Pye, Ltd.), at 7.0 on March 28th at the Cinematograph Exhibitors' Association, 164, Shaftesbury Avenue, London, W.C.2.

Leicester Centre.—"The Design and Application of Television Gear" by R. Freeman and E. D. Groom (Waveforms, Ltd.) at 7.0 on March 31st at the Leicester College of Technology, The Newarkes, Leicester.

Institution of Electronics

North Western Branch—"Electroencephalography" by W. Heaton, B.Sc. (Ferranti) at 7.0 on March 19th at the College of Technology, Manchester.

Radio Society of Great Britain

"Microphone Acoustics for the Radio Amateur" by H. A. M. Clark (G6OT) at 6.30 on March 28th at the I.E.E., Savoy Place, London, W.C.2.

Institute of Practical Radio Engineers

Thames Valley Branch.—"The Alignment of Television Receivers" by M. Molem (Cossor) at 8.0 on March 4th at the Wheatsheaf Hotel, Kingston Market Place, Kingston-on-Thames, Surrey.

THE "BELLING-LEE" PAGE

Providing technical information, service and advice in relation to our products and the suppression of electrical interference

Well Worth the Effort

It is worth while repeating that interference from unsuppressed motor cars is the greatest single obstacle to the full development of television.

As it is the signal-to-ignition interference ratio which ultimately decides whether or not a television receiver is worth while in "fringe" areas, the range of any of

Picture caused by inconsiderate motorist . . .

the transmitters could be considered to be much greater if all cars were fitted with ignition suppressors. Nor would the benefit be confined to "fringe" areas; in districts relatively close to a transmitter it is generally ignition interference which makes it necessary to erect an outside aerial. This means that if all cars were suppressed more indoor aerials could be used, landlords would grumble less, and the saving of raw materials and labour would be really enormous; probably amounting to three or four pounds per installation. Surely this is worth an effort.

Very great credit must be given to members of the Scottish Radio

. . . Same picture, but a more considerate motorist.

Retailers' Association, who have spent a great deal of time and money on an extensive campaign, spread over most of last year. This campaign has been very well reported by the lay press, and must have done a tremendous amount of good.

Wenvoe

We earnestly suggest that readers to be served by the new Wenvoe transmitter get together, and by a concerted effort, make their neighbours suppressor-conscious. We wonder just how many of you (yes, including trade readers), are running around without suppressors on your distributors.

Having mentioned trade readers in districts to be served by Wenvoe, it might not be out of place to remind them that "Belling-Lee" are, even at this date, working on the organisation of a series of conventions. These will be similar to those held in the North and in Scotland, where we met over 2,000 members of the trade, and discussed television aerial problems.

The towns where these conferences will be held, are Swansea, Cardiff, Bristol, Swindon and later on, in Exeter and Taunton. If you have not received your invitation, please apply to us at once on your business letter-heading.

It Speaks for Itself

The following letter, which we publish by the courtesy of the contributor, and by kind permission of the Editor of "The Autocar," will no doubt, interest readers of this page; especially those regular readers, who may recall our words concerning the effect of suppressors on engine performance. See this page, "Wireless World" December 1951, under the heading "Is it the Car or is it the Suppressor?" Reprints of this page are available to readers who may require them for reference.

"Suppressors—Touchstones to Improved Performance?

"Now that winter is with us again I would like to bring to motorists' attention the report of tests carried out by the United States Signal Corps. The tests were to determine the effect of suppressors in the ignition system and they prove that their addition improves cold-weather starting.

"The report was published in "Radio & Television News" of February 1951 (page 132), and here is a brief synopsis of the report, with the relevant figures.

"I own neither car, television nor interests in suppressor manufacturers so I am completely neutral regarding the arguments about the effects of suppressors, but the tests mentioned are very comprehensive and the data may be of interest to motorists.

"Tested on quarter-ton, four by four, truck; mileage 21,335.

"Performance before test, below normal. With no artificial starting aids, such as primers or heaters, the engine started 18 times out of 18 tests at temperatures of minus 30 to minus 40 deg. F. with resistor-suppressors applied in the spark plugs, distributor, or both, in an average of 57.3 sec. cranking time and at an average of 77 per cent. of rated primary voltage during cranking.

"With no resistor-suppressors in the ignition system, the engine started only once (at minus 30 deg. F.) out of 13 attempts in same temperature range, with an average cranking time of 215 sec. and an average of 79.2 per cent. of rated primary voltage.

"The principal effect of inserting a resistor-suppressor of approximately 10,000 ohms at the spark plug appeared to be smoothing out the inductive reactance component, allowing the energy stored in the inductance of the secondary to dissipate uninterruptedly through the gap. Nor did suppressors at the distributor outlets, in addition to those at the spark plug, have any apparent effect on starting ability. Shielding on the ignition cables with suppressors in the spark plugs appeared to further improve starting.

"On the basis of these tests Signal Corps engineers have concluded that the effect of resistor-suppressors on the starting ability of engines, even at low temperatures, is beneficial rather than detrimental.

Luton, Bedfordshire. L. F. SINFIELD."

"Belling-Lee" Distributor Suppressor L.630.

Consideration

Easter holidays, will no doubt be uppermost in the minds of many readers; especially the motorists busy in their garages, preparing for the first run of the year to sea or country. Many other people will wish to stay at home and catch up on their viewing. The considerate motorist, not wishing to spoil the enjoyment of the stay-at-homes, will make sure that his car is efficiently suppressed.

Written 31st January, 1952.

BELLING & LEE LTD
CAMBRIDGE ARTERIAL RD., ENFIELD, MIDDX., ENGLAND

SELENIUM SenTerCel RECTIFIERS

rectifiers
for the radio industry

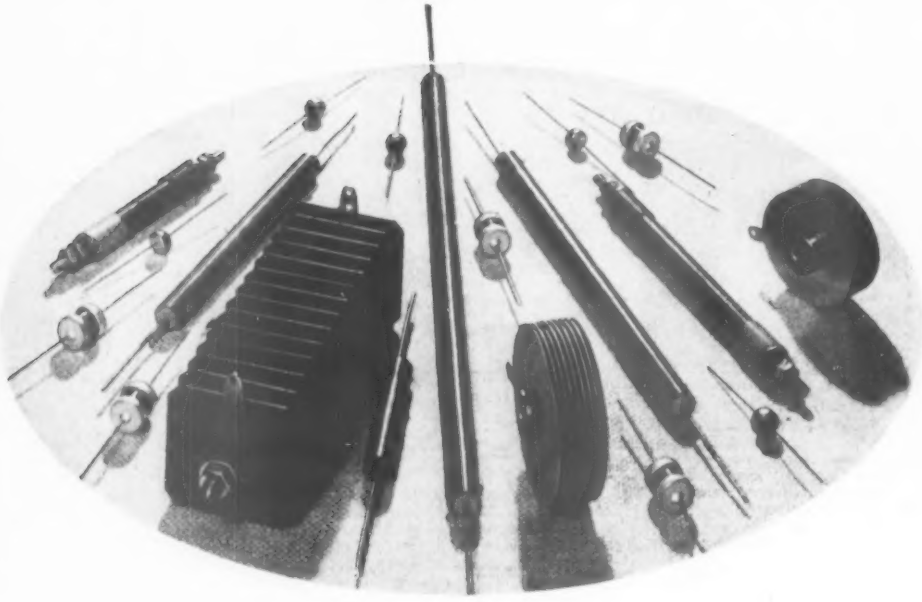

WHEREVER a radio or television diagram shows a rectifier operating at 0·5 Volts or higher, at a frequency below 5 mc/s there is almost certain to be a SenTerCel Selenium Rectifier which will do a better job because it:

- Saves space and weight
- Reduces wiring
- Withstands an unlimited instantaneous overload
- Reduces heat dissipation
- Needs no "warming-up" period
- Saves the cost of a valveholder
- Is practically indestructible in service
- Imposes no limit on the size of the reservoir capacitor
- Is low in cost

Please write for leaflets **F/SRL9, 9a, 10 & 11**

Standard Telephones and Cables Limited

Registered Office: Connaught House, Aldwych, London, W.C.2

RECTIFIER DIVISION WARWICK ROAD, BOREHAM WOOD, HERTS.

Elstree 2401 Telegrams: Sentercel Borehamwood

LETTERS TO THE EDITOR

The Editor does not necessarily endorse the opinions expressed by his correspondents.

I.F. Interference

WHILE in full agreement with Richard Donald, G3DJD (February), I do not think he goes far enough. The transmitting amateur operates within the framework of national and international law, and so long as he emits no energy on frequencies outside amateur bands recognized by his licensing administration, he is then surely as authentically licensed as Holme Moss!

If this is so (and surely it is his moral right, or why take his licence money?), we should not have to plead with designers and constructors to choose their i.f. They would simply have to "carry their own can back" if they didn't.

Where a dealer, maybe a self-styled "expert" with a pitiable lack of technical knowledge, sells a set to a purchaser who will take his word rather than that of an amateur (simply because the semi-literate confuse the words "amateur" and "novice"), then the can is surely for one of these to carry and is not the concern of the transmitting amateur, whose knowledge of radio technology sometimes far exceeds that of the dealer!

Some time ago I asked the G.P.O. engineers to check a complaint of television interference from my transmitter. They handled the matter admirably, but the viewer was amazed to learn his unselective receiver was the cause. His dealer had told him to *expect* interference caused by me! The fault is blamed on the amateur always by the public and often by the dealer, who finds it a Heaven-sent "alibi" for all kinds of troubles.

It is noteworthy that the G.P.O. require greater harmonic suppression from amateurs than the international regulations require from government and commercial stations.

We ought to be upheld by all concerned in taking the stand that if no emission takes place outside the licensed frequency limits, we are beyond reproach. By all means let my neighbours buy or build sets which stand up and beg for interference, but why should I have to concern myself about it, after I have spent a good deal of time and money to ensure that I am abiding by the regulations in my licence?

H. S. CHADWICK, G8ON.

Short Weight in Energy?

"CATHODE RAY," in his article on "Energy" (January issue), touches a sore point when he states "The electrical people might assume that their pressure was, on the average, constant, too, and install meters taking account of current and time only, but fortunately for us in these days, when the variations are always downward, they don't."

He misses one class of electricity consumer out; i.e., those like myself connected to a d.c. supply with meters taking account of current and time only. Mine records energy supplied based on the assumption of a constant voltage of 240 volts. I have on several occasions measured my supply voltage and it is, on the average, between 210 and 220 volts. I have only known it to rise to 240 volts at about midnight, when all the other consumers are in bed.

It would be interesting to know whether the B.E.A. are prepared to reimburse such electricity consumers as myself for electricity recorded but not actually consumed.

S. YARROW.

London, N.16.

Avoiding Hum in Pickup Transformers

I HAVE found the following tip useful in avoiding hum pick-up in the coupling transformer of a low-impedance gramophone pickup. If the first a.f. valve has a top-cap grid the transformer can be conveniently mounted on the top of the valve screening can. This gives a short grid lead and direct earthing through the can and at least one degree of freedom in rotating the transformer to find zero hum.

Thornton Heath, Surrey. S. HEATH.

Critique of Colour Coding

I KNOW, from the fact that statistics state that one male in every six suffers from colour blindness, that I can expect at least 17 per cent of your readers to agree with the contents of this letter.

How pleasant it is to handle a piece of radio equipment made on the Continent and find that all the small components are plainly marked with values and tolerances! No wondering whether a dot or a band is yellow or orange, brown or red or even green!

As for the use of such colours as blue and violet, well, I have even heard women, who do not normally suffer from colour blindness arguing about these.

I believe that a case cannot be made out to justify the continued use of colour coding. If it is claimed that it is cheaper to code than print, I should like to know how much is involved, for I find it difficult to believe that all the manufacturers in the world who print the values are functioning uneconomically. I contend that when a resistor is old and charred it is easier to read a printed number, especially if this appears in more than one place on the body, than to determine whether a spot is, say, yellow or orange.

Now, in case I am accused of being entirely destructive and having nothing new to offer, I should like to propose for the consideration of your readers and the resistor manufacturers a scheme which, to my mind, embodies the advantages of the two aforementioned methods.

Resistors should be body-colour coded in groups as follows:—

0—100Ω	black
101—1,000Ω	red
1,001—10kΩ	yellow
10,001—100kΩ	green
100,001—1MΩ	blue
1,000,001—∞	white

The depth of colouring to be so chosen that the higher-value groups should reflect more light than the lower ones, thus enabling a completely colour-blind person to assess the group to which a component belongs, i.e., dark red and light blue should be used in all cases.

Tolerance (for 10% and better).—Gold, silver, etc., tips.

Wattage (necessary because with the new high-rating resistors it is impossible to assess their durability

by examination).—Designated by a number of bands of any colour distinctive to base. I suggest for black bodies use white and for all other colours use black.

1 watt	1 band
½ "	2 bands
¼ "	3 "
⅛ "	4 "

Lower wattages not coded. Higher wattages plainly marked.

The value printing should be impressed at 90 deg intervals around the resistor and be at one or both ends (heat is less at the ends). For smaller resistors, which are normally used in "powerless" circuits, values could be printed centrally. Very small resistors would probably have to be colour-coded as at present.

Capacitors might also be colour-coded in groups as already mentioned, with the addition of the value, tolerance, etc., printed on *both* sides if of flat construction. D.C. working voltage might be spot- or band-coded.

L. G. WOOLLETT.

Petts Wood, Kent.

LOCATING TELEVISION PIRATES

Post Office Detection System

IN its new campaign against unlicensed television viewers, the General Post Office is employing vans fitted with apparatus which can detect any ordinary television set in operation within a radius of about 100ft. The van carries three horizontal loop aerials on its roof; they are fitted one at the front and two at the rear at the three corners of an "L."

By means of a switch a sensitive receiver can be connected to any one of the aerials and the receiver output operates a meter and a loudspeaker.

A normal television receiver, using electromagnetic deflection, necessarily produces a strong magnetic field varying at line and frame scanning frequencies. It is impracticable to confine this entirely within the receiver, but it falls off quite rapidly as the distance from it increases.

In the detection equipment it is the line-scanning field which is utilized and the receiver is tuned to the second harmonic, 20.25 kc/s.

In operation the receiver is normally connected to the front aerial and the van cruises until a signal is heard. The van then slows up and the receiver is switched backwards and forwards between the front aerial and the rear one immediately behind it. The aerial nearer the television set gives the stronger signal and the signals from the two only reach equality when the bisector of the line joining the aerials passes through the television set. When they are equal the van is stopped. It is then known that the television set is in a house alongside the van.

View of the van showing the three aerials.

To determine on which side of the road this house is the receiver is switched to the third aerial, and since this must be either nearer to or farther from the television set it immediately reveals the side of the van on which the set lies by an increase or decrease of signal. Reference to a list of licence-holders then shows whether or not the television set which has been detected is being used legitimately or by a pirate.

The apparatus is claimed to be capable of locating the position of a television set when the van is within 100ft of it. In addition to its primary object of locating pirates the van has an obvious secondary use in that in a rapid cruise round a given area it would be possible quite quickly to determine how many television sets were in use at a given time. By comparing this figure with the known number of television sets obtained from the records of licence-holders, the percentage of viewers using their sets at a given time could be obtained. This information would presumably be of value to the B.B.C. as evidence of viewers' reaction to programmes. This use is perhaps one to which the vans will be put when they have fulfilled their primary job, and there are no more pirates for them to detect.

The fact that television sets provide a field which makes them so easily detectable may serve to bring home to users the possibilities of their interfering with other broadcast receivers. The second harmonic of the line-scanning frequency is used for their detection, but the twentieth harmonic is quite strong near the set, and its frequency is very close indeed to that of Droitwich. It is quite strong enough for serious interference with a broadcast receiver on the other side of a party wall.

This was pointed out in *Wireless World** some time ago. In fact, broadcast interference is probably more usually due to the electric field than the magnetic and set makers minimize it by screening. Sometimes the line-scanning circuits are enclosed in a metal box and quite often the inside of the cabinet is "painted" with colloidal graphite to form a screen. Such screening is relatively ineffective on the magnetic field, and in any case complete screening of a television set is impossible until someone invents a transparent material which is also a good conductor. One must be able to see the tube face!

The fact that a television set gives away its presence and so enables pirates to be traced thus cannot be regarded as an entirely unmixed blessing by law-abiding citizens. The very fact that it does so means that it is liable to interfere with nearby broadcast listeners. If it were possible completely to remove this possibility of interference, then the possibility of detecting pirates would also vanish.

This is a unique case in which the Post Office might well be tempted to aim at less than perfection in the suppression of interference!

* "Interference from Television Receivers," by M. G. Scroggie, *Wireless World*, April 1950, p. 126.

"Trustworthy" Valves

Greater Reliability Achieved by Improved Mechanical Design

By E. G. ROWE,* M.Sc., A.C.G.I., D.I.C.

MANUFACTURE of valves for domestic receivers is controlled primarily by the need to produce them at minimum cost, and despite this limitation it has been possible to maintain a low failure rate during the normal life of sets. This fact was particularly noticeable during the war, when it was clear that even with the most antiquated receivers valve troubles were much less frequent than those of other components. However, the rapid increase in the number of television sets, with their average complement of twenty valves against the sound receiver's five, has revealed that the failure risk can be embarrassing, and so manufacturers have been steadily improving their quality within the close confines set by economics.

The fact that valves in domestic receivers have a very long life is partly because the mechanical shocks to which they are subjected are very mild. Over the last fifteen years, however, there has been a growing enthusiasm for electronics in the industrial field, and here the conditions of operation are more severe. The military uses of radio received a strong impetus during the war and we have now reached a point where the whole tactics of attack and defence are greatly dependent on the electronic equipment used. Moreover, since the war many of the devices developed for destruction have been adapted to peacetime uses and the safety of the traveller now depends very much on them.

The use of valves in industrial applications is, of course, a very different matter from their use in domestic receivers. Industrial use frequently involves conditions of extreme vibration and shock, extreme ranges of temperature and humidity and so on. Further, the failure of a valve in a domestic receiver simply means that one loses a certain amount of pleasure until the valve is replaced, whereas in industry a valve failure can cause a catastrophe with serious loss of life, while in war it may perhaps result in defeat in a vital conflict.

The unsuitability of the ordinary radio valve for such vital applications becomes very obvious, and while the valve-maker has been very much aware of this, the great expense of a programme of reliable valve development has been prohibitive, except for types used in certain specialized equipment such as deep-sea repeater cables.

In this article the name "Trustworthy" is used to describe a type of valve that is perhaps more generally known as "reliable". In America, the term "ruggedized" has much the same meaning. "Reliable" valves are generally improved (and more costly) versions of existing commercial types; the electrical characteristics are kept the same but the mechanical structure is redesigned to give a better performance under conditions of vibration and shock. Moreover, the description "reliable" usually denotes a very definite standard of reliability. This is expressed in terms of the percentage of failures in a batch of samples tested over a certain time (usually 1,000 hours), and is generally less than one per cent. Reliability does not necessarily mean long life, although in practice it often does. The valves in a guided missile, for example, must have extremely good reliability for the short while they are in existence but there is obviously no requirement for long operating life.

An engineer interested in the subject of "reliable" valves very quickly realizes that any attempt to give an accurate definition of reliability depends very much on the application in which the valve is used. For example, a valve may be considered reliable if it operates for a long time in a normal circuit without giving trouble; alternatively, its reliability may necessitate that it performs with negligible changes in certain essential parameters throughout life. Again, another user would consider reliability attained if he could have a guaranteed short term of life without early failures, whilst still another would be satisfied with an extremely short guaranteed operational life following immediately after an undefined shelf life. Finally, there is the well-known requirement for trouble-free performance under conditions of extreme vibration and/or shock.

One of the best general definitions is that a "reliable" valve is characterized by having a very high probability that it will operate normally when taken from stock and installed in equipment for which it was intended, and an extremely low probability that it will fail during subsequent operation in that equipment for some definite period of time.

It is quite possible to make "reliable" valves that will achieve any or all of the above requirements, but this article is concerned only with valves to be manufactured in large quantities and required to operate reliably up to one or two thousand hours, under conditions where extremes of ambient temperature may be encountered, either in storage or in operation, and where the valve and equipment may be subject to considerable mechanical shock or vibration. To be still more specific, the immediate objective is to achieve valve types having characteristics corresponding to existing designs but with a failure risk of the order of 1 per cent in 1,000 hours.

The subject of valve reliability has been exhaustively investigated in the United States, where various military and civil authorities have quoted the valve as being responsible for more than 50 per cent of the equipment breakdowns. An analysis was

* Brimar Valve Division, Standard Telephones & Cables Ltd.

Some of the information in this article has been taken from a paper by the same author in the November, 1951, issue of the *Journal of The British Institute of Radio Engineers*.

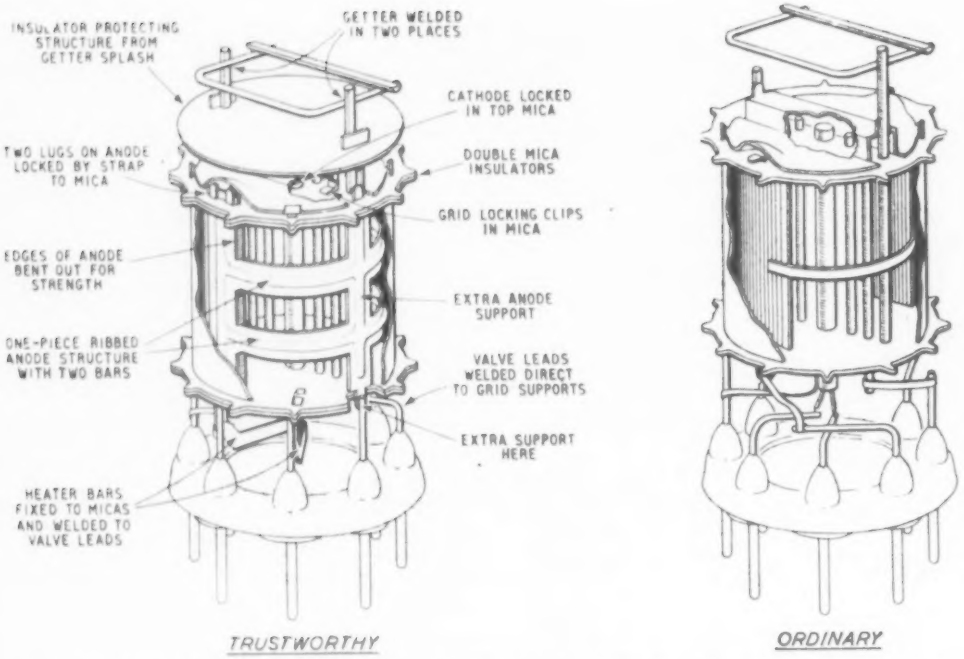
INSULATOR PROTECTING STRUCTURE FROM GETTER SPLASH
GETTER WELDED IN TWO PLACES
CATHODE LOCKED IN TOP MICA
TWO LUGS ON ANODE LOCKED BY STRAP TO MICA
DOUBLE MICA INSULATORS
GRID LOCKING CLIPS IN MICA
EDGES OF ANODE BENT OUT FOR STRENGTH
EXTRA ANODE SUPPORT
ONE-PIECE RIBBED ANODE STRUCTURE WITH TWO BARS
VALVE LEADS WELDED DIRECT TO GRID SUPPORTS
EXTRA SUPPORT HERE
HEATER BARS FIXED TO MICAS AND WELDED TO VALVE LEADS
TRUSTWORTHY
ORDINARY

Fig. 1. Showing some of the ways in which the "Trustworthy" valve differs from its "ordinary" counterpart. This does not represent any particular valve type but is merely a general illustration of the technique.

Fig. 2. Equipment for studying valve noise caused by vibration. The valve (indicated by arrow), working under Class A conditions, is mounted on a moving-coil vibrator and its output is displayed on the oscilloscope. A small calibrating signal is applied to the grid so that the noise level can be measured against it. The equipment has a telescope and stroboscopic lamp to enable a vibrating part to be studied when it is in resonance.

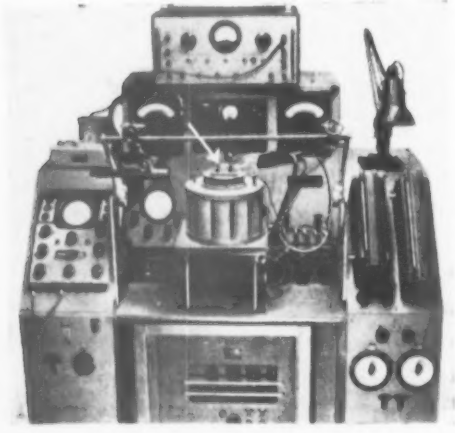

made of valve failures in civil aviation and the information obtained was used to improve the design of the particular types concerned. It is claimed that they are now at least 10 times as reliable as they were. Work in this country has been centred on valve types in the Services Preferred List and mainly on miniatures and sub-miniatures. The author's company has concentrated on miniatures and novals.

A valve is basically a mechanical structure having electrical properties that must be maintained throughout its life. Because it is built up from metal, mica and glass, it is subject to the failures common to all structures made of these materials, such as breakage, distortion, loosening of component parts, etc. In addition, mechanical weaknesses can directly affect electrical and chemical properties.

Complete analysis of many large groups of standard commercial valves returned as failures from operational equipment has shown that the faults occurring are as follows:—

(a) Electrical failures such as noise, instability.
(b) Mechanical failures of the assembly giving short-circuits and open-circuited elements.
(c) Mechanical failures of the heater structure.
(d) Glass faults.

Group (a) is caused by vibration and is a preliminary to group (b), so there are really three main sources of trouble: mechanical faults, often aggravated by vibration; heater faults; and glass faults.

It was fairly obvious that re-design efforts had to be directed towards shorter and more rigid structures that would be more stable under vibration, and what has been done can be seen from Fig. 1. The modified structures have the following main features:—

(a) Tight mica holes for the grids and double micas of optimum thickness.

(b) Locking straps in the micas to hold the grids.
(c) Locking of the bottom insulator to the stem in as many positions as possible.
(d) Straps welded across the anode lugs to lock the anodes into the micas.
(e) General changes giving greater strength to the anodes and improved location and fixing methods.
(f) Shorter valve mount made possible by increased-diameter cathodes.
(g) Minimum number of welds throughout the structure.

By applying many of these modifications it is possible to reduce the valve noise due to vibration to a very low general level as shown in Fig. 3, although there are still a few sharp peaks in the region above 1,000 c/s. These latter resonances are in general much lower in height than those of the original valve but usually occur at the same frequencies, indicating that they are fundamental resonances of components and can only be removed by a complete change of design technique. As the immediate aim is to produce valves of similar electrical properties (including capacitances) to an existing range, complete re-design is generally out of the question.

Heater failures resulting in open-circuits and short-circuits have been due to three causes:

(a) Excessive core temperature.
(b) Movement of the heater inside the cathode under vibration conditions and consequent damage to the heater coating at the cathode ends.
(c) Incipient fracturing of the core wire at any sharp bends.

While the operating temperature was satisfactory for normal receiving valves, it was thought advisable to reduce it for the "Trustworthy" types by the use of thicker core wires. This necessitated a longer length of heater wire, which meant extra loops, giving a tighter fit into the cathode. The improvement was not as much as was expected, as the heaters still had sharp bends that led to breakage, so the reverse helical heater has now been adopted, permitting the use of a large wire size and having no sharp bends to cause incipient failure. This design of heater is now being used for most of the "Trustworthy" valves and it has been found that the core temperature can be kept down to a safe figure. The heater is flexible with no sharp bends, and it fits the round cathode sleeves exceedingly well and is easy to insert into the cathode without damage to itself.

A further design feature was the use of heater bars that lock into the bottom mica and project below the cathode (see Fig. 1). The heater can then be inserted into the sub-assembly and welded to the heater bars before the sub-assembly is mounted on the glass base and the working space is restricted. Thus we have ensured good heater welds which can be adequately inspected before the final mount is put on to the stem. Furthermore, the stem wires can be welded to the thick heater bars near the mica periphery, giving valuable support to the lower mica and at the same time enabling this weld to be performed away from the congested inner section of the mount.

For the glasswork of "Trustworthy" valves the usual methods are still employed, but the controls are very much tighter, with rigid rejection limits and complete batch rejection if the limits are exceeded. As an envelope material, glass has the advantage of transparency, chemical inertness, electrical insulation, hardness and the ability to be welded by flame heating, but it is a brittle rather than a tough material and therefore requires a considerable number of refinements in technique to ensure freedom from cracking in service.

Glass is strong in compression and relatively weak

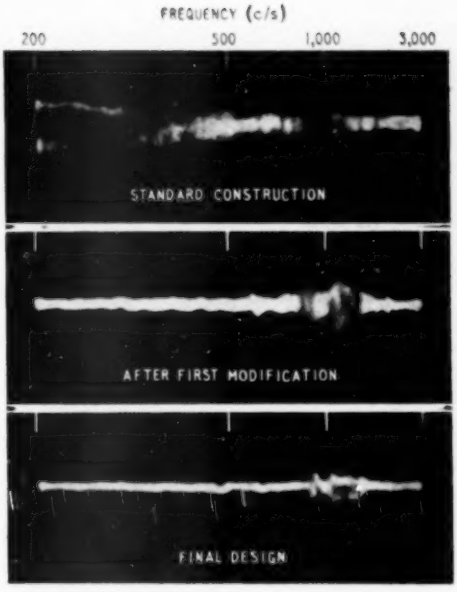

Fig. 3. Records from the vibration test equipment in Fig. 2, showing the noise output from a "Trustworthy" valve at three stages in its development. The peaks at the higher frequencies are mechanical resonances in the grid and cathode, while the general noise level at the low-frequency end is caused by looseness of the structure.

List of "Trustworthy" Valves and their "ordinary" Counterparts

"Trustworthy" Type	Commercial Equivalent	Description
13D2	6SN7GT	Double triode
5749	6BA6	Variable-mu r.f. pentode
5750	6BE6	Heptode frequency changer
6042	25SN7GT	Double triode
6057	12AX7	Double triode
6058	6AL5	Double diode, separate cathodes
6059	6BR7	Low-noise amplifier, pentode
6060	12AT7	High-slope double triode
6061	6BW6	Output pentode, 6V6 characteristics
6062	5763	R.F. amplifier, pentode
6063	6X4	Full-wave rectifier
6064	8D3	High-slope r.f. pentode
6065	9D6	Variable-mu r.f. pentode
6066	6AT6	Double-diode triode
6067	12AU7	Double triode
6132	6CH6	Video output pentode
6157	R17	Half-wave rectifier
6158	13D3	Double triode

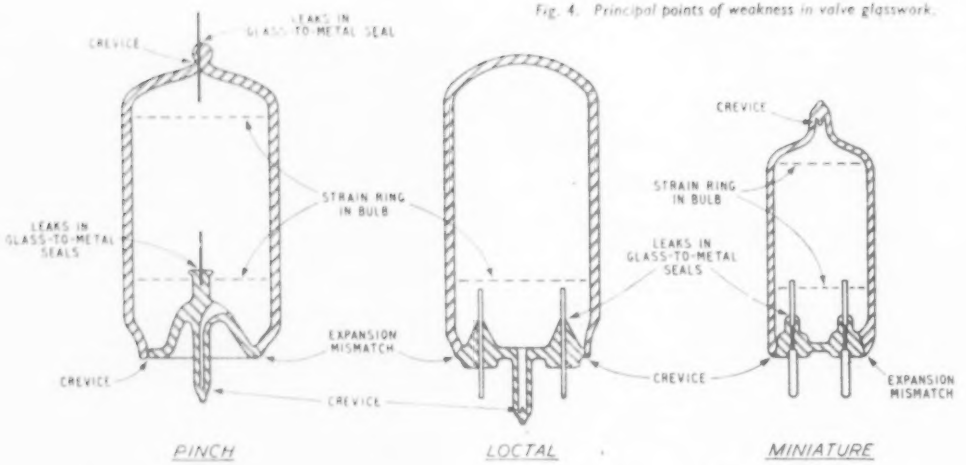

Fig. 4. Principal points of weakness in valve glasswork.

in tension, and small surface scratches and any crevices are likely to become cracks under quite small stresses. In addition, residual stresses can lead to ultimate failure of glass structures; the two best known are "mis-match stress" arising from the differential contraction of two glasses welded together and "thermal strain" due to the differential contraction of glass near to a weld relative to the glass farther away from the weld. There are also the problems of glass-to-metal seals that are an inevitable consequence of leading metal conductors through the glass. Fig. 4 shows some of the weak points which have to be carefully watched.

During the process of manufacture the valves undergo very stringent testing. There are two main groups of tests. Those in the first group are to ensure that the valves are uniform and line up with the design specification and these tests are applied to every valve that comes off the production line. They include inspection of the mounts and glasswork, a thermal shock test, short-circuit tests, a heater test, tests for characteristics and a 10-hour life run under Class A conditions. The tests in the second group are made on samples at various stages in manufacture and ensure that the original quality is being maintained. They are largely mechanical and include vibration tests, a resonance test, a shock test and a fatigue test, with a 2,000-hour life test at the end.

In conclusion, evidence so far obtained shows that early-life failures, which are the cause of most of the heartburnings, are due almost entirely to mechanical and glass troubles. If these are eliminated by attention to design and manufacturing methods, together with a short life run, there is a great hope that for at least 1,000 hours the failures will be negligible.

It is a hazardous thing to prophesy, but within five years the reliability of the valve can be such that the present criticisms will then be directed towards other components. As reliability work must inevitably take considerable time, adequate pressure should be maintained on manufacturers of other components to ensure that all the constituent parts of an equipment keep in step.

CLUB NEWS

Bath.—We are asked by the new secretary of the Admiralty Electronics Society, G3BPU, to announce that, whilst membership of the society is primarily for civilian and service members of the Admiralty, members of other Government Departments are admitted at the discretion of the Committee. Workshop facilities are available, including test equipment, at the headquarters, Electrical Engineering Dept., Admiralty, Bath. Sec.: W. J. Green, G3FBA, Room 110A, Block "A," Admiralty Offices, Bath.

Cleckheaton.—F. E. Henderson of the General Electric Company will speak on "The Development and Application of the Germanium Crystal Valve" at the meeting of the Spen Valley Radio & Television Society on March 26th at 7.30 at the Temperance Hall, Cleckheaton. Sec.: N. Pride, 100, Raikes Lane, Birstall, Nr. Leeds.

Coventry.—At the March meetings of the Coventry Amateur Radio Society W. Grimbaldeston, G6WH, will speak on "Frequency Modulation" (3rd) and L. W. Gardner, G5GR, "25 Years of Amateur Radio" (17th). Meetings are held at 7.30 on alternate Mondays at the Y.W.C.A., Queen's Road, Coventry. Sec.: K. G. Lines, G3FOH, 142, Shorncliffe Road, Coventry.

Downham.—Meetings of the radio class run in conjunction with the Downham Men's Institute, are held on Wednesdays at 8.0 at Durham Hill School, Downham, Kent. The class is linked with the Ravensbourne Amateur Radio Club (G3HEV) of which W. H. F. Wilshaw, 4, Station Road, Bromley, Kent, is secretary.

Exeter.—The meeting of the Exeter Radio and Television Club on March 13th, at which P. W. Crouch (Post Office) will talk on "Broadcast Interference," will be open to the public. The club meets each Thursday at 7.30 at the Hobbies Association Hut, Haldon Road, Exeter. Sec.: L. R. Jenkin, 16, South Avenue, Exeter.

Manchester.—The South Manchester Radio Club (G3FVA) has acquired new premises at Ladybarn House, Mauldeth Road, Manchester, 14, where meetings are held on alternate Fridays at 7.30. Sec.: F. H. Hudson, 21, Ashbourne Road, Stretford, Manchester.

3-WAY MIXER & peak programme meter for recording and large sound installations etc.

One milliwatt output on 600 ohm line (.775 V) for an input of 30 microvolts on 7.5—30 ohm balanced input. Output balanced or unbalanced by internal switch. The meter reading is obtained by a valve voltmeter with 1 second time constant which reads programme level, and responds to transient peaks.

Calibration in 2 db steps, to plus 12 db and minus 20 db referred to zero level. Special low field internal power packs supplies 8 valves including stabilising and selenium rectifier, consumption 23 watts.

Manufactured by:

VORTEXION LIMITED

257-263, THE BROADWAY, WIMBLEDON, LONDON, S.W.19

Telephones: LIBerty 2814 & 6242-3 *Telegrams: "Vortexion, Wimble, London."*

MARCONI

serves

mankind

Marconi came into a world in which communications were adolescent. When he left it, the marvels of radio were a commonplace. His name had achieved immortality; his work was established in the service of mankind. It is therefore no coincidence that the Company which he founded should supply communication and navigation equipment for aircraft like the Canberra and Comet, which are the most advanced of their class in the world.

MARCONI'S WIRELESS TELEGRAPH COMPANY LTD · CHELMSFORD · ESSEX

Speech Reinforcement in St. Paul's Cathedral

(*Concluded from page 57 of the previous issue*)

Details of the Equipment and Results of Tests

By P. H. PARKIN,* B.Sc., A.M.I.E.E., and P. H. TAYLOR,† A.M.I.E.E.

WE have so far been concerned mainly with the directionality in the vertical plane, but directionality in the horizontal plane may also be desirable. For example, the columns to be used in the dome area of St. Paul's were required to cover a horizontal area in front of them of about 60 degrees on either side of the axis; but radiation to the back was not required and would only have decreased α and increased β in equation (3) of the previous issue.

Kalusche[‡] has described two arrangements for obtaining directionality in the horizontal plane, one of which will be briefly described here. Consider a loudspeaker mounted in an "open-backed" baffle of cross-section as shown in Fig. 5(a), employing a certain quantity of packing material. At the front of the loudspeaker there is a pressure p_f, emitted directly, plus a pressure p_b from the back of the loudspeaker which has been diffracted round the baffle. At a given frequency, the vector diagram, Fig. 5(b), illustrates the behaviour; p_b is 180 degrees behind p_f, but is additionally delayed by an angle corresponding to the the path length from back to front, l, and also by an angle corresponding to the time taken, A, to pass through the packing material, the velocity of sound in which is lower than in air. Fig. 5(c) illustrates the behaviour at the back of the loudspeaker; the pressure p_f' from the front is delayed by an angle corresponding to the path difference l and the pressure p_b' from the back, already 180 degrees out of phase with the front, is in addition delayed by an angle corresponding to A. If A is adjusted so that these two angles are the same, then the resultant pressure R is zero providing the intensities of p_f' and p_b' are equal.

If for the packing we use a material in which the velocity of sound is independent of frequency, then the angle corresponding to A can be equal to l at all frequencies. Now at a certain low frequency the attenuation through the packing material can be such that p_b' is attenuated as much as p_f' is attenuated by diffraction. With increasing frequency, p_f' is more attenuated by diffraction and thus the material must have an attenuation which increases with frequency at the same rate; the resultant pressure at the back will then always be zero.

In the front of the loudspeaker at this certain low frequency, p_b will be attenuated by diffraction and by passage through the material; the resultant pressure is given by R in Fig. 5(b). As the frequency increases, the angle corresponding to l plus A increases so that p_b is coming closer in phase to p_f, and R increases; eventually p_b would be more than 360 degrees behind p_f and R would begin to decrease. However, the intensity of p_b is being decreased by diffraction and by attenuation through the material, so that in practice p_b becomes negligible compared with p_f before this stage is reached.

Kalusche describes a design of this type using "packwatte" (which appears to be cotton waste) as the material; at 200 c/s the emission to the back is about 20 db lower than that to the front.

The requirements for the loudspeaker columns for the dome area of St. Paul's have been discussed above in general terms. The length of the low-frequency section was required to be 11 feet; eleven 10-inch (nominal) loudspeakers were mounted as closely together as possible in a cabinet. The high-frequency section (2ft 9in long) was made up of nine 3½-in loudspeakers; the cross-over network was a half-section operating at 1,000 c/s. Each section of the column was tapered in intensity from the centre toward each end by inserting T-attenuators between each loudspeaker and a load resistance equal to the nominal impedance of the speaker; in this way all the speakers in each section could be connected in series, thus providing a convenient impedance for the cross-over network while keeping reasonable damping across each speaker. The back of the cabinet was left open, and cotton waste was used for the attenuation material. Accurate free-field measurements on this column were

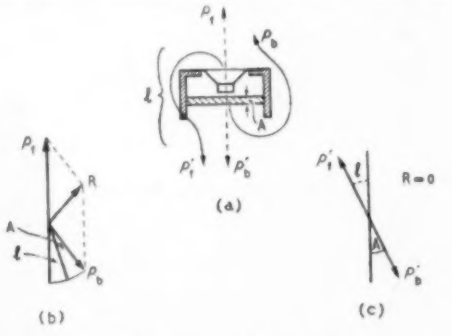

Fig. 5. Principle of directionality in the horizontal plane.

* Building Research Station, Department of Scientific and Industrial Research.

† Pamphonic Reproducers, Ltd.

‡ Kalusche, H., *Zeitschrift für Angewandte Physik*, 1950, **2**, (10) pp. 411-415. (Available in English from Building Research Station as Library Communication No. 765.)

not possible as it was too big for an echo-free chamber, but some approximate measurements made in the open air, although confused to a certain extent by reflections, did indicate that the directional characteristics in the vertical plane had been realized (Fig. 6).

The frequency response on the axis measured at 30-ft distances showed that the output of the 3½-in loudspeakers was on the average 3 db lower than the 10-in loudspeakers. A 3-db attenuator in the low-frequency section equalized the response. (The gain factor, k, of a line source, defined as the ratio of the sound pressure of the line source on the axis to the sound pressure of a single radiator of the same power,[1] is given by $k = 0.73\sqrt{fl}$, where f is in kc/s and l is in feet. This formula predicts a frequency response rising 3 db per octave for a given value of l. No such rise was noticed in the measured frequency characteristic, but this may have been because each section of the column covered only two octaves and because the output from the individual loudspeakers may have been falling.)

The speech in the nave area was reinforced using loudspeaker columns mounted on the sides of piers away from the pulpit (Fig. 1). Their design followed the general principles outlined above, but as they each had a much shorter distance to cover (about 35ft) it was not necessary to make them as long as the dome columns. A length of 6ft appeared to be the best compromise between height above ear level and directionality; their low-frequency sections reached the permissible limit of directionality at about 1,400 c/s and the cross-over was therefore designed for this frequency. The length of the high-frequency section was about 2ft. It was thought that the size of the piers

[1] Meyer, E., Building Research Congress Report, 1951, Division 3, Part 1, pp. 43-48.

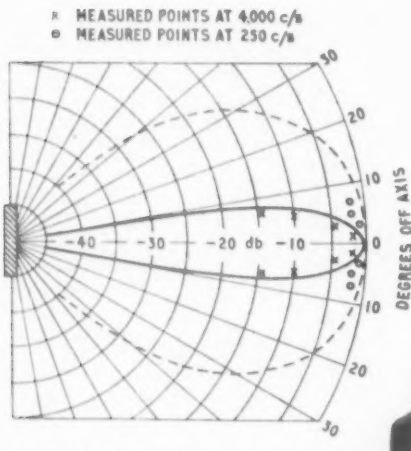

Fig. 6. Directionality in the vertical plane of 11-ft column. The full line is for 1,000 c/s in the l.f. section and 4,000 c/s in the h.f. section; dotted line, 250 c/s in l.f. section and 1,000 c/s in h.f. section.

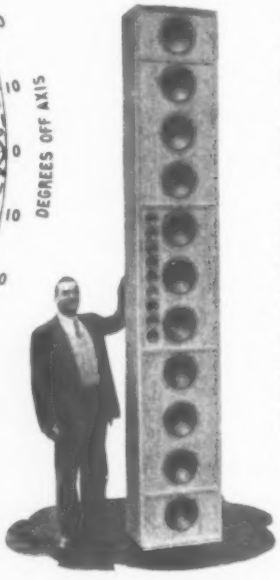

Loudspeaker column for the dome area of St. Paul's consisting of eleven 10-inch (nominal) units for low frequencies and nine 3½-in high-frequency units. The cross-over filter is centred at 1,000 c/s.

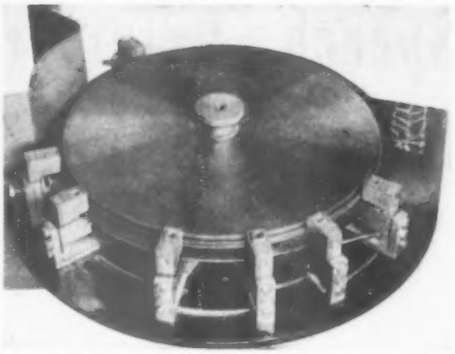

Time delay mechanism for the nave loudspeaker columns, using a disc of magnetic recording material and adjustable playback heads.

they were mounted on provided sufficient directionality in the horizontal plane, so the directional arrangement using cotton waste backing was not employed.

Time Delays.—A previous article[2] has described the use of time delays to preserve realism, and this technique was employed in the Cathedral. The first pair of nave loudspeaker columns (Fig. 1) was delayed by a time interval corresponding to the path difference between the pulpit column and the nave columns, plus 5 msec. The second and third pairs were delayed correspondingly, but plus 10 msec and 15 msec respectively. The amplitude of these nave columns was also reduced, and the Haas effect ensured that all the sound appeared to be coming from the pulpit.

The time delay mechanism consisted of a turntable carrying an 11-inch diameter disc of plastic magnetic recording material. This disc extended beyond the periphery of the turntable[3] and provided an annulus supported only at its inner radius. Recording, playback and erase heads were mounted on the deck of the unit in such a way that the underside of the annulus was in contact with the pole pieces of the heads. Small felted weights carried in slides over each head maintained contact between the annulus and the pole pieces.

The recording head was permanently fixed and the playback heads were attached to radius arms which allowed them to be moved and clamped at any position on the circumference of the annulus. A graduated scale, marked off in feet and milliseconds, facilitated the setting-up of the heads to give the required delay times. The maximum overall delay obtainable on this unit corresponded to a distance of 200 yards, the peripheral speed of the annulus being 30in per second. The

[2] Parkin, P. H., and Scholes, W. E., "Recent Developments in Speech Reinforcement Systems," *Wireless World*, 1951, **57**, (2), pp. 44-50.

[3] Patent Application (Pamphonic Reproducers, Ltd.), No. 22287/1951.

minimum delay between adjacent playback heads corresponded to a distance of 20ft.

Erasure of the recorded sound took place at each revolution of the turntable just in advance of the recording head. In an installation of this sort it is essential to guard against failure of the erasing mechanism; should this happen the recorded sound is continually repeated from the loudspeakers. To cover such an eventuality, the recording was first erased by permanent magnets and then again by a supersonic head. Although the permanent magnets removed the recorded sound the residual noise level was high, and this was removed by the supersonic head.

The recording and playback amplifiers were conventional in design. The main power amplifiers were standard 25-watt public address amplifiers feeding the loudspeaker columns at 100 volts.

Power Requirements.—The tapered columns as designed for St. Paul's are inefficient electrically since nearly all of the acoustic power is radiated from the centre loudspeakers while the electrical power is distributed equally between all the loudspeakers. This could be avoided in a final design, e.g., by use of a tapped transformer, but the loss of power is not important when, as in St. Paul's, the columns are used for speech only and the total acoustic power required is only of the order of milliwatts.

However, another important use of this type of loudspeaker arrangement is to cover large numbers of people, as, for example, at sport stadiums; in these cases the acoustic power required may be considerable, particularly when music has also to be amplified. The loss of electrical power must then be avoided, and in any case it is probably better to use a uniform line source; the secondary lobes are still small compared with the main lobe, and the directivity of the line source results in a saving of power. Thus the gain factor, $k = 0.73\sqrt{fl}$ for an 11-ft column at 1,000 c/s is 8.03, or 18 db. Meyer[4] quotes the example of a 3-metre column with a total electrical power of 75 watts, producing a sound pressure level of + 94 db relative to 0.0002-dynes/cm^2 at a distance of 100 metres.

At the time of writing several details of the St. Paul's installation remain to be settled, but they concern this particular installation only and are not of general interest. For example, there is a requirement for speech at the altar to be amplified while maintaining the illusion that the sound is coming from the altar. This will probably be done by installing another column out of sight near the altar and then delaying the dome and lectern columns.

Using the pulpit column plus the six nave columns, the word intelligibility was measured in the empty Cathedral at the six positions indicated in Fig. 1 of the previous instalment, with and without the delays, but otherwise with the system unchanged. It was mentioned in a previous article[1] that time delays would probably improve intelligibility and this is, in fact, the case as is shown by Table I. It is seen that even in the empty Cathedral the intelligibility is high, and from equation (7) we can expect it to be better still when the congregation is present.

TABLE I

Position	Word Intelligibility		Corresponding Sentence Intelligibility	
	Delayed	Undelayed	Delayed	Undelayed
1	99	92	100	97
2	95	93	98	97
3	92	89	97	97
4	93	85	97	96
5	85	61	96	85
6	85	52	96	78

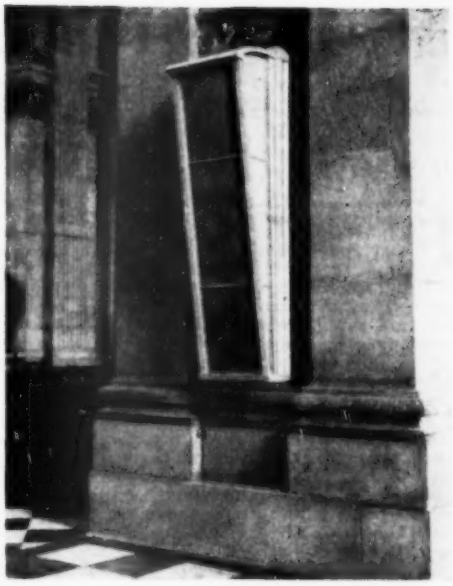

One of the 6-ft loudspeaker columns mounted on the piers in the nave in St. Paul's.

However, the main advantage of the columns plus the time delays is the naturalness of the reinforced speech, a quality which is difficult to measure. With the new system, the illusion that all the sound is coming from the pulpit is maintained over the seating area except, not surprisingly, for the few small areas behind the pillars in which the pulpit is screened acoustically and visually. More important, probably, is the apparent lack of reverberation when the column system is used.

Acknowledgments.—This work is part of the research programme of the Building Research Board of the Department of Scientific and Industrial Research. Thanks are due to the Dean and Chapter and the officials of the Cathedral for help freely given at all times.

TWO-COLOUR P.V.C. WIRES

WIRES with two-colour P.V.C. covering have recently been introduced by Tenaplas Ltd. of Upper Basildon, Pangbourne, Berks, to provide greater possibilities in colour coding without departing from the small basic range of strongly contrasting colours which are in common use. This is done by superimposing a spiral of coloured lacquer on the P.V.C. covering, so that any number of code variations are made possible by the use of different spiral colours, while the basic identifying colour can be kept the same.

ECONOMICAL METERING

Using a Single Meter to the Best Advantage

By H. B. DENT

FOR some years past there has been a plentiful supply of reasonably cheap single-range meters in the surplus market and one acquired a habit of using them fairly lavishly in all kinds of radio equipment. In many cases built-in meters are nothing more than a luxury, a very convenient luxury it must be admitted, but there are some equipments in which the inclusion of meters of one kind or another is an indispensable necessity.

The supply of these cheap meters is now beginning to show signs of drying up and thus it has become necessary to consider ways and means of being a little more sparing in their use, but at the same time retaining all the essential monitoring facilities hitherto available. The pressing questions that arise from this are; how best can a single meter be employed? how much can it usefully do? and should it or should it not be permanently wired into the apparatus?

Only the individual user can find the right answers to these questions since there are so many unknown factors involved, but a little guidance might possibly be given in the light of recent experience and after studying the various ways of utilizing a single meter to the best advantage.

One way is to employ a series of jacks distributed throughout the equipment and plug the meter in each as required. It has the advantage of releasing the meter for other purposes, but as the currents required to be measured will most likely vary widely, a multi-range instrument is necessary. This entails first converting the single-range meter into one to cover the range of currents involved, but this is not a difficult matter.

A single-range meter can be made to answer most requirements if suitable shunts are joined across each jack and they are easily made up from a few inches of resistance wire. When the current to be measured is within the range of the meter these jacks are left unshunted. Fig. 1 shows a circuit in which an unshunted jack is used, this being a type in which there is a middle spring (a) normally in contact with the spring (b) and wired externally to the frame (c), so that when the plug is withdrawn the two "live" contacts (b) and (c) are short-circuited.

Shunted Jacks

In order to avoid even a momentary break in the circuit, which in audio equipment can give rise to quite shattering crashes in the loudspeaker, a resistor of 100 ohms or so (½-watt will suffice) can be joined across (b) and (c). It is never in circuit for more than a fraction of a second (unless the plug is only partially inserted) so it is not additive to any other resistance, such as a bias resistor, which may be included in the same lead.

When shunted jacks are employed the single type as shown in the circuit of Fig. 2 will meet requirements as the shunt R maintains circuit continuity with the plug out. The resistance of R will rarely be more than an ohm or two, so that it has a negligible effect on the circuit resistance. Inserting and withdrawing the plug will produce no objectional noises in the loudspeaker.

One advantage of wiring the meter shunts across the jacks is that it provides a simple, but most reliable, protection to a low-reading meter and it becomes impossible under normal conditions to burn it out, or bend its pointer, by plugging the meter into a 50-mA circuit when set on its 5-mA range, or whatever the equivalent might be.

Duplication of resistance shunts becomes inevitable with this scheme, but the amount of resistance wire needed is so small as to be of little consequence.

Jacks have the disadvantage of being rather cumbersome and sometimes awkward to accommodate in accessible positions, while in the ordinary variety the frame and fixing bush form one of its contacts. This restricts the jack to use in circuits where the frame can be at the same potential as the chassis, usually h.t. negative, otherwise it must either be mounted on an insulating plate or a type used that has both its contacts fully insulated from the body of the jack. For example, insulated jacks would have to be used if the metering points were anywhere on the h.t. positive side of the valves, as in a small transmitter where it is generally required to know the values of anode, screen and grid currents separately and not lumped together as would be the case if the jack were fitted in the

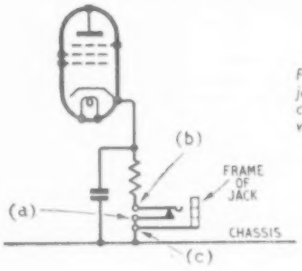

Fig. 1. Self-shorting jack wired into the cathode circuit of a valve.

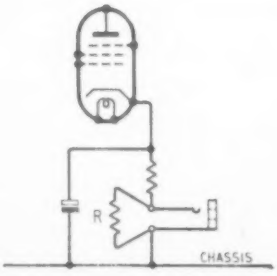

Fig. 2. With a meter shunt R permanently joined across the jack it is not usually necessary to employ the self-shorting type.

cathode lead with its frame "earthy."

A scheme which avoids many of the aforementioned difficulties, yet which provides all the safeguards of individually shunted jacks, is to have just one insulated jack for the meter and a rotary, or wafer, switch to connect the meter across appropriate shunts wired into the circuit at points where current measurements are required. A variation of this scheme is to include the meter in the actual equipment, and while it means tying up a meter permanently for every piece of apparatus fitted with metering facilities, the small 2½-in type are not yet so scarce nor so expensive that it makes this idea impracticable. Moreover, the meter, and the right one at that, is always where it is wanted at the time it is needed, and by merely rotating a switch the operating condition in several valve stages can be seen at a glance.

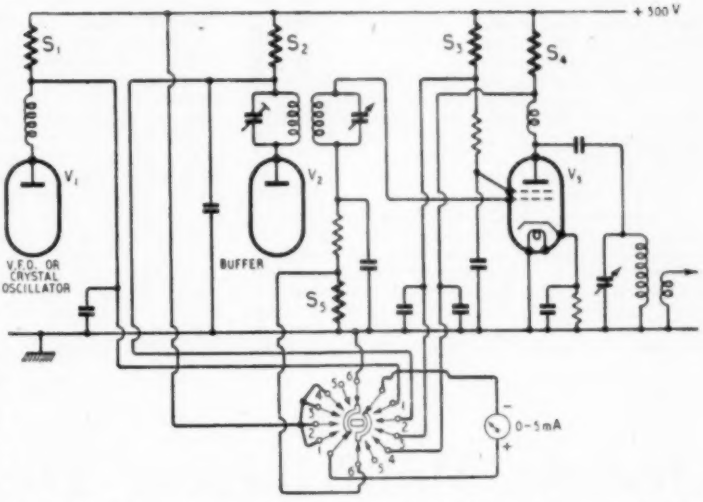

Fig. 3. Skeleton circuit of a small transmitter showing positions in which meter shunts are required for routine checking and tuning of the equipment.

Fig. 4. Set-up of the apparatus used for adjusting the meter shunts and described in the text. That on the left of the broken line is external to the set.

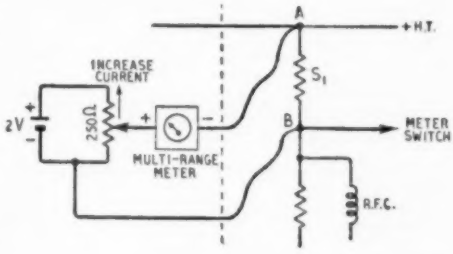

In a transmitter current readings often serve as a guide for tuning and for keeping a check on current consumption of valves, which may be operating very close to their maximum limiting conditions.

Fig. 3 shows a skeleton circuit of a small 10-watt transmitter in which the monitoring scheme discussed here is employed. The transmitter covers the amateur "top-band" only (1.715-2 Mc/s), includes a v.f.o. (variable frequency oscillator) and a band-pass coupling between the buffer stage V_2 and the power amplified V_3, thus minimising the amount of retuning for any change in frequency.

As used in Fig. 3 provision is made to measure the combined anode and screen currents of V_1, the v.f.o. and of V_2, the buffer, but the anode, screen and grid currents of V_3, the power amplifier, are measured separately. Incidentally the first two valves are VR91s (EF50), and the final a VT501 (TT11).

Grid current of V_3 is measured by switching the meter across the shunt S_5, which is not a shunt in the sense that S_1-S_4 are, as it does not modify the meter's reading: it is a 150-ohm resistor and merely serves as a point across which to connect the meter for reading over its normal range of 0-5 mA.

It was convenient to make the shunts S_1, S_2 and S_3 of such value that the meter reads full scale with 25 mA flowing, thus applying a multiplying factor of 5 to the existing scale. Shunt S_4 was adjusted to give a full-scale deflection with 50 mA, the multiplying factor being 10.

The actual amount of resistance required for S_1, S_2 and S_3 depends on the internal resistance of the meter. The small 2½-in 0-5 mA moving coil meters the writer has used have internal resistances ranging from about 13 to 15 ohms, so that for 0-25 mA conversion shunts S_1, S_2 and S_3 each require to be about 3.3 ohms and S_4 about 1.5 ohms. When the meter resistance is known exactly, and means are available for measuring low values of resistance accurately, the shunts can be made to calculated values and measured before fitting into the circuit. The following simple formula gives the value of the shunt in each case:—

$$R_s = \frac{R_m}{n-1} \text{ ohms}$$

where R_s = resistance of shunt
R_m = resistance of meter
n = scale multiplying factor.

Where no such facilities are available a very simple test rig will enable the shunts to be adjusted by the trial and error method.

The set-up used for the purpose is shown in Fig. 4 and consists of a 2-V accumulator (a 1½-V dry cell could be used instead), a 250-ohm potentiometer and a multi-range meter. These are connected up as shown and joined to the two points A and B across which points is joined also the length of resistance wire to be adjusted to form S_5. Points A and B are already wired up to the meter shunt switch and to the

0-5 mA meter in the transmitter. About 36in of No. 28 s.w.g. (silk or enamel covered) Eureka resistance wire is used to commence with and progressively shortened until the potentiometer can be moved to register 25 mA on the multi-range meter and 5 mA on the built-in meter.

Fig. 5. Constructional details of the shunts are shown in this drawing.

In all cases about ½in is allowed for connecting and the length of wire wound on a bakelite rod which is then fixed to the chassis. Two more identical shunts are made for S_2 and S_3. S_2 is made by starting with 18in of wire and adjusting to give full-scale deflection on the 0-5-mA meter with 50 mA registered on the multi-range meter. This shunt is finished off as already described, one method adopted by the writer being shown in Fig. 5. The former measures 1¼in × ½in × ½in. The two pegs are ½in apart.

Although there are only five points in the circuit of Fig. 3 where measurements were required it was necessary to use a 2-pole 6-way switch, shown diagramatically as a single-plate wafer, but it could take any convenient form. A blank position (No. 5 in this case) must be allowed at the point of change-over from anode-current to grid-current measurement so as completely to isolate the meter from all circuit wiring during the change-over from the h.t. line to the earth line.

In other types of equipment where there is no such transition from a high- to a low-voltage circuit, switching sequences can be continuous, but if any change is made which results in the meter being switched to entirely different parts of a circuit, as illustrated in Fig. 3. then a blank contact must be allowed at each transition.

Decade Multivibrator Design

Method of Stabilizing Frequency Division from a Crystal Drive

By J. E. ATTEW

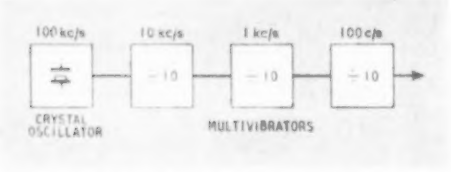

Fig. 1. Schematic diagram of crystal-controlled multivibrator chain.

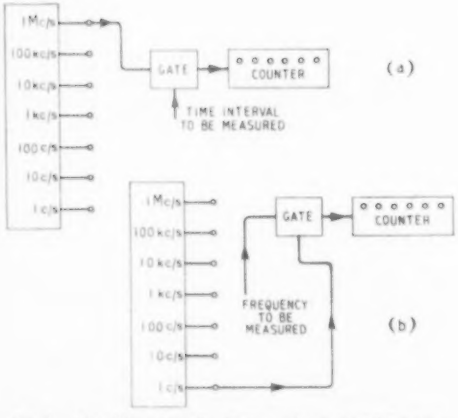

Fig. 2. Use of decade multivibrator and counter (a) for time measurement, when the gate is opened for the time interval to be measured (b) for frequency measurement, when the gate is opened for exactly one second.

IT is well known that a crystal oscillator controlling a chain of decade multivibrators (Fig. 1) can provide a very accurate source of frequencies. Such a system has been used for controlling clocks, frequency checking, time interval measurement, etc.

The writer had occasion to investigate such systems for accurate frequency and time interval measurements, in conjunction with a commercial electronic counter capable of registering counts up to 10^6 (See Fig. 2).

Various multivibrators were investigated but all suffered to some degree from a particular fault, which unfortunately causes large errors when the multivibrator is used for the purpose mentioned. This fault is the effect of the multivibrator momentarily jumping to the next lower ratio of division (in this case ÷9), although synchronizing was injected to discriminate

Fig. 3. Details of synchronizing pulse waveforms. (a) Output of 10-kc/s multivibrator. (b) After differentiation by circuit with time constant approximately 1·5 pulse time. (c) Anode waveform of 1-kc/s multivibrator showing timed locking. The synchronizing pulses are inverted after passing through the circuit of Fig. 4.

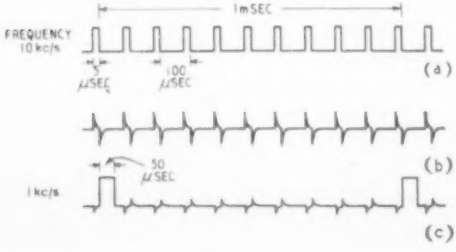

for even division. This effect is very spasmodic in nature, causing an increase in the number of pulses counted over a given time period. It is thought to be due to an increase in amplitude of the injected synchronizing voltage (due to heater or h.t. voltage changes), causing the multivibrator frequency to be "drawn" towards the synchronizing frequency. The multivibrator was never found to "jump" to a higher ratio of division.

It was found that if a pulse of opposite polarity were inserted just before the true synchronizing pulse, this would prevent the multivibrator triggering if it was about to trigger early, so holding it off until the true synchronizing pulse arrives (see Fig. 3).

This method of synchronizing is most economically carried out with an asymmetrical multivibrator which gives a short pulse out. The basic circuit is shown in Fig. 4, using a double triode. The oscillator gives a positive pulse out of first anode and requires a negative synchronizing pulse, as shown.

The final circuit (Fig. 5) shows that each frequency is available via a cathode follower, all with positive-going pulses and synchronized to a 100 kc/s crystal.

The anode circuit of the modified Colpitts crystal oscillator is over-compensated by L_2, causing a large positive overshoot which is differentiated and shaped by the cathode-follower circuit.

The 1-Mc/s circuit consists of various shaping circuits (L_1 and C_n resonating at 1 Mc/s), producing a $\frac{1}{2}$ μsec positive pulse at the output.

The synchronizing condenser between each multivibrator is adjusted to give the correct differentiation for each preceding value of pulse which, the synchronizing being largely independent of injected pulse amplitude.

The unit is supplied from a stabilized h.t. supply, as shown in Fig. 5.

Setting up presents no difficulties if a double-beam

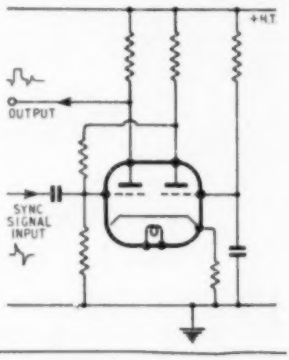

Fig. 4. Basic multivibrator circuit. A negative synchronizing pulse is normally required.

COMPONENT VALUES FOR OTHER MULTIVIBRATORS

f	R_1	R_2	C_1	C_2	C_3	C_4
1 kc/s	2·2 MΩ	1 MΩ	0·005 μF	0·05 μF	500 pF	0·1 μF
100 c/s	2·2 MΩ	1 MΩ	0·05 μF	0·25 μF	0·005 μF	1 μF
10 c/s	3·3 MΩ	2·2 MΩ	0·5 μF	0·5 μF	0·05 μF	2 μF
1 c/s	6·8 MΩ	4·7 MΩ	2 μF	0·5 μF	—	DIRECT

Fig. 5. Complete circuit diagram of stable decade multivibrator source. Component values for decade frequencies of 1 kc/s and below are shown in the table.

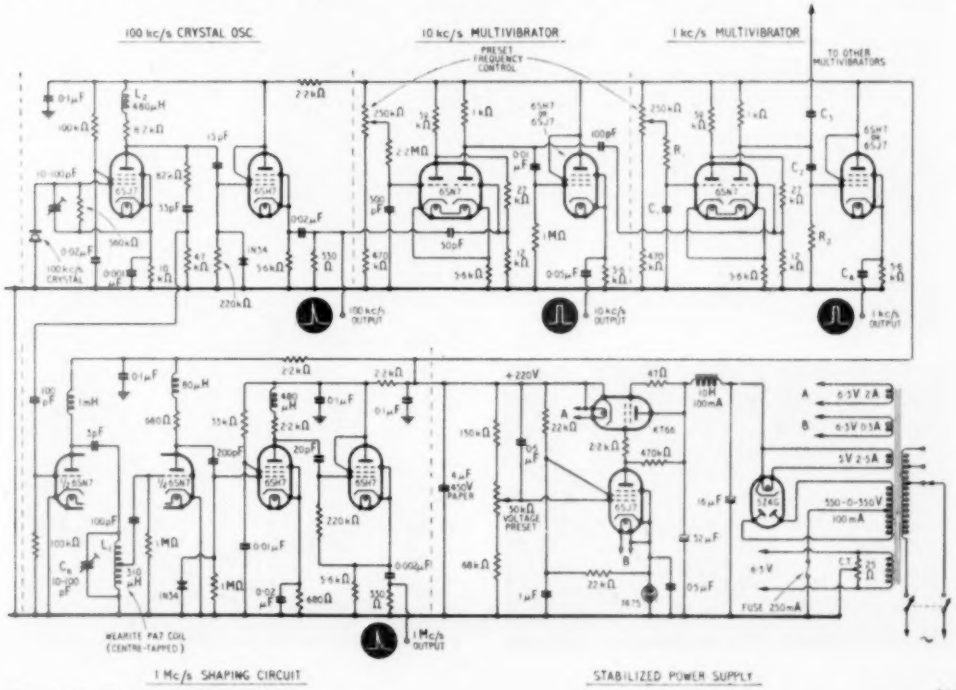

oscilloscope is used. After setting the crystal to a standard (or by means of beats between the B.B.C. Light Programme on the long-wave band (200 kc/s) and the second harmonic of the crystal), the crystal output is applied to one beam, and the oscilloscope time base is synchronized to display ten pulses (one at least will be observed in the flyback). The next lower multivibrator is then applied to the second beam and its frequency adjusted until one pulse is apparent, the process being repeated downwards. The 1 c/s pulse was timed in conjunction with the electronic counter.

The original unit has been in continuous use for a period of more than six months, and during this time it has not required resetting, nor has any ratio-jumping been observed.

BUSINESS RADIO

Some New Applications

DURING the latter half of last year there was a tremendous increase in the number of stations licenced by the Post Office for mobile radio services (business radio). According to figures quoted at the annual meeting of the Radio Communication & Electronic Engineering Association fixed stations increased by some 50 per cent and mobile stations by over 70 per cent. The total number of stations at the end of the year—excluding equipment issued to police and public utilities—was nearly 2,800.

The most recent application is the equipping of a number of the large ocean-going tankers delivering crude oil to the new refinery at Fawley, Hants. The operating company, Esso, has found the tests carried out with three tankers since September so successful that the whole fleet is ultimately to be fitted. Initially 37 are being equipped.

The problem facing the authorities was how to organize the arrival of tankers so as to maintain a steady supply of oil without causing congestion. It is only when the tankers have reached the Solent that the Marine Superintendent at Fawley can estimate the volume of traffic, but advice and instructions cannot be given by radio to the ships' masters on the normal shipping wavebands because of the wireless silence imposed. As there is, however, no such ban on the use of v.h.f. business radio, the obvious solution was to use this means of communication, which, it was found, provided complete coverage of the Solent and its approaches.

Unlike other mobile stations which, being usually in cars or vans, have to depend on batteries for their power supplies, the tankers' sets can be operated by the ships' mains. It has been possible, therefore, to employ heavier and more powerful equipment.

Another special application of business radio is that of British Field Products, Ltd., at Walsingham, Norfolk, which has the largest grass-drying plant in the country and is now producing much-needed animal foodstuffs from fresh grass, lucerne and other green crops. To obtain the maximum protein value the greenstuffs must be cut at the appropriate time, transported and dried within a few hours.

As the area from which crops are obtained extends to some 15 miles from the factory, the problem facing the originators of the scheme was how to ensure a steady delivery of freshly cut crops. This involves reports by cropping managers and analysts and the passing of instructions to field managers and even to drivers of tractors. Business radio provided the solution and the company now has a 15-watt fixed station and a number of 5-watt mobile sets in use.

Another company using business radio is the Pressed Steel Co., manufacturers of refrigerating plant. Having installed over 13,000 refrigerators, some in hospitals and laboratories for the preservation and freeze-drying of valuable substances such as blood-plasma, penicillin, streptomycin and certain vaccines and viruses as well as for special foodstuffs, the problem was, how to ensure prompt attention in the event of a breakdown in any such plant. The company has thirty service vans engaged mainly on routine visits in the Greater London area and v.h.f. radio-telephone equipment has been installed in twenty-two of them. So as to cover the whole area served by the vans two transmitters have been used, one at Richmond and the other at Highgate, both being operated by remote control from the company's service depot at Gunnersbury. The fixed stations are Pye PTC 704's and the vans have PTC 113's.

(Right) Pye PTC 704 transmitter-receiver installed by Rees Mace in a tanker. (Below) The control equipment (with microphone and receiver for each fixed station) at the service depot of the Pressed Steel Co.

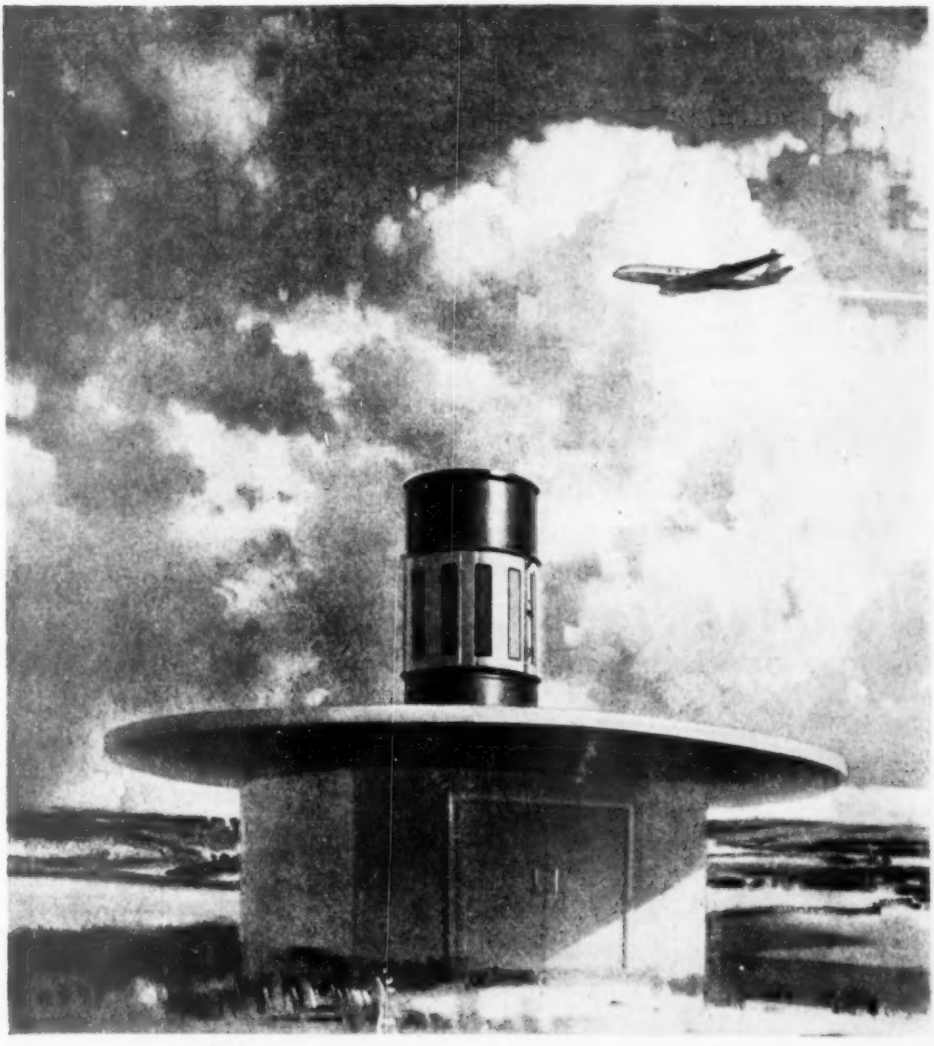

Safe arrivals — The operation of modern high speed aircraft has shown the need for an omni-directional aid which will provide direct bearing information within the aircraft exclusive of communications facilities, and a performance practically unaffected by the prevailing atmospheric conditions.

Marconi V.O.R. equipment will fulfil this important requirement

MARCONI V.O.R

MARCONI'S WIRELESS TELEGRAPH COMPANY LTD · CHELMSFORD · ESSEX

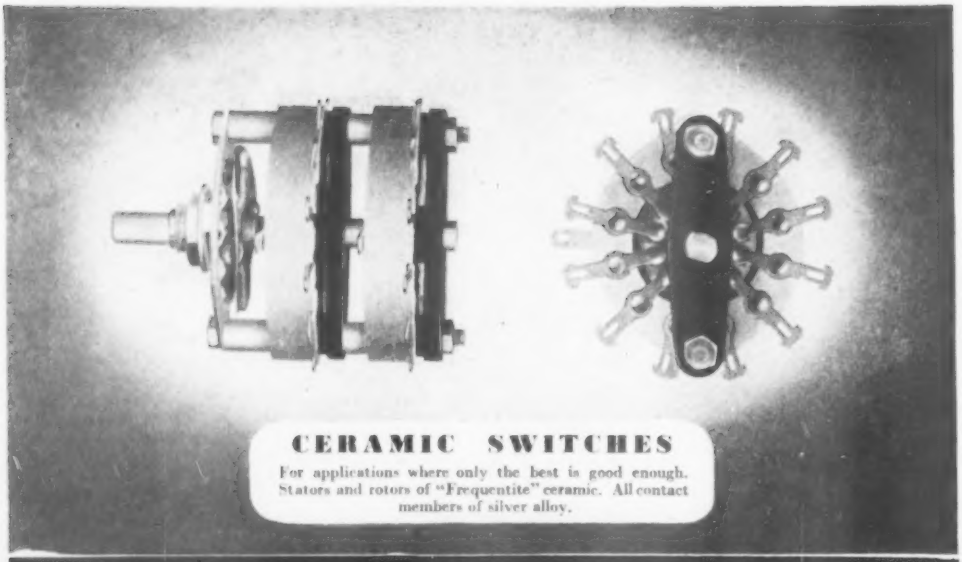

CERAMIC SWITCHES

For applications where only the best is good enough. Stators and rotors of "Frequentite" ceramic. All contact members of silver alloy.

Wright and Weaire Limited

138, SLOANE ST., LONDON, S.W.1. TEL: SLOANE 3214-5. FACTORY: SOUTH SHIELDS, CO. DURHAM.

THE GREATEST ADVANCE TOWARDS PERFECT REPRODUCTION

AMAZING

THE NEW TONE COLOUR UNIT PLUS THE AZ TYPE AMPLIFIER £32.10.0

SOUND SALES LIMITED

DEMONSTRATIONS at our London Showroom:

LLOYDS BANK CHAMBERS, 125 OXFORD STREET, W.1 (Entrance in Wardour Street)

Telephone: GERrard 8782

(Works: West Street, Farnham, Surrey. Telephone: Farnham 6461)

N.P.L. CERTIFIED PERFORMANCE

TOTAL POWER

How to Find It When Several Currents Flow in the Same Circuit

By "CATHODE RAY"

HAS any wisecracker ever remarked that the obvious is seldom true? If not, I will; in spite of the grave risk that some well-meaning but literal-minded person will write me several learned pages to show where the proposition breaks down. But I am sure I can count on the support of readers of detective fiction, and probably also of the more experienced and disillusioned students and experimenters. What, after all, is the obvious? "Something one learnt yesterday" might be the cynic's answer. Or is it often something we haven't bothered to think about very thoroughly?

For instance, suppose G_1 and G_2 in Fig. 1 are two a.c. generators. When G_1 is working alone it develops 10 watts in the circuit. And when G_2 is working alone it develops 2 watts in the same circuit, at some higher frequency—say four times that of G_1. If now G_2 is started up when G_1 is working, its current, i, will be a harmonic ripple on the G_1 current, I; and isn't it obvious that the total power cannot possibly be 12 watts, for, as Fig. 2 confirms, i subtracts from I just as much and as often as it adds to it? What is gained on the swings is lost on the roundabouts; Q.E.D., and all that.

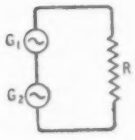

Fig. 1. *If two generators are driving currents through the same circuit, what is the total power in terms of the power of the separate currents?*

If anybody liked to be particularly awkward he might point out that if G_2 happened to generate a third harmonic it would reduce the effect of G_1 twice as often per cycle as it increased it (Fig. 3(a)), so what then? Or if the phase slipped a little the proportions would be reversed (b). It is obvious then, is it not, that calculating the total power of a number of different alternating currents flowing in the same circuit must be a complicated business?

There are two other cases that might be thrown into the collection before trying to sort it out. One is when the two currents are of the same frequency. If they happen also to be of the same amplitude, and opposite phase, they cancel out and there is no current and so no power. If they are in the same phase there is double current. This, surely, helps to confirm the

Fig. 2. *(a) and (b) represent what might be the currents from G_1 and G_2 in Fig. 1. The total current, plotted by adding (a) and (b), is shown as (c), in which I is repeated in dotted line to show more clearly how i alternately strengthens and weakens it.*

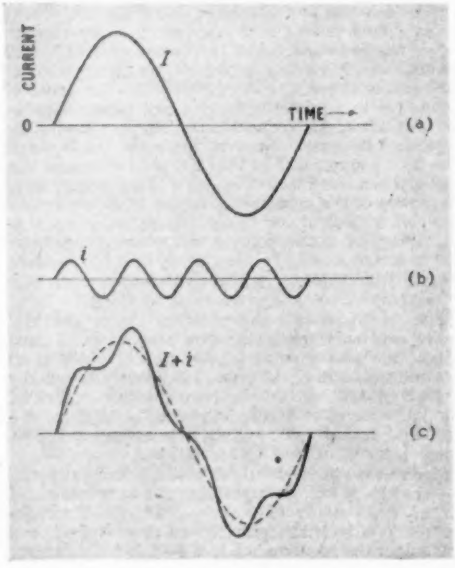

Fig. 3. *In this case i has three times (instead of four times) the frequency of I. The effect of adding it to I is shown for two different phase relations.*

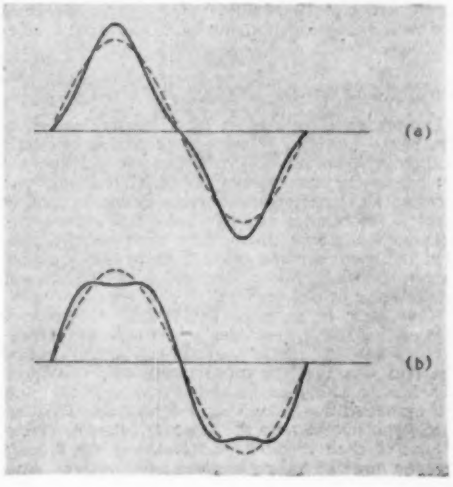

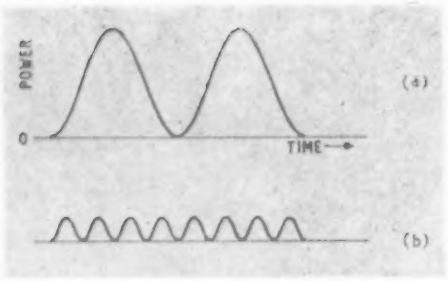

Fig. 4. Here at (a) is shown the power graph corresponding to Fig. 2(a), obtained by plotting the square of the current; and (b) corresponds to Fig. 2(b). What corresponds to Fig. 2(c)?

Fig. 5. A combination of currents (d.c. and square-wave a.c.) that lends itself to easy calculation of separate and combined power.

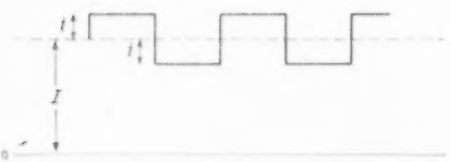

impression one gains from Fig. 3, that the power in the circuit depends on the relative phases of the currents?

The other case is a.c. superimposed on d.c., which concerns us all, because it happens in every valve. There can be no doubt that adding a ripple of a.c. to a larger d.c. makes no difference to the average current reckoned over any number of complete cycles. A milliammeter in the anode circuit of a Class A power amplifier reads the same whether or not the valve is delivering signal power—or at least it would if the valve were a perfectly linear one. Yet in one event power is not going into the load, and in the other it is.

Adding Currents

I have now assembled an exceptionally fine collection of red herrings. Have you succeeded in clearly identifying them all? If so, there is perhaps not much point in pursuing the matter. But if you have accepted all the foregoing obvious things as true, or perhaps suspected there was something wrong but were not quite sure where, or are not satisfied with what the books say and prove mathematically if they seem to contradict the evidence of your eyes, then it may be some help to read on.

First, there is no catch about the way we have been adding the currents due to the separate generators. What is usually called the Superposition Theorem says that the total current due to two or more e.m.fs acting in the same circuit is the sum of the currents due to each e.m.f. separately. In other words, you just add up the separate currents, taking account of their direction—a current in the reverse direction must, of course, be given a minus sign. And there is one important proviso—the circuit must be linear; that is to say, current must be exactly proportional to voltage as in Ohm's Law, so that their graph is a straight line passing through the origin. Strictly, that rules out all circuits containing valves and iron-cored coils; but under favourable conditions and within certain limits these can sometimes be reckoned as approximately linear. To keep things simple, non-linear circuits are excluded from the present discussion. So the current-adding method used in Figs. 2 and 3 is quite correct.

Another basic principle we can take for granted is that the *average* value of any alternating current (or voltage), reckoned over a complete cycle, or any number of complete cycles, is nil. In fact, an alternating current could almost be defined as one of which that is true. If any current is found to have an average value, then that much of it is d.c. In a waveform graph, such as Figs. 2 and 3, average value is represented by average height above the base-line, and is equal to area above the base-line divided by horizontal distance. In the graph of one cycle of any purely alternating current the areas above and below the line are equal and cancel out. So it is perfectly correct to say that adding i in Fig. 2 has no effect on the average value of the current. It is zero in every case shown. (True enough, one sometimes reads that the average value of a.c. is 0.64 times the peak value; but that is when it is averaged over *half* a cycle.)

While it is easy to see that the positive and negative half-cycles cancel out everywhere in Fig. 2, there may be a flicker of hesitation about Fig. 3, because of the third harmonic strengthening the fundamental twice as often per cycle as it weakens it (or vice versa). The answer to this, of course, is that although the third harmonic (unlike the fourth harmonic in Fig. 2) admittedly alters the average value of the fundamental-frequency half-cycle, it alters both half-cycles equally, so they still cancel one another out.

So much for average values of currents. How about their power? It is proportional not only to the current but also to the voltage, and since the voltage across a linear resistance is proportional to the current, the power is proportional to current-squared. And the square of a number is positive, no matter whether the number is positive or negative. So the graph of a.c. power in a purely resistive circuit never falls below the base-line. In an electric lamp or heater the negative half-cycle is just as useful as the positive. The power graph of I in Fig. 2(a) is as shown in Fig. 4(a), and that for i as in Fig. 4(b). Presumably, then, the power of the combined currents is shown by the result of adding (a) and (b) in Fig. 4, and is equal to the powers of the separate currents added together? But how can this be, seeing that there is no doubt (Fig. 2(c)) that i reduces I as often and as much as it increases it?

The short answer is that although the net result of adding and subtracting an equal amount is nil, that is not true of the square. Adding 20 to 100 gives 120 and subtracting 20 from 100 gives 80, and the average of 120 and 80 is 100—the same as before. But 120 squared is 14,400 and 80 squared is 6,400—4,400 up but only 3,600 down, so the average is 10,400, which is the square of 100 *plus* the square of 20.

Fig. 5 shows more clearly how this principle applies to electrical power. It represents the simplest case I can think of—square-wave a.c. added to d.c. Throughout the positive half-cycle the current is $I+i$, and throughout the negative half it is $I-i$. If for simplicity

we suppose the resistance is 1 ohm, the power is $(I+i)^2$ and $(I-i)^2$ respectively. To find the average power we have to add these together and divide by 2:—

$$(I+i)^2 = I^2 + 2Ii + i^2$$
$$(I-i)^2 = I^2 - 2Ii + i^2$$
$$\therefore \frac{(I+i)^2+(I-i)^2}{2} = \frac{2I^2+2i^2}{2} = I^2 + i^2$$

So the power when both currents are flowing is the sum of the separate powers. The same applies with a circuit of any resistance R, as can be seen by doing the same little bit of algebra with that factor included. It is because power increases more rapidly than the current that the increase in power during the positive half-cycle more than outweighs the decrease during the negative half. The algebra simply demonstrates the general truth of what we found with the particular numbers 100 and 20.

"Brick-built" Waveforms

The proper way of demonstrating the principle more generally still, for all waveforms and any number of simultaneous currents, is by the integral calculus. But I am writing for those who either lack the calculus or who, while accepting its proofs, like to "see" them as well. I sympathize with this desire, for I am never really happy about a conclusion that has only an involved chain of mathematical manipulation to link it with familiar territory. So, assuming that the case of Fig. 5 has been clearly seen and accepted, let us see how we can extend its application. It would make no difference to the principle if the amplitudes of the a.c. cycles were varied, say by modulating them. It would merely vary the value of i, which can be anything. Nor would the principle be affected if batches of positive half-cycles were lumped together, and likewise their negative partners, so long as the averaging process embraced both. Fig. 6 shows how this amplitude-varying and rearranging process can be used to make a batch of 15 square-wave cycles into a rough approximation to a single sine-wave cycle. It could be made as good an approximation as one wished—still without affecting the power-addition principle—by using a large enough number of sufficiently high-frequency square waves. So it is reasonable to conclude that what we have proved for a square wave holds good for any a.c. waveform.

Although i in Fig. 2 is added to another a.c., the same line of reasoning that we have used for d.c. can be applied to that case too, because Fig. 2(c) is so symmetrical. At every point in the I cycle where the effect of i is to increase the total current, one can find another point where I has the same amplitude and i decreases the current by the same amount. Thus the fourth half-cycle of i can be set off, bit by bit, against the first; the third against the second; and so on.

Fig 3 is not quite so easy. But the apparent inconsistency—that the "ups" are twice (or half) as numerous as the "downs"—disappears when one realises than an "up" from an already large current has more effect on power than one from a smaller current. The power increases of the added current is, in fact, proportional to the amplitude of the current to which it is added. So in Fig 3(a) the effect of the positive half-cycle of i at the peak of I is matched by *two* negative half-cycles centred on 30° and 150°, where I is *half* its peak amplitude. If you are sufficiently interested you might like to try extending the algebra to cover this case, averaging $(I+i)^2$ and $2\,(I/2-i)^2$ (and remembering to divide by 3 because there are 1 + 2 half-cycles of i).

Even if I did try it on, I could hardly expect to get away with the bluff that I have proved the case for Fig. 3. Somebody would be sure to point out that the half-cycles of i are not concentrated exclusively at the 30°, 90°, and 150° points of I, and that the matching of equal-amplitude points that worked with Fig. 2 won't with Fig. 3. And that—unless someone can think of a dodge for extending the "building brick" technique to include combinations of a.c. such as those in Fig. 3—is regrettably true. But at least we can see, as we may not have done at the start, that (a) and (b) are at least roughly equal as regards total power, and that the more elegant mathematical demonstrations which prove exact equality are not so hard to believe as they might have been at first.

One red herring waiting to be disposed of is the power of a combination of currents of the *same* frequency. Obviously (and it really is true this time!)

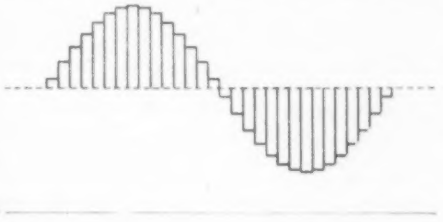

Fig. 6. How the principle established for Fig. 5 can be extended to cover other waveforms.

Fig. 7. I_1 and I_2 are equal and opposite a.c. of the same frequency. Their power curves, (b) and (c) respectively, are identical. Yet the combined current, and its power, are zero.

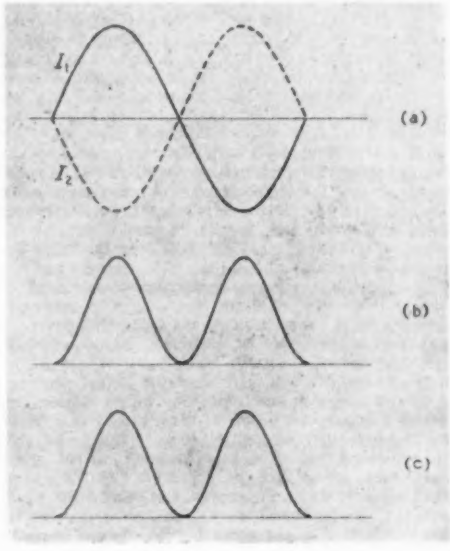

it is possible to add two powerful currents together and get no power. If they are equal and opposite they just cancel out. Suppose I_1 in Fig. 7(a) represents one of the currents. Its instantaneous power graph, obtained as before by plotting current-squared, is shown at (b). I_2 is the equal and opposite current, which would cancel I_1 out and leave no current or power. Its individual power graph (c) is an exact duplicate of (b). So in this case at least it is glaringly untrue to arrive at the total power by adding the separate powers. This method having been discredited once, how can it be trusted at all? Well, if what I said about Fig. 4 led anybody to believe that adding the separate power graphs was in any way a proof of the power-adding principle, then I apologize for one more little leg-pull. (I did say "presumably," and presumptions are often wrong, as this one is!) This is an example of the logical fallacy called (for no obvious reason) begging the question. The fault lies in assuming the truth of what one is ostensibly setting out to prove. It is quite true that (with certain qualifications) the power of any combination of currents is equal to the sum of their powers when flowing separately. But in general it is not true that if you draw the graphs of power against waveform for the individual currents and then add them together the result will be the power graph of them all flowing at once. We have seen one case (Fig. 7) where it is quite clearly untrue. And even when the frequencies are different it is quite possible for the two separate currents occasionally to have equal and opposite amplitudes, and at such moments the total power is less than that of either current separately.

What this amounts to is that our power-addition principle does not apply to *instantaneous* power, such as is shown by a waveform graph. It applies only to the power averaged over a suitable period. And now we are really getting to the heart of the matter.

Period for Averaging

When reckoning the power of a single current there is no doubt about the suitable period; it is one whole cycle. It could be averaged over any number of whole cycles, but one is the minimum. Often (as in Fig. 7) it could be averaged over half a cycle with correct results, but that cannot be safely relied upon for all waveforms. In the two-current combinations of Figs. 2 and 3, one whole cycle of the lower frequency is enough, because it includes a whole number of cycles of the other. After that the whole sequence repeats, so the average power for each successive period would be the same. But if the frequencies of I and i were in the ratio of 3 to 5 it would be necessary to sit through three cycles of the lower frequency to see the whole programme, and that would be the minimum averaging period.

In case the necessity for averaging over a whole "programme" is not quite clear, suppose two equal currents have almost exactly the same frequency. If they start off precisely in antiphase, the power of the combination will begin by being zero. Quite a large number of cycles will have to elapse before this state of affairs alters appreciably; and when it does the power will rise very slowly. After very many cycles the currents will arrive in phase, making the total current twice that of each separately, and the power *four* times. And then it will wane slowly to zero. That happens when one current has gained one whole cycle on the other. In such a case it is easy to see that the power would have to be averaged over the entire slow beat to get a fair figure. That figure—yes, you have guessed it!—is twice the power of each current separately. The minimum period for averaging is that which includes an exact whole number of cycles of both—or all—component currents.

The case in which both currents are of exactly the same frequency still seems to stick out as an exception to this rule. A single cycle contains a whole number of cycles (one) of each current, but we have already seen that the power-addition principle fails to apply over this period. If you have what is supposed to be the typically British mind, unperturbed by arbitrary and illogical rulings so long as they work, you will just accept this as one of those things. But if you insist on tidy regularity you will talk this exception into the rule by arguing that the logical conclusion to considering pairs of currents of progressively more nearly equal frequency, requiring progressively longer periods for averaging the power, is to say that an equal-frequency pair of currents requires an infinitely long period of time. After all, unless one extends the time to infinity, how can one be certain that their frequency really is identical and that there is not an enormously slow beat, which in the (very) long run would make the power-addition rule apply?

But perhaps we had better descend from this rarified theoretical atmosphere to some ground-level practice. What happens when one measures an audio output power with the usual "output meter," consisting of a metal rectifier voltmeter across a known resistance? It is scaled to read watts by making use of the fact that the wattage is equal to voltage-squared divided by the resistance. But there is a catch—the meter responds to the *average* value of the rectified a.c. And we can see that the average value of the combined current in Fig. 3(a), for instance, is less than that of the single low-frequency current, which in turn is less than that of the (b) combination, though that has the same power as the (a) combination. So this type of meter is apt to be misleading, at least with the odder waveforms. It is wildly inaccurate with narrow pulses, which have considerable r.m.s value but little straight average. So for this kind of thing one ought to have an indicator that responds to r.m.s. values, such as a moving-iron or thermojunction meter, or a valve voltmeter of the rather inconvenient type that works over a selected slice of bottom bend. Noise has a peaky kind of waveform, so signal/noise measurements in particular are the better for being performed with an r.m.s (square-law) meter.

But how about the programme-repetition rule in this connection? The characteristic feature of noise is that it is *not* regularly periodic. And there is no strict regularity about the waveform of, say, a broadcast performance. True enough, and the theory becomes too complicated to embark on at this stage; sufficient to say that the power fluctuates, and so will the meter reading, but the chance of the total power differing appreciably from the sum of the separate powers (unless some of their frequencies are equal) is small.

All this may seem to have been a lot of to-do about one small by-way of theory. But unless one goes into the matter closely it does seem rather incredible that when a lot of signal currents of different frequencies are flowing together, with so much mutual cancelling out, their individual powers nevertheless add up by simple arithmetic to give the total. And even if one knew that already, this discussion goes to show, does it not, that even small and apparently straightforward by-ways have some curious twists?

COSSOR ELECTRONIC INSTRUMENTS

DOUBLE BEAM Model OSCILLOGRAPH 1049

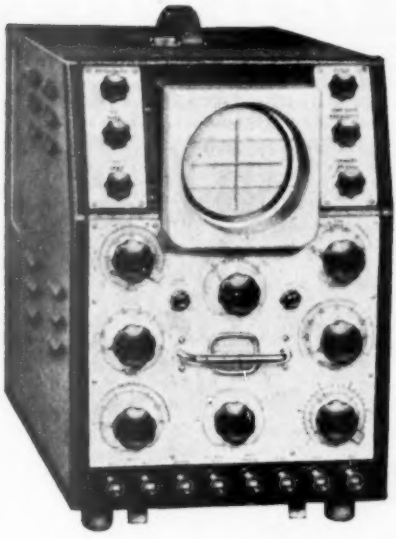

This instrument is designed to meet the requirements of Industrial Concerns and Research Laboratories who require to measure phenomena of zero or very low frequency and to make photographic records of transients requiring a high photographic writing speed.

The Oscillograph incorporates the Cossor 4" flat-screen Double-Beam tube (type 89) operating at 2 K.V. but provision is made for operation at 4 K.V. when maximum spot brightness is required.

The amplifier circuits are direct-coupled throughout and provide independent amplifying channels for the Y1 and Y2 Beams with a gain of 900 and 25 respectively from zero frequency to 100 Kcs. Input signal voltages and frequency may be measured on either channel using the calibrated dials and special anti-parallax graticule. The direct-coupled time base is arranged to provide a repetitive and triggered scan with a time range of 1.5 seconds to 150 microseconds and can be synchronised from a pulse derived either from the internal work circuits or from an external source. A continuously variable control adjusts the amplitude of the sync. or trigger signal and selects the polarity of the pulse from which synchronisation is desired. A Z modulation system is incorporated for time-marking purposes. Stabilization against mains variations up to 10% is provided for amplifiers and cathode ray tube supplies. Long-period stability is reached within 5-10 minutes of switching on.

D.C. PRE-AMPLIFIER Model 1430

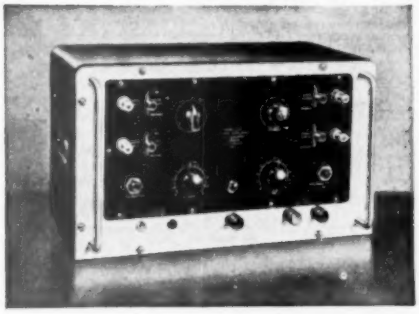

This instrument is a directly coupled pre-amplifier of high stability which has been designed for use with a further amplifier or with a recording device. Used in conjunction with a Cossor Model 1049 Double-Beam Oscillograph it will give a maximum overall gain of 45,000 and a maximum sensitivity of approximately 0.75 mV/cm. The frequency range is from D.C. to 30 Kc/s.

The input and output switching has been designed so that the instrument may be used to amplify either balanced or unbalanced input signals, and will provide a balanced or unbalanced output as required from either kind of input signal. The arrangement also makes it possible to check the amplifier balance and the setting up of the recording device without disconnecting the signal input or output leads.

COSSOR ELECTRONIC INSTRUMENTS

Please address enquiries to:—

A. C. COSSOR LTD., INSTRUMENT DIVISION (DEPT. 1), HIGHBURY GROVE, LONDON, N.5

Telephone: CANonbury 1234 (30 lines) CI.35

WESTON *Test Sets*

High sensitivity wide range coverage, robust construction and simplicity in operation have established "Weston" as the pre-eminent instruments for the testing and servicing of radio and television equipment and also for laboratory and research work. Full details will gladly be supplied on request.

ABOVE *Weston Model S.75. 53 ranges for measuring A.C. and D.C. current and voltage, resistance and insulation.*

RIGHT *Weston Model E.772 Analyser. Sensitivity as on Model S.75—namely 20,000 ohms per volt on all D.C. ranges and 1,000 ohms per volt on A.C.*

SANGAMO WESTON LIMITED

ENFIELD, MIDDLESEX

Tel: Enfield 3434 (6 lines) & 1242 (4 lines) Grams: Sanwest, Enfield

Branches: Glasgow, Manchester, Newcastle-on-Tyne, Leeds, Liverpool, Wolverhampton, Nottingham, Bristol, Southampton, Brighton.

Audix B.B. Ltd.

Suppliers of Specialized Equipment for

SCHOOLS (B.B.C. Approved)
HOSPITALS
HOTELS, ETC.

Write for details

Amplifiers, Radio-amplifier Units
Loudspeakers Pillowphones
Control Units, etc.

Contractors to:-

Local Government and Educational Authorities, Hospital Boards, Government Depts., etc.

Main Scottish Agent

CAITHNESS BROS., KIRKCALDY

Tel. DYSART 3457

Head Office and Works

HOCKERILL WORKS, BISHOP'S STORTFORD, HERTS.

Tel. Bishop's Stortford 1394.

SUCCESS?

START HERE

In Radio, Television, and Electronics there are many more top jobs than engineers qualified to fill them. Because we are part of the great E.M.I. Group we have first-hand knowledge of the needs of employers, thus our Home Study courses are authoritative and based upon modern industrial needs. Alternatively, our courses will prove equally valuable to you in furthering your hobby.

POST THIS COUPON NOW

E.M.I. INSTITUTES, Postal Division, Dept. 16,
43, GROVE PARK ROAD, CHISWICK, LONDON, W.4.

Please send, without obligation, your FREE BROCHURE. I have marked the subjects which interest me.

☐ Mechanical Eng. ☐ Electrical Eng. ☐ Draughtsmanship.
☐ Radio. ☐ Television. ☐ Production Eng. ☐ Automobile Eng. ☐ Aeronautical Eng. ☐ General Cert. of Education (Matric). ☐ Civil Service.

Also Courses for A.M.I.Mech.E., A.M.I.C.E., A.M.Brit.I.R.E., A.F.R.Ae.S., CITY and GUILDS EXAMS. in Mech. Eng., Elecs. Eng., Telecommunications, etc.

Other Subjects .....

NAME .....

ADDRESS .....

E.M.I. INSTITUTES The College backed by an Industry

I.C.4.

Ionosphere Review: 1951

Greatly Reduced Rate of Decrease in Sunspot Activity and M.U.Fs

By T. W. BENNINGTON*

DURING the latter part of 1950 sunspot activity had undergone a large and rapid decrease, and there had been a corresponding large decrease in the maximum usable frequencies for short-wave transmission. These variations were dealt with in *Wireless World* for March 1951, where it was mentioned that it would not be surprising if, during 1951, sunspot activity were to remain relatively constant, or even to rise somewhat. If the current sunspot cycle was to run anything like a normal course this seemed a likely thing to happen.

In Fig. 1 the full line curve gives the monthly mean value of the sunspot relative number for each month since the last sunspot maximum, whilst the two dashed line curves give the monthly mean of the F_2 layer critical frequencies for noon and midnight respectively, as measured at the Slough station of the D.S.I.R. In April 1951 there was a considerable increase in sunspot activity, which was maintained for several months, and, in fact, for the greater part of 1951 the activity was higher than it had been during the last few months of 1950. The effect of this upon the ionosphere is shown by the behaviour of the noon critical frequency. This decreased towards its summer minimum much more slowly than is usual, this being due, no doubt, to the temporary increase in the solar activity which started in April. In fact, the lowest monthly value recorded for the year

* Engineering Division B.B.C.

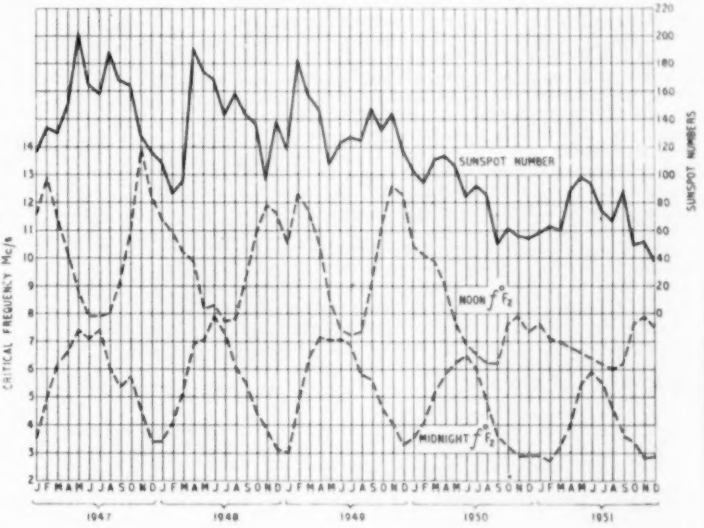
SUNSPOT NUMBER
NOON $f^{\circ}F_2$
MIDNIGHT $f^{\circ}F_2$
CRITICAL FREQUENCY Mc/s
SUNSPOT NUMBERS
J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D
1947
1948
1949
1950
1951

Right: *Fig. 1. Monthly mean sunspot numbers and noon and midnight F_2 critical frequencies since the last sunspot maximum.*

Below: *Fig. 2. Twelve month running averages of sunspot numbers and noon and midnight F_2 layer critical frequencies since the last sunspot minimum.*

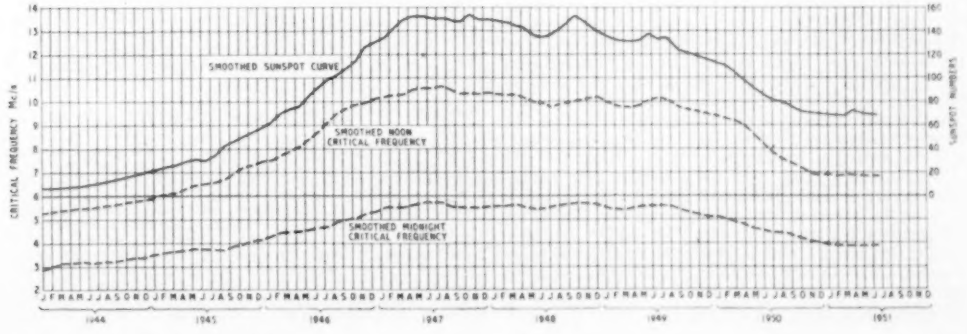
SMOOTHED SUNSPOT CURVE
SMOOTHED NOON CRITICAL FREQUENCY
SMOOTHED MIDNIGHT CRITICAL FREQUENCY
CRITICAL FREQUENCY Mc/s
SUNSPOT NUMBERS
J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D J F M A M J J A S O N D
1944
1945
1946
1947
1948
1949
1950
1951

(for August) was very little lower than the lowest monthly value for 1950, whilst the winter values for 1951 were no lower than those for 1950.

The arrestment of the fall in both sunspot activity and critical frequencies during 1951 is well brought out in Fig. 2, which gives the 12-month running means of sunspot numbers and Slough critical frequencies since the last sunspot minimum. By taking such means the short term variations in these quantities are smoothed out, and the long-period variations are more clearly seen. The curves, it is thought, speak for themselves, and, as to the variations during the past ten months, they have been very small, and such as to maintain in the ionosphere, and for short-wave propagation, a condition of little change. Propagation conditions at the end of 1951 were thus not very different from what they were at the end of 1950; m.u.fs. being very slightly lower, both by day and night.

It is, of course, impossible to be in any way certain about the variations in solar activity likely to occur during 1952, but it is likely that it will begin to decrease again, but to do so at a slow rate, so that by the end of the year the running-average sunspot number may have fallen to about 48. This would imply that, during 1952 the frequencies of use for long distance communication will also decrease slowly, so that, by the end of the year, the m.u.fs. for these latitudes will be about 4 Mc/s lower by day, and about 1 Mc/s lower by night than what they are at present. Frequencies of use for short-wave communication will therefore be somewhat lower on all circuits than those which have been usable this year. This will mean somewhat less use of the higher daytime broadcasting frequencies—like 21 Mc/s for southerly and 17 Mc/s for westerly circuits—and more use of those bands of somewhat lower frequency. At night 11 and 9 Mc/s bands will probably remain usuable during the summer, but next winter the situation is likely to be even more difficult than at present, with 6 Mc/s the only usable frequency over some circuits. At that time a lower frequency than any now available for short-wave broadcasting to North America would seem to be desirable in order to maintain good service at night.

INTERNATIONAL EXCHANGE OF STUDENTS

NUMERICALLY and geographically the work of the International Association for the Exchange of Students for Technical Experience (I.A.E.S.T.E.) has extended during the past year. In the annual report of the association it is recorded that the number of students sent abroad during last summer for experience in industry increased by 761, bringing the total to 2,433. The normal period for which students are employed is eight weeks, although in some instances it is longer.

The students came from 16 countries. So far as this country is concerned, we sent 422 students overseas for technical experience and received 457 from other countries, compared with 353 and 368, respectively, the previous year. More U.K. students went to Sweden (106) than to any other individual country, the next highest being received by France (68). The arrangement is, of course, reciprocal and the intake of overseas students into this country was proportional—from Sweden, 85; France, 79 and Holland, 63.

It is not known how many of the students went into the radio and electronic industries in the various countries but it can be assumed from the few radio concerns listed among the organizations participating in the scheme that the number was comparatively small.

Details of the scheme, which was started in 1948, are available from J. Newby, I.A.E.S.T.E., Imperial College, London. S.W.7.

Short-wave Conditions

Predictions for March

THE full-line curves given here indicate the highest frequencies likely to be usable at any time of the day or night for reliable communications over four long-distance paths from this country during March.

Broken-line curves give the highest frequencies that will sustain a partial service throughout the same period.

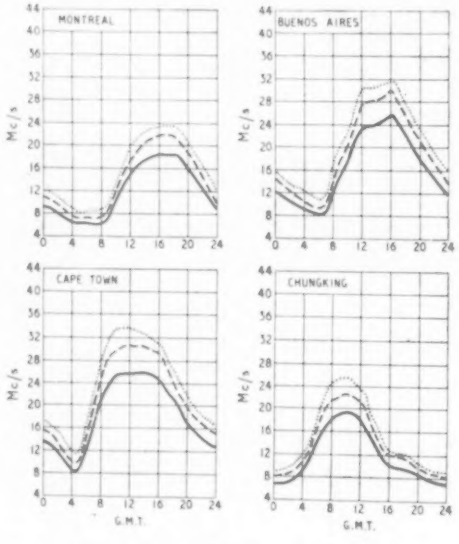
MONTREAL
BUENOS AIRES
CAPE TOWN
CHUNGKING
Mc/s
G.M.T.
FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE ON ALL UNDISTURBED DAYS
PREDICTED AVERAGE MAXIMUM USABLE FREQUENCY
FREQUENCY BELOW WHICH COMMUNICATION SHOULD BE POSSIBLE FOR 25% OF THE TOTAL TIME

MASS AND ENERGY

ORDINARY chemical explosions are just the same as atomic explosions, so far as the principle of the mass-to-energy exchange is concerned, and "Cathode Ray" asks us to convey his apologies for having, in "Energy" (January issue), misled readers into thinking there was a difference between the two because of the greater loss of mass in atomic explosions. Although the loss of mass in a chemical explosion is too small actually to measure, theory indicates that a very small loss should take place. In fact, the mass/energy rate of exchange he quoted, $E=c^2m$, holds for *all* energy changes. So the distinction he drew between the two kinds of explosion is really only one of degree, not principle.

Manufacturers' Products

NEW EQUIPMENT AND ACCESSORIES FOR RADIO AND ELECTRONICS

Television Tuner

ALL five B.B.C. television frequencies can be received on a television set with the aid of the permeability-tuned television tuner recently introduced by The Plessey

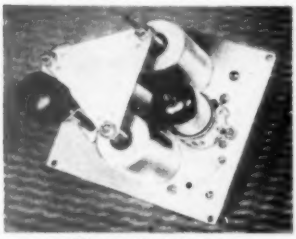

Plessey television tuner

Company of Ilford. It comprises a tuned r.f. stage, covering the frequency band 40-70 Mc/s, and a mechanically-ganged system of three coils—r.f. grid, r.f. anode and oscillator. The oscillator valve is not mounted on the unit. A calibrated scale is provided to facilitate tuning, while good tracking is achieved by the use of padding coils. When the oscillator is working below signal frequency the auxiliary padding coils are connected in parallel with the r.f. circuits and when it is above signal frequency the oscillator coil itself is shunted. The r.f. grid-circuit padding coil is mounted outside the ganged r.f. coil and serves also as an aerial coupling coil. Electrical stability is achieved by the use of temperature-compensated tuning capacitors in the oscillator circuit, and attention has been given to the tuning coils to make them mechanically stable.

Corona Stabilizer

NEARLY twenty years ago it was found that voltages could be stabilized by a corona discharge between coaxial cylinders in gas, but only recently has the principle been utilized commercially. A British tube is now being produced by Nucleonic & Radiological Developments, Ltd., of 77, King's Road, London, S.W.3. This is used in the same way as a neon stabilizer, with a series resistor, but works at a much higher voltage and is distinguished by having a positive a.c. resistance. Because the current consumption is only of the order of micro amps the stabilizer is particularly suitable for high-voltage low-current e.h.t. supplies. For a 500-V tube the striking voltage is 550 V, the current range for regulation is 1 μA to 100 μA (the extinction current being below 1 μA) and the a.c. resistance is about 75 kΩ. If the load is very small, a 10-MΩ resistor in series will give a regulation of 1 per cent. Types are available for voltages between 500 V and 1.3 kV in steps of 100V.

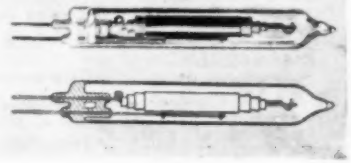

N.R.D. corona stabilizer.

Coaxial Relay

ALTHOUGH the coaxial relay recently introduced by Londex appears to be quite a simple device, it performs the difficult task of switching a coaxial line without interfering appreciably with the transmission characteristics. It is a changeover device and is suitable for such purposes as switching a common aerial between a transmitter and a receiver. The energizing coil, which consumes 1 watt and can be supplied for 6 V, 12 V or 24 V, switches the "inner"

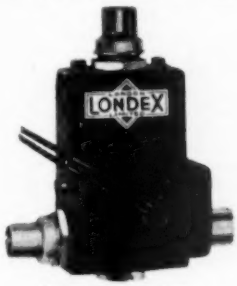

Londex coaxial relay

of the top connector (see picture) to the "inner" of either of the bottom two, the three "outers" being common. Care has been taken with the internal mechanical configuration to maintain the coaxial characteristics throughout and the result can be judged from the fact that when the relay is inserted in a line, the standing wave ratio measured at 200 Mc/s is only 1.08. Models are available for either 45-ohm or 70-ohm cable and are supplied by the makers from their works at 207, Anerley Road, London, S.E.20.

TRIX

Quality

SOUND EQUIPMENT

HIGH FIDELITY MICROPHONE

Model G7808, moving coil type. New design, neat and unobtrusive, with die-cast alloy grille. Fitted with switch and plug and socket connection.

ENCLOSED RACK EQUIPMENT

For medium powered installations, incorporating 20 or 30 watt amplifier unit, radio receiver with monitor speaker, and gramophone unit if required. Provision for microphone input and multiple speaker matching.

Send for latest catalogue and price list of the Trix range of Sound Equipment.

THE TRIX ELECTRICAL CO. LTD.
1-5 Maple Place Tottenham Court Road, London, W.1. 'Phone: MUSeum 5817
'Grams & Cables: "Trixadio, Wesdo, London"

AMPLIFIERS MICROPHONES LOUDSPEAKERS

RANDOM RADIATIONS

By "DIALLIST"

Radio Eavesdropping

How PUZZLING those intermittent cases of interaction between the G.P.O. telephone and one's wireless receiver can be! This one, for instance. Some weeks ago, while we were listening to the 9 o'clock news, my wife was called to the telephone (which is in another room and a good thirty feet from the wireless set). To my surprise, the loud-speaker delivered both sides of the conversation as a clearly audible *obbligato* to what the announcer was saying; but try as I will, I cannot arrange a repeat performance. I had a shot, for instance, just before sitting down to write this, and not a sound of the 'phone conversation was to be heard. When I say that I have done my best to obtain a repeat performance, I mean, of course, with the same telephone connections: either we called the neighbour in question, or we arranged for her to call us. In the course of the fourteen years in which we have been in our present house there have been three other instances of this radio eavesdropping. The calls in progress were all to different numbers; one, in fact, was a trunk call.

Over to You

If this sort of cross-talk occurred regularly, there would be nothing particularly strange about it. One would suspect induction or re-radiation effects between telephone and aerial wires, the cause of which should not be hard to track down. But four cases in fourteen years! During that time there has been no alteration in the positions of the wireless set used for broadcast reception, its aerial, the telephone and the telephone wires. Inward and outward calls have taken place almost daily while the set was working on the Home Programme wavelength. The aerial used with the broadcast receiver is an indoor one, consisting of 25 feet of flex stapled to the picture rail. It is true that the telephone wires do run parallel with it for some distance, where they are brought along the outside wall of the house; but they are some 20 feet from it *and* they run through earthed lead sheathing. I have no doubt that readers have equally mystifying experiences of occasional receiver-telephone interaction. Perhaps some of the brainy ones can suggest an explanation. I can't.

Not So Hot

MAY I BE ALLOWED, just for once, to turn to the programme side of broadcasting? I don't see why I shouldn't, since the livelihood of so many of us depends, directly or indirectly, on the programmes being good enough to maintain the interest of those who are already listeners and to attract new ones into the fold. Here's an example of how *not* to do either. On the last Saturday in January running commentaries were broadcast on the rugger matches, France *v* Ireland in Paris and South Africa *v* the Barbarians at Cardiff, commentators at each match being switched in turn by turn. The score was 11 points to 5 against the French towards the end of the second half; but they were pressing hard and there was a chance that they might snatch a last moment win. With two minutes of play to go and a Frenchman's foot poised to take a penalty kick right in front of the posts, Paris was faded out! We were taken back to Cardiff, where eight minutes of play remained. Four minutes before the end the commentator announced that he was returning General Overseas listeners to the studio. That sort of thing should not happen. You can never tell to a minute when a match will end; the necessary flexibility in programme timing could surely be achieved by billing a short gramophone record period to follow any important commentary.

Sing: or Pl:?

THOSE WHO WRITE scientific books and articles seem to have different opinions about the status of the word "data." Some use it as a singular noun, writing "the data is insufficient." Others (of whom I am emphatically one) maintain that this is just as much a linguistic crime as "Cows is queer beasts." Everyone admits that the word is a Latin neuter plural, meaning "given things"; but those who write "data is" claim that it has been absorbed into English as a singular collective word. In support of their contention they often quote "agenda" as a parallel case. Actually, there is no similarity at all, for agenda is just a shortened form of "agenda paper." Data, on the other hand, is the plural of datum; and we do regularly use terms such as "datum line" and "datum level." I await epistolary half-bricks with no misgivings!

Germanium

UNTIL FAIRLY RECENTLY germanium was to most of us nothing more than an element appearing in the Periodic Table under atomic

ASSOCIATED ILIFFE TECHNICAL BOOKS

"WIRELESS WORLD" PUBLICATIONS

	Net Price	By post
MICROPHONES. By the Staff of the Engineering Training Dept. B.B.C.	15/-	15/5
FOUNDATIONS OF WIRELESS. M. G. Scroggie, B.Sc., M.I.E.E. Fifth Edition	12/6	13/-
RADIO VALVE DATA: Characteristics of 2,000 Valves and C.R. Tubes. 2nd Edition	3/6	3/9
TELEVISION RECEIVING EQUIPMENT. W. T. Cocking M.I.E.E. 3rd Edition	18/-	18/8
SHORT-WAVE RADIO AND THE IONOSPHERE. T. W. Bennington. 2nd Edition	10/6	10/10
WIRELESS SERVICING MANUAL. W. T. Cocking, M.I.E.E. 8th Edition	12/6	12/11
RADIO LABORATORY HANDBOOK. M. G. Scroggie, B.Sc., M.I.E.E. 5th Edition	15/-	15/5
WILLIAMSON AMPLIFIER. Articles on Design of a High-quality Amplifier	3/6	3/9
GUIDE TO BROADCASTING STATIONS. Compiled by "Wireless World." 6th Edition	2	2/2

A complete list of books is available on application.

Obtainable from all leading booksellers or from

ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1.

number 32 and with an atomic weight of 72.60. It's a pretty important metal now, for it may have far reaching effects on the future of radio. I wonder if you know the story of its discovery? In 1869 the great Russian chemist, Mendeléev, announced his periodic law and produced the first table of the elements. Though founded on atomic weights (for the significance of atomic numbers was not to be discovered by H. G. J. Moseley until nearly half a century later), it came much nearer to the truth than anything that had preceded it. It contained many gaps, representing elements then unknown. Mendeléev was so sure that three of these elements would soon be found that he named them provisionally eka-boron, eka-aluminium and eka-silicon. The last-named, he foretold, would turn out to be a dull-grey metal, not readily attacked by acids, with a density of 5.5 and an atomic weight of 72. All three were found within the next six years and were given names commemorating the mother countries of their discoverers.

The first two "eka" elements found were scandium and gallium. The last was germanium, found by the German chemist, Winkler, and having properties very close to those predicted for eka-silicon.

Solder-proof Tags

I EXPECT you have come across at some time or other the tag on to which even 60/40 cored solder cannot be made to flow unless you use an iron far too hot for a proper job, and keep it applied much longer than is good for the health of many components. The solder behaves just like a drop of water on a greasy surface, remaining as a little bead and refusing to spread evenly and thinly. That's what happens with the tag that is obviously allergic to solder; but there are other kinds, perhaps even more undesirable owing to the deceptive behaviour of solder when applied to them. At first it refuses to flow on, but your perseverance is eventually rewarded (?) by what looks like a proper "wetting" of the tag. You fix on a wire and the joint looks good enough. But is it? Give the wire a good pull and see. It comes away, bringing most of the solder with it—a dry joint. In their own interests all component makers should be careful to see that all tags used can be easily and quickly soldered, even by the not very skilled. Quickness is essential, for the longer a joint is in the making, the hotter does the component to which the tag is attached become.

BULGIN FUSE-LINKS & HOLDERS

BULGIN glass-enclosed Cartridge Fuses are instantly replaceable and instant in their safety action. Sensitive to overload and rapid in rupture, Bulgin Cartridge fuses clear overloaded circuits before dangerous results can take place preventing fire risk. Different models and different current-ratings cover all requirements, and replacements are inexpensive. Manufactured and tested to the highest exacting standard, ensuring the closest consistency of performance —and even greater safeguard.

MANY types of Bulgin fuse-holders are manufactured to accommodate the vast range of Bulgin Cartridge fuses. Types include : Single, double and treble-pole base mounting made in highest grade S.R.B.P. with all metal parts highly silver-plated. Also moulded, enclosed, base-mounting, flex lead, and panel-mounting types. Moulded types are manufactured in finest quality thermo or thermo-setting plastics materials, all contacts and clips are of course non-ferrous spring material, silver-plated.

SEND FOR CATALOGUE No. 190 WW. PRICE 1/- POST FREE

MANUFACTURERS OF RADIO AND ELECTRONIC COMPONENTS

BULGIN Components
A.F. BULGIN & CO. LTD
BYE-PASS ROAD BARKING
TELEPHONE Rippleway 3474 (5 lines)

UNBIASED

By FREE GRID

Thirty Years of It

IT is by no means too early to start thinking about what improvements we should like to see at the Earls Court Show in the autumn. Now I hate to strike a jarring note in the Hallelujah chorus which was heard on all sides after last year's show, but one thing I missed was the intimate and homely atmosphere of Olympia. This is not, however, a plea for returning there but for removing the air of sepulchral gloom from Earls Court by filling up certain vast spaces which were left almost bare last year.

In particular, I would instance that section of the hall that, in the Motor Show, is filled with yachts and launches. At the Radio Show this large space contained but a few scattered stands and reminded me of one translator's version of Dante's graphic description of "the awful place of doom, where dead men lie as in a tomb."

Surely this space can be filled, this year at any rate, by a replica of the first All-British Wireless Exhibition held just thirty years ago at the Horticultural Hall, London. I feel certain that the big radio and electrical manufacturers who exhibited at the 1922 show would be willing to co-operate by reproducing, as far as possible, the stands—and above all the exhibits—just as they were three decades ago. But we don't want just a dead museum.

It is, of course, the B.B.C.'s thirtieth birthday too and so let the Corporation play its part by feeding a programme complete with 1922 distortion to the stands, and the vintage sets and loudspeakers on show will add their own quota of cacophony. Also, could we not have a reproduction of the Marconi House studio complete with, as far as possible, the original announcers and artistes of that year, not forgetting Captain Eckersley—"Please don't do it."

Another suggestion is for a special Psychic Section where Radiæsthesia and suchlike things would be exhibited and demonstrated. I would undertake to run a stand there myself and demonstrate not only Radiæsthesia itself — or Rhabdomancy, as it used to be called—but also Psycheuresis.

Shades of 1922

Give Us Jacks

APART from their function of providing an extra horror to the so-called delights of picnics, the small mains-battery attaché-case receivers are very useful as second sets for plugging in at home; or at least they would be if they had the small addition of a jack so connected that the loudspeaker is cut out when phones are plugged in. I also find my portable useful in my car to while away the interminable hours spent in the back streets near Oxford Circus while Mrs. Free Grid is choosing a new hat. One does not, of course, need an additional licence when using a portable in a car, so long as the set is not *installed*.

Reverting to the question of phones, it may be objected that nobody uses them nowadays, but I would retort that if they don't do so then a second set in the average household is simply a wanton extravagance. In these days of housing shortage there is no chance of retiring to a separate room if we want to listen to a different programme; the only solution to the problem is a jack on every portable and a *comfortable* pair of headphones — and this means the hearing-aid type. So far as I am aware, no manufacturer turns out a set fitted with a headphone jack; if I am misinformed, please correct me.

I think, too, that in certain households a jack would be a useful feature on the domestic set, but in this case the connections should be such that the loudspeaker is *not* cut out when the phones are plugged in. I refer, of course, to households like my own where some of us who are on the churchyard side of forty are beginning to suffer, not only from presbyopia, which makes us need glasses for reading, but also from what I will call presbyotia, which makes us need something a little more intimate than the loudspeaker; in other words, we are a little hard of hearing, more especially where certain frequencies are concerned, and would welcome a pair of headphones with a variable tone-correcting unit to flatten out the hills and dales of our particular auditory response curve.

Interminable hours

Oriental Statistics

"SAUL hath slain his thousands and David his tens of thousands." Most readers of *W.W.* will, I feel sure, be familiar with this quotation and won't think it comes from Shakespeare. I should, however, have hardly thought that Government officials, who only appear to read their own Blue Books, would have been acquainted with the ancient Eastern custom whereby the higher a person stands in the hierarchy or in popular estimation the greater the number of things he is allowed to dabble in, be it wives, scalps or merely statistics.

That this is so, however, is clear from recent newspaper reports. In the morning papers a person described as "an official of the Post Office" said that the number of television licence dodgers was to be reckoned in thousands. In the evening papers a "*high* official of the Post Office" had played David to the lowlier Saul by raising the estimate to "tens of thousands." But now a very much higher official has quite properly donned the mantle of a much greater than David — presumably Solomon—and we are told that the defaulters are to be numbered in hundreds of thousands—200,000 to be exact.

Is your amplifier good enough for use

by the B.B.C. and many Commonwealth and foreign broadcasting Corporations in Monitor systems and as a driver amplifier in the speech modulator chain of broadcast transmitters ?

by famous record manufacturers for disc recording ?

Professional audio engineers have chosen the TL/12 amplifier for the above applications to help bring to you the music on which you rely for your pleasure.

This is a unique distinction for an amplifier available to the general public.

Used with the RC/PA/U pre-amplifier and the best available complementary equipment the TL/12 power amplifier gives to the music-lover a quality of reproduction unsurpassed by any equipment at any price.

These amplifiers are built to a tropical specification and they are distributed throughout the world. During 1951 to date orders totalling over 2,000 have been received from the U.S.A. for RC/PA/U and TL/12 amplifiers for high quality radio gramophone reproducers for the home.

This illustration shows the RC/PA/U pre-amplifier mounted in a console cabinet designed for armchair operation. The TL/12 amplifier is mounted in the base of the cabinet. The Leak Dynamic pick-up and Leak radio unit are also incorporated. This console was presented to Harold Rawlinson, Esq., conductor of the Insurance Orchestra Society, on the occasion of the Society's Silver Jubilee.

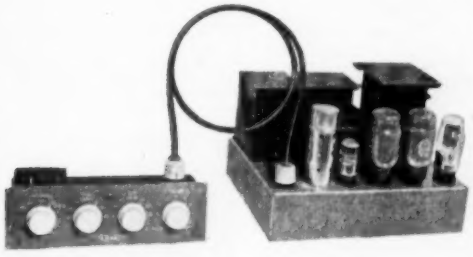

RC/PA/U	"POINT ONE" TL/12
REMOTE CONTROL	TRIPLE LOOP FEEDBACK
PRE-AMPLIFIER	12 WATT AMPLIFIER
PRICE 9 GUINEAS	PRICE 27 GUINEAS

Craftsmanship is apparent on inspection. Performance is certified by the N.P.L.

★ A 28-page illustrated booklet describing these amplifiers and containing much information of interest to music lovers seeking the highest standard of reproduction is available free on request. ★

H. J. LEAK & CO. LTD. (Established 1934)

BRUNEL ROAD, WESTWAY FACTORY ESTATE, ACTON, W.3

Phone: SHEphords Bush 1173 Telegrams: Sinusoidal, Ealux, London Foreign: Sinusoidal, London

ELPREQ PAGES

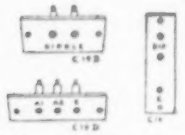

SOCKET STRIPS. Paxolin mounted.

Two socket engraved L.S. **6d.** each. Bin. C16B.

Two socket engraved A.E. **6d.** each. Bin. C18A.

Two socket engraved P.U. **6d.** each. Bin. C19B.

Two socket engraved Dipole **6d.** each. Bin. C19B.

Two socket plain. **5d.** each. Bin. C18B.

Three socket engraved DIP and E. **9d.** each. Bin. C16D.

Three socket engraved A1, A2 and E. **9d.** each. Bin. C19D.

Four socket engraved A.E. Pickup, **9d.** each. Bin. C19E.

Four socket engraved P.U. Ext. L.S. **9d.** each. Bin. C16E.

Five socket plain. **9d.** each. Bin. C16C.

TAGSTRIPS. Paxolin mounted

Two lugs, one earthed, **5d.** each. Bin. C17A.

Three lugs, centres earthed, **4d.** each. Bin. C17B.

Four lugs, one end earthed, **5d.** each. Bin. C17C.

Six lugs, two ends earthed, **6d.** each. Bin. C17E.

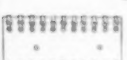

GROUP PANELS. Paxolin mounted.

5 components (10 lugs), **7d.** each. Bin. C18CL.

6 components (12 lugs), **8d.** each. Bin. C18CC.

11 components (22 lugs), 1/- each. Bin. C18CR.

TERMINALS.

Earthing screw terminals, 2BA, also used for connecting two spades (as C20A) together, **9d.** each. Bin. C20C.

Screw down terminal 4 B.A. with plain insulated head. **5d.** each. Bin. C80F.

Screw down terminal all metal, 6 B.A., **4d.** each. Bin. C21C.

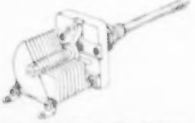

AIR SPACED TRIMMERS

We have a good assortment of air spaced trimmers. The one illustrated is a 30 p.f. with long (2¼in.) spindle. Price **2/3.** Another interesting one is a 2-gang 75 p.f. with short spindle. Price **4/9.**

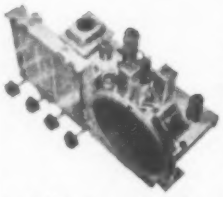

THE ELPREQ SUPERIOR FIVE

This is a long, medium and short wave superhetrodyne receiver for A.C. mains working, built by one of our famous manufacturers, fully aligned, tested and guaranteed. Complete as illustrated, less knobs. **COVERAGE :** L.W. 800-2,200 metres; M.W. 230-500 metres; S.W. 16-50 metres. **CHASSIS :** Heavy gauge cadmium plated steel, size 15¼in. × 8in. × 2¼in. **DIAL :** 7¼in. square, edge lit, glass, printed in three colours. **SPEAKER :** 8in. P.M. built on to chassis but easily removable. **TUNING :** two-speed tuning with nylon drive. **VALVES :** all by B.V.A. makers, ref. Nos. 6K8, 6V7, 6R7, 6V6 and 6X5. **EXTENSIONS :** sockets are provided for pick-up and low impedance extension speaker. **TECHNICAL POINTS :** (a) I.F. filter; (b) delayed A.V.C. to 1st and 2nd valves; (c) controls to vary tone and volume; (d) tone correction; (e) high gain amplifier comprising triode section of D.D.T. and pentode gives undistorted output of 4 watts with good frequency response. **GUARANTEE :** 12 months written gusrantee included with each receiver. **CIRCUIT :** diagram is available free with chassis or separately price 1/9. **CABINET :** no ready cabinets are available at present but constructional details of an easy to make type is given free with circuit diagram. **PRICE :** complete ready to work £10/19/6. Non-callers please add 10/6 to cover carriage and insurance. **H.P. TERMS :** £3/13/0 deposit and nine monthly payments of 18/9 each (carriage extra as above).

ELPREQ " WOLSEY " RECEIVER

This is a semi-portable long, medium and short wave superhetrodyne receiver for A.C./D.C. mains by one of our famous manufacturers, fully aligned tested and guaranteed, complete in cabinet.

PRICE £9/5/-

COVERAGE : long wave 800-2,200 metres, medium wave 200-500 metres, short wave 13-50 metres. **CHASSIS :** heavy gauge polished aluminium, size 9½in. × 5¼in. **DIAL :** size 7in. × 1¾in., illuminated, calibrated in metres and with printed station names. **SPEAKER :** 6¼in. permanent magnetic type, finest make. **TUNING :** long scale large drum and slow motion drive give perfect control. **VALVES :** very latest types, all B.V.A. makers. **AERIAL :** Built-in frame aerial with provision for external aerial if greater volume is required. **A.V.C. :** delayed A.V.C. to 1st and 2nd valves gives good quality with minimum of background noise. **CONTROLS :** 3 only—tuning, volume on/off switch, and wave change. **CABINET :** 12in. × 7in. × 7¼in. high, made from selected hardwood satin finish. **CIRCUIT DIAGRAM** is available free with receiver or separately with each receiver. **GUARANTEE :** 12 months written guarantee included with each receiver. **PRICE :** complete in cabinet ready to work, £9/5/0, carriage and insurance 5/-. H.P. terms £3/2/6 deposit and 10 monthly payments of 14/- each, carriage extra as above.

MAKE A CONVECTION HEATER

Using Ex-Admiralty HEATING UNITS fitted with 3-pin brass plug and socket. Copper-clad enclosed elements are used and those again are enclosed in sheet metal half-cylindrical containers. Fit one of these into a metal cabinet, and you have an excellent convection heater. In places where appearance is not important, all you need extra is the wire as the heaters work perfectly well as they are, without extra casing the actual element being totally enclosed.

PRICES

2 K.W. 220/230 v.	12 0
500 W. 220/230 v.	12 0

Carriage 2/- extra per heater.

Sketches and details of suitable cabinet are supplied with each heater. 2 K.W. 110 v. heating units are also available at 7/6 each. These are ideal working in series for greenhouse heating, etc., or for space heating under benches, etc. Eight of these in series will consume 1 K.W. and will spread the heat out over a wide area.

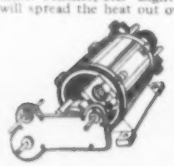

MULTI-SPEED MOTORS

You can adjust this motor to almost any speed you want, it will work directly off A.C. mains, or if you require greater power or greater speed work it through a metal rectifier. This motor is fitted with a gear box enabling speeds down as low as 1 r.p.m. to be obtained. Price **14/6,** postage and packing 1/6 extra.

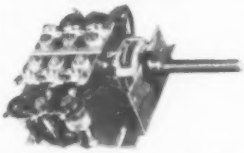

'ELPREQ' 3 WAVE BAND COIL PACK

This is a really first class pack for long medium and short waves with iron dust cored coils, IF 465 kc/s. Size 3in. × 3¼in. × 1¾in. Guaranteed pack complete with circuit diagram. Price **29/6.**

I.F. TRANSFORMERS

465 kc/s iron dust cores fitted in aluminium can size 1¼in. × 1¼in. × 3¼in. Price **12/6** pair.

Midget type, 465 kc/s size 1¼in. × 1¼in. × 1in. (M400B). Price **17/6** pair. 465 kc/s. ex-equipment in good condition fitted in standard size can, dust cored. Price **7/6** pair.

TWO-VOLT ACCUMULATORS

Made for the Forces by one of the most famous firms in the world. 15 amp.-hour size approx. 6in. × 1¾in. square in ebonite case, pre-charged, only need filling with acid, **5/9** each, plus **1/3** post and insurance. Six or more post free.

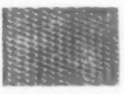

SPEMET.

Made from polished aluminium, an excellent material for fronts of cabinets or for special cabinets you are making, and for air conditioners, etc.

Close mesh 8 holes to the inch. 24in. × 12in., **10/-**, 12in. × 12in., **5/3**, 6in. × 6in., **1/9.**

Wide mesh 4 holes to the inch. 24in. × 12in., **9/-**, 12in. × 12in., **4/9**, 6in. × 6in., **1/6.**

Postage and special packing 1/6 extra for any quantity up to 12 sheets. Over 12 sheets post free.

PLUGS FOR MODERN VALVE HOLDERS

Each is fitted with a rubber shroud.

Type 1, or B7G button base. Type 2, or B9A noval base. Price **1/4** each, discounts for quantities.

A MILLIBAR BAROMETER

If you are interested in meteorology, or if you think a good barometer would help you to explain some tricky radio problem, then you will be interested to know that an article appeared in one of the leading meteorological journals, showing how the Ex-R.A.F. Sensitive Altimeter can become a first-class highly sensitive yet robust aneroid barometer. We offer the sensitive altimeters in good condition with instructions at 17/6 plus 1/- postage.

ROOM HEATER CLOTHES DRIER

Chrome plated clothes drier/room heater dries and airs washing, towels, etc. Ideal for flats, hotels, hairdressers, etc. Works off A.C. or D.C. mains —only 750 watts. (State voltage). Size 3ft. × 3ft. × 5in. Made to sell at £12/12/0. **Our price only £5/19/6** plus 7/6 carriage.

MILNES H.T. UNITS

120 volts 60 m/a., you charge these from a 6 v. car battery. Price 67/6 each—callers only or carriage at your risk.

ELECTRIC BELLS

Ex-equipment small round type, e.g., all the works under the dome for operation from dry batteries Price 3/6 each.
Similar ditto, but for use on A.C. mains or magneto. Price 3/6.

500-W. PORTABLE HEATER

Made by G.E.C. for the Navy, waterproof and almost indestructible, safe in the garage or other inflammable atmospheres. Price 19/6, plus 2/6 post and pkg.

CLIX 15 AMP. FOOT PLUG

Made to B.S.S. specification, shuttered in moulded bakelite case, 8/6 each.

SLIDER RESISTORS.

Heavy duty type size.
Size 7in. × 1¼in., 1.2 ohms 15 amps. Price 15/-.
Size 9in. × 1¼in., 3 ohms 10 amps. Price 15/-.
Size 13¼in. × 1¼in., 11 ohms, 4.5 amps. Price 22/-.

PYREX AERIAL INSULATORS

Ideal for aerial connections through cabin walls or through panels Consists of glass dome with threaded rod and terminal ends, and metal fixing flange. Price 2/- each.

ONLY £12/10/-

RADIO CHASSIS AVAILABLE

RADIOGRAM CABINET

This is a really well made cabinet which will do credit to any home. Size 2ft. 6in. wide, 2ft. 6in. high and 1ft. 3in. deep.
FINISH: fully grained walnut, nicely polished. Latest satin finish.
MOTOR BOARD: is the right position to take any standard record changer. **SPEAKER GRILLE:** gold lacquered metal adequate to take up to a 12in. speaker. **INSIDE LID:** flock sprayed, with felt edging. Perfect fit eliminates pick-up noise.
BACK: Removable, size 25in. × 20in. **PRICE: £12/10/0,** plus carriage or £4/4/- deposit and 10 monthly payments of 19/3. **RADIO:** The space available for the radio chassis is adequate for most types which use a separate speaker. A suitable chassis is "The Elpreq Radiogram Five." We have a limited number complete. Price £10/19/6 or on H.P. Terms specification almost the same as the Elpreq Superior Five given opposite. Guarantees are also the same. **MOTOR:** Single speed with pick-up. Price £5/5/0, carriage and insurance 3/6. Three-speed, motor only, price £4/15/0, carriage etc., 3/6. Suitable crystal pick-up with two plug-in heads, price £4/4/6. With dual purpose head, price £2/13/0. **RECORD CHANGERS:** Standard speed with pick-up. Price £11/15/0. Three-speed with dual purpose pick-up, price £15/10/0. H.P. Terms on Motors and Record Changers—details on request.

THIS MONTH'S SNIP

SPECIAL 3-SPEED 'GRAM. MOTOR

With records that play for almost 30 minutes there is really no need for an automatic changer, therefore we anticipate a heavy demand for this low priced but nevertheless very reliable motor. We are able to sell at this price because we bought a cancelled shipment, obviously only a limited quantity is available so we advise prompt action.
SPEEDS: 33, 45 and 78 r.p.m. covering standard and long playing records at present sold in this country and also the new American types which will soon be available. **TURNTABLE:** 9in. heavy pressed steel with rubber mat (essential for long playing records). **MOTOR:** Extra silent running induction type, suitable for A.C. mains only. **DRIVE:** the modern rim method is employed, this is especially trouble free as no belts or governors are needed and speed is automatically controlled by the mains. **FIXING:** a fixing and drilling template is supplied. Clearances measured from the top of the motor board—depth required is 3in. and height 1¼in. **GUARANTEE.** The motor is guaranteed for a period of 12 months. **PRICE: £3/19/6,** plus 2/6, carriage and packing. H.P. Terms £1/7/0 deposit and 5 monthly payments of 10/-.

CONSTRUCTORS' PARCEL, SPECIAL OFFER

Modern design, bakelite cabinet in ivory, blue or brown, complete with metal chassis punched out for speaker and 5 valves, etc. Parcel also includes moulded perspex window, matched set of knobs, scale and hardboard back. Price 27/6, carr. and pkg. 2/6.

Orders by post are dealt with by our Ruislip depot. To avoid delay address to Electronic Precision Equipment, Ltd., Dept. 2, Windmill Hill, Ruislip, Middlesex.

BOOKS & PUBLICATIONS

"DEMOBBED VALVES." Gives the commercial equivalents of many thousands of service valves, and conversely gives the service equivalent of many thousands of commercial type valves, an invaluable publication recently revised. Price 2/3. **"AN ELECTRONIC TIMER."** Shows how to build a device for controlling timed operations. The timer can be set to any timing up to 3 minutes. Price 2/3. **"THE ELECTRONIC SWITCH."** Shows how to make a device for switching without mechanical contact. Price 2/3. **"THE IMPULSE RELAY."** Explains the working of an ingenious relay, and gives several circuits including radio control. Price 1/9. **"3½-WATT CONVERTIBLE AMPLIFIER."** Shows how to construct a 3-stage amplifier with an output of 3½ watts, a unique feature is that this amplifier fits into our "Occasional" cabinet. Price 1/6. **"THE I.F. A.F. AMPLIFIER."** Gives details of a 465 kc/s. amplifier with A.V.C. detector and power output stage. Designed to fit into our "Occasional" cabinet, it is useful for aligning coil packs and for use as a signal tracer in radio servicing, etc. Price 1/6. **"THE OCCASIONAL T.R.F."** Shows how to build a T.R.F. Receiver for medium and long wave reception, of looks and quality output comparable with sets priced between £10 and £14. This costs less than £6 to build including cabinet. Price 1/6. **"THE 'OCCASIONAL SUPERHET.'"** In areas where field strength is low and interference is high, a superhet receiver is essential. For less than £8 one can be built into our "Occasional" cabinet. This publication gives all details. Price 1/6. **"VALVE EQUIVALENTS."** These are the best equivalents charts available today. Also the booklet can be used for keeping records of valve stocks. Price 2/6. **"I.F. ALIGNMENT PEAKS."** This book gives the I.F. frequencies of more than 4,700 receivers, British, American and Continental. A very popular British set is covered, and hints on finding the frequencies of unknown British sets are also given. Price 4/6. **MAKING COIL PACKS.** Shows how standard type coil packs can be made and aligned at very low cost, 1/6. **VISUAL ALIGNMENT SIGNAL GENERATOR.** Reprint from "Radio Constructor" describes a very useful combined signal generator and oscilloscope. 9d. **T.V. FROM RDF1.** Reprint of the articles which recently appeared in "Practical Television." 1/3, post free.

Orders under £2 add 2/6, under £1 add 1/9. Postable items can be sent C.O.D., additional charge approx. 2/6. List 6d.
Early Closing days: Wednesday, Ruislip; Saturday, City.

ELECTRONIC PRECISION EQUIPMENT

WINDMILL HILL, RUISLIP, MDX. Phone: RUISLIP 5780

152-153 FLEET STREET, E.C.4. Phone: CENTRAL 2833

ELPREQ PAGES

15 WATT AC/DC AMPLIFIER

Made by one of our most famous Amplifier manufacturers. Unused with instructions, slightly soiled. Complete as illustrated. £40.

SPEAKERS

Excellent quality, fully guaranteed.
P.M. Type: 2½in. 14/9, 3in. 14/9, 3½in. 14/9, 5in. 14/9, 6½in. 14/9, 8in. 16/6, 10in. 27/6, 12in 70/-.

ENERGISED TYPE. 6½in. 600 ohm field 13/6. 10in. 1100 ohm field 17/6. Non-callers add 1/- to cover packing and insurance.

MINIATURE 7-PIN PLUG AND SOCKET

With non-breakable plastic rubber shroud. Overall size 1¼in. long, diameter approximately ½in. Price 2/-.

COILS

T.R.F. Long and medium wave, complete with circuit diagram 5/6 pr. Superhet, long wave 900-2000 metres, medium wave 185-550 metres, short wave 16-50 metres with aerial and oscillator coils that is set of six. Coils with circuit diagram, price 10/6.

LIGHT WEIGHT TRIPOD

All wooden, fully adjustable, extends to 4ft. Ideal for photographers. Price 35/- each.

5-VALVE IF/AF AMPLIFIER

(For AC/DC working)

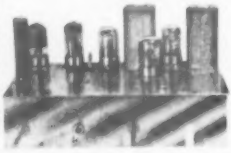

This is on an aluminium chassis, size 11½in. × 7in. × 3in. deep. The layout is neat and simple and provision is made and in fact holes are drilled so that tuning condenser and coil pack may be easily fitted if same are required. Alternatively this vacant space can be used for mounting a control panel to which various points of the circuit can be brought to plugs, this making faults tracing by circuit substitution a very simple job. It uses one of the latest valve line-ups as follows: 14S7 Triode Hexode, 7B7, IF Amplifier, 7C6 D.D.T. 35A5 output, 35Z3 Rectifier. The IFs are present at 465 Kc/s, but are variable over a fairly wide range. Price £6/10/-.

PROFESSIONAL RADIOS YOU CAN MAKE

You will find that the building of our all-mains radio receivers is simplicity itself, and the more you make the less time each takes, everything down to the last nut and bolt is supplied, and everything fits together in a professional manner. When finished the receiver looks and plays as well as those being offered in radio shops at anything between £10 and £14.

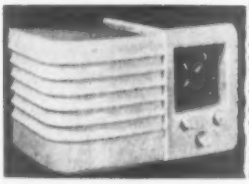

The one illustrated above we call "The Occasional" in a choice of colours. Ivory, Walnut or Green, and the T.R.F. costs £6 to make.

The other radio illustrated we call the "White Lady," this is an extra fine cabinet of pure white. The complete T.R.F. receiver costs about £6/5/- to build. Constructional data for either set is available at 1/6 post free.

BATTERY CHARGERS

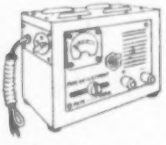

Motorists you should have one of these, it will repay its cost the first night you leave your ignition switched on or otherwise run down your battery. Madison type charging 6 or 12 v. at 1 amp. Price 59/6. Amplion type charging 6 or 12 v. with ammeter and variable charging rate up to 2 amps. Price £6/6/-.

FLUORESCENT LIGHTING CONTROL UNIT

This is a combined condenser and choke unit for controlling 40 watt fluorescent tubes. The only other item needed is a starter switch which can be an automatic type or an ordinary on/off manually operated type.
We offer these well-made units at less than half price, namely 19/6 each.

APPLIANCE LEAD

As fitted to H.M.V. appliances, it is 9ft. long, made of almost indestructible non-kink flex with rubber end support; ends are all prepared and bound. Price 2/9 each, 30/- doz.

CHARGING CUT-OUT

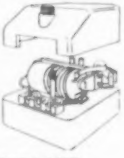

This is in effect a reverse current relay, its purpose is to prevent the battery discharging itself through the generator. 14/6 each.

INDICATOR LAMP

This is fitted with a clear Perspex top, it is therefore highly suitable as an indicator lamp or for illuminating inside a radiogram or similar cabinet or even as a map reading light in a car. Takes standard screw-in flash light bulb. Price 1/6 complete.

PORCELAIN CABLE CLEATS

For temporary or semi-permanent wiring jobs. Double groove as illustrated. 2/- dozen pairs. Treble Groove, 2-screw fixing, 3/- doz. pairs.

ANNOUNCING THE OPENING OF A SPECIAL EX W.D. DEPARTMENT TO HELP OVERSEAS AND HOME CUSTOMERS WHO REQUIRE SPECIAL EX-GOVERNMENT INSTRUMENTS AND GEAR.

We list here some of the equipment which is available (mostly in good used condition). Enquiries regarding these and other ex-Government items should be addressed to (Dept. F.P.) F.P.E. Ltd., Windmill Hill, Ruislip.
Please note at present telephone enquiries cannot be dealt with.

TEST EQUIPMENT

Cable Tester Type 209. Mains operated insulation tester up to 18 cores, breeze plugs etc.
WAVEMETER Type 4. Covering 205-220 mc/s.
WAVEMETER 1191A. Covering 100-800 kc/s. 8-20 mc/s.
WAVEMETER 1617. Covering 460-600 mc/s.
WAVEMETER 1239. Covering 15-53 mc/s.
WAVEMETER W1117. Covering 125 kc/s.-20 mc/s.
WAVEMETER 1615. Covering 20-26 mc/s. 25-34 mc/s.
WAVEMETER 1432. Covering 160-250 mc/s.
SIGNAL GENERATOR. Type 106. Salford instruments 5-50 mc/s. in 4 channels.
SIGNAL GENERATOR. T.F. 390/F3 Marconi Ekco 1.6-2.4 mc/s. 18-32 mc/s. 32-58 mc/s. 58-100 mc/s.
SIGNAL GENERATOR. T.F. 390/G3 Marconi Ekco, 1.6-2.4 mc/s. 8-16 mc/s. 16-32 mc/s. 32-60 mc/s.
OSCILLATOR UNIT. Type 12A Covering 31-40 mc/s.
OSCILLATOR UNIT. Type 55A, 1000-3000 c.p.s. 2.8-10 kc/s. 9.8-30 kc/s.
MONITOR Type 25
MONITOR Type 27 & 28
CRYSTAL MONITOR Type 4A.

TEST SET 44
" " 160-A
" " 210
" " 211
" " 165
" " 76
TEST SET 219
" " 239
" " 240
" " 276 × 2
" " 205
" " 292

MODULATORS

BC 1203-A.
29
208
155
216
64

POWER UNITS

Type 87
" 38
" 35
" 280
" PP.32 A.R.
" 525

RECEIVERS

25
R.111-APR-5A
1626
3085
1466
1124
3540
3601
1622
3515
BC-639.A
1132.A
1139
1120

TRANSMITTER RECEIVERS

1196
5043
3174
1133G
3152

MISCELLANEOUS

DRIVE UNIT Type 114.
RACK. Containing:
Panel Amplifier Type 6.
Power Unit Type 6.
SOUND REPRODUCING APPARATUS. Type 11.
STROBE UNIT Type 61.
AMPLIFIER UNIT A.3562.
RELAY UNIT BC-687-A.
Buzzer Valve Type 2 (morse practice set).
Junction Box JB70A.

MANY OTHER UNITS AVAILABLE—SEND DETAILS OF YOUR REQUIREMENTS

EX-GOVERNMENT VALVES

We carry large stocks of government valves and invite enquiries for all types. Here are brief details of just a few of our varied stock.
V.T. 31 250 w. Transmitting Tetrode 18/6 each.

RECTIFIERS. Note figures given are peak rating.

CV19 63KV, 800 mA. £4/17/-.
CV1504 60KV, 1200 mA. £5/17/-.
CV74 40KV, 600mA. £2/17/6.
CV1111 14KV, 350 mA. 4/3.
CV1120 14KV, 50 mA. 4/3.
CV1508 8KV, 1000 mA. 17/6.
CV54 7KV, 400 mA. 6/6. Note we are told this is a good substitute for the GU21, also we have a few of these with loose bases otherwise new and perfect. 12/6.

MERCURY RECTIFIERS

CV2946 1KV, 1.8 Amps. 6/6.
CV1029 2KV, 2.5 Amps. 9/6.
BD10 1KV, 25 Amps. £6/10/-.

MISCELLANEOUS TYPES

The following are also available and we shall be glad to give further information of price and quantity to customers wanting these types. Others are available in smaller quantities, please state your special needs.

CV 12	CV 665	CV 1102
CV 13	CV 686	CV 1104
CV 18	CV 755	CV 1105
CV 19	CV 849	CV 1106
CV 31	CV 852	CV 1107
CV 32	CV 922	CV 1108
CV 37	CV 1000	CV 1110
CV 51	CV 1018	CV 1111
CV 54	CV 1020	CV 1118
CV 57	CV 1023	CV 1120
CV 63	CV 1025	CV 1124
CV 65	CV 1029	CV 1125
CV 71	CV 1031	CV 1126
CV 72	CV 1033	CV 1127
CV 73	CV 1035	CV 1128
CV 74	CV 1037	CV 1129
CV 82	CV 1047	CV 1133
CV 85	CV 1051	CV 1135
CV 93	CV 1053	CV 1136
CV 115	CV 1054	CV 1137
CV 118	CV 1055	CV 1139
CV 120	CV 1056	CV 1141
CV 129	CV 1057	CV 1152
CV 133	CV 1060	CV 1175
CV 138	CV 1061	CV 1191
CV 147	CV 1061A	CV 1197
CV 148	CV 1062	CV 1199
CV 185	CV 1065	CV 1284
CV 187	CV 1066	CV 1313
CV 193	CV 1074	CV 1366
CV 271	CV 1075	CV 1367
CV 321	CV 1078	CV 1368
CV 585	CV 1090	CV 1504
CV 594	CV 1091	CV 1913
CV 619	CV 1092	CV 2710
CV 640	CV 1094	CV 2941
CV 656	CV 1095	CV 2945
CV 659	CV 1101	CV 3793

INFORMATION WANTED

Can any reader help us with information of Government Surplus Type CV 1368, especially as to its suitability for domestic or industrial applications?

GUESS WHAT FOR £5

The valve illustrated in our January "Guess What" Competition was a 12A6, of course it could have been one of several types but this particular illustration was cut out of Page 109 of "Brimar Radio Valve and Teletube Manual", this page describes the 12A6. Prizes were sent to the readers whose solutions were the first three correct opened.
This month's "Guess What" is a little harder. We invite you to identify the object illustrated. By way of a clue please note we mention it again somewhere on these four pages and also the object is on show in the window of our Fleet Street branch. We offer prizes of £5 to the first, £3 to the second, and £2 to the third correct answers opened on March 29th. There is no need to rush your answer to us, you can send it in when you next order from us. You have until the first post on the 29th.

TABLE RADIOGRAM CABINET

Walnut finish, outside dimensions 9¼in. high, 14in. deep, and 14¼in. wide. Designed to take our "Occasional 4" radio chassis and any non-auto gram unit. Price 49/6, carriage and packing 5/-.

10,000 B.V.A. VALVES AT PRE-BUDGET PRICES

RAPID ACTION REVERSING MECHANISM

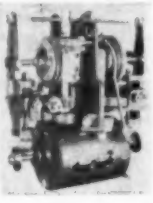

This consists of a shunt wound D.C. motor fitted with clutch at each end. A spring loaded arm keeps the drive engaged in the forward direction until hydraulic or other pressure causes the bellows to expand. This counteracts the action of the spring, engages the clutch on the other side and hence reverses the drive. The motor itself always rotates in the same direction, therefore reversing is almost instantaneous.
If pressure control is not required the bellows can be replaced by a solenoid. These mechanisms (really beautifully made by an American company) have couplings for and are designed to take two (flexible) drives simultaneously, each drive, however, is independent of the other.
Motor details are 27 v.—1.5 amps., 5,400 r.p.m. approximate overall dimensions of complete unit 6in. wide × 7in. deep × 4in. high. Limited quantity only. Price 47/6 each.

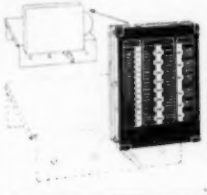

FULL VISION DRIVE

Parcel consists of scale pan with 4 pulleys, glass scale, size 6in. × 8in. calibrated in metres and with station names printed, 4 scale fixing clips. Also included is drive drum, nylon cord and pointer with diagram showing cord arrangements. Will make up as illustrated either vertically or horizontally, price 12/6.

Orders by post are dealt with by our Ruislip depot. To avoid delay address to:— E.P.E. Ltd., Dept. 2, Windmill Hill, Ruislip, Mddx.

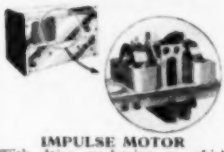

IMPULSE MOTOR

With drive mechanism to which two additional switches have been coupled. Mounted in totally screened box measuring 8½ × 3½ × 6¼in. Price 25/- each.

UNSPILLABLE ACCUMULATORS

Very best make clear celluloid case. Size 4½ × 2½ × 3¼in. 11 Amphour. Price 14/6.

VARIOMETER ASSEMBLY

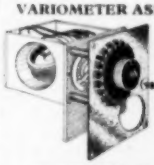

As illustrated this is useful for experimental circuits, crystal sets, etc. Price 3/9 each.

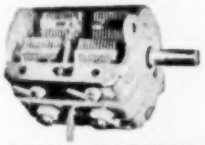

2-GANG .00035 TUNING CONDENSER

Complete with Perspex dust cover and built-in trimmers. Super job for tuning personal receivers. 8/6 each.

BRASS CASED PLUG

Seven way brass cased plug ideal for portable apparatus. Price 2/3 each half. Bin D33BR and D33BL.

ADJUSTABLE THERMOSTAT

These have silver contacts rated at 1 amp. 250 v. and can be adjusted to operate from 70° to 300° F. These are suitable for directly controlling aquarium heaters, electric blankets, etc. 3/6.

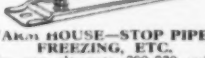

WARM HOUSE—STOP PIPES FREEZING, ETC.

Use our elements 200-230 volts 325 watts, almost flat, length 9¼in., width 1¼in., thickness ¼in., copper clad, fitted terminals, 5/6 each. Suitable thermostat, 3/6. Constructional data of convector heater, 1/6.

Orders under £2 add 2/6, under £1 add 1/9. Postable items can be sent C.O.D., additional charge approx. 2/6. List 6d. Early closing days: Wednesday, Ruislip: Saturday, City.

ELECTRONIC PRECISION EQUIPMENT

WINDMILL HILL, RUISLIP, MDX. Phone: RUISLIP 5780

152-153 FLEET STREET, E.C.4. Phone: CENTRAL 2833

GARLAND BROS. LTD

LANE PRECISION BUILT TAPE TABLE

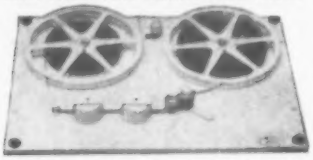

High fidelity high impedance record-playback and erase heads in mumetal shields. Heavy balanced flywheel giving freedom from "wow" and "flutter." Fast rewind. Heads are half-track, giving one hour's playing time with 1,200-foot reel of tape. **£16 10**/-, plus carriage, etc., 10/-. Demonstrations at Deptford and Lewisham.

TAPE DECK AMPLIFIER UE6. A six-valve record-playback amplifier suitable for use with high impedance heads. Features include variable bass and treble lift, recording level indicator and built-in oscillator supplying h.f. bias and erase sufficient for the highest coercivity tapes. Supplied in kit form, with punched chassis, all valves, components, circuits and full instructions. **£10 10**/-, plus carriage 5/-.

TAPE DECK AMPLIFIER HNE5. a five-valve record-playback amplifier suitable for use with high impedance heads. With built-in oscillator supplying h.f. bias and erase. Supplied in kit form, with punched chassis, all valves and components, circuits and full instructions. **£7 10**/-, plus 5/- carriage.

MODIFICATION KIT UE2. Enabling the use of any good-quality amplifier for tape recording and playback. For use with high impedance heads, or (with suitable input transformer) for low impedance heads. Incorporating pre-amplifier, oscillator supplying h.f. bias and erase sufficient for the highest coercivity tapes, and recording level indicator. In kit form, with valves, punched chassis, circuits and instructions. (NOTE: H.T. and L.T. supplies required for this unit, viz., 250 v. at 40 mA. D.C. and 6.3 v. 1 a. A.C. can normally be obtained from the main amplifier.) Price **£4 4**/-, plus 5/- carriage and packing.

MAGNETIC RECORDING TAPE. Emitape, Grade A, 600ft., **21**/-; 1,200ft., **35**/-. Scotch Boy (Durex), 1,200ft., **35**/-.

MAGNETIC RECORDING HEADS. Record-playback half-track high impedance heads, shielded. Mumetal laminations with half-thou. gap of beryllium copper, enabling twin tracks to be accommodated on standard ¼in. tape. Price **39**/6. High Impedance Erase Heads to match the above. Radiometal laminations. Price **39**/6.

AMPLIFIER AC1V

We hope to have ironed out some remaining supply difficulties by publication date. Output will be 11.5 watts from two KT61's in push-pull; output transformer will be a Goodmans H6 to our specification, tension-wound on silicon iron laminations, with a primary inductance of 100H and negligible leakage inductance and capacitance. Negative feedback will be of the order of 30 db, giving frequency response and low distortion unequalled in any amplifier in a similar price bracket. Other features will include high and low gain inputs; tone control; power supplies for tuner unit, etc.; output to 15 or 3 ohm speakers. Price is provisionally fixed at **14 guineas** wired and tested. Please send stamp for further circuit details and performance figures.

AMPLIFIER AC11. This popular amplifier is still available for those who desire good quality at a low cost. Output is 5 watts, and volume, tone, and variable feedback controls are incorporated. High-grade output transformer. H.T. and L.T. supplies are from mains transformer, thus isolating chassis from mains. Amplifier wired and tested, **£6 2 6**, plus 5/- carriage.

COLLARO 3 RCS11 3-SPEED AUTO-CHANGER. Non-mixing, plays eight 7in., 10in., or 12in. records at 33⅓, 45, or 78 r.p.m. Supplied with two plug-in pick-up heads incorporating sapphire styli, and made by Acos. Price **£18 14 1**, incl. P.T.

I.F. TRANSFORMERS. 465 kc standard size ⅞in. x 1⅝in. x 1⅜in., **12 6** per pair. Small size, 2¼in. x 1¼in. x 1in., **13 6** per pair. Made for us by a leading manufacturer.

SPECIAL PURPOSE VALVES. CV73, **4**/-; 9003, **5**/-; 954, **3**/-; CV66, **6 6**; VR136 (EF54), **7 6**; VU111, **5**/-; VU133, **3 6**; CV54, **3 6**; E1148, **3 6**; VU33, **3 6**; CV265, **3 6**; VU134, **9 6**; VR65A, **4 6**; MS Pen, **6 6**.

MAINS TRANSFORMERS. MT1, 250-0-250 v. 80 mA., 0-4-6.3 v. 4 a., 0-4-5 v. 2 a., **19 6** each. MT2, 350-0-350 v. 80 mA., 0-4-6.3 v. 4 a., 0-4-5 v. 2 a., **19 6** each; MT3, 0-30 v. tapped to give 13 different voltage outputs at 2 a., **19 6** each; All above transformers tapped 200-220-240 v. 100 w. auto. 0-10-120-200-230-250 v., **19 6** each.

CARBON RESISTORS. Large and comprehensive stocks at following prices: ¼ w., **4d.**; ½ w., **5d.**; 1 w., **6d.**; 2 w., **9d.**; 4 w., 1/- each. Among the values available at press date are the following:

Quarter Watt: 10, 12, 13, 20, 22, 33, 39, 43, 51, 56, 68, 82, 100, 150, 180, 220, 270, 300, 330, 390, 430, 450, 470, 560, 680, 700, 1 k, 1.5 k, 2.2 k, 2.4 k, 2.7 k, 3.2 k, 3.3 k, 3.9 k, 4 k, 4.7 k, 5.6 k, 6.2 k, 6.8 k, 7.5 k, 8 k, 10 k, 12 k, 15 k, 16 k, 18 k, 20 k, 22 k, 24 k, 25 k, 27 k, 30 k, 33 k, 36 k, 39 k, 40 k, 47 k, 50 k, 56 k, 60 k, 62 k, 68 k, 82 k, 100 k, 120 k, 180 k, 220 k, 270 k, 330 k, 350 k, 390 k, 470 k, 500 k, 600 k, 680 k, 750 k, 820 k, 1 m, 1.5 m, 2 m, 2.2 m, 2.7 m, 3.3 m, 4.7 m, 5 m, 6 m.

Half Watt: 27, 30, 43, 68, 82, 120, 130, 150, 270, 300, 400, 470, 500, 560, 600, 680, 750, 820, 1 k, 1.5 k, 2.2 k, 2.4 k, 3.9 k, 5.1 k, 6.2 k, 8.2 k, 10 k, 12 k, 13 k, 15 k, 18 k, 20 k, 27 k, 39 k, 40 k, 50 k, 60 k, 68 k, 100 k, 500 k, 560 k, 600 k, 680 k, 820 k, 1.5 m, 2 m, 2.2 m, 2.7 m, 4.7 m.

One Watt: 20, 27, 33, 50, 56, 68, 82, 120, 240, 330, 470, 600, 750, 1.2 k, 1.5 k, 1.8 k, 2.2 k, 2.4 k, 3 k, 3.9 k, 4.7 k, 6.8 k, 8.2 k, 18 k, 20 k, 22 k, 24 k, 30 k, 50 k, 55 k, 68 k, 70 k, 80 k, 100 k, 330 k, 470 k, 680 k, 750 k, 1 m, 1.2 m, 1.8 m, 3.3 m.

Two Watt: 47, 220, 270, 470, 600, 1 k, 1.5 k, 3 k, 3.3 k, 4.3 k, 6 k, 8 k, 8.2 k, 10 k, 18 k, 22 k, 27 k, 30 k, 47 k, 50 k, 68 k.

Four Watt: 20 k, 40 k, 56 k, 68 k; 240 k, 470 k.

HIGH STABILITY RESISTORS. 1% ¼ w.: 10 k, 25 k, 100 k, **1**/- each. 1% 1 w.: 1 m, **1 3** each. 2% ½ w.: 4 k, 10 k, 13 k, 55 k, 250 k, 1 m, **9d.** each. 5% ½ w.: 3.9 k, 10 k, 39 k, 75 k, 130 k, 600 k, **8d.** each. 5% 1 w.: 8 k, 510 k, 910 k, 1.8 m, **9d.** each. 5% 2 w.: 10 m, 11 m, 12 m, **1 3** each. We have at press date large stocks of many of these values.

WIRE ENDED WIREWOUND RESISTORS. 4 watt: 50, 90, 1,000, **1 3** each. 6 watt: 14, 25, 35 k, **1 8** each. 10 watt: 90, 145, 170, 350, 950, **1 9** each. 12 watt: 5, 30, 40, 120, 150, 3.5 k, 15 k, **2**/- each. 15 watt: 5, 100, 2.5 k, 3.6 k, 11 k, 30 k, **2**/- each.

CLIP FIXING WIREWOUND RESISTORS. 25 watt: 4, 350, 717, 5 k, 10 k, 75 k, **2**/- each. 45 watt: 14 k, tapped 2 k, at **2 3** each. 65 watt: 50 k, at **2 6** each. 200 watt: 430, 10 k, 20 k, 50 k, at **3**/- each. We have large stocks of the heavier wattage resistors; quantity prices on application.

TELEVISION MAGNIFYING LENS. 9in. clear, **55**/-; 9in. filter, **60**/-; 12in. clear, **75**/-; 12in. filter, **80**/-. Carriage and packing 5/- each, all types.

LUSTRAPHONE MOVING COIL MICROPHONES. Type CS1. Response substantially flat to 8 kc/s. Impedance 20 ohms. Fitted with switch, **£5** each. Type CS1/Z. As above, but impedance 200,000 ohms, **£5 12 6** each.

CARBON HAND MICROPHONES. Type No. 3. With G.P.O. type carbon insert, press switch in handle, lead and jack plug. New and unused, **5**/- each.

SLEEVING. 2 mm. oiled silk, etc., **3 6** per 24 nominal yard lengths, assorted colours, **33**/- per two gross ditto.

COLLARO RCS11 SINGLE-SPEED AUTO-CHANGER. Non-mixing, plays eight 78 r.p.m. 10in. or 12in. records. Supplied with Acos made plug-in pick-up head incorporating sapphire stylus. Magnetic, price **£11 14 11**, incl. P.T. Crystal, price, **£12 3 2**, incl. P.T.

STABILIVOLT TYPE VS16. Similar to STV280/40. Operating voltages 280, 210, 140, 70 v. Max. electrode current 60 mA. **10**/- each, **£5** per doz. Further supplies now available.

THYRATRONS. Type NGT1 (CV1141) 4 v. heater, anode volts 350. Anode current, peak 1 a., average 200 mA. Control ratio 40. 5-pin British base, with anode top cap. **6 6** each, **72**/- per dozen.

HEAVY DUTY OUTPUT PENTODES. Type PT25H. 4 v. filament, British 5 p. base. Have been successfully used strapped as triodes in quality amplifiers. **5**/- each, **48**/- per dozen.

CONDENSERS (pFs). 2, 4, 10, 15, 20, 30, 50, 75, 100, 160, 200, **6d.** each, **5 6** doz. 220, 300, 330, 500, 1,000, 2,000, 4,000, 4,500, 4,700, **9d.** each, **7 6** doz.

PAPER CONDENSERS. 1μF 500 v. wkg., 2½in. x 2in. x ¾in. Inverted mounting, 1/- each, 9/- per doz., **£3 12**/- per gross. 1μF 600 v. wkg., 2¼in. x 1⅜in. x 1in. upright mounting, 1/6 each, 15/- per doz., **£7** per gross. 3μF 2,000 v. test, upright mounting Mansbridge type, ex-Govt. **2 9**. 4μF 500 v. wkg., inverted mtg., **2 9**.

HIGH VOLTAGE MICA CONDENSERS. 0.1μF 1,500 v. wkg., by a leading manufacturer. Bakelite case upright mounting, 3in. x 2¼in. x 1⅝in. overall. Price **2**/- each, **21**/- per doz. Ceramic feed-through type, 10C/2178, 0.0002μF 5 kv. wkg., **2/6** each.

HIGH VOLTAGE PAPER CONDENSERS: 10C/12541. In black bakelite cylindrical case, single screw fixing. 0.02μF, 5kv. wkg., **1 9** each.

AMPLION TESTMETER. 10 Ranges A.C. and D.C. Up to 500 v. A.C. and D.C. Resistance up to 200,000 ohms, 1,800 ohms per volt A.C. and D.C. Price **£5**.

CLOSE TOLERANCE SILVER MICA CONDENSERS. 10,000 pF (0.01μF) plus or minus 2%. Ideal for service bridges, etc., 1/- each, 9/- per doz., **£4 10**/- per gross. 1,000 pF (0.001μF), ± 1%, **1 3** each. 100pF (0.0001μF) ± 1%, **9d.** each 400pF (0.0004μF) ± 1%, **9d.** each.

HIGH CAPACITY PRECISION MICA CONDENSERS. We are again able to offer a complete range of these condensers, of which we have now sold over 25,000. Accuracy plus or minus 0.5 (point five) per cent of stated value. Pure mica and copper foil or silver.

(a) 0.017970μF ...	1 3	(b) 0.023570μF ...	1 3
(bi) 0.027400μF ...	1 6	(c) 0.035020μF ...	1 6
(d) 0.040710μF ...	1 6	(di) 0.048010μF ...	1 6
(e) 0.055820μF ...	1 6	(f) 0.065350μF ...	1 6
(fi) 0.082910μF ...	1 6	(g) 0.087460μF ...	1 6
(h) 0.108435μF ...	1 9	(i) 0.123750μF ...	1 9
(j) 0.147000μF ...	1 9	(k) 0.205276μF ...	2/-

Many standard values to better than 1 per cent. can be made up by parallel or other combinations of above, e.g., 4j + 2k = 1μF; 2k + g = 0.5μF; c + f = 0.1μF. A table of over 150 series and parallel combinations of these condensers, invaluable in calculating filter networks, etc., is available on receipt of 2½d. stamp.

BAKELITE CABINETS

As illustrated, complete with chassis drilled for T.R.F. receiver, back, glass dial, speaker plate, brackets, three knobs. With each cabinet, we give circuits and instructions, with priced parts list for 3 valve T.R.F. receiver, thus enabling you to use the parts you already possess. Each **27 6**.

ALL GOODS NEW AND UNUSED OTHERWISE STATED. GOODS SHOWN AS EX-EQUIPMENT HAVE BEEN FULLY TESTED AND ARE IN GOOD WORKING ORDER. **PLEASE ADD POST OR CARRIAGE ON ALL ITEMS. KINDLY PRINT NAME AND ADDRESS.** POST ORDERS TO OUR DEPTFORD ADDRESS. EARLY CLOSING THURSDAY, OPEN ALL DAY SATURDAY

PRIORITY TO DEFENCE AND EXPORT ORDERS

GARLAND BROS. LTD

CHESHAM HOUSE, DEPTFORD BROADWAY, S.E.8
TELEPHONE: TIDEWAY 4412/3

9 OBELISK PARADE, LEWISHAM, S.E.13
TELEPHONE: LEE GREEN 4078

LASKY'S RADIO

TELEVISION CONSOLE CABINETS

DE LUXE BEAUTIFUL WALNUT VENEER

For 12in. cathode ray tubes. Beautiful figured medium walnut finish, with high polish. Fitted with shelf for receiver, glass, speaker baffle and fret, and castors for easy movement. Undrilled. Suitable for use with the Viewmaster, "Practical Television," "Practical Wireless," and "Wireless World" televisors.

LASKY'S PRICE

£8 . 10 . 0

Carriage 12/6 extra.

Outside dimensions of cabinet: 17½in. x 16½in. x 32in.

Why not convert your table receiver to a console?

Adaptor frames for fitting 9in. or 10in. C.R. tubes available if required.

W.B. & PLESSEY T.V. COMPONENTS.

Tube Supports	16/-
Line E.H.T. trans.	27/6
Frame trans.	22/6
Boost choke	5/9
Scanning Coils	29/6
Heater trans. 103	37/6
103A	52/6
Focus ring	21/6
Main choke	15/6
W.11th control	10/-

Postage extra.

SUPPLEMENT YOUR E.H.T. FROM THE LINE FLYBACK, AND USE A LARGER C.R. TUBE, by using a BOOST E.H.T. KIT. Comprises one selinium rectifier, one 2-meg. resistance and two T.C.C. .001 mfd. 6 kV condensers. For converting 9in. T.V. receivers to 12in.

LASKY'S PRICE 20/-

Post Free.

METAL RECTIFIERS FOR TELEVISION

WX3	3/7
WX6	3/7
14A86	18/3
14D36	11/-
36 EHT 25 1.8 Kv.	13/10
36 EHT 35 2.5 Kv.	18/2
36 EHT 40 2.9 Kv.	20/6
36 EHT 45 3.4 Kv.	22/6
36 EHT 50 3.6 Kv.	24/10
36 EHT 100 7 Kv.	28/-

Postage 6d. per item extra.

FRAME BLOCKING OSCILLATOR TRANSFORMERS. **LASKY'S PRICE 4/6** each. Post 4d. extra.

CO-AXIAL CABLE

Standard impedance.
Single screened, 1/- per yard.
Twin screened, 1/6 per yard.
Twin balanced feeder, 7½d. per yard. Post extra. Any length cut to your requirements, 10% discount on 50 or more yards.

CATHODE RAY TUBES. All types and sizes available from stock. Brand new and fully guaranteed.

12in.	from £18 4 10
15in.	from £22 16 10
16in.	from £24 6 5
14in. rectangular	from £22 8 5

WENVOE & KIRK O' SHOTTS COILS for the VIEWMASTER. 10 coils and 4 filter coils, by Wearite. Exactly as specified in the construction data. Available from stock. **PRICE 28/-**, postage 1/- extra.

EVERYBODY IS BUILDING THE VIEWMASTER

The television set you can build at home from standard parts.
Wenvoe, Kirk o' Shotts, Holme Moss, Sutton Coldfield and Alexandra Palace operation.
Brilliant high definition black and white picture.
Superb reproduction.
Uses 9in. or 12in. Cathode Ray Tube.
Table or Console Model.
Incorporates all the latest developments.
Television for the home constructor at its finest.
Send to-day for the CONSTRUCTION ENVELOPE, a 32-page booklet crammed with top-rate information and all the necessary data, also 8 full-size working drawings and stage by stage wiring instructions. Model "A" for use in London and Home Counties. Model "B" for use in Sutton Coldfield Area. Model C for Holme Moss. Model D for Kirk o' Shotts. Model E for Wenvoe.

PRICE 5/- per copy
Post free.

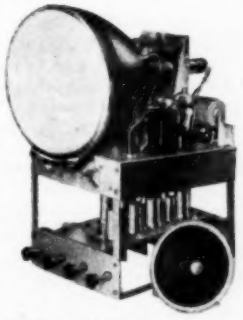

ALL COMPONENTS IN STOCK AND SOLD SEPARATELY

9in. CLOSED FIELD LOUDSPEAKERS. Ideal for television receivers. Less o/trans. 3 ohms. Will not affect your C.R. tube.

LASKY'S PRICE 17/6
Post 1/6 extra.

T.C.C. VISCONOL HIGH VOLTAGE CONDENSERS (Cathode ray).
.001 mfd. 6 kV. Price 4/6 each.
.001 mfd. 12.5 kV. Price 7/6 each.
.1 mfd. 7 kV. Price 15/- each.
.1 mfd. 6 kV. Price 10/- each.
All post extra.

ENGRAVED KNOBS. 1¼in. diameter, ¼in. Spindle. For television, radio and amplifiers. All types. (Brilliance, tone, etc.)
PRICE 1/6 each. Post extra.

WIREWOUND COLVERN POTMETERS. Most values.
LASKY'S PRICE 3/6 each.
Post extra.

TELEVISION VALVES. MOSTLY AT PRE-BUDGET PRICES. EL38, EL33, 6P25, 6K25, EY51, 6ZBT, 7C5, PL38, PZ30, GZ32. Etc. **NO SHORTAGE AT LASKY'S.**

CATHODE RAY TUBE MASKS

9in., with fitted armour plate glass	10/6
less glass	7/6
10in.	9/6
12in. soiled white	10/-
Brand new white	19/6
Special for flat-face tubes	22/-
Grey rubber sorbo. Flock spraved	7/6

Postage 1/6 each extra.

E.H.T. TRANSFORMER FOR VCR97. Primary 200-250 v., 50 cps. Secondary: 2.5kV 4 m.a. 4v. 1.1a. 4v. (CT) 1.5 a.
LASKY'S PRICE 45/-
Postage 1/6 extra.

TINTED SCREEN FILTER PLATES. 9in.-10in., 18/6. 12in., 25/-, Postage 1/- each extra.

A FEW LEFT. VCR140 C.R. TUBES. Ex. Government, 12" magnetic focus and deflection. Green screen. Suitable for TV. New and unused.
LASKY'S PRICE £5/10
Carriage 12/6 extra.

EX-A.M. RECEIVER TYPE 3515. Contains the well known 194 I.F. Strip. Uses 21 valves, 10 VR65, 1 EA50, 1 EB34, 7 VR56, 2 VR53, and a host of components, condensers, relays resistances, etc. Built on a strongly constructed chassis, totally enclosed in a metal case 18in. x 12in. x 9in. BRAND NEW AND UNUSED. Supplied less all valves.
LASKY'S PRICE 35/-
Carriage 7/6 extra.

VCR97 C. R. TUBES. BRAND NEW AND UNUSED. In makers original sprung wood transit case. Supplied with fully insulated and totally enclosed base holder.
LASKY'S PRICE 40/-
Carriage 5/- extra.

ARMOUR PLATE SAFETY GLASS. For 9in. tubes 3/-, 12in. 4/- per piece. Post 1/- each.

LASKY'S RADIO

LASKY'S (Harrow Road) LTD.

370 HARROW ROAD, PADDINGTON, LONDON, W.9

(Opposite Paddington Hospital)

Telephones: CUNningham 1979 and 7214

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m., Thurs. half day 1 p.m. Send 2½d. stamp with your name and address (in block letters please) for a copy of our current stock list giving details of our supplies of new manufacturers' surplus equipment and ex-government radio radar and valves, etc.

LASKY'S RADIO

World Renowned for Service & Reliability

LASKY'S OWN TEST PRODS

Made for safety. Fused test prods. Fully insulated pencil type with retractable point. Contact is only made when desired by pressing top. Each prod contains a cartridge type fuse and spring.

LASKY'S PRICE 4/11 per pair (one red, one black). Post 6d. extra.

COIL PACKS

No. 1. 3 Wavebands, 12-35 metres, 35-100 metres, 200-550 metres. ⅜in. spindle, 1¼in. long wavechange switch. Completely assembled and wired. Size: 4½in. × 4½in. × 3½in. BRAND NEW.

LASKY'S PRICE 16/- Postage 1/- extra. Circuit available price 1/-.

No. 2. Midget Coil Pack, 3 wavebands. Standard long, medium and short. ⅜in. spindle, ⅝in. long wavechange switch. Complete by assembled and wired. Size: 2¾in. × 1¼in. × 2¼in. BRAND NEW.

LASKY'S PRICE 24/6 Postage 1/- extra. Circuit available, price 1/-.

ALL OTHER TYPES AND MAKES OF COIL PACKS AVAILABLE

Osmor, Weymouth, Wearite, etc., etc.

COLLARO AUTOMATIC RECORD CHANGERS

Model RC.500. Magnetic pick-up	£11 15 7
Model RC.500. Xtal pick-up	£12 3 0
Model RC.511. 3 speed, with dual purpose pick-up head	£15 10 6
Model RC.511. 3 speed, with 2 crystal pick-up heads	£18 14 1

WEARITE L.F. TRANSFORMERS. Type 550

Permeability tuned, 445-526 Kc/s. Type 551 Critically coupled, with top grid connection. Type 552. Closer coupling for feeding diode circuit. Q115, inductance 700 micro-henries at 465 Kc/s.

Bandwidth of each of the above transformers is 7-20 Kc/s at 2-20 dbs. Size: 3½in. high, 1¼in. square. Supplied with fixing screws and nuts.

LASKY'S PRICE 6/6 each. 12/6 per pair.

TANNOY HAND-POWERED MICRO-PHONE AND HEADPHONES (M/C).

LASKY'S PRICE 12/6 Post free. per set.

SMOOTHING CHOKES

20 mA. 40 H.	3/11
40 mA. 8 H.	3/11
40 mA. 10 H.	4/3
80 mA. 10-20 H.	4/11
120 mA. 10-20 H.	7/6
150 mA. 10-20 H.	10/6
150 mA. 3 H.	3/3
250 mA. 5 H.	10/6

Postage extra.

EXPANDED METAL SPEAKER FRET

Metal one side finished gold, other side silver. Size: 15in. × 12in.

LASKY'S PRICE 4/3 per piece

Post 6d. extra.

RADAR INDICATOR UNITS TYPE 162C

BRAND NEW IN MAKER'S ORIGINAL WOOD CASE. Contains 1 cathode ray tube, 6in. VCR517. Also the following valves: three SP61, one 6J5, three EA50, one D1. Dozens of components, coils, resistance, condensers, screen pot. meters, etc. Enclosed in metal case, size 13in. × 9½in. × 19in. Weight 45lb.

LASKY'S PRICE 75/- Carriage 7/6 extra.

FILAMENT TRANSFORMERS

All primaries 230 volts 50 c.p.s.

FIL.2. 6.3 v. 1.5 a.	Price 7/11
FIL.3. 6.3 v. 3 a.	Price 10/6
FIL.4. 7 v. 2 a.	Price 4/11
FIL.5. 6.3 v. 4 a.	Price 12/6
FIL.6. 12 v. 3 a.	Price 15/-

Special Transformer. 30 volts at 3 amps, with the following tappings: 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volts. Price 19/6

All 50 cycle trans. 1/- extra per item postage.

OUTPUT TRANSFORMERS

Miniature Pentode (1S4, 3S4)	3/11
Midget Pentode 40 mA	4/3
Multi-Ratio Standard	6/11
Push-Pull, 60 mA. Ratios of 40 : 1 and 80 : 1	8/6
Push-Pull for PX4's	12/6
80 mA heavy duty, multi-ratio	12/6
10 Watt multi-ratio	16/11
50 Watt, 70 mA. Multi-ratio	29/11
Bolgin inter-valve transformers. Ratio: 4 : 1	3/11
5 : 1	5/11
Standard Pentode, 60 mA	3/11

Postage extra.

ALL WAVE RADIO! AT HALF PRICE

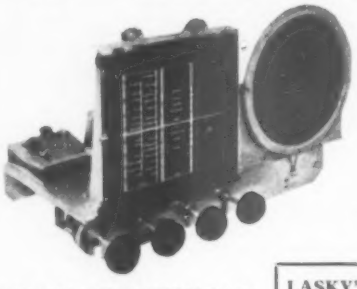

- 5 new valves.
- 8 in. Elac p.m. speaker.
- Variable tone control.
- Large edge lit dial, 7¼in. square.
- 2-speed tuning with nylon drive.
- 4 wa. ou pu.
- Sockets for p.u. and extension speaker.
- 465 Kc/s I.F.
- A.V.C.
- Circuit diagrams.

Size of chassis: 15½in. wide, 8in. deep, 2¼in. high.

NOT A KIT, BUT A FACTORY BUILT JOB. FULLY ALIGNED AND TESTED.

Enclose 2½d. stamp for full details, circuit diagrams and illustrations.

LASKY'S PRICE

£10.19.6

Complete with 5 valves and speaker.

Carriage and insurance 10/6 extra.

MAINS TRANSFORMERS

All 200-250 volts 50 c.p.s. primary. Finest quality, fully guaranteed.

MBA 3. 350-0-350 v. 80 mA., 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts. An ideal replacement trans. Price 18/6

MBA 5. 350-0-350 v. 120 mA., 6.3 v. 4 a., 5 v. 3 a. With mains tapping board Price 27/6

MBA 6. 350-0-350 v. 100 mA., 6.3 v. 3 a., 5 v. 2 a. With mains tapping board Price 22/6

MBA 7. 250-0-250 v. 80 mA., 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts Price 18/6

AT 3. Auto transformer. 0-10-120-200-230-250 volts, 100 watts Price 19/6

AT 4. Auto transformer. 100 volts and 230 volts. Step up or down. 60 watts Price 9/6

Postage 1/6 extra per transformer.

DECCA GRAM MOTORS

Single Speed	£3 14 4
Three Speed	£7 3 4

B.S.R. GRAM UNITS

3-speed unit, with pickup and change over crystal head. Supplied with two sapphire styli £9 19 11

LARGE STOCKS OF RESISTANCES ALWAYS AVAILABLE

All values. Prices: 1/10th and 1 watt, 7½d. each; ½ and ¼ watt, 6d. each; 1 watt, 8d. each. Postage extra.

MIDGET YAXLEY SWITCHES

4 pole 3-way. Long spindle.

LASKY'S PRICE 2/11 Postage 3d. extra

TABLE MICROPHONE STAND

Two sections, chrome plated. Crackle finished base.

LASKY'S PRICE 17/6 Post, packing 2/6 extra.

CARBON POT METERS

All with long spindle. ½, 1, 1 and 2 meg.

LASKY'S PRICE, less switch 3/3 each. With switch 4/3 each.

All post extra.

Short Spindle and pre-set. PRICE 1/6 each. Post extra.

ALL YOUR RADIO VALVE REQUIREMENTS AT LASKY'S

ANTENNA ROD SECTIONS

Each section is steel heavily copper plated. 12in. long and ⅜in. in diameter. Any number of sections can be fitted together. LASKY'S PRICE 2/6 per doz. 6/- for 3 doz.; 11/- per half gross; 20/- per gross. Post free.

J.BA.2. 10-12 WATTS CHASSIS AMPLIFIER

Uses an L63 feeding 2 KT61's in push-pull. Rectifier type U50. Size: 9in. × 12in. on 2in. chassis. £7/19/6

LASKY'S PRICE

Carriage and packing 10/- extra.

Send 3d. stamp for further details of J.BA.2 Amplifiers

P.M. LOUDSPEAKERS

All less o.p. trans. New and unused. First quality.

5in.	12/11
6in.	12/6
6½in.	12/6
8in.	14/6
10in.	24/6
12in.	75/-

SETS OF ENGRAVED KNOBS

1 each Tuning, Volume, L.W.S.G., and Tone.

LASKY'S PRICE 4/- the set. Post extra.

MAINS DROPPERS

All types from 2/6 each. 12 assorted, 25/-. Post free.

CAR BATTERIES

By DELCO-REMY. Ex-American Army. Absolutely perfect, brand new and unused, in maker's original packing No. 1. 6-volt 140 A.H. approx. Size: 7in. deep, 13in. wide, 8½in. high. In genuine hard rubber case.

LASKY'S PRICE £4/19/6 Carriage 7/6 extra.

No. 2. 6-volt 90 A.H. Size: 9in. wide, 7in. deep, 8in. high. In genuine hard rubber case.

LASKY'S PRICE 87/6 Carriage 7/6 extra.

LASKY'S RADIO

Lasky's (Harrow Road) Ltd.,

370 HARROW ROAD, PADDINGTON, LONDON, W.9

(Opposite Paddington Hospital) *Telephones:* CUNningham 1979 and 7214

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m., Thurs. half day 1 p.m. Send 2½d. stamp with your name and address (in block letters please) for a copy of our current stock list giving details of our supplies of new manufacturers' surplus equipment and ex-Government radio, television, radar and valves, etc.

EX-A.M. COMMUNICATION RECEIVER TYPE R1155

BRAND NEW IN WOOD TRANSIT CASE. Actual-tested before despatch. Supplied complete with 10 valves. Circuit: R.F.O., A.V.C., R.F. Amp., two I.F. stages, magic eye, etc. 8 frequency ranges: 18.5-7.5 Mc/s.; 7.5-3.0 Mc/s. 1,500-600 Kc/s.; 500-200 Kc/s.; 200-75 Kc/s.

LASKY'S PRICE **£12 10 -**

Carriage (in wood case) 7 6 extra. Full modification data and circuit details supplied.

VIBRATOR PACKS

12 volt input. Fitted with synchronous vibrator. Brand new and unused.

No. 1. Output 250 v. 100 mA.
LASKY'S PRICE Complete **29 6**
Less vibrator 20 -.

No. 2. Output 150 v. 80 mA.
LASKY'S PRICE Complete **25 -**
Less Vibrator 17 6.
Carriage 2 6 per pack extra.

No. 3. For use with P.C.R. Philips Communication Receiver. Supplied complete with metal rectifiers, and vibrator, etc. LASKY'S PRICE **39 6**
Carriage 5/- extra.

RECEIVER TYPE 25

Rx. section of TR1196 equpt. Size: 8½in. x 6in. x 6½in. Contains 6 int. octal valve holders, condensers, coils, tuning, etc. Ideal for conversion to an all wave receiver. In black metal case. LASKY'S PRICE **10 6** Carriage 3.6 extra.

R.F. UNITS TYPE 24

Suit 4 tuning.
LASKY'S PRICE Boiled, less valves **12 6**
Carriage 2 6 extra.
Soiled, with valves **21 -**
Carriage 2 6 extra.

EPICYCLIC DRIVES

Long 1in. spindle. Special double type. Standard reduction.

LASKY'S PRICE **2 6** each
Post 4d. extra.

ALL YOUR TEST GEAR AT LASKY'S

RADAR RECEIVER UNITS TYPE R3584

BRAND NEW AND UNUSED IN ORIGINAL WOOD TRANSIT CASE. Contains 23 valves: 13 EF50; 2 VR65; 3 EB34; 1 VR56; 1 RA99; 1 VR53. Hundreds of components, resistances, condensers 12 pot/meters, etc. Relays, amphenol and ceramic valve holders. Totally enclosed in metal case, size 7½in. x 13in. x 21in. Supplied Less IF strip.

LASKY'S PRICE **79 6**
Carriage 7 6 extra.

CRYSTAL DIODES

Wire ends. Supplied with circuit. B.T.H. type.
LASKY'S PRICE **3 11** each.
G.E.C. type 4 6. postage 3d. each extra.

EX-A.M. FREQUENCY METER TYPE W1191. USED CONDITION

Frequency range 100 Kc s to 20 Mc/s. Uses 4 valves and 100 Kc/s crystal. Battery operated L.T. 2 volts and H.T. 60 volts. Unit contained in grey metal case, with hinged lid and carrying handle. Size 13in. x 10in. x 10in. Weight 36lb. Supplied complete with all valves, crystal. Accuracy: 0.1 per cent. and with crystal 0.01 per cent.

LASKY'S PRICE **£7 19 6** Carriage and packing 10 - extra.

TANNOY 60 WATT AMPLIFIERS

Standard 230 volts 50 c.p.s. mains input. Standard rack mounting. Comprises 2 rectifiers. 4 6L5's feeding 4 6L6's in parallel push-pull.
LASKY'S PRICE. Complete with all valves **£11 19 6**
Carriage and packing 12 6 extra.

6 and 12 VOLT VIBRATORS

4 pin type.
LASKY'S PRICE
Soiled **5 -** each
Post 6d. extra.
New **9 6** each
Post 6d. extra.

A GENUINE MINIATURE 2-GANG TUNING CONDENSER

No. 1. .0005 mfd. Size: 1¼in. deep, 1¼in. high, 1in. wide. ¼in. spindle. With fixing feet.
LASKY'S PRICE **6 6** each
Post 6d. extra.
No. 2. .0005 mfd. Size 2¼in. x 2in. x 1¼in. ¼in. spindle.
LASKY'S PRICE **7 6** each
Post 6d. extra.

SERVISOL

The cleaning fluid no service man can do without. Standard size half pint tins.
PRICE **5 -** per tin.
Postage 9d. extra.

CABINETS FOR INTER-COM CHASSIS

Medium walnut finish drilled for switches, indicator bulbs, etc.
LASKY'S PRICE **25 -** Carriage 2 6 extra.

INTER-COM UNIT SCOOP

Manufacturer's surplus. Brand new. For 6 station operation, uses 3 valves, 1 each 25Z4, KT32, and 6J7. AC DC mains.

AT A FRACTION OF USUAL COST.

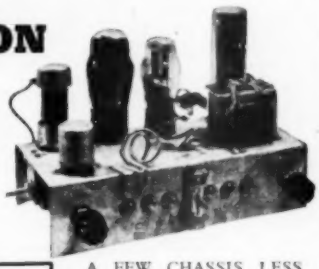

LASKY'S PRICE
£5 . 5 . 0
Carriage 2/6 extra.
Complete with all valves, speaker and indicator bulbs.

A FEW CHASSIS LESS VALVES, BULBS, AND SWITCH.
LASKY'S PRICE **35 -**
Carriage 2/6d. extra

WRITE FOR FURTHER DETAILS

HIGH VOLTAGE CONDENSERS

.1 x .1 mfd. 3 kV. Price 5 6 each. Post extra.
.1 x .1 mfd. 5 kV. Price 12 6 each. Post extra.

TOGGLE SWITCHES

Bulgin S/P. Rotary on-off. Long spindle. LASKY'S PRICE **2/6** each
S.P.D.T. On-off switch.
LASKY'S PRICE **1/-** each
Post extra.

ANTENNA RELAY UNITS TYPE CBY/29125.

BRAND NEW AND UNUSED IN ORIGINAL CARTONS. American Air Corps equipment. Contains a 0-5 mA moving coil meter, also relay, insulators, 0.75 amp heating element, switch, etc. A .50 pf. vacuum condenser 5 kV working. Fitted in black metal case, crackle finished, size: 44in. x 5in. x 3¼in.
LASKY'S PRICE **16 6**
Postage 1 6 extra.

PLIERS

Round nosed. Various sizes.
LASKY'S PRICE **1 3** per pair
Post extra.

SPEAKER CABINETS

For use with a 3in. speaker. Medium walnut finish ideal as extensions for the inter-com. units.
LASKY'S PRICE **12 6**
(Less speaker)
Carriage 2/- extra.

HEADPHONES

DLR1. Low resistance, new and unused. Supplied complete with headband and cord.
LASKY'S PRICE **7/6** per pair.
Postage 1/- extra.

AMERICAN AIR CORPS TYPE

Lightweight. Supplied complete with headband and cord.
LASKY'S PRICE **9/6** per pair.
Postage 1/- extra.

CONDENSER CORNER

8 mfd. 500 v. w.	3/-
8 mfd. 450 v. w.	2 6
8 x 8 mfd. 500 v. w.	4 6
12 mfd. 50 v. w.	1 -
16 mfd. 450 v. w.	4 11
16 mfd. 500 v. w.	5 3
16 + 16 mfd. 450 v. w.	5 6
24 mfd. 450 v. w.	6 11
25 mfd. 25 v. w.	1 6
20 + 40 mfd. 350 v. w.	6 11
32 mfd. 450 v. w.	5/11
32 mfd. 500 v. w.	6 6
32 + 32 mfd. 350 v. w.	5 6
50 mfd. 12 v. w.	1 9
50 mfd. 50 v. w.	3 9
50 mfd. 350 v. w.	4 11
65 mfd. 350 v. w. A.C.	17 6
15 x 12 mfd. 350 v. w.	3 11
16 mfd. 350 v. w.	2/11

Postage extra.

EX-GOVERNMENT TEST INSTRUMENTS.

PERFECT CONDITION. Evershed and Vignoles, 250 volt bridge meg. tester. In leather carrying case.
LASKY'S PRICE **£18 18 -** Carriage extra.

CIRCUIT TESTING OHMMETER. By Evershed and Vignoles. In leather carrying case.
LASKY'S PRICE **£4 19 6** Carriage extra.

I.F.F. RECEIVER TYPE R3108.

BRAND NEW AND UNUSED. IN ORIGINAL CARTONS. Contains 8 new valves: 4 8P41, 1 EA50, 1 VR78, 2 CV8. Also a host of components, coils, condensers, resistances, etc. A motor generator with input of 24 volts, and output of 400 volts.
LASKY'S PRICE
Carriage 3 6 extra. **25 -**

EX. A.M. RECEIVER TYPE R1481.

IN WOOD TRANSIT CASE. Frequency coverage 60-86 Mc/s. Description:—Valve line up:—1 VR65; 1 VR66; 4 VR53; 2 VR54; 1 6J5; 1 VR70; 1 VR57. Large tuning scale with slow motion dial and drive. 0-5 mA tuning meter, RF. and I.F. gain controls, jack sockets for line and 'phone. Totally enclosed in metal case, grey enamelled, with plated handles. Size: 18in. x 10in. x 11in. Weight packed 54lb. Supplied complete with all valves, also circuit and calibration chart. Soiled condition.
LASKY'S PRICE **69 6** Carriage 10/- extra

METAL RECTIFIERS

No. 1. 125 volts at 60 mA. Price 3/11. Post 6d.
No. 2. 125 volts at 100 mA. Price 4 3. Post 6d.
Any number can be used together, either in series or parallel
No. 3. 50 volts at 5 mA. Price 2 6. Post 4d.
No. 4. 800 volts at 5 mA. Price 9 6. Post 6d.

METAL CHASSIS. BRAND NEW AND UNUSED

No. 1. Drilled for 4 valves, I.F.'s etc. Size 11in. wide 5in. deep, 2in. high.
LASKY'S PRICE **1/-** Postage 9d. extra.

No. 2. 7½in. wide, 5in. deep, 2½in. high. Fitted with 4 international octal valve holders drilled for I.F.'s, etc. Aerial and earth tag board fitted.
LASKY'S PRICE **2/11** Postage 9d. extra.

No. 3 11½in. wide, 8in. deep, 2½in. high. Fitted with 4 international octal valve holders, and 1 British 4 pin holder. Also aerial and earth tag board. Drilled for I.F.'s, smoothing condenser, etc. (A.C./D.C. Chassis).
LASKY'S PRICE **3/11** Postage 9d. extra.

No. 4. 11½in. wide, 8in. deep, 2½in. high. Fitted with 4 international octal valve holders, aerial and earth tag boards and mains input plug. Drilled for I.F.'s, smoothing condenser, and cut out for mains transformer size 2¾in. x 2¼in. (A.C. chassis.)
LASKY'S PRICE **4 6** Postage 9d. extra.

MONEY BACK GUARANTEE
Everything ordered from Lasky's is guaranteed to be as advertised. If you are not more than satisfied return goods for cash refund.

BUILD A PROFESSIONAL RADIO OR AMPLIFIER AT LESS THAN HALF TODAY'S PRICE

You're SURE to get it at

STERN'S

ESTABLISHED 25 YEARS

ALL KITS INCLUDE "EASY TO FOLLOW" POINT-TO-POINT WIRING DIAGRAMS

A MAINS OR BATTERY PORTABLE KIT

A Midget 4-valve Superhet Portable Set covering medium and long wavebands.
Designed to operate on A.C. mains 190-240 volts, or by an "All-dry" battery. The set is so designed that the mains section is supplied as a separate unit which may be added at any time. The Kit-form can be supplied (as an "All-dry" Battery Superhet Personal Set which can then be accommodated in the Attache Case as illustrated above (size 9½in. × 4½in. × 7½in.). This is attractively finished in Dark Green or Blue Rexine (to or as a Combined Mains Battery Superhet Portable Receiver, for which a polished Wood Cabinet is available to accommodate both Mains Unit and Battery) together. Circuit incorporates delayed A.V.C. and Pre-selective Audio Feedback. Kit is complete in every detail and includes ready wound frame aerials, fully aligned I.F. Transfs. and drilled chassis, etc. Overall size of assembled chassis 8in. × 4in. × 2½in.
We can supply the set either as a complete Kit of Parts for £10 7 6 (incl. P.T.) (plus Cabinet and Mains Unit), or by supplying the components separately. The complete Assembly Instructions, which include full price details (including prices of individual components), Circuit and Component Layout, etc., are available for 1 9 (incl. postage.

A T.R.F. BATTERY "PERSONAL" KIT

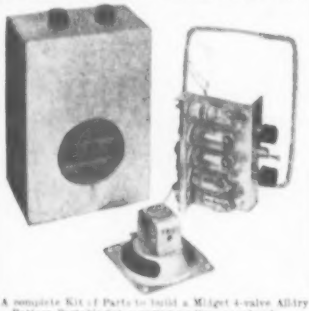

A complete Kit of Parts to build a Midget 4-valve All-dry Battery Portable Set, covering medium wavebands.
Circuit of Regenerative T.R.F. circuit, employing Flat Tuned Frame Aerial with Denco Iron Dust Cored Coil.
Valve line up: two 1.T.4's (R.F. Ampl. and Det.), 185 and 384 output.
Kit is complete in every respect and includes drilled chassis and latest type Rola 3in. P.M. speaker. Overall size of assembled chassis 4½in. × 9in. × 5½in.
We can supply the Complete Kit (less cabinet) for £6 12 6 (inc. P.T.), or by supplying the components separately. The Complete Assembly Instructions, including individual component prices, Circuit and Component Layout, etc., are available for 1 -, (incl. post.

A KIT OF PARTS

Complete in every detail, to build a 3-valve Amplifier for A.C. (50 cycle) mains 200/250 volts.
Has an output of 3 watts, and incorporates a Tone Control.
Valve line up: 6SA7, 6Q7, U31.
Our price of £4 18 9 for complete kit includes a matched 6½in. P.M. speaker.
This Amplifier can also be supplied assembled and ready for use for £5 19 6.

A MIDGET 4-STATION "PRE-SET" RECEIVER

A complete Kit to build a 4-Station "Pre-Set" Superhet Receiver for A.C. mains operation.
The Set is designed to receive any three stations on medium wavebands and one on long waves, each station being received by the turn of a Rotary Switch—No Tuning being necessary.
It is of midget size, being 8½in. × 4½in. × 7in. high, and has the performance of a far more expensive ready-made set, but can be built for half the price.

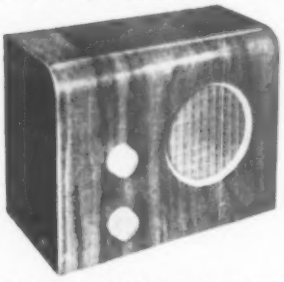

Price of complete Kit of Parts (including aligned I.F. Trans. and drilled chassis, etc.), £9 15 - (incl. P.T.) (plus Cabinet 25 6), or the components can be purchased separately. The complete Assembly Instructions, including Individual Component Price List, Circuit and Component Layout, etc., are available for 1 9.

STERN'S "RADIO TUNER MANUAL," Price 2 6. (Plus 3d. Post). Contains complete and detailed assembly instructions showing how to make:—
A **1-Valve T.R.F. Tuning Unit**, covering Long and Medium Wavebands.
A **4-Station "Pre-Set" Superhet Tuning Unit**, producing 3 Stations on Medium Waveband and 1 on long Waves.
A **2-Valve Superhet Tuning Unit**, covering Short, Medium and Long Wavebands.
Each Tuner is for A.C. Mains operation. Circuit Diagrams and Practical Component Layouts are shown, together with complete component Price Lists.

THE WIRELESS WORLD MIDGET A.C. MAINS 2-VALVE RECEIVER

We can supply all the components to build this set, including Valves and Moving Coil Speaker for £3 10 -, including Designer's complete building instructions (these are available separately for 9d.).

THE "SUMMER ALLDRY" BATTERY PORTABLE

As published in June issue of "Practical Wireless." We can supply, from stock, all the components to build this Midget 3-valve Portable for £3 2 0 (less valves). This also includes dials, top panel and alv. sheet for chassis. The complete article and circuit, including Practical Layout and Price List, is available for 9d.

PICK-UPS

Cosmocord "G.P.20," for standard records, £3 11 5; interchangeable (G.P.19) Head for L.P. records, £2 3 4.
Decca lightweight "turnover Head" type, for L.P. and standard records, £3 19 2.
Marconi, Standard, lightweight Magnetic £1 15 10.
Marconi Matching Transformer, 7 6.
Goldring, Standard, lightweight, Magnetic, 29 6.

THE WIRELESS WORLD 3-VALVE SET

A Midget 3-valve T.R.F. Receiver for operation on A.C. mains, covering long and medium wavebands.
We are able to supply all of the components to build this set, as designed, and specified in the Feb. 1950 issue, including the drilled chassis, valves and moving coil speaker, etc., at the following prices:—
To construct complete chassis, less dial and drive assembly, £5 5 0. Ditto, including dial and drive assembly, £6.
To construct the complete set, including dial and drive assembly and cabinet, £7 3 6.
Overall size of cabinet is 7½in. × 9½in. × 11½in.
A reprint of the designer's article, giving Circuit and Assembly Instructions, is also available separately for 9d., together with a Practical Component Layout is included with each of above assemblies.

BATTERY CHARGER KITS

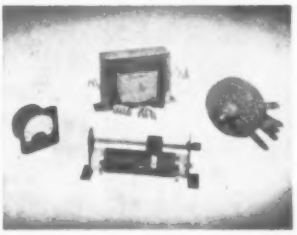

All Kits incorporate Metal Rectifiers, and are for use on A.C. mains 220-250 volts. All Kits include an easily followed Wiring Diagram.
For charging 6 v. battery at 1½ amps., £1 4 9.
For charging 6 volt battery at 1½ amps., with Variable Resistor and Meter, £2 9 3.
For charging 12-volt battery at 1½ amps., £1 9 3.
For charging 12-volt battery at 1½ amps., with Variable Resistor and Meter, £2 14 0.
For charging 6 or 12 volt battery at 3 amps., £2 1 0.
For charging 6 or 12 volt battery at 3 amps., with Variable Resistor and Meter, £3 8 3.

THE WIRELESS WORLD MODERN CRYSTAL SET

Designed for the Pre-selection of THREE STATIONS to suit local conditions, each station being received by the turn of a rotary switch. We are able to supply all components, including drilled chassis to build this new type of Receiver, to the designer's specification, as published in October issue, for 47 4 (including cost of selected coils).
A reprint of the designer's article (available separately for 9d.), together with a practical component layout, make the assembly very easy.

★ *Send 6d. P.O. for our STOCK LIST, it shows "hundreds" of Wireless*
When ordering please include

STERN RADIO LTD., 109

Tel.: CENtral

AN A.C. MAINS "ALL-WAVE SUPERHET" CHASSIS

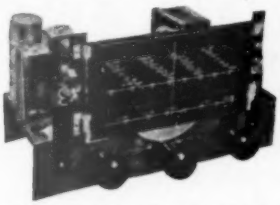

A completely assembled chassis for A.C. mains 200-250 volts, designed for good selective and quality reproduction, and serves as an ideal replacement chassis for that "old radiogram, etc."

It incorporates in addition to the three controls shown above a Tone Control and a Radio-Gram switch. These two are left on "floating leads" to enable them to be placed in any position on cabinet.

The set employs a modern 5-valve line up, and covers three waveb ands, 16-50, 190-550 and 800-2,000 metres. Flywheel tuning is incorporated.

Overall size of assembled chassis, 13½in. × 6in. × 8½in. high. Dialsize 8in. × 4½in., anattractive Dial Escutcheon Plate is supplied.

Price of complete chassis, wired and ready for use, **£14 19 6**.

A QUALITY "PUSH-PULL" AMPLIFIER KIT

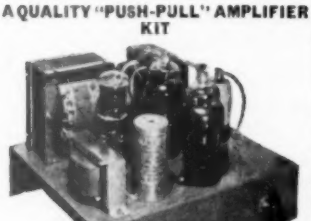

A Kit of Parts to build a 6-8-watt Push-Pull Amplifier for operation on A.C. mains 200-250 volts.

Incorporates a simple arrang ment to enable either a magnetic, crystal, or high-weight pick-up to be used.

A 10-watt Output Transformer is designed to match from 2 to 15 ohm speakers. Tone control is incorporated.

The overall size of the assembled chassis is 10in. × 8in. × 7½in. high. Price of kit, complete in every detail, including drilled chassisand valves, **£6 12 6**. Component layout is supplied.

Price of assembled chassis, supplied ready for use **£8 2 6**.

"PERSONAL SET" BATTERY ELIMINATOR

A complete kit of parts to build a Midget "Alldry" Battery Eliminator, giving approx. 69 volts and 1.4 volts.

This Eliminator is for use on A.C. mains and is suitable for any 4-valve Superhet Receiver requiring H.T. and L.T. voltage as above, or approx. to 69 volts.

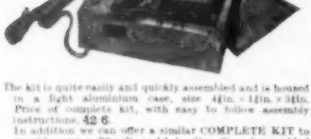

The kit is quite easily and quickly assembled and is housed in a light aluminium case, size 9½in. × 4½in. × 3½in. Price of complete kit, with easy to follow assembly instructions, **42 6**.

In addition we can offer a similar COMPLETE KIT to provide approx. 90 volts and 1.4 volts. Size of assembled Unit 7in. × 2½in. × 4½in. Price **47 6**.

You're SURE to get it at

STERN'S

ESTABLISHED 25 YEARS

TWO NEW DENCO ULTRA MIDGET SUPERHET COIL TURRETS

Both having a Rotary Turret Action

(a) The C.T.9 Turret consists of 4 STATION "PRESET" UNIT, from which any three Stations on Medium Waveband and one on Long Waves can be received by a turn of the Turret Switch.

(b) The C.T.10 Turret being a 3 Waveband Coil Pack, incorporating a fourth switch position providing for completely switching out Radio when using gram. The complete coverage is: Long Waveband 700 to 2,000 metres; Medium Waves 190 to 570 Metres and Short Waves 15 to 50 Metres.

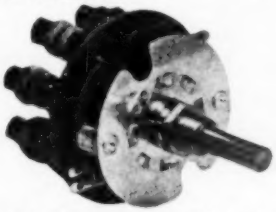

The outstanding advantages these units have over other similar units can be readily seen, the main features being:

(a) Neat and Compact, the overall size being only 2¼in. dia. × 1¼in. deep.

(b) Fitting is simplicity itself, each Turret having one hole fixing and requiring only four connections.

(c) The Rotary Turret design switches the actual Coils, which incorporate variable iron dust cores, on to positive contacts, thereby reducing stray capacities to the absolute minimum.

(d) They are supplied Factory wired and aligned and have been designed to operate with any conventional circuit arrangement of 465 kc/s, and due to their unique design are extremely sensitive and efficient.

Price: C.T.9 Turret less Coils, C.T.10 Turret, **52 -**.

A complete Receiver circuit together with leaflet containing all necessary data is included with each Turret. These can be supplied separately for **6d**.

THE FAMOUS W.B. "STENTORIAN" RANGE OF P.M. SPEAKERS.

Size.	Impedance.	Watts.	Price
2½in.	2-3 ohms	1	18 6
3½in.	"	2	19 6
5in.	"	2½	21 -
6in.	"	3	24 6
7in.	"	3½	23 6
8in.	"	5	32 6
9in.	"	7	36 9
10in.	"	10	44 6
12in.	15 ohms	13	£9

New Mins. Surplus Speakers. All 2-3 ohms 2½in. **15 -**; 3½in. **14 6**; 5in. **14 6**; 6½in. **16 9**; 8in. **18 -**; 10in., **25 -**; New Type Rola, 3in., **21 -**; 4in., **22 6**.

Output Trans. Midget 60-1 (or 90-1) 1in. × 1in. × 1¼in., **3 9**. 5-watt Multi-ratio, 12 tappings between 24-1 and 114-1 (some C.T.), **8 6**. Wharfedale, 12-watt, push-pull, multi-ratio, **25 -**. P.pull, 20-watt, multi-ratio, **37 6**, and many others.

New Electrolytic Condensers. Not Ex-Govt. All 450 500 volts: 8 mfd. (1¼in. × 1in. dia.) **3 -**; 8-8 mfd. (1¼in. × 1in.), **4 9**; 16-8 mfd. (1¼in. × 1in. dia.), **5 6**; 16-16 mfd. (1¼in. × 1¼in. dia.), **5 9**; 32 mfd. (1¼in. × 1¼in. dia.), **5 9**; 32-32 mfd. 350 volt, **5 9**; Cardboard Tubular 4mfd. 800 v. **3 6**; 8 mfd. 500 v., **4 -**; 16 mfd. 500 v. **5 9**. Can. Standard size all 500 volts, 4 mfd., **3 6**; 8 mfd., **4 3**; 8-8 mfd., **5 9**; 16 mfd., **5 6**; 16-16 mfd., **7 9**; 32 mfd., **6 9**.

Denco I.F. Liner, for accurately lining 465 K/c. and 1.6 m/c I.F. channels, and associate circuits. Battery operated small and completely self-contained. **49 6**.

Potentiometers. New, not Ex-Govt. 2K, 5K, 10K, 25K, 50K, 100K, 250K, 1, 1 and 2 meg. Price, less switch, **3 9**. Price with S Pole switch, **5 9**. Price with D Pole switch, **6 6**.

Surplus Potentiometers. All standard with extended spindles, 5K, 10K, 15K, 20K, 25K, 50K, 100K, ½, 4 and 1 meg., **2 -** each.

THE FAMOUS "SHAFTESBURY" HIGGS MIKE. Incorporating internal line Transformer having transformation ratio from ribbon impedance up to 500 000 ohms. Reduced from £10 10 0 to **£8 0 0**.

A special line to grid, 500 000 ohm. Transformer is also available.

Coils. Denco "Maxi Q" midget size, Litz wound on Polystyrene Formers, with adjustable iron cores. Available for Aerial H.F. and Oscillator 465 K.c. or 1.6 M.c., **3 11** each, or with reaction winding **4 9**. Denco Matched pair T.R.F. Coils for long and medium waves, **8 -** pr. Wavemith matched pairs of coils, for T.R.F. covering long and medium waves, **10 3** pr., or for Superhet covering Long, Medium and Short Waves, **12 3** pr. All types of Wearite "P" coils in stock at **3 -** ea.

Coil Packs. Osmor Midget Coil Pack. Size 3½in. × 2½in. × 1¼in., covering S., M. and L. waves. Coils wound on Polystyrene Formers with adjustable iron cores ensure efficient performance. Factory wired and aligned. Price, including full circuits for Superhet 465 K.c. Unit, **52 -** (incl. P.T.). This Osmor Coil Pack is also available for Midget Superhet BATTERY Portable sets, including a medium ready wound Frame Aerial. Price **54 2** (incl. P.T.). **Wearmouth** Midget 3½ × 2½ × 1¼in. covering S.M.L. waveb ands, for 465 Kc/s., employing Matched Iron Cored Coils on each w bband, **51 6**.

Wearite Pack, 4½ × 3½ × 1¼in., Type 706, covers two short w bands and medium w band and Type 703 covers short-medium-long waves. Both for 465 kc/s. Incorporates gram. position, and employs adjustable cored coils, **53 4**.

All of the above Coil Packs include Switching, Padding and Trimmer Condensers.

L.F. Chokes. Midget 10 henry 250 ohms 40 mA., **4 6**. 20 hnry. 250 ohm 60 mA., **6 6**; 20 hnry. 300 ohm 100 mA., **13 0**; 8 hnry. 30 ohm. 250 mA., **28 6**; 20 hnr. 350 ohms 120 mA., **15 6**; 9 hnr. 200 ohm. 120 mA., **6 6**; 18 hnr. 200 ohm. 250 mA., **26 6**.

I.F. Transformer 465 K.c. New well-known manufacturer's surplus, ½in. × ½in. × 1¼in. Iron Core, **9 -** each and also size 1in. × 1½in. × 2½in. at **12 9** per pair. Each have adjustable Iron Core. Denco Iron Core, 465 K.c. or 1.6 m.c., 1½in. × 1½in. × 3½in. **19 6** pair. New Surplus 465 K.c. Iron Core, 4in. × 1½in. sq., **10 -** pr.

Transformers. (a) Input 230 volt, output 200 volt 22 m.a., and 6.3 v., 9 amp., **11 -**; (b) Input 230 volts, output 350 volts 30 m.a., and 6.3 volts 1 amp., **13 9**.

E.H.T. Transformer. Prim. v. Sec. 5 Kv. and 4-volt tapped 2 volt, **59 6**. Do. but 4 Kv., **54 -**.

Heater Auto Transformers. (a) tapped 2 v. 4 v. 5 v. and 6.3 volts 3 amp., **0 9**; (b) 4 v. 3 amp. to 5 v. 2 amp. Reversible, **7 9**; (c) 4 v. 3 amp. to 6.3 v. 2 amp. Reversible **7 9**.

Filament Transformer. Inputs 230 volts, outputs 6.3 v. 1½ amp., **8 3**; 4 v. 1½ amp., **7 6**; Input 200/250 v. output 4 v. (C.T.), 1½ amp., 4 v. 2 amp., 6.3 v. 2 amp. **18 6**. Input 230 v., output 6.2 v. (C.T.) 4 amp., **17 6**.

Metal Chassis, substantially made with four sides, 7in. × 4in. × 2in., **3 11**; 9 × 5 × 2½in., **5 3**; 10 × 6 × 2½in., **6 -**; 10 × 7 × 2½in., **6 3**; 12 × 8 × 2½in., **7 9**; 14 × 9 × 2½in., **8 3**; 16 × 8 × 2½in., **9 -**.

Mains Transformers. All New Stock with Primaries tapped for 200-250 volts. Secondaries (a) 250-0-250 volt, 80 mA. 6.3 v. (tapped 4 v.) 4 amp. and 5 v. (tapped 4 v.) 2 amp., **22 6** (also available with 350-0-350 volt at **22 6**). Stern's 350-0-350 volt, 150 mA., 6.3 v. (tapped 4 v.) 4 amp. and 5 v. (tapped 4 v.) 2 amp., **41 6**; (c) 350-0-350 v. 250 mA. 4 volt 8 amp., 4 v. 3 amp., 6.3 v. (tapped 2 v.) 2 amp. and 6.3 v. 6 amp., **54 -**, and many other ratings.

Westinghouse Rectifiers. (a) H.T. 31. Rated 350-0-350 volts 100 mA., **35 -**; (b) H.T.32. Rated 350-0-350 v. 200 mA., **37 6**; (c) H.T.33. Rated 500-0-500 v. 200 mA., **50 -**.

Types. 14D1E36, **11 3**; 1GHT28, **12 6**; 16EHT56, **17 9**; 36EHT25, **13 10**; 36EHT35, **18 2**; 36EHT40, **20 6**; 36EHT45, **22 6**; 36EHT50, **24 10**; 36EHT60, **25 6**; 36EHT100, **29 5**; 38EHT13, **7 9**.

F Wave Bridge Rectifiers:

For charg ng 2, 4 or 6 volts at 1½ amps.	9 6
For charging 6 or 12 volts at 1½ amps.	12 6
For charging 6 or 12 volts at 3 amps.	21 6
For charging 6 or 12 volts at 5 amps.	26 10
For charging 12 or 24 volts at 3 amps.	25 9

A Variable Resistor for control of Charging Equipment (or Models) up to 3 amps., **17 9**, or for 1½ amps. **15 -**.

Meter Rectifiers. Westinghouse 250 micro amp., **12 9**; 1 mA., **11 9**; 5 mA. **6 9**.

Selenium Rectifiers. H.T. H wave 250 v. 50 mA., **6 6**; 250 v. 100 mA., **9 6**; 250 v. 170 mA., **15 6**.

Charger Transformers. Suitable for use with preceding Rectifiers. Each has input of 220 volts. Outputs:

(a) 24 volts tapped 15 v. 9 v. and 4 v. at 3 amps., **25 0**;
(b) 30 volts tapped 15 v. and 9 v. at 3 amps., **26 3**;
(c) 15 volts tapped 9 v. at 3 amps., **21 -**; (d) 12 volts 1½ amps., **12 3**; (e) 15 volts tapped 9 v. at 6 amps., **24 3**; 15 volts tapped 9 v. at 1½ amps., **15 9**; 12 volts 1 amp., **7 6**.

A Battery Charger Wiring Diagram is included with purchase of Charger Transformer and Rectifier.

Adjustable Mains Droppers. 1½in. dia. × 2½in. (a) 15 amp. 1,000 ohms, **5 -**; (b) .7 amp. 1,000 ohms, **4 3**; (c) 3 amp. 600 ohms, **5 -**.

Television. We have been a very comprehensive range of T.V components. The Viewmaster T.V Assembly Instructions showing Practical Layout and Price List in stock, price **5 6** (incl. post). We can supply all the specified components for the T.V. ex stock either by way of individual components or by the published stages.

"Q" Max Chassis Cutters. The quickest and most simple method of Chassis cutting consists of a die, punch and Allen screw.

To cut ¼in. dia. (B7G)	10 6
To cut ⅜in. dia. (B8a)	10 6
To cut 1in. dia. (Octal)	13 6
To cut 1¼in. dia. (English)	13 -
To cut 1½in. dia. (EF50)	14 6
Key for any of above	1 -

The new **Pyrobit Soldering Iron**, with instrument-tyrebit for use on A.C. or D.C. mains, **22 -**. Spare elements and bits always in stock.

Ex-Govt. complete set of **Moving Coil Headphones and Microphone** with headgear, **12 6**.

Components and many KITS OF PARTS for both Sets and Battery Chargers.
approx. cost of Post and Packing.

& 115 FLEET STREET, E.C.4

5814 and 2280

MONEY SAVING OFFERS

AN/APA-1 AIRCRAFT RADAR SETS. 11 valves: one 2X2, one 6G6G, one 6X5, seven 6SN7, one 6H6, one 3BPL Cathode Ray tube (in separate unit). Cables, etc. Absolutely brand new. £9 each, carr. 10/-. 40 available.

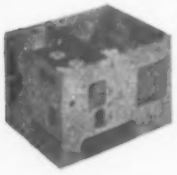

G.E.C. MR SERIES VHF RECEIVERS. Easily modified for 2 metres TV Sound or VHF RT. Typical valve complement. 1 Det 19, 1 L63, 1 H63, 1 D63, 3 KTW63, 2 RCA 954 acorns. We have about 200 of these sets and there are slight variations in the valve content. Some have 2 EF50 in lieu of 954s. All are basically similar and identical in appearance. Valve value alone exceeds £10 at to-day's prices. Designed for crystal control. (No crystals). Frequency 70-98 mcs. Grey enamel steel case. 10in. x 8in. x 7in. Weight 22 lb. The extremely interesting possibilities of these sets will be apparent to the discerning amateur. Outstanding value at 49/6d plus 5/- carr. Export orders specially invited. F.O.B. Liverpool.

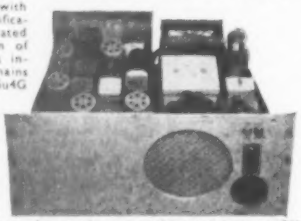

G.E.C. RECEIVER, with power pack. Same specification as MR. series illustrated above, with the addition of A.C. power pack. This incorporates heavy-duty mains transformer and choke, 5u4G rectifier valve, smoothing condensers, circuit breaker, 6in. P.M. speaker, H.T. switch, mains switch, jewel light, output attenuator. Front panel size 19 x 8in., grey enamel finish. Front to back width, 12½in.; weight, 60 lbs. First-class condition. Bargain price **6 gns.**, plus part packing and carriage 12/6.

JUNCTION BOX. Type 204 Ref. 10A/16002. Length 7¼ x 3 x 3in. 5 4-pin outlets, 2 2-pin outlets, grey enamel. Brand new. Weight 2 lbs. Useful round the shack. 2/- each, post 6d. As illus.

TELEVISION PRE AMPLIFIER. Makes an amazing improvement in both vision and sound reception in all fringe areas. Available for London (type A), Birmingham (type B), Holme Moss (type H).
Very small dimensions. Length, 4in. Width, 3½in. Chassis depth, 1¾in. Overall depth from top of valve, 4¼in. Fitted with EF50 valve. Ready for use. Power requirements 6.3 v. L.T. 200/275 v. H.T., Coax. Input and Output sockets. Unique value. **10/-**, post paid.

115S POWER PACK AND OUTPUT STAGE, complete with U50 and KT61 valves (not surplus). Black crackle case 12 x 8 x 5in., built-in 5in. P.M. speaker and phone jack. Operates on 200/250 v. A.C. Connections terminate in Jones plug which enables instant operation of receiver without any modifications whatsoever. Made to "Wireless World" specification. Matches in appearance with receiver. Price **£7/10/-**, plus carriage 3/6.

C 3 VOLTAGE CONTROL UNIT, Ref. No. 5U 1269. Contains on/off switch, pilot light, 6 bank fuse panel, 5 plus 3 mfd. Heavy duty fully filtered mains suppressor. Handsome case. Size 11 x 8 x 7½in. **10/-** each, carr. 2/6.

PAMPHONIC P.A. SPEAKERS. 10in. high flux unit (not surplus). Handsome maroon cellulose metal cabinet 20 x 9 x 13in., impedance 3 ohms. Price **55/-**, carr. 4/-.

CONTROL UNIT 454A. Brand new in sealed packing. Size 8¼ x 6¼ x 3¼. Fitted with 0-1 mA. meter, four 50k pots., 1 5k pot., 1 250k pot., 1 D.P. toggle switch, 3 jewel light jacks, 1 G.P.O. type 2 pole switch, 1 Yaxley 5-pole switch. Suitable as basis for a good test meter. Price **30/-**, carr. paid.

CAY TUNING UNITS 461SA. 800-1,500 kcs. Brand new in metal case with lid, 3 slow motion dials, 4 switches. Many fine components. **15/-**, or without case, **10/-**, carriage 2/6.

AMPLIFIER A1271. Brand new. Size 5in. cube. Fitted VR56 (EF36) D.P.D.T. switch. Relay. 2 mfd. potmeter, 2 trans. Neat case. Unique value. **10/-** each, post 1/6.

SATISFACTION GUARANTEED AS ALWAYS

2½d. STAMP WITH ALL ENQUIRIES, PLEASE

H.P. RADIO SERVICES LTD.

BRITAIN'S LEADING RADIO MAIL ORDER HOUSE

55 COUNTY ROAD, LIVERPOOL, 4

Established 1935. Telephone: AINTREE 1445.

EXPORT AND WHOLESALE ONLY

VALVES RECEIVING VALVES TRANSMITTING

TUBES CATHODE RAY

- Govt. Surplus & Regular Types
- Special purpose tubes
- No Dollar Expenditure
- Rapid Delivery from Ample Stocks
- One of the Largest in England

Also large stocks of

- P.M. Speakers 2½"—12"
- Mains Transformers
- Resistors :- ½, ¼ and 1 Watt
- Condensers:- Mica, Electrolytic, Oil, etc.

SEND US YOUR REQUIREMENTS

V.E.S. WHOLESALE SERVICES LTD.,

11, GUNNERSBURY LANE, W. ACTON, W.3.

Telephone: ACOrn 5027 (3 lines).

FREE! to those who wish to Qualify in any of these subjects*

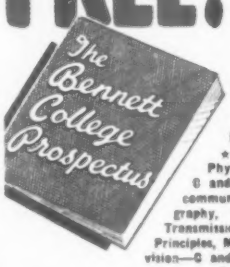

Applied Mechanics ★ Aviation Wireless ★ Draughtsmanship—Electrical or Mechanical ★ Electrical Engineering ★ Electrical Instruments ★ Electric Wiring and Lighting ★ General Cert. of Education ★ Mechanical Engineering ★ —M.I.Mech.E. ★ Mathematics ★ Physics ★ Radio Service Engineering—C and G Radio Servicing Cert. ★ Telecommunications C and G—Telephony, Telegraphy, Radio, Lines Plant Practice, Line Transmission, Telecomm. Practice, Telecomm. Principles, Mathematics for Telecomms. ★ Television—C and G Servicing Cert. ★ Telegraphy—P.M.G. Exams ★ Works Management All Commercial Subjects.

This book costs you nothing. But it offers you success in terms of your career.

TEAR OUT

★ BY POST, specialised Tutors in these and many other subjects give individual and understanding attention to Bennett College Students to whom books are free. Tuition is guaranteed until you qualify. State your subject. Send coupon for prospectus as it applies to you.

To the Governor, Dept. C.41

The BENNETT COLLEGE

Sheffield, England. Send me the free book on how I can qualify in .....(subject)

NAME .....

ADDRESS .....

..... AGE (if under 21).....

PLEASE WRITE IN BLOCK LETTERS

You can start on a BENNETT COURSE FOR ONLY 30/- and monthly instalments of 15/-

UNIVERSITY RADIO LTD.

Offer Guaranteed Used Equipment at Attractive Prices

Decca Long Playing Record Unit, in portable rexine case, as new £8 10 0
Acoustical 30 Watt Amplifier, with M.C. Mike and Gram. inputs A.C. 200/250 volts, complete in metal case, as new £16 10 0
Evershed & Vignolls 500 volt Constant Pressure Megger, in leather case, as new £19 10 0
As above, 100 volt £12 0 0
Cambridge Unipivot Galvanometer, patt. "L" 0-120 millivolts, 6in. scale, as new £8 0 0
Marconi-Ekco Signal Generator type TM2571, coverage 3.5 to 150 megs., A.C. 200/250 volts, with calibration charts, etc., perfect £40 0 0
Ex-W.D. TX RX, Type A Mlll, in portable attache case with built-in A.C. power pack, 100/250 volts or D.C. 6 volts, complete with key, etc., as new £12 10 0

B.S.R. Disc Recording Amplifier Type AR.15, in portable metal case, as new £30 0 0
Eversheds 500 volt Wee Megger in leather case £10 10 0
Avo 1948 Signal Generator, as new £12 10 0
Cossor Double Beam Oscilloscope, model 339A, as new £40 0 0
Taylor Valve Tester, model 47A with several extra valve adaptors, charts, etc., complete and as new £20 0 0
Avo Minor, A.C./D.C., as new £7 0 0
Eddystone 640, as new £21 0 0
Avo 1949 Capacity and Resistance Bridge, as new £8 0 0
Shaftesbury Ribbon Mikes, as new £6 0 0
Garrard Auto Changer, model RC70A, in portable rexine case, as new, 78 r.p.m. £13 10 0

General Electric (U.S.A.) Tube Checker, in portable case, 110 A.C., as new £11 10 0
E.D.C. Rotary Converter, D.C. 200-240 to A.C. 220-240, 50 cycles, 120 watts, in metal silencing case, complete with filter unit, as new £10 10 0
As above, 110 volts to 230 A.C. 100 watts with filter unit, as new £10 10 0
Avo Electronic Valve Tester, latest model, as new £28 0 0
Avo Wide Range Signal Generator, as new £23 10 0
We have in stock several of the latest models of Marconi Signal generators, etc.
Mullard Oscilloscope, Type G.M.-3152, as new £30 0 0
S.T.C. Oscilloscope, Type 74340, complete and as new £30 0 0
Hunts Resistance Capacity Bridge, model C.R.B., perfect and as new £10 0 0

WE NEED GOOD USED EQUIPMENT URGENTLY PLEASE SEND, BRING OR PHONE FOR OFFER

Collaro Bar-type Centre-driven A.C. Mixer Changer, as new £15 0 0
Taylor 65C Signal Generator, as new, A.C. 200/250 ..... £15 0 0
Taylor Valve Tester 45A, with charts, as new £15 0 0
Sound Mirror Tape Recorder, table cabinet model with spare tape, as new £55 0 0
Vitavox Bitone Speaker, as new, in polished wood cabinet listed at £60 our price £40 0 0
C.D.P. Disc Recorder, less amplifier, as new £21 0 0
B.P.L. Signal Generator, A.C. 200/250 volts £9 0 0
Taylor Windsor Oscilloscope, model 30A, as new £22 10 0
Trixette Portable Auto Changer (mixer type) with built-in amplifier and speaker, as new.... £27 10 0

B.C.348, with built-in A.C. power pack, as new £21 0 0
B.C.342, as new with all valves... £21 0 0
Cossor Impedance Bridge, mod. 3389, as new £19 10 0
M.C.R.I., complete with coils, power pack, phones, etc., as new £8 0 0
B.S.R. Disc Recording Unit, in portable case, as new £65 0 0
M.S.S. 1950 Disc Recorder, in portable case, complete less amplifier, as new £45 0 0
Sangamo Weston Industrial Circuit Tester, model 785 in portable case, as new £18 10 0
Ward Rotary Convertor, 12-volt D.C. input to 230 A.C. output, 50 c., 1 ph., with built-in radio filter unit, as new £11 10 0
Advance Signal Generator Type E2, as new £22 0 0

R.C.A. AR77E, complete and perfect, A.C. 220-240 ..... £27 10 0
Eddystone Model 556, perfect £24 10 0
R-1155, converted to mains A.C. 200-250 volts with conversion to 31 megs. by well-known firm Cost £33, our price, as new..... £19 10 0
National NC46 Receiver, A.C./D.C. 10 valves, 100-250 volts, 30 megs. to 550 kc/s., as new... £40 0 0
Janette D.C./A.C. Rotary Convertor, 220-240 D.C. to 220-240 A.C., 1 ph., 50 c., 250 watts, as new £10 10 0
TO CALLERS ONLY. Ex-W.D. U.S.A. Amplifiers Chassis, 20 watt, less valves, A.C. 220-240 volts, each £1 15 0
TO CALLERS ONLY. Pre-war Large D.C. Avo, working order £4 0 0
As above, A.C./D.C. £5 10 0

WE NEED AR 88's - BC 221's - 348's - 342's ALSO COSSOR DB'SCOPES 339A OR 3339 ETC.

Evershed-Vignoll's Wee Meggers, 250 volt, 0-10 megohms, perfect £5 10 0
Evershed-Vignoll's Megger Ohm-meters, battery operated 2 range, with leather case, as new £5 10 0
U.S.A. Flux-Meters, brand new, complete in leather case..... £11 10 0
Ex-W.D. Rotary Convertor, 24 v. D.C. to 230 A.C., 100 watts, 50 c., 1 phase, as new £5 0 0
E.D.C. Rotary Convertor, D.C. 220-230 to A.C. 220-230, 550 watts, perfect £12 0 0
Trix Portable Mobile 10-watt Amplifier, self-contained, battery operated, complete with microphone, speaker and 6-volt battery, as new £19 10 0

Pam 25 Watt Amplifier, with 2 Pam 8 watt speakers, A.C. 200 to 250 volts, complete with M.C. mike and floor-stand, as new £34 10 0
Latest Model Metro-Vic Minniscope, 2½in. tube, complete and as new £19 0 0
Marconi CR100, complete with all valves, perfect £22 10 0
Vitavox Latest Model 40-watt 16in. Speaker, 15 ohms P.M., as new £16 10 0
Vitavox K-12-20 15-ohm P.M. Speaker, as new £10 10 0
Vitavox 10-watt Pressure Unit, 15 ohms, as new £6 0 0
Vitavox 3-cell Tweeter, complete with 10-watt pressure unit 15 ohms, as new £11 10 0
Vitavox K-12-10 P.M. Speaker, as new £5 10 0

H.R.O. Receiver, ex-U.S. Navy, complete with 5 coils, 30 megs. to 550 kc/s., with H.R.O. power-pack on 2ft. 6in rack, as new £29 0 0
Eddystone 358X Receiver, with Eddystone Power-pack and 8 coils, 31 megs. to 100 kc/s., as new £21 10 0
Wharfedale Super 8csB/AL, as new £3 10 0
Hallicrafter Skyrider Pre-war Marine Receiver, A.C./D.C. 110-250 volts, 25 megs. to 550 kc/s, complete with 9 valves, perfect £16 10 0
W.B. Dual Concentric 12in P.M. Speaker, with built-on matching transformer, as new ... £11 10 0
R.C.A. AR88, model D. First class condition, complete with all valves £48 0 0
As above, model LF £50 0 0

★ We have a large selection of British and U.S.A. Valve Testers, Test-Meters and Signal Generators, etc. Your enquiries are welcome. S.A.E. please.

THESE ITEMS ARE ONLY A SMALL SELECTION FROM OUR STOCK OF EQUIPMENT. YOUR ENQUIRIES FOR ANYTHING THAT YOU MAY NEED WILL BE WELCOME. WE HAVE OTHER EQUIPMENT ARRIVING DAILY!

CASH OR CHEQUE WITH ORDERS. ALL ITEMS LISTED ARE CARRIAGE EXTRA.

22 LISLE STREET, LEICESTER SQUARE, LONDON, W.C.2

OUR BRANCH AT 39a (opposite) IS OPEN ALL DAY THURSDAY.

Phone: GERrard 4447, 8582 and 5507. Hours 9 to 6. Thursdays 9 to 1.

HENRY'S

5 Harrow Road, Paddington, W.2

PADdington 1008/9 and 0401

OSCILLOSCOPE TYPE 3BPI

We have pleasure in offering a 'scope designed primarily for simplicity and low cost at the same time giving reliable and consistent results. The Service engineer will find this an invaluable instrument due to its compactness, simplicity and speed of interpreting faults in radio receivers, checking transmitters, modulation, depth, etc.

SPECIFICATIONS

Amplifier : Max. Gain, Peak to Peak — .3 volts per cm. Frequency response 10 c.s.—100 k.c. Flat — 100 c.s. to 50 k.c. Time base : frequency range 5 c.s.—30 k.c.

Dimensions : 8½ x 6½ x 11½. Weight 17½lb. Black crackle finish.

PRICE : Brand New, £14.14.-, carr. pd.

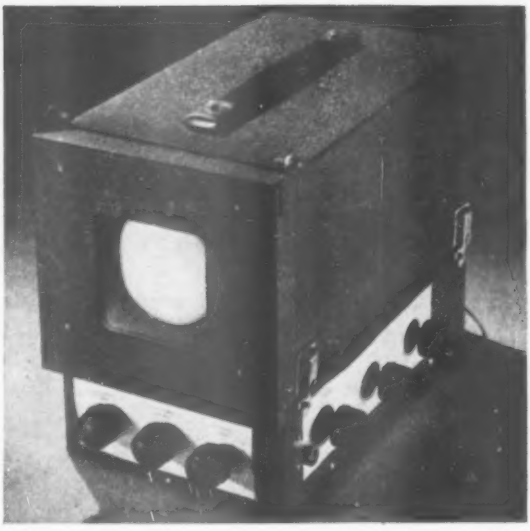

BOWTHORPE CONTINUITY METER

Dual scale 0-500 ohms and 100-200,000 ohms Moving Coil operated from 4½-volt internal battery. Size 6 x 3 x 4-in. Original price £8 19.-. OUR PRICE, BRAND NEW £4 4.-.

VIBRATOR POWER UNITS, 2 volt. As for Canadian 58 set. Completely smoothed, output 1.5 v. L.T. and 90 v. and 180 v. H.T. at 35 mA. Complete in grey metal box. Size 8 x 3½ x 4½in. 50.-.

POWER UNIT. Complete with 5Z4G, VU120, 1 mfd., 2,500 v. wkg. relay and 80 v. input trans., 15.-, new condition (post 1.6).

RECEIVER UNIT TYPE 159. Containing VR91, VR92, VR65 and 24 v. selector switch. New condition. 15.- (post 1.6).

RCA 931A PHOTO-ELECTRIC CELL AND MULTIPLIER. For facsimile transmission, flying spot telecine transmission and research involving low light-levels, 9-stage multiplier. Brand new and guaranteed, only 30.-. Data sheets supplied.

WALKIE-TALKIE TYPE 46. Complete with six valves, 2 VP23, HL23 DD, QP25, TP25 and ATP4, 8 aerial rods, I.F. trans., 1.6 Kc/s. In new condition but less transmitting components and coils removed by M.O.S., 35.-, carr. pd.

No. 38 "WALKIE-TALKIE" TRANS. RECEIVER. Complete with throat mike, 'phones, junction box and aerial rods in canvas bag. Freq. range 7.4 to 9 mc/s. All units are as new and tested before despatch. As supplied to Overseas Police Forces. £4 19 6, carriage 2.6.

PUSH-PULL OUTPUT TRANSFORMER. U.S.A. potted type primary 10,000 Ω, sec., 2 Ω, 8 Ω, 15 Ω, 15 watts. 21.-.

'SCOPE UNIT in steel case 6in. x 6in. x 15in. Containing VCR138/ECR35. 3½in. C.R.T. with mu metal screen. 2-EF50's, 2-EB34's. Pots and the usual resistors and condensers. Can be modified as a standard scope in a few hours and only requires external power pack (cost £3). Price 70.-. Conversion circuit 2.6.

6-VOLT VIBRATOR UNITS. Complete in black steel case 7½in. x 5½in. x 3½in. Output 200 volts, 40 mA. Price 22.6.

2-VOLT BATTERY RECEIVERS—190-200 Mc/s. Complete with 2 valves. Unused. 14.-. Easily modified for 144 Mc/s.

ARMY PRACTICE MORSE KEY AND BUZZER SETS. New and boxed. 6.6.

RF24 UNITS. Converted to 28 Mc/s Band. Variable tuned with 100-1 geared S.M. Dial. Complete with plug and leads for immediate use. £3.

MAINS TRANSFORMER. Input 200-240 v. Output 350-0-350 or 250-0-250 volt, 80 mA, 4 and 6.3 v. 4 a. and 4 and 5 v. 2 a. Price 21.3. Input 200-240 v. Output tapped 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30 volts, 2 amps. 21.3. All with one year's guarantee.

NEW MINIATURE VALVES. DL72, CK512AX 9.-; 6AG5 10.6; 9001, 9002 7.6; 9003 6.6.

D.P.D.T. RELAYS. Operate at 200-300 volts D.C. 6 mA. 13.-. D.P. make and break 8.6. We can supply any type of voltage and contacts at varying prices.

EXIDE P.O.2 UNSPILLABLE ACCUMULATORS. 4¼in. x 3¼in. x 2¼in., 11 a.h., 19.6.

TYPE 18 Tx. CHASSIS, partly dismantled but can easily be put into working order, less valves, 16.6.

NEW SELENIUM RECTIFIERS. F.W. 12.6 volt 3 amp., 14.6; 4.5 amp., 26.-; ½ amp., 5.6; 250 v. 120 mA., H.W., 9.6.

All the above Post Paid from: Dept. W.W.,

The RADIO & ELECTRICAL MART

253B PORTOBELLO ROAD, LONDON, W.11

Phone: PARK 6026

UNIVERSAL ELECTRONICS

We carry a wide range of Guaranteed New and Used High Quality Communication and Test Equipment, etc.

B.S.R. Audio Oscillator L050A, good condition	£35 0
R.C.A. AR77s from £35, AR88s from	£55 0
HALLICRAFTERS, S24, £30; S38, £25; S20R, £27; SX43	£80 0
EDDYSTONE, 640, £22; 740, £35; 750	£50 0
MARCONI CR100	£26 0
NATIONAL NC200, £65; HRO Seniors from	£35 0
AVO Test Equipment, Model 7, as new, £15; AVO Minors	£6 10
Model 40, £13 10.-; All wave Signal Generator	£11 0
TAYLOR Oscilloscope Model 30A, as new	£24 0
COSSOR Double Beam Oscilloscopes from	£35 0
BC221s from	£22 10
B-2 Transmitter Receiver in working order	£12 10
BC348s and **BC342s** from	£17 10
R.M.E. Pre-selector in good condition	£11 0
MARCONI Signal Generator, type 60	£45 0

MEGGERS 500 v. £10; Bridge types in stock.

VHF Test Equipment in stock; enquiries invited.

In addition to the above equipment we also have in stock:—Tape Recorders, Marine and Aircraft radio and many items of P.A. equipment.
Your enquiries will be attended to promptly. S.A.E. please.

Shop hours: 9.30 a.m. to 6 p.m. Thursdays to 1 p.m.

OUR ONLY ADDRESS Telephone: GERrard 8410

27 LISLE STREET,
LEICESTER SQUARE, LONDON W.C.2

CLYDESDALE

Bargains in Ex-Service Radio and Electronic Equipment

NO. 9 SET MK. 1 RECEIVER UNIT, WITH POWER SUPPLY UNIT

A Ten valve 7 ARP3, 2 12SC7, 12Y4, Band-Pass, superhet Receiver frequency range, 2 to 3 mcs., with built in calibrator, switched H.T. and "S" meter, HF and LF gain, R.F.O., etc., etc.
Separate Power Unit operation from 12 v. D.C., 115 v. A.C. or 230 v. A.C. 0Z4 cold cathode rectifier, with spares kit, all valves, Aerial, Insulators, Headphones.

CLYDESDALE'S PRICE ONLY **£10 0 0** CARRIAGE PAID

W.S. 18 RECEIVER SECTION

Superhet Chassis, range 6-9 mc/s (50-33.3 metres) with 4 valves 3 ARP 12, etc., etc., on 8½ × 5½ × 1¼in. Chassis, front panel 9½ × 5½in.

CLYDESDALE'S PRICE ONLY **25 -** EACH POST PAID

Circuit 2/3.

Also available with partly stripped (M.O.S.) Tx-section, no valves or meter, in metal carrying case. Dimensions 11 × 10 × 15in.

CLYDESDALE'S PRICE ONLY **37 6** EACH CARRIAGE PRICE

Circuit for 4/6.

FOR EXPORT ONLY WIRELESS SET NO. 38 MK. 2 BRAND NEW

A haversack type transceiver range up to 5 miles. Frequencies 7.7 to 9 mc/s. 5 Valves, 4 APR12, ATP4, operated from dry batteries. H.T. 120 v., L.T. 3 v. (not supplied) complete with headphones, junction box, spares, satchel and instruction card.
4 complete units packed in wood case 57½ × 14 × 14in.

PRICE ON APPLICATION

THE R.3601 RECEIVER UNIT

A 13 valve (6V6, VU39A, 4 SP61, 4 EA50, 2 EF54, EF50, EC52, VU111) dual chassis radar receiver for 225 Mc/s. with 13 Mc/s. I.F. Strip, R.F. Section, high cycle power section, antenna switch, relay, etc., etc. In metal case 18 × 9 × 9in.

CLYDESDALE'S PRICE ONLY **£4 12 6** CARRIAGE PAID

R.3170A RECEIVER UNIT

A 16 valve (2 EF54, EC52, 8 EF50, 2 EA50, CV138, VU111 5Z4). Radar Chassis with 30 Mc/s. I.F. Strip, etc., original range about 200 Mc/s, suitable for T.V. conversion. In metal case 18 × 9 × 9in.

CLYDESDALE'S PRICE ONLY **£4 12 6** CARRIAGE PAID

NEW LIST NO. 8

Giving details and illustrations of ex-service items and cancelling all previous lists and supplements.
NOW READY—PRICE 1/6. Price credited on first purchase of 10/- or over.

12 VOLT MOBILE AMPLIFIER

A compact 4 valve (2 EL33, EF36, EC21) 3 stage Amplifier Output 15 watts. Rotary generator power unit, input 12 volts 96 watts. Provision for 10 ohm L.S., M.C. Mic., and Gram. In metal cabinet 13 × 9 × 9in.

CLYDESDALE'S PRICE ONLY **£9 9 0** CARRIAGE PAID

METAL (MINE) DETECTOR NO. 4

Of Coln. design and construction, using 1T4 pentodes. Comprising TC Amplifier, Search Coil, Sweep Pole, Control Box, Headphones, Test Unit and Rucksack. Complete less batteries in fitted transit case.

CLYDESDALE'S PRICE ONLY **£6 19 6** CARRIAGE PAID

HEADSET HS-30

With cord CD-874 and jack plug PL-55 miniature earpieces (50 ohms each) fit into ear and are rubber padded for comfort. U.S.A. made. 100 ohms impedance overall.

CLYDESDALE'S PRICE ONLY **21 -** PER PAIR POST PAID

U.S.A. THROAT MICROPHONES

Pair carbon Button throat pieces with strap, lead and plug

CLYDESDALE'S PRICE ONLY **5 -** PAIR POST 6d.

THROAT MICROPHONES

Pair electro-magnetic throat pieces (7.5 ohms each) with strap, lead and jack plug. Ref. ZA13935.

CLYDESDALE'S PRICE ONLY **3 6** POST 6d.

MULTICORE CABLE

8 core screened and P.V.C. covered 1/9 per yd. post 3d.
6 core rubber covered, 1/6 per yd. post 3d.
2 core metal braided, 6d. per yd. post 3d.
Metal Braided sleeving 3 mm. 1 yd. long, 3 for 1/- post 3d.

COMPONENTS FOR THE CONSTRUCTOR. MANUFACTURER'S SURPLUS

8 INS. P.M. LOUDSPEAKER

With transformer, standard chassis trim. Brand new in original carton.

CLYDESDALE'S PRICE ONLY **17 6** EACH POST PAID

3 GANG VARIABLE CONDENSER

Cap. per section. 0.0005 mfd. Size: 4 × 2¾ × 2¼in. with standard spindle.

CLYDESDALE'S PRICE ONLY **7 6** EACH POST 9d.

2 GANG VARIABLE CONDENSER

Cap. per section. 0.00035 mfd. Size: 2¾ × 2¼ × 1¾in. with standard spindle.

CLYDESDALE'S PRICE **7 6** EACH POST 9d.

CHOKES

25 henries, 60 mA. 200 ohms D.C. with half-shroud drop thru' chassis. Size 2¼in. H. × 3 × 2¼in.

CLYDESDALE'S PRICE ONLY **6 6** EACH POST 6d.

20 henries, 120 mA. 500 ohms D.C. with half-shroud drop thru' chassis. Size 3in. H. × 3 × 2¼in.

CLYDESDALE'S PRICE ONLY **12 6** EACH POST PAID

RADIO CABINET

A handsome walnut finish wooden cabinet well ventilated with removable back panel.
External dimensions: Ht. 9½ × 17 × 8in. approximately
External appearance facing cabinet.
Speaker opening right side. Ht. 5¼in. Lth. 4¼in.
Dial opening, left side Ht. 3¼in. Lth. 5¼in.
Internal dimensions: Ht. 8¼in. × 7¼in. approximately.

CLYDESDALE'S PRICE ONLY **25 -** EACH POST PAID

RADIO CABINET

Smart Plastic Cabinet, with ornamental speaker grill and dial apertures, top front centre.
Colours, walnut, mahogany, white and black
External dimensions: Ht. 12 × 7½ × 6¼in.
Internal dimensions: Ht. 11 × 6¾ × 4¾in.

CLYDESDALE'S PRICE ONLY **15 -** EACH POST PAID

TRANSFORMERS
MAINS TRANSFORMER. TYPE 5084

Primary: 200, 230, 250 volts, 50 cycles.
Secondary: 0-350-0-350 volts, 200 ma. 6.3 volts, 4 amps. 5 volts, 4 amps.
Dimensions: 4½ × 4¼ × 3¾ins. Shrouded. Weight 10lbs.

CLYDESDALE'S PRICE ONLY **49 6** EACH POST PAID

OUTPUT TRANSFORMER TYPE AFS084 IA. 24 WATTS

Primary: 6600 ohms C.T.
Secondary: 3.5, 5, 7.5, or 15 ohms.
Dimensions: 3½ × 2¾ × 3¼in. Shrouded. Weight 3lbs.

CLYDESDALE'S PRICE ONLY **29 6** EACH POST PAID

CONDENSERS

Tubular waxed, (pitch covered) 600 V. wkg.
0.05, 0.02, 0.01, 0.005, 0.0025, 0.001 Mfd. 9d. each
400 V. wkg. 0.05, 0.02, 0.01, 0.005, 0.0025, 0.001, 0.0005, 0.0025, 0.0015, 0.001, 0.0005 Mfd. 6d. each
Ceramic Tubular, 180, 120, 100, 97, 82, 68, 56, 47, 39, 33, 27, 15, 12, 8, 5.6, 4.7, 3.9 pf. 6d. each
Silver Mica, 2%, 6000, 4850, 4000, 1000, 500, 300, 250, 230, 220, 150 pf. 9d. each
5000, 2000, 564, 450, 432, 350, 175, 135, 75, 47, 43, 30, 20, 10, 8 pf. 6d. each

RESISTORS

Wirewound fixed & watt, 80, 35 ohms 1/6 each
3 watt, 2.5K., 2.2K., 1.8K., 1.5K., 320, 200, 150, 140, 33 ohms 1/- each
1.5 watt, 1.5K., 1.2K., 1K., 200, 150, 33 ohms 6d. each
70/80 ohms. CO-AXIAL CABLE. Dia. 5 mm. 7/0076, polythene insulation, ideal for T.V. Aerials. Price 1/3 per yard. Minimum Quantity 10 yds. or 100 yard coils at £5 each.

FOR THE LOW COST "PRACTICAL TELEVISION" RECEIVER.
INDICATOR UNIT TYPE 62, IN MAKER'S ORIGINAL CASE

CLYDESDALE'S PRICE ONLY **£5 9 6** CARRIAGE PAID

Also available in used, fair condition.

CLYDESDALE'S PRICE ONLY **79 6** EACH CARRIAGE PAID

E.H.T. TRANSFORMER

Primary tapped 230-250 V. A.C. Sec. (1) 3000 V. tapped 2500 V. Sec. (2) 4 V. 1A Sec. (3) 4 V tapped 2.3 V. 1A

PRICE. POST PAID 45 -

MAINS TRANSFORMER

Primary tapped 200-250 V. A.C. Sec. (1) 350-0-350 V. 160 ma. Sec. (2) 6.3 V. 3A. Sec. (3) 6.3 V. 6A. Sec. (4) 5 V. 3 A.

PRICE. POST PAID 55 -

Also available potentiometers, resistors, condensers, etc.

I.F. A.F. AMPLIFIER UNIT R.1355

CLYDESDALE'S PRICE ONLY **67 6** EACH CARRIAGE PAID

THE SCPI CATHODE RAY TUBE. IN ORIGINAL CARTON

A 6 inch electrostatic tube. Heater vig. 6.3 v. 0.6 A. H.T. 4,000 V. max. intensifier gives high definition. Trace colour green. Short persistance.

CLYDESDALE'S PRICE ONLY **£1 15 0** POST PAID

MOVING COIL METERS
AMPMETERS

E784 Range 0-1 Amp. 2¼in. Round flush mtg., drilled flange Price, Post paid 12 6 each
E785 Range 0-10 Amps. 2¼in. Round flush mtg., plug-in. Price, Post paid 12 6 each

D.C. VOLTMETERS

E729 Range 0-750 volts, 200 ohms per volt Price 25 - each
E730 Range 0-1500 volts, 250 ohms per volt Price 26 - each
E731 Range 0-5000 volts, 200 ohms per volt Price 27 6 each
All 2¼in. Round flush mtg. drilled flange. POST PAID

GLASS DOMED INSULATOR 156

Ref. 1648 std. 1/2B/567. With metal clamping ring. Insulated bush with rubber washer, top dome enables insulator to be water proof by tightening.

CLYDESDALE'S PRICE ONLY **7 6** EACH POST 1/-

L.T. CHOKE, ADM. AP.65069

0.5 Henries 0.1 ohms at 2.5 amps.
Made by Parmeko, Dim. 3 × 2¾ × 1¾in. 4 hole fixing

CLYDESDALE'S PRICE ONLY **3 6** EACH POST 9d.

ELECTRONIC IGNITION TESTER

Type W.E.D. Pat. 863962, made by English Electric in Original Maker's case.
A Cathode Ray Tester employing an entirely new technique in ignition testing of internal combustion engines. Enables the electrical performance of the entire ignition system to be observed on the screen of the Cathode Ray Tube while the engine is running. Will operate from 6, 12 and 24 volts D.C. or 230 v. A.C. Built into a black crackle case, with hinged front and carrying handle, dim. 15½ × 8½ × 11½in.

CLYDESDALE'S PRICE ONLY **£35 0 0** CARRIAGE PAID

220 VOLT D.C. CHARGING BOARD

For charging 1 to 60 cells at 5 amps. Made by Bepco, Canada, with 100 ohm resistance, 5A meter, 220 v. controls, fuses and switches, all mounted on metal case 21½ × 17½ × 4½in. Well ventilated with rings for wall mounting.

CLYDESDALE'S PRICE ONLY **£2 5 0** CARRIAGE PAID

BATTERY CHARGER

Rectifier Type 42A. Ref. 10148/1630. A compact battery charger, output 4 amps at 6 or 12 volts D.C. Input 230 v. AC 50/c with ampmeter, removable fuses, control switch for each circuit, input and output points, contained in well ventilated black crackle metal case for wall or bench mounting.

CLYDESDALE'S PRICE ONLY **£5 19 6** EACH CARRIAGE PAID

POWER SUPPLY UNIT NO. 7

Ref. ZA17571.
For charging 6 volt Accumulators by hand. Designed for the W.S.C.1.—could be used for many other purposes. Consists of a stout metal case, dim. 17 × 10½ × 7½ins. with detachable lid, containing hand driven generator, with gear mechanism which delivers 6 volts D.C. at 4 amps., also 6 volt cut out and battery clips.

CLYDESDALE'S PRICE ONLY **£2 5 0** EACH CARRIAGE PAID

VIEWMASTER TELEVISION

Build it yourself Circuit with templates and all data. London, Sutton Coldfield, Holme Moss or Kirk-o-Shotts. Priced 5 - each
All components normally in stock. Subject to manufacturers production.
Coils for All Areas including:
Holme Moss and Kirk-o-Shotts 2 - each
Set of Coils Filters and Choke 30 - each
Post Paid.
Large and varied selection of Books on Radio and Television always available. Also Circuits of Ex-Service Units.

Order direct from —

CLYDESDALE SUPPLY CO. LTD. 2 BRIDGE STREET GLASGOW . C5

Phone: South 2706/9 Branches in Scotland, England and Northern Ireland

TO HAMS & DEALERS

WE WANT TO BUY

AMERICAN SURPLUS EQUIPMENT OF EVERY KIND

FOR RADIO HAM SHACK—
NEW YORK'S LEADING DEALERS

RECEIVERS • TRANSMITTERS
TEST SETS • SIG GENS
TELETYPE EQUIPMENT
EVERYTHING ELECTRONIC

We are interested in any quantity, from one upwards. 'Phone us immediately, transfer charge.

ALTHAM RADIO CO BRAZENNOSE ST
MANCHESTER 2 *Tel.: DEAnsgate 5387*

MICROPHONES

A NEW BOOK PUBLISHED
FOR "WIRELESS WORLD"

Written by the Staff of the Engineering Training Department, B.B.C. This book, originally produced for use in training B.B.C. engineers, has now been made available for general publication.

The requirements for microphones in a broadcasting studio are set out in an introductory chapter, and this is followed by chapters on the laws relating to sound waves and their behaviour. The design and characteristics of various types of microphone are then described, together with full details of the ribbon, moving-coil, crystal and condenser instruments used in B.B.C. studios during recent years.

The book will be invaluable to all concerned with microphones in sound engineering, in which field the Corporation has gained unique experience over many years.

ASSOCIATED ILIFFE TECHNICAL BOOKS

15s. net *By post 15s. 5d.*

Obtainable at all booksellers or direct from:—

ILIFFE & SONS LTD., DORSET HOUSE, STAMFORD STREET, LONDON, S.E.1

AVOID BOTTLENECKS!

We hold large and comprehensive stocks of components and units. Contact us; we may solve your production problem.

CONDENSERS. Silver Mica, Tubular, Mansbridge.
CRYSTALS. American FT241 & FT243 Etc.
HEADPHONES. DLR1, DLR5, IBA5 Etc.
METERS. Thermo, Moving Coil, Moving Iron.
RESISTORS. High Stability, Carbon, Wire wound.
VOLUME CONTROLS. Morganite Types H, M, LH, BJ. Colvern, 1-5 watts.
PLUGS & SOCKETS. Pye Patterns, Belling, etc.

Wholesale and Export Only.

ANDERS RADIO LTD.
167, HAMPSTEAD ROAD, LONDON, N.W.1.
EUS 1639 EST. 1928

WALTON'S OF WOLVERHAMPTON

60 VOLT STANDARD H.T. BATTERIES. 6/-, post 1/-, 2 for 11/-, post 1/6. **72 VOLT + 1½ VOLT.** Layer Type. 6/-, post 9d.
2 WAY TELEPHONE SETS. Consisting of 2 Telemicrophones and approximately 12 yds. of twin cable. 10/6 each, post 1/6.
A.F.3. INTERVALVE TRANSFORMERS. 3/6 each, post 9d.
25 WATT "COLLINS" MODULATION TRANSFORMERS. Ratio 1-1, Impedance 6,000, New, boxed. 15/- each, post 1/-.
4,000 OHM SUPER SENSITIVE PHONES. By S. G. Brown, complete with special ear-pads, lead, and plug. Brand new in boxes. 15/- each, post 1/-.
POWERFUL 24 VOLT CAMERA MOTOR. A.C. or D.C. 15/- each, post 1/6.
HEAVY DUTY 8in. EXTENSION SPEAKERS, 25/- each p. 1/-
2 VOLT ACCUMULATORS. Approx. 14 A.H. 5/- each, post 1/6.
AERIAL RODS. 3 Tapered rods, screwed joints, assembled length 12ft., complete in fibre case. The finest rods made. 10/6 each, passenger train, 2/6.

SEND S.A.E. and 3d. FOR SPECIAL LIST.

WALTON'S WIRELESS STORES, 48, STAFFORD STREET, WOLVERHAMPTON.

ALL SECTIONS OF THE ELECTRONIC INDUSTRY IN THE U.K. AND OVERSEAS ARE INVITED

To send for our 1952 Wholesale Price List, giving full details of A.W.F. Loudspeaker replacement Cone assemblies, for quick, cheap, repairs in your own Workshops. A.W.F. Chokes and Transformers for all Electronic replacements. A.W.F. Repairs to Speakers. Transformers, Vac. motors, Gram motors, etc., Current stocks of Tungsram and other valves. T.C.C. and Dubilier capacitors, Erie Resistors and Pots. Brass B.A. Screws and nuts. Taflon Cabinets and all the specified components for View Master and Electronic Engineering Televisors, and hundreds of bargain lines. Viewmaster envelopes, etc., for Kirk O' Shotts now available. We specialise in giving overseas dealers rapid service, and have full experience of all export packings.

SEND YOUR TRADE CARD (Trade Only Supplied), with 3d. Inland U.K. or 2/- Overseas Air Mail (stamps or P.O.).

A.W.F. RADIO PRODUCTS
TATLER CHAMBERS THORNTON ROAD
BRADFORD YORKS
TEL. 24008 GRAMS & CABLES "TESTUBE"

DEALERS & SERVICE ENGINEERS

HOME AND OVERSEAS TRADE

Large stock of servicing accessories for Radio and Television Receivers.
COILS — POTENTIOMETERS — RESISTORS — LOUDSPEAKERS
CONDENSERS — MAINS TRANSFORMERS — CHOKES
Many other useful, low-priced items.
Send for our monthly bulletin, which always announces special bargain lines.

Trade only supplied.

VES
V.E.S. WHOLESALE SERVICES LTD.,
11, GUNNERSBURY LANE, W. ACTON, W.3.
Telephone: ACOrn 5027.

MAINS TRANSFORMERS

These transformers are all famous radio manufacturers' surplus and are fully interleaved, impregnated and guaranteed.

Primary 200-250 v. P. & P. on each 1/6 extra.

350-0-350, 100 mA., 4 v. 4 amp., 4 v. 2 amp., upright or drop-through, 16/-.

300-0-300, 100 mA., 6 volt 3 amp., 5 volt 2 amp., 17/6.

320-0-320, 120 mA., 6 volt 4 amp., 5 volt 2 amp., 25/-.

350-0-350, 150 mA., 6 volt 3 amp., 5 volt 2 amp., drop-through or upright mounting, 27/6.

250-0-250, 100 mA., 6 v. 3 amp., 4 v. 3 amp., 4 v. 3 amp., 17/6.

Drop thro', 350-0-350 v. 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., 14/6.

Semi-shrouded, drop-thro' or upright mounting 280-0-280, 80 mA., 4 v. 6 amp., 4 v. 2 amp., 12/6.

Auto-wound, H.T. 280 volts at 360 mA., 4 v. 3 amp., 2 v. 3 amp., or 6 v. 3 amp. Separate 4 v. 3 amp. rectifier winding (upright or drop-through), 10/6.

350-0-350, 120 mA., 4 v. 6 amp., 4 v. 3 amp., drop-through, 21/-.

Auto-transformer, various combinations of voltages including 110 v. 70 watt, and 3/4 volts windings at 1 amp., 2 volt 1 amp., drop-through or upright mounting, 10/6.

Heater Transformer, Pri. 200-250 v., 6 v. 1½ amp., 6/-; 2 v. 2½ amp., 5/-. P. & P. each 9d.

ELECTROLYTIC CONDENSERS

Ex-Govt. 8 mfd. 500 v. wkg., size 3½ × 1¼in., 2 for 2/6, post paid.

P.M. SPEAKERS

	with trans.	less trans.
2½in.	—	13/6
3½in.	—	11/6
5in.	15/-	12/6
6½in.	14/6	11/6
8in.	17/-	14/6

10in. M.E. Speaker Field Coil, 1,100 ohms, speech coil 2-3 ohms, 17/6.

P. & P. on each of the above 1/- extra.

Constructor's Parcel, comprising chassis 10½ × 5½ × 2in. with speaker and valve holder cut-outs, 5in. P.M. speaker with transformer, twin gang with trimmers, pair T.R.F. coils long and medium iron cored four valve holders, 20K volume control and wave-change switch. Post paid 21/-.

Constructor's Parcel, comprising 4-valve T.R.F. chassis, 8½ × 4 × 1¾in., 3 VR65A (using one as an output valve), heater trans. pri. 200-250, choke, OP trans. 3 valve holders, pair medium-wave coils, 47K. pot, twin gang, and scale, 20/-, post paid.

Volume Controls, by famous manufacturer. Long spindle less switch, 5 K., 50 K., 500 K., 1 meg. 2/6 each. P. & P. 3d. each.

Frame Blocking Oscillator Transformer, 4/6.

D. COHEN

RADIO & TELEVISION COMPONENTS

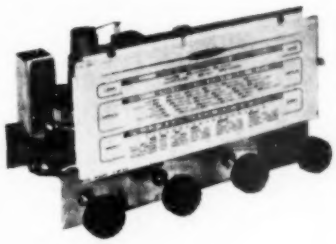

RADIOGRAM CHASSIS. A.C. Mains 230-250 v. Manufactured within the last six months. Four controls, tone, on-off, volume, wavechange, gram switch and tuning. Coil pack by Weymouth or Allen. 0.1 mfd. condensers etc., by T.C.C., pots by Erie, mains transformer, gang and electrolytics by Plessey, 470 Kc. I.F.s by Wearite. Valves by Brimar, 7S7, 6Q7GT, 6V6GT, 6X5GT and Osram KTW63. Wave-range 15-50, 180-550 and 900-2000 metres. Size of scale 11½ × 4½in. approx. Size of chassis 12½ × 6½ × 2½in. Mains lead for gram motor, extended A.E. sockets. 2 pilot bulb holders and 2 Osram bulbs. Knobs not included. **THESE CHASSIS ARE BRAND NEW. £7/10/-** post paid.

PERSONAL PORTABLE CABINET in cream-coloured plastic; size 7 × 4½ × 3in. Complete 4-valve chassis scale and 3 knobs. Takes miniature 90 v. and 7½ v. batteries. **9/-.** Post Paid. 2½in. P.M. Speaker to fit above, **13/6.** Miniature output transformer **5/-.** Miniature wave-change switch **1/6.** Miniature 1-pole 4-way used as Volume and Off **1/6.** 4 B7G valve holders, **2/-.** Midget twin gang ½in. dia., ½in. long and pair medium and long-wave TRF coils ½in. long × ½in. wide; complete with 4-valve all-dry mains and battery circuit **8/6.** Condenser Kit, comprising 11 miniature condensers, **3/6.** Resistor Kit, comprising 12 miniature resistors, **3/-.**

THREE WAVE-BAND COIL PACK, iron-cored coils, 16-50, 180-550 1,000-2,000 metres I.F. frequency 465 Kc. Size, 4½ × 1½in. × 2½in., **24/-,** post paid. Double-ended perspex trimming tool given free with each pack.

CONSTRUCTOR'S PARCEL comprising 5-valve superhet chassis with transformer I.F., and valve holder cut-outs, size 18 × 5½ × 2½in., with L.M. & S. scale size 7 × 5in. Back plate, two supporting brackets, drive drum pointer, two-speed spindle, spring, three pulleys and five international Octal valve holders, **11/6,** post paid.

N.B.—To the purchasers of this parcel. Coil pack at the reduced price of **17/6,** post paid.

P.M. FOCUS UNIT. For any 9in. or 12in. tube, except Mazda 12in., state tube, **12/6.**

P.M. FOCUS UNIT. For Mazda 12in., **15/-.**

Similar to the above but with front adjustment **2/6** extra.

MAINS or BATTERY SUPERHET PORTABLE COILS. Comprising medium-wave frame aerial and long-wave loading coil, used as aerial coils. Midget iron-cored screened L.M. osc. coils., complete with circuit I.F. frequency 465 Kc., **9/6.**

METAL RECTIFIERS, 250 v. 60 mA., latest midget Selenium type, **6/6** post pd.

OUTPUT TRANSFORMERS. Standard type 5,000 ohms imp., 2 ohms speech coil, **4/9**; Push-Pull 6 v. 6 matching 10-watt 2-ohms speech coil, **6/9.** 42-1 speech coil 2 ohm with extra feed-back winding, **4/3**; Miniature 42-1 2 ohm speech coil, **3/3.**

SET OF 3 BROWN KNOBS marked "wave change," "tuning," and "volume," **1/6.**

6-pin 6-volt synchronous vibrator	8/6
6-volt standard 4-pin vibrator	8/6
Vibrator transformer 250-0-250 80 mA. 6 volt Pri.	8/6

EXTENSION-SPEAKER CABINET

Polished in a pleasing light and dark shade. Complete with an 8in. P.M. Rubber feet and back. Size 10in. × 10in. × 4½in., **22/6,** post paid.

TELEVISION MASKS

White Rubber. 9in. with glass, **10/6.** White Rubber, 12in. with glass, **15/-.** 15in. white rubber mask, soiled, **12/6,** plus 1/- P. & P.

All-Dry A.C. Mains Supply Unit, size 3¼in. long × 2¼in. wide × 1¼in. deep. We can supply a complete all-dry circuit, using the above Midget Components to incorporate the above Power-Unit, **19/6,** post paid with circuit.

Midget Bakelite Cabinet. 7in. × 5¼in. × 5in. c/w 5-valve S.h. chassis med.-long-wave scale and back (takes std. twin gang condenser and 3½-in. speaker). 15/-. P. & P. 1/6.

Wave-Change Switches. 6-pole 3-way, 2/-; 4-pole 3-way, 1/9; 5-pole 2-way midget, 1/9; 5-pole 3-way, 1/9; 3-pole 3-way, 1/9; 2-pole 1-way midget, 1/3; 2-pole 1-way 1/3; 9-pol 3-way, 3/6. P. & P. 3d. each.

Pre-Aligned Midget 465 Kc. Q 120 9/- per pair, post 6d. **Miniature 465 Kc. I.F.s.** Q 120, per pair, 10/-.

465 Kc. Midget I.F.s. Q 120, size 1¼in. long, 1in. wide, ¾in. deep, by very famous manufacturer. Pre-aligned adjustable iron-dust cores, per pair, **12/6. 465 Kc. Iron-Cored.** Q 120 size 3½ × 1in. dia., **7/6.**

Iron-Cored 465 Kc. Whistle Filter, 2/6.

T.V. Chassis. Size 9½ × 9½ × 3½in., 3/-.

Standard 465 Kc. I.F.s. Q 120 iron-cored, 3¼ × 1¼ × 1¼in., per pair **10/6.**

Valve Holders. Paxolin international octal **4d.** each. Moulded international octal, **7d.** each. EF50 ceramic, **7d.** each. Moulded B7G, slightly soiled **6d.** each.

Line Cord 3-way 0.3 amp., 180 ohms per yard, **1/3** per yard. **Ceramic P.F.S.** 3 each of the following: 330, 220, 180 and 82, **2/6.**

Trimmers. 5-40 pf., **5d.**; 10-110, 10-250, 10-450 pf., **10d.** Three bank 50 pf. **1/3.** Four bank, 50 pf., **1/8.**

Twin-Gang .0005 Tuning Condenser 5/-. With trimmers, 7/6. Post and packing 6d. **Twin-Gang Midget .00037** with perspex dust-cover and trimmers, **8/6.** Post and pkg. 6d.

Mains Droppers. 0.3 amp. 460 ohms, tapped 280 and 410, **1/6**; 0.2 amp. 717 ohms, tapped at 100 ohms, vitreous, **1/6**; 0.3 amp. 950 ohms, tapped 700 and 825, **2/6**; 0.2 amp. 1,000 ohm, vitreous, tapped, **2/6.** P. & P. on each 3d.

Volume Controls by famous manufacturer. Long spindle and switch: ¼, ½, 1 and 2 meg., 4/- each; 20, 25 and 50 K., 3/6 each. Post and packing 3d. each.

Constructor's 465 kc. I.F. Kit, comprising 4 double pie wound coils on ¾in. Aladdin formers, 4 iron cores, 2 cans 3½ × 1¼ × 1¼in., four hundred pf. silver mica 5%, and two paxolin mounting panels, **4/6,** post paid.

THIS MONTH'S OUTSTANDING OFFER

Rola Sin. P.M. with O.P. trans. **16/6** Post Paid.

Terms of business: Cash with order. Dispatch of goods within 3 days from receipt of order. Where post and packing charge is not stated please add 6d. up to 10/-, 1/- up to £1 and 1/6 up to £2. All enquiries and Lists, S.A.E

23 HIGH STREET (Opposite Granada Cinema), ACTON, W.3

Hours of Business: Saturdays 9—6 p.m. Wednesday 9—1 p.m. Other days 9—4.30 p.m. ***Telephone: ACOrn 3901***

1 KW TELEGRAPH TRANSMITTERS. Two HF 300's output. Operation 3.5 mc to 16 mc.

RCA TRANSMITTERS. Type ET-4336. Complete with speech amplifier, crystal multiplier and VFO units. Brand new.

LM-300 TRANSMITTERS (U.S.A.). 140 kc to 400 kc and 650 kc to 1,600 kc. 300 watt output.

No. 12 TRANSMITTERS. With coupling units, remote control, etc.

AR-77's, NC45, HRO and others.

AUTOMATIC HIGH SPEED TELEGRAPH EQUIPMENT, "BOEHME" (U.S.A.). Up to 400 signs per minute on line and wireless.

NAVY MODEL TBY-8 TRANSMITTING-RECEIVING EQUIPMENT. Output 0.75 watts on M.C.W. telegraphy and 0.5 watts on telephony. Frequency range 28-80 mc.

All above items in excellent working condition.

Working demonstration upon request.

TX VALVES 801, 805, 807, 814, 861, 866A, DET-16 and many others.

Large stock of Tx condensers, crystals and other components. Alignment and repair of communication receivers and all other short-wave equipment undertaken.

P.C.A. RADIO

Transmitter Division :—
The Arches, Cambridge Grove, London, W.6. *Tel. RIV 3279*

Receiver Division :—
170 Goldhawk Road, London, W.12. *Tel. SHE 4946*

RADIO EXCHANGE CO.

HIGH RESISTANCE HEADPHONES. Ericsson's first grade, 4,000 ohms per pair, brand new, boxed, **17/6**.

RECEIVER P40. Complete with valves, tuning 85-95 mc/s., these are ideal for Wrotham or "2" metre conversion. Housed in attractive robust grey cases these contain 4 EF54s (RF, mixer, Xtal multipliers), EC32 (Xtal oscillator), 2 EF39s (2.9 mc/s IFs), EB34 (det), 6J5 and 6V6 (audio). In original cartons, complete with circuit, **69/6**. Post 1/8. (Circuit only, 1/8).

TRANSMITTER 21. Sending CW, MCW or speech on 4.2—7.5 and 18—31 mc/s these are complete with valves, circuit, control box, key and front panel. Wire (not formers) from PA coils, and relays, have been stripped by the M.O.S. but may easily be replaced with the aid of our circuit and data. In excellent condition, **25/-**.

POWER UNIT S441B. With separate individually controlled HT and LT transformers, jewelled indicator lights, attractive appearance, modest size (14 in. x 7½in. x 7in.) these delivering 300 v. at 200 mA., fully smoothed, 12 v. at 3A. AC and 5 v. DC, from 200/250 v. 50 cps. In ORIGINAL CARTONS. Only **65/-** (carr. 5/-).

VIBRATOR UNIT 21. 6 v. input, approx. 160 v. at 40 mA. smoothed DC output; designed for the Tx/Rx 21. In new condition. ONLY **17/6**.

BRAND NEW ACCUMULATORS in transparent, unspillable, plastic cases. 7 A.H. 2 v., **6/6**.

POWER UNIT S532. With 5Z4 rectifier, choke, condensers, transformers, etc., our conversion will produce a fine little HT unit for mains input, providing approx. 450 v. at 50 mA. ONLY **15/-**. (P. and P. 2/6.)

NEW 1355 CONVERSION data for all 5 TV channels, **3/-**.

MIDGET AMPLIFIERS with two 12SH7s, one 12SJ7, these measure 5in. x 3½in. x 3in. OUR PRICE **15/-**.

H.T. BATTERIES. 60 v., **4/9**; 2 for **8/11**, plus 1/8 postage etc.

HEMISPHERICAL CARBON MICROPHONES, with switch, new, boxed, **5/-**.

9 CAULDWELL STREET, BEDFORD

Phone 5568.

TRADE SUPPLIED

L. WILKINSON

Wholesale and Export

19, LANSDOWNE ROAD, CROYDON

Phone: CRO 0839 Telegrams: "WILCO" CROYDON

RELAYS P.O. TYPE 3000
RELAYS SIEMENS HIGH SPEED
RELAYS TELEGRAPH 4181C
UNISELECTOR SWITCHES
KEY SWITCHES
HANDSETS P.O. TYPE
'PHONE PLUGS AND JACKS
SELENIUM RECTIFIERS
BATTERY CHARGERS
BRIEZE PLUGS AND SOCKETS
YAXLEY SWITCHES
FUSE BOXES J.C.
SIPHAN PLUGS AND SOCKETS
ELECTRICAL COMPONENTS

SLYDLOK FUSES
RESISTORS, WIREWOUND, ETC.
POTENTIOMETERS, WIREWOUND etc.
CONDENSERS
VALVEHOLDERS B9A, ETC.
TEST EQUIPMENT
SLOW MOTION DRIVES
SANTON AND ARROW SWITCHES
KLAXON MOTORS
GLASS INSULATORS
15 AMP. MK. KICK SWITCHES
GLOSSY CABLE
METERS
M.E.S. BULBS

Large Stocks held at Competitive Prices

LYONS RADIO Ltd.

VCR97 C.R. TUBES. As brand new and unused. Supplied in maker's transit cases. All tested before despatch. **PRICE 39/6**, carriage and insurance 7/6.

MICROPHONE CABLE, Etc. A screened copper conductor with outer insulating cover which gives it the appearance of co-ax cable. Ideal for mike lead, etc. 12 yards, **8/6**; 13-30 yards, **8d.** per yard; over 30 yards, **2d.** per yard; or 100-yard coil, **50/-**.

TEST SETS TYPE 45. This set is an R.F. oscillator providing a test signal at the frequency of 360 M/c, unmodulated or modulated at 500 cps. Valves employed are one each of VR99 and VR118. Batteries required for operation are 120 v. H.T. and 2 v. Acc. Extremely well made test sets housed in strong wooden instrument cases 12 - 10½ - 9in. Supplied complete with valves (not batteries) in new condition. **PRICE 50/-**, carriage 5/-.

POWER UNITS TYPE 229. Contain rotary converter for 24 v. D.C. input with twin D.C. output of 12 v. 5 A. and 300 v. 70 mA. Principal components fitted are carbon pile voltage regulator, wire wound pots, 2 mfd. electrolytics, 2 stabilizer valves (type QV45, etc. **PRICE 22/6**, carriage 7/6.

COSSOR DOUBLE BEAM OSCILLOSCOPES. We have a limited stock of these well-known Oscilloscopes type 339A which we have reconditioned throughout as new and fitted with new C.R. Tubes. In perfect working order. **PRICE £45**, carriage 22/6 (10 - returnable on crate).

3 GOLDHAWK ROAD (Dept. M.W.), SHEPHERDS BUSH, LONDON, W.12. *Telephone:* **Shepherds Bush 1729.**

3-COLOUR TELEVISION FILTERS

These screens, delicately tinted to give blue skies, pink centre and green foreground will add to your viewing pleasure. Easily fitted.

For Screens 9" or 10" **10/9**, 12" **12/6**, 15" and 16" **19/6**

T.V. MAGNIFYING LENSES WITH STRAPS

9in. size makes 12in. picture. Clear type **55/-** ea.
9in. size makes 12in. picture. Filter type **60/-** ea.
12in. size makes 15in. picture. Clear type **75/-** ea.
12in. size makes 15in. picture. Filter type **80/-** ea.

Trade Enquiries Invited

MAYCO ELECTRIC 43 ROSEBERY AVENUE LONDON, E.C.1 Tel. 5958

COILS • COILS • COILS

T.R.F. • SUPERHET • FILTERS • PACKS

TELEVISION COILS • I.F. TRANSFORMERS

FOR DEPENDABLE COMPONENTS CONTACT

OLYMPIC RADIO COMPONENTS

COIL WINDING SPECIALISTS & MANUFACTURERS

224, HORNSEY RD., N.7. **NORTH 2914**

For Quality Bargains Always

-Best Buy at Britain's

SPECIAL OFFER. Ex-Admiralty Amplifier chassis, complete in metal case with lid. Size 17in. x 8in. x 12in. **FOR A.C. MAINS OPERATION** 200-250 volts 50 cycles. Contains a complete power pack—husky choke, 1000 volt working paper block smoothing condensers and mains transformer. This has a tapped input—210, 230, 250 volts, and the outputs are 350-0-350 v. 150 mA., 6.3 v. and 5 v. The circuit diagram of the unit is included and the original valve line-up was 6J7, 6K7, 6V6 and 5Z4. It should be an extremely simple job to convert this into a standard A.F. amplifier. Certain relays have been removed and the unit is supplied less valves. Condition is as new. This is a real snip at only **39/6** plus 5/6 carriage. Get your order in early as only a limited number are available. We can thoroughly recommend this item as being one of the BEST BUYS we have offered for some time.

RESPONSER UNIT TYPE R3118. 15 valve 1½ metre superhet for A.C. mains 200-250 volts 50 cycles. This unit would be extremely suitable for alteration to T.V. or the Wrotham transmission on 90 megs. Contains 2-EF54, 1-EC52, 6-SP61, 1-P61, 1-5Z4G, 3-VR92 and 1-Y63. Supplied complete with valves for **97/6** plus 7/6 carriage.

6in. MAGNIFYING LENS FOR VCR97, SCPI, ETC. First grade, oil filled Perspex, special price **22/6** plus 1/6 post. Almost doubles your picture area.

SPECIAL PURPOSE VALVES. VT501 (TT11) **5/-** ; 954 **2/6** ; 955 **4/-** ; VR136 (EF54) **6/6** ; E1148 **2/6** ; VR65A (SP41) **3/-** ; VR65 (SP61) **3/6** ; 2C34 (RK34) **3/-** ; 8308 **8/6** ; Hundreds of other types in stock. Postage 6d. extra on 1/4 valves.

EF50 (VR91) RED SYLVANIA American types at **8/6** each. Brand New. British makes also available at **5/-** each, tested.

SPEAKERS. Brand new and boxed. Moving coil P.M. Truvox 6½in at **13/6** ; Goodmans 10in. 15 ohm voice coil **35/-**.

CO-AX CABLE. Brand New 75-80 ohm at **1/-** per yard—minimum 10 yards. This is standard ¼in. dia.—not ex-Govt.

PAXOLIN VALVEHOLDERS International octal at **4/3** per dozen.

CERAMIC TWO BANK SWITCH. Each bank four pole two way. List price £1/1/-.—Our price **4/6**.

METAL RECTIFIERS. 12 v. 2 A. full wave bridge **12/6** plus 6d. post. Miniature H.T. rectifiers, type RM2—125 v. 100mA. at **4/3** each or two for **8/-**. RM3—125 v. 120 mA. at **5/-** each or two for **9/6**, plus 6d. postage on one or two. Selenium rectifiers 150 v. 40 mA. at three for **10/-** post paid. 230 v. 60 mA. at two for **10/-** post paid. 12 v. 5 A. full wave bridge rectifiers at **17/6** plus 6d. post.

HEAVY DUTY RECTIFIERS. Funnel cooled, full wave, 30 volt 20 amp. Selenium. Each rectifier consists of 20 discs size 112 mm. Brand new and boxed at **£4/10/-** plus 3/6 carriage.

STANDARD TRANSFORMERS of current manufacture. Two types both standard primaries. Universal mounting. (1) 350-0-350 v. 80 mA., 0-4-5 v. 2 A., 0-4-6.3 v. 4 A. (2) 250-0-250 v. 80 mA., 0-4-5 v. 2 A., 0-4-6.3 v. 4 A. Both these transformers are brand new and boxed, fully guaranteed and priced at only **18/6** plus 1/- post.

30 VOLT TRANSFORMER, standard primary, secondary 30 volts 2 A., tapped at 3 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v. Has countless uses, i.e., for chargers, train sets, filament transformer, etc. Price **17/6** plus 1/- post. Brand new, boxed and guaranteed.

MULTI-PURPOSE TRANSFORMER. Upright mounting, primary 230 volts 50 cycles Secondaries 500-0-500 volts 400 mA., 300 volts 100 mA., 4 vo ts 7A., 10 volts centre tapped 11A, 12 volts 1A centre tapped, 6.3 volts 3 Amp., centre tapped. Size 6½in x 6½in x 7½in. Brand New **59/6** plus 5/- carr.

AMERICAN CONDENSERS. .01 mF. 1000 volts, .02 mF. 750 volts, at **7/6** per doz. .005 mF. 1000 volts., .002 mF. 1000 volts at **6/-** per doz. All metal cased, tubulars wire ended. Micamold ditto .1 mF. 350 volt at **7/6** per doz. Small Mica Condensers—.001 mF. CM2ON at **6/-** per doz.

COMMAND RECEIVERS. We have two types of these well known sets, one covers the Top Band, 1.5 to 3 Mc/s. (100-200 metres) and the other 6-9 Mc/s. (33-50 metres). Both these receivers are in brand new condition and contained in black crackle cases. Complete with six valves and circuit diagram, less dynomotor at **£4/10/-** carriage paid. Valve types employed : RF — 12SK7, F.C. — 12K8, 1st I.F. — 12SK7, 2nd I.F. — 12SK7, Det. and B.F.O.—12SR7, Output-12A6.

AMERICAN CAR OR STORAGE BATTERY. 6 volt 90 A.H., Brand new and individually boxed. Hard rubber cases size 8½in. long, 6½in wide and 7½in. high. Price **79/6** plus 5/- carriage.

We have a large range of units and components, some of which are in insufficiently large quantities to advertise. We suggest you pay us a visit to secure some real bargains. Many items are of interest to Schools, Laboratories, Manufacturers and others connected with the Electronic Industry.

CHARLES BRITAIN (Radio) Ltd.
11 UPPER SAINT MARTIN'S LANE
LONDON, W.C.2 *TEM 0545*

3 minutes from Leicester Square Station (up Cranbourn Street) *Shop Hours* : 9—6 p.m. (9—1 p.m. *Thursday*) *Open all day Saturday.*

I.F. STRIP TYPE 194. An easily modified I.F. Strip recommended for T.V. constructors who want good results at moderate cost, or for those who have built televisors but are having trouble in the vision or sound receivers. Can also be modified for 2 Channel working as per details in "Practical Television" October issue. This 6-stage strip measures 18in. x 5in. x 4in. and contains 6 valves VR65, 1 of VR92, and 1 of VR53 or VR56. Mod. data supplied. BRAND NEW. ONLY **45/-** (carriage, etc., 2/6).

RDF 1 RECEIVER. A very powerful 14-valve receiver with 4 I.F. stages of 12 mc/s. with 4 mc/s. bandwidth. Will convert into a first-class T.V. receiver for 2 Channel working as described in "Practical Television," October and November issues, a reprint being supplied. Valve line-up : 5 of SP61, 2 of P61, 3 of EA50, and 1 each CV63, EB34, EC52, SZ4G. ONLY **47/6** (carriage, etc., 5/-).

10-VALVE 1¼-METRE SUPERHET ZC8931. For long-distance T.V. results. Valve line-up is 6 of VR65, 2 of VR92, and 1 each VR136 and VR137 and the 12 mc/s. 6-stage I.F. Strip gives tremendous amplification with ample bandwidth of 4 mc/s. Easily modified. Full details supplied. ONLY **59/6** (carriage, 5/-).

RECEIVER R.3118. The A.C. MAINS VERSION of the above ZC8931, having a built-in power pack for normal mains supply. ONLY **97/6** (carriage, etc., 7/6).

T.1154 TRANSMITTER. The famous ex-R.A.F. Aircraft Transmitter offered at only a fraction of cost. Covers frequency ranges 200-500 kc/s., 3.0-5.5 mc/s., 5.5-10.0 mc/s. in 3 switched bands. Complete with 2 valves ML6 and 2 of PT15. Circuit diagram supplied. ONLY **59/6** (packing and carriage 25/-, 12/6 being refunded on return of transit case).

CHOKES. 20 H.80 120 m/a., **9/6**; 5 H.200 300 m/a., **6/-**; 30 H. 150 m/a., **12/6** (postage, 1/-).

TRANSFORMERS. E.H.T. for VCR97 tube with 4 v. for tube heaters and 4 v. tapped 2 v. for E.H.T. rectifier. ONLY **37/6**. HEAVY DUTY FULLY SHROUDED 350-0-350 v. 160 m/a., 5 v. 3 a., 6.3 v. 6 a., 6.3 v. 3 a., ONLY **42/6**. HEAVY DUTY FULLY SHROUDED 250-0-250 v. 100 m/a., 5 v. 3 a., 6.3 v. 6 a., ONLY **32/6**. UNIVERSAL MOUNTING 350-0-350 v. 80 m/a., 0-4-6.3 v. 4 a. and 0-4-5 v. 2 a., ONLY **18/6**. TOP SHROUDED DROP THROUGH 260-0-260 v. 70 m/a., 6.3 v. 3 a., 5 v. 2 a., ONLY **16/6**. (POSTAGE, 1/6 EACH TRANSFORMER, PLEASE.)

FOR EXPORT ONLY
Transmitter Receivers Type 18, Walkie-Talkies Type 38, R.A.F. Dinghy Emergency Transmitters T.1333.
Prices on application.

TRAIN TRANSFORMER, giving tapped outputs of 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v., 30 v. at 2 amps., from normal mains input. ONLY **17/6** (postage 1/-).

6in. MAGNIFYING LENS FOR VCR97 TUBE. First-grade oil-filled. ONLY **25/-** (postage, 1/6).

"PYE" 45 MC/S. I.F. STRIP. Ready made for London Vision Channel. Complete with 6 valves EF50 and an EA50, and details of very slight mods. required. ONLY **57/6** (postage, etc., 1/6).

100 MICROAMPS METER. 2½in. Flush mounting. Widely calibrated scale of 15 division marked "Yards," which can be re-written to suit requirements. These movements are almost unobtainable to-day, and being BRAND NEW IN MAKER'S CARTONS are a "snip" at ONLY **39/6**.

CAR OR STORAGE BATTERIES by famous American makers. Brand new and unused, these have genuine hard rubber cases 6 v. 77 a.h. "PHILCO" size 10¼in. long x 7in. wide x 8¼in. high, ONLY **82/6** ; 6 v. 90 a.h. "THOR," size 8¼in. long x 6¼in. wide x 7¼in. high, ONLY **87/6** (carriage, 5/- each battery).

EX-W.D. TRANSFORMERS. All heavy duty with 230/250 v. primaries. Type A has secondaries of 330-0-330 v. and 4 v. 3 a. ONLY **22/6**. Type B is an EHT transformer with secondaries of 2 v. 1.5 amps., 300 v. 10 m/a., 520 v. 10 m/a., 1,400 v. 2 m/a. ONLY **21/-**. Type C is a Filament Transformer with secondaries of 6.3 v. 7.7 amps., 4.2 v. 2.5 amps., 4 v. 1 amp. ONLY **19/6** (postage 1/8 each item). ALL ITEMS BRAND NEW AND UNUSED.

Cash with order please, and print name and address clearly. Amounts given for carriage refer to inland only

U.E.I. CORPORATION

Radio Corner, 138 Gray's Inn Road, London, W.C.1. Phone : TERMINUS 7937.

(Open until 1 p.m. Saturdays. We are 2 mins from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

OUTSTANDING OFFERS FOR EXPORT ONLY

U.S.A. Radio & Radar Equipment
RCA TRANSMITTERS, Type ET-4336-B, H. K. L.
Westinghouse AIRCRAFT TRANSMITTERS, Model GO-9
TRANSMITTERS RECEIVERS SCR-536.
TEST EQUIPMENT IE-46 (Signal Generators I-196-B, Frequency Meters BC-906-D, Radio Receivers BC-1066-B).
Model ASE-1 RADAR AIRCRAFT EQUIPMENT (200 Units).
AN APS-3 Coastal Defence RADAR.
Hallicrafters SCR-299, 399 and 499 (BC-610).
Western Electric SCR-517-B.
RADAR Mk. 26 (Models 3 & 4).
INTERROGATORS-RESPONSORS BM-1 (and BN-1).
REPEATER-INDICATORS AN APA-1.
RADAR INDICATING EQUIPMENT, Model VF.
AIRCRAFT RADAR EQUIPMENT APS-3, 4 and 6.
GISHOLT-BALANCING METERING UNITS.
AN APN RADIO ALTIMETER EQUIPMENT.

Spares (Radio and Radar—U.S.A.)
Full range of spares for most U.S.A. Naval, Aircraft and Ground Radar and Radio Units.
Crystals (for SCR-610 and AT-4C).

British T.R. (X 42, W.S No. 58, W/S No. 11, W/S No. 17).

Power Units, Wavemeters, Motor Generators, Dynamotors and large quantities of various components.

Aircraft Instruments and Accessories
Large selection of Bendix Instruments.
Aircraft Generators and Motor Assemblies. Oxygen installations.

Individual Test Certificates and A.I.D. Certificates can be supplied upon request.

Enquiries to

BRITISH SAROZAL LTD.
(Export Branch)
1 BRISTOL HOUSE, SOUTHAMPTON ROW, LONDON, W.C.1
Telephone: HOLborn 6763/4/5 *Cables: Sarozal, London*

OVERSEAS BUYERS ARE CORDIALLY INVITED TO VISIT OUR WAREHOUSES, SHOWROOMS AND LABORATORY

G2AK *This Month's Bargains* G2AK

HEAVY DUTY ADJUSTABLE RHEOSTATS 4 ohms, 25 amps. Beautifully made, 3/- each. Post and packing 1/6.
C.R. TUBES, Type 5CP1 brand new in cartons, 17/6 each, plus 1/6 postage.
PARMEKO H.D SHROUDED CHOKES. 8H at 250 mA. Weight 11lbs. 16/6 each. Post and packing 1/6.
MOVING COIL HEADPHONES with moving coil microphones. Price 6/- Post 1/-. Transformer to match 2/-. Balanced Armature L.R. Phones, 9/6 per pair.
TWIN RIBBON FEEDER. Heavy duty 300 ohm, 5d. per yd. Standard K25 300 ohm ribbon, 9d per yd. Co-ax. cable, ¼in. dia. 50 ohm., 8d per yd., ⅜in. dia., 1/3 per yd. 7ft. length ¼in. dia. Co-ax. with Pye plug one end, 1/6, post free. All other Co-ax., and feeder, plus 1/6 post any length.
POTENTIOMETERS. 5 watt wire-wound 20 k., 25 k., 2/- Carbon Type Potentiometers, 50 k., 100 k., 1 meg., 2 meg. 1/6.
TRANSMITTING TUBES. Type 807, 10/- ea. Type 813 New and Boxed £3/10/- each. Type 866A, 17/6 each. 3E29 (829B) £4/10/- each. Few only.
METERS. 2½in. Flush mounting M.C. 100 m/a., 500 m/a., and 20 m/a., 12/6 each. 2in. Flush M.C. 500 microamp., 10/-. 5 m/a., 7/6 0.5 amp. thermo., 5/-. Special offer 2½in. flush 0—1 m/a. Rectifier Meter, scaled 0—10 volts, 22/6 each. Few only.
CERAMIC 2-bank, 4-pole, 4-way Swirches, 3/9 each. Post free.
CERAMIC COIL FORMERS. 5in. long by 2½in. diameter; threaded 24 grooves, 4/6 each, post free.
JONES PLUGS. 8-pin, male and famale, 1/6 per pair, 12/- per dozen pairs.

Carriage paid on all orders over £1 except where stated. Please include small amount for orders under £1.

Please print your name and address.

CHAS. H. YOUNG, G2AK
All Callers to ***110 DALE END, BIRMINGHAM***
'Phone: CENTRAL 1635.
Mail Orders to ***102 HOLLOWAY HEAD, BIRMINGHAM***
'Phone: MIDLAND 3254.

AMPLIFIER XL

5 valves. For record player, microphone or radio use. Incorporating push-pull output (8 watts) for 3 ohm or 15 ohm speaker. High-class components. Complete with valves, ready for use, £7/7/- plus 3/- carriage.

723 A/B Special Purpose Valves, complete with holders and screens	£4 10 0
725A Special Purpose Valves	£5 10 0
1B24 " "	£4 10 0

Large stocks of radio and radar spares and equipment. Trade and Export enquiries invited.

TELEKIT SUPPLY COMPANY
(Mail Order Dept.)
LUXTED FARM, DOWNE, KENT.

VALVES?

We probably have just the one you want, such as **6A7, 18, 30, 39, 42, 43, 45, 75, 77, 78, 80,** etc. We hold one of the largest stocks in the country at current B.O.T. prices. Why not drop us a card or 'phone **Luton 2677**? We will send off next post.

You can Rely on

COVENTRY RADIO
189 DUNSTABLE ROAD, LUTON, BEDS.

B. & H. RADIO
EAST STREET, DARLINGTON

BASS & TREBLE SEPARATOR
Cross-over 1,000 c.p.s. and including treble matching transformer.
Kit of Parts, Mod. A, 6Db per octave £1 19 0
Kit of Parts, Mod. B, 12Db per octave £2 16 0

SCRATCH FILTER
Easily fitted to pick-up and gives very marked reduction of scratch with little effect on treble £1 5 0

9 K.C.S WHISTLE FILTER
Easily fitted giving a cut guaranteed better than 40Db with negligible effect on adjacent frequencies £2 12 6

TONE COMPENSATOR
Adjustable for microgroove recordings and easily fitted £2 5 0

We specialise in
Components, Cables, Speakers and High Fidelity Equipment.
Sole Importers and Distributors to Trade and Industry of the
CONTINENTAL MIDGET POTENTIOMETERS WITH & WITHOUT SWITCH
Made in France.
Write phone or call at our trade counter.
WHOLESALE ONLY.
V. L. DEWITT LTD.
53, MUSEUM ST., HOLBORN, LONDON, W.C.1
Telephone: HOL 9466

FIRE!
WHERE'S YOUR
NU-SWIFT?

The World's Fastest Fire Extinguishers — for every Fire Risk
Pressure-operated by sealed CO_2 Charges
NU-SWIFT LTD. · ELLAND · YORKS
In Every Ship of the Royal Navy

HIFI LTD., 150, HIGH STREET, LYE, STOURBRIDGE, WORCS. Telephone: LYE 261

Wireless World Classified Advertisements

Rate 7/- for 2 lines or less and 3/6 for every additional line or part thereof, average lines 6 words. Box Numbers 2 words plus 1/-. (Address replies: Box 0000 c/o "Wireless World" Dorset House, Stamford St., London, S.E.1.) Trade discount details available on application. Press Day: April 1952 issue, Thursday, February 28th. No responsibility accepted for errors.

WARNING

Readers are warned that Government surplus components which may be offered for sale through our columns carry no manufacturers' guarantee. Many of these components will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

NEW RECEIVERS AND AMPLIFIERS

UNIVERSAL ELECTRONIC PRODUCTS, 36 Marylebone High St., London, W.1. Welbeck 4056. SPECIALISTS in the design and manufacture of high fidelity reproducing equipment from 5-100 watts for domestic or industrial purposes. Our new twin channel amplifier (type U.E.57), with independent bass and treble outputs, provides the most advanced of reproduction we have yet experienced. It is now being demonstrated in our showrooms daily (we close Thursday 1 p.m., Saturday 4.30 p.m.), and we invite those who seek perfection from recorded music to hear this superb instrument. We also offer tuning units or complete chassis designed and constructed to individual requirements. [0124

12-watt high quality amplifiers, bass and treble boost, £12/15/-. lists.—Broadcast & Acoustic Equipment Co., Ltd., Tombland, Norwich. [0065

MIDLAND RADIO COIL PRODUCTS offer a service for the production of high quality amplifiers and radio equipment to specification; list of standard products is available; suppliers of audio and radio equipment to the Northamptonshire Education Authority.—Enquiries to 28, Winstanly Rd., Wellingborough. [6336

C.J.R. ELECTRICAL & ELECTRONIC DEVELOPMENT, Ltd., Bickford Rd., Witton, Birmingham, 6 (Eas. 0435), the Midlands specialist manufacturers of high fidelity sound reproduction equipment for the world-famous Williamson amplifier and associated accessories including tone control stages, loudspeaker crossover units, distortionless contrast expanders and radio feeders; send for details and prices. [0105

TELRAD ELECTRONICS 70, Church Rd., Upper Norwood, London, S.E.19.—Designers and manufacturers of Telrad quality amplifiers, established as the most outstanding value in high-quality amplifiers, thanks to faithful reproduction at unrivalled price, these unique amplifiers are the first choice of the enthusiast, built to satisfy the discriminating ear; bass and treble independent controls, providing the greatest possible variation to suit all recordings and varying acoustic properties of one room with another; full details on request.—Write call or 'phone Livingstone 4879.

RECEIVERS, AMPLIFIERS SURPLUS AND SECONDHAND

AR 88D, good condition, with handbook; £50.—Box 6692. [8139

BC 348, £19, little used; demonstration.—55, Palace Rd., London, N.8. [8065

HALLICRAFTER SX28 for sale, in perfect condition, £105.—Box 6726. [8161

R.F. units, type 25, 26, B.C. 453; £5, or separate.—Barclay, 5, St. James Man., Muswell Hill, London, N.10. [8122

PAM 25-watt amplifier, type 601-B, speaker and record player, little used, superb condition, offers over £30.—Box 6624. [8089

HRO Rx's and coils in stock, also AR88, BC348R, CR100, etc.—Requirements please to R.T. & I. Service, 254, Grove Green Rd., Leytonstone, London, E.11. Ley 4966. [0093

EDDYSTONE 640 communication receiver, as new, complete with signal meter, speaker, handbook and Brownes headphones, seldom used; first £22 secures.—Box 6751. [8172

AR 88 and 5×28 receivers for sale; purchased privately (not Government surplus).—Details, appointment to view, from K. Blackwell, 41, Meadway, Old Southgate, N.14. [8162

HT-4B (B.C. 610) 2 to 30 mc/s, complete with A.T.U., speech amplifier, crystals, etc., as new, best offer over £225; trade, 1154 £5, 1190 £17; buyer collects.—Box 6620. [8079

ACOUSTICAL Quad, tuner, Axiom 12in B/R cabinet, £28, Goodsell Williamson, preamp., Axiom 12, £20; Garrard 2-speed, £7; Wegner, £2; 'soupe, £3; other items, all as new.—Taylor, 75a, Aldwick Rd., Bognor. [8163

ALL-LEAK equipment.—TL/12 amplifier with cover and baseplate, RC/PA/U preamp and RC/PA fitted pu transformer, dynamic pu with both SP and LP movements, VS tuner (as brand new); total cost over £90; £65.—Box 6623. [8088

Partridge News

FAMOUS "EXPORT ONLY"

CFB TRANSFORMER

now available

"AT HOME"!

From its inception a year ago the C.F.B. was acclaimed (by those fortunate enough to obtain them) the finest audio transformer yet produced. Hitherto this model has been for "export only"—and it literally swept the American continent. Now, an allocation is permitted for home users.

Those familiar with the performance of our WWFB series must raise a speculative eyebrow when we say that the CFB series is as far ahead of the WWFB as the latter was of ordinary output transformers. For instance, at 16 watts, 50 c.p.s., the WWFB has 0.5 per cent core harmonic distortion. The CFB has 0.05 per cent! The CFB shows as little as 10 m.h. series leakage inductance and has therefore more than twice the ratio of Primary Shunt L to leakage series L of the WWFB. This plus the ability to handle up to 60 watts with less than 1 per cent distortion and a 15 octave bandwidth, even without feedback, a low 88 ohm half-primary resistance but with a primary shunt inductance in excess of 120 Henries, extremely low phase angle at even the highest frequencies and many other features combine to make this the most outstanding output transformer available regardless of price. Its outstanding performance lies in the use of a grain oriented, strip wound C core. The extraordinary characteristics made possible by this type of construction permit of a very considerable amount of feedback across several stages of triodes and it therefore becomes the very finest of output transformers for the Williamson circuit where only perfection of performance, and not price, is the consideration.

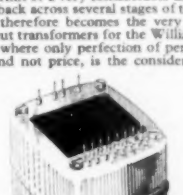

PARTRIDGE

TRANSFORMERS LTD

ROEBUCK ROAD KINGSTON BY-PASS

TOLWORTH SURREY

Telephone ELMbridge 6737-8

RECEIVERS, AMPLIFIERS SURPLUS AND SECONDHAND

1951 Eddystone 670 marine receiver; £50, or nearest offer.—BM/DNYQ, London, W.C.1. [8155

LOUDSPEAKERS—SURPLUS AND SECONDHAND

VOIGT with twin diaphragm, plus rectifier; £7/10.—Snow, Ardingley. 82. [8087

GOODMAN'S 12in. twin cone 15ohm speaker, almost new; £9 or near.—Box 6610. [8043

BARKER 148, £9, Goodman's Audium 60, £6 (new).—Main, The Cottage, Dulverton, Som. [8114

VOIGT domestic corner-horns, painted black, reconed en. Voigt speaker units; offers.—Box 6646. [8129

GOODMANS Axiom 12, specification reflex cabinet felt lined £17.—Tyler, 37, St. Antony's Rd., London, E.7. [8091

VOIGT H.C. horn, pol. veneered, corner cabinet, £12. Hadley Turner/Voigt p.m. unit, £4.—Jones, 205, Lynmouth Ave., Morden, Surrey. [8096

VOIGT domestic corner horn in oak with special 2h.f. 12 watt Lowther set, built as radio-gramophone, in oak cabinet; offers.—15, Rothesay Road, Bournemouth. [8154

PA 30in re-entrant metal horn speakers, 10watt 6.5ohms, 90/-; P/A 30in straight metal horns, 55/-, like new.—Radiovox Sound System, 5, Oxford Place, Leeds, 1. [7698

NEW DYNAMOS, MOTORS, ETC.

ALTERNATORS, 3kva, 230v/50cs, 3,000 rpm, with exciter and v/control unit, new, £58.—Champion, 45, Uplands Way, London, N.21. [0171

H.F. alternators, 1,500 cycles, 80 volts, 25 amps, motor driven, 220v d.c., brand new.—E.W.S. Co., 69, Church Rd., Moseley, Birmingham. [8133

BATTERY chargers, 4 models, 2-6-12v, 1-2-4 amp D.C., any mains voltage; also larger types special transformers, chokes, test gear, interior car heaters, etc.—The Banner Electric Co., Ltd., Hoddesdon, Herts. [0122

ALL types of rotating electrical machinery up to 20kvs available, including rotary converters, rotary transformers, motors, petrol and diesel-engined generating plants, alternators and d.c. generators. We are also in a position to quote for power transformers; as actual manufacturers we will be glad to quote for any quantity for home or export.

DIESEL Electric generating plants, 3kva, 230v with push-button remote control, starting equipment, ready for use; £275.

ROTARY transformers, input 20v d.c., outputs 6.5v d.c. and 500v d.c., permanent magnet field, 20/-, ditto, input 28v d.c. and 1,200v 70ma d.c. output; energised field 35/-, ditto, input 12v d.c., output 500v, 90ma d.c., energised fields 35/-, reasonable delivery.

CHAS. F. WARD, Lordscroft Works, Haverhill, Suffolk. Tel. 255. [0039

DYNAMOS, MOTORS, ETC.—SURPLUS AND SECONDHAND

ROT. converter, 200 d.c. to 230 a.c. 180w, filter, £9.—Campion, London Rd., Windlesham, Surrey. [8120

D.C./A.C. 110/230 convertor, No. 20629K (Electro Dynamic Construction Co.), as new; Pye table model television, plus magnifying mask, at moderate price.—Box 6657. Tel. Chelwood Gate 59. [8118

THE Pearce new model diesel alternator plant, on welded steel frame, 250/1/50 5kva, plus 32v 15a d.c. Petters latest AV/A1, air-cooled diesel engine, belt-driven alternator, self-energised, automatic voltage control by winding on stator, at govern. speed 1,500 rpm, d.c. output trickle charges or charges lighting and starter battery up to 15 amps, 24v lighting is used when plant is not in use, start and stop by remote control push-buttons, complete with main switch & fuses, battery cables, 24v 72 amp-h. batt, instruction book, spares, engine covered by Petters' inspection service; £260, free delivery 100 mls. London, where remote start and stop not required, but only push start on engine; reduction of £6/10/- for those making quick delivery, if you collect, or we deliver, battery is charged and a 10 cu. ft. concrete bed given free.

ALTERNATORS, type as fitted in above plant, 110/1/60, or 230/1/50, 5kva, wt. 240lb, £72 del.; also 110/1/60 or 230/1/50 6kva, wt. 400lb, £95 del.; 8kva, £77; 6kva, £102; f.o.b. Liverpool or London docks; please state direction of rotation at pulley end; fullest details of plant or alternators by return post; the above are not surplus but current products of British manufacture.

6V BATTS., 110-125 amp/h., £5 del.; rotary converters, 24v d.c. to 250v 50, 80-100 watts, switch, metal box, tested, £3/17/6 del.; shunt dynamos, 52v 8a, £6/5, used but good, 90/- del.; sliding res. Zenith 2Ω 15a, 5Ω 10a, 19/6 del. 12 and 24v battery chargers, see "W.W." August, p. 74.

PLEASE see displayed advert, page 100, for S.T.C. selenium rectifiers; terms c.w.o., pro forma invoice, c.o.d. (post goods only).—T. W. PEARCE 66, Great Percy St., W.C.1 (near Angel). [0014

MORE THAN VALUE FOR MONEY

Before the war the Hartley-Turner speaker cost £9. When we reintroduced it in 1946, in a greatly improved form, it was still £9 and it stayed at £9 for a considerable time. What other commodity do you know that cost no more than in pre-war days – But when steel became short and we had to change to an aluminium cradle the price had to go up to **£10 10 0** because the cost to us was considerably more. And still costs have been on the up and up and in some cases the rises have been fantastic.

On the other hand we have been making more profit from our American sales because American salaries are much higher than British. In any event our American price, as in Britain, was miles below what others charge for speakers which high-fidelity enthusiasts do not think so good, but we didn't need to "give the 215 away." The price we asked was fully justified, and the extra profit we were making was used by us to "subsidise" the British price out of a sense of loyalty to all those thousands of music lovers who helped to build this firm.

The continuing rise in material costs has wiped out that little extra profit we were making from our American sales, and from now on the British market must be self-supporting. The whole cost of the rises must be allowed for in fixing the price in sterling. We are sorry that our long-sustained efforts to keep the cost of your pleasure down have ultimately failed, but they have failed through no fault of yours or ours. As from February 1st the price of the 215 speaker became

£14/10/0

including postage, packing and insurance, but everyone who had sent for our catalogue was given the opportunity of buying at the old price.
Even at this new price the 215 will still give you a fuller measure of satisfaction than any other whatever the price, and with materials now getting scarcer as well as dearer you should not delay.

We have appointed the M.O.S. Radio Centre, 33 Tottenham Court Road, London, W.1, as our leading London agents. They will be happy to give you real Hartley-Turner service and supply your needs on either a cash or deferred terms basis.

H. A. HARTLEY Co. Ltd.

152 HAMMERSMITH ROAD, LONDON, W.6
Phone: RIV. 7387

TRANSMITTING EQUIPMENT

MAGSLIP transmitters from 10/-; ideal for remote control of radio apparatus, including Antenna direction indication; stamp for details.—ENGINEERING FACILITIES, LTD., 29, Rea St., Birmingham, 5. [7507

AIRCRAFT radio harness in factory-new condition, "W" sockets, ground-to-air portable T.R stations with own genemotors operating parts for W.S.19, teleprinters, aircraft sets SCR 522 and 1466.—Gilfillan & Co., 52, South St., Worthing. Tel. 8719. [8059

AMATEUR changing QTH has for disposal RCA ET4336K transmitter, complete speech amp., master oscillator, crystal multiplier, as brand new, working £100. American amateur transmitter 150/s, all bands switched, aerial switched coupler, built-in oscilloscope, £100. Offers the following: Hallicrafters SX28 receiver, 1151 modulator less valves, Collins TCS receiver, Bell-Howell 16mm sound projector, model 156, splendid condition, spare lamps, film splicer, etc.—Box 6609. [8042

TEST EQUIPMENT SURPLUS AND SECONDHAND

TAYLOR 65B sig. gen., little used; £11/10.—Ford, 17, Chattern Rd., Ashford, Middx. [8064

AVO, 7, recently purchased; £16 or best offer secures.—100, Owenford Rd., Radford, Coventry. [8067

WESTON E772 analyser, 20,000 o.p.v., as brand new, £20; Wearite multimeter 1,000 o.p.v. volts, amps, i., c. & r. ranges, £5; 24 service sheets, 1/- ea.—47, Avon Rd., W. Christchurch. [8121

SIGNAL generators, oscilloscopes, output meters, valve voltmeters, frequency meters, multi-range meters in stock; your enquiries are invited.—Requirements to R. T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986.

COSSOR 339 oscilloscope, £35; BC.221 frequency meter, 20mcs—120mcs, complete with crystal, £15; also Naval version (modulated), £30; both complete with calibration charts and crystal; callers preferred, Tindey's condenser, microphone tester, offers.—HAYNEONS, 14, St. Mary's, Bedford. Tel. 5568. [0150

NEW GRAMOPHONE AND SOUND EQUIPMENT

FRITH RADIOCRAFT Ltd., offer from stock:—
COLLARO 3-speed auto-changers; basic 3-RC-511 unit without pickup heads, £12/9/5; Acos GP27 pickup heads in three types, standard, long-playing or dual-purpose, £5/2/4 each; complete unit with dual-purpose head, metal table cabinet, £18/15; ditto in de luxe walnut cabinet, £26/16/2.
COLLARO 3-speed single record players; basic 3-514 unit without pickup heads, £8/4/2; GP27 heads as above.
COLLARO single-speed auto-changers, RC-500, magnetic PU £11/16/9; crystal PU, £12/2/11.
COLLARO AC-514 single-speed 7/8 unit, mag PU, £6/-/5.
PESSEY multi-speed auto-changers to play 8-10 records 10in and 12in mixed at 33 or 78 rpm, or 8-10 records 7in only at 33 or 45 rpm; Acos dual sapphire head, £25/15.
CONNOISSEUR super de luxe 2-speed motors with 12in machined turntable, instant change from 33 to 78 rpm, £21/8/8; de luxe pickups with twin heads and sapphires, £10/9/8; Connoisseur Stroboscopes for 33 and 78 rpm at 25, 50 and 60 c/s, 3/11.
W. B. "Stentorian" speakers, 2½in 18/6, 3½in 19/6, 5in 21/-, 8in 32/6, 9in 36/9, 10in 44/6; dual concentric types 10in £6/15, 12in £17/17 or with transformers £7/15 and £8/18.
GOODMANS 12in speakers, Audiom 60, £8/12/6; Axiom 150, twin-cone, £10/5/6; Celestion P-44 speakers, 12in PM, 3 ohms, £4/5; Ekco moulded plastic speaker grille 16½in×12in cream or gold, entirely free from resonance, 6/6 plus 1/3 post; sample on request; Escutcheon moudina, flexible cream plastic 5/16in U section, 1/6 per yard.
RESLO ribbon microphones type URA £7/10, moving coil type WM, £6.
ACOS crystal microphones MIC 21/1 or 22/2 for floor or desk stand fitting, £6/6; table stands, 25/-; 3-section folding floor stands, £3/7/6.
RECORDING tape EMI 65A, 65B or H60, 35/-; Scotch Boy (Dupex), 35/-; Philips, £2; all 1,200ft reels, spare reels 4/-.
RECORDING motors, BSR SR-1, 32/-, SR-2, 25/-; FP-10 clockwise or anti-clockwise, 38/-; Collaro ditto, 42/-.
AMPLION multi-range meters, 1,800 ohms per volt, 9 ranges £5; Pullin series 100 multi-range meters, 10,000 ohms per volt, 21 ranges, £11/11.
FRITH Radiocraft Ltd., 69-71 Church Gate, Leicester. Tel. 58927. [0024

MAGNETIC tape new high coercivity Emitape 35/- spool 1,200 feet tape decks, blank recording discs, 10in, 3/- from stock; full trade terms.—SOUND DISCS (SUPPLIES), LTD., 178, Bispham Rd., Southport, Lancs. Tel. 88155. [7765

GENUINE Armour magnetic recording wire, new in maker's sealed tins on standard spools, one hour speech, half hour music, £2/10.—Francis, 93, Wardour St., W.1. [7071

LIMITED number "Verity" tape recorders available ex. stock double track, supersonic erase and bias mixing for radio and mic, etc., £45.—Write, 82, East St., Epsom, Surrey. [8055

YOUR tape R/P amplifier kits assembled expertly and cheaply, also complete amplifiers for Lane desks, etc., 12ans and 16ans.—Harding Electronics, 120a, Mora Rd., London, N.W.2. [8073

They're worth waiting for...

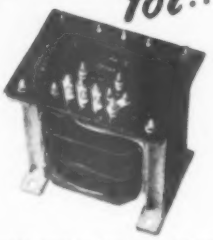

A lot more people than ever before have been ordering a lot more Savage Transformers than ever before. This, and the shortages of raw materials are extending deliveries more than somewhat. As one of our Welsh customers said, however, "Savage Transformers are worth waiting for."

SAVAGE TRANSFORMERS OF DEVIZES Limited

SAVAGE TRANSFORMERS LTD.
Nursteed Road, Devizes, Wilts.
Telephone: Devizes 536

"AUTOMAT" HOME CHARGERS, SELENIUM RECTIFIERS, CHARGER KITS

All New Goods with Full Guarantee

"AUTOMAT" HEAVY DUTY HOME CHARGER, for car or radio cells. Virtually unwreckable. Selenium rectification. Impregnated transformer of large size. Fine workmanship and appearance. 12 months' guarantee. For A.C. mains only. Standard model 6 v./12 v. 2 amp. output, 8lb. wt., **59 6**. Post 2/-.

ELIMINATOR KIT. Transformer, selenium h.t. rect., l.t. rect., 2 × 15 mfds. condensers for 120 v. 20-30 mA. eliminator with 1 amp trickle charge, **35/-**, or with handsome steel case, **43/-**, post 1/2.

POOLPROOF CHARGER KITS, standard model, 45 watts trans., triple tapped, large 12 v. 2 amp. selenium rectifier, ballast indicator bulb for 2 v., 6 v., 12 v. charger, simple and foolproof, **38 6**, post 1/4; or with handsome steel case, screws grommets, **52 6**. Ditto kit, but 60-watt trans. and 12 v. 3 amp. rectifier, **46/-**, or with case **58/-**, weight 8 lb., post 1/6 extra. Junior kit, 6 v. 1.5 a. rect., 40 w. trans., ballast bulb, case, screws, for 6 v. 1.5 a. charge, **42/-**, wt. 7lb. Senior model kit, 12 v. 4 amp. S.T.C. rectifier 4in. diam., 70 watt transformer, ballast bulb for 6 v., 12 v. charger, **55/-**, post 1/-, ammeter **12 6** extra (not essential). Heavy duty kit for 5 to 6 amp., 6 v./12 v. 100 watt trans. large fixed 6 a. rect., shunt resistance, ammeter flush type, **£4 16/-**, post 2/-. 2 v. trickle rectifier, ½ amp., with high-grade layer wound transformer, **12/6**.

SELENIUM RECTIFIERS. New stock not surplus, 12/15 v. 2 amp., **15 6**; 6 v. 2 amp., **9/-**, post 8d. 12 v. 1 amp. half wave, **9/-**; 12 v. 3 amp., **16 6**, post 9d.; 6 v. 4 amp., **16 6**; 12/15 v. 5 amp. **27/-**, post 9d. Giant finned type, 12 v. 6 amp., **35/-**, post 1/3; 24 v. 4 amp., **54 6**; 24 v. 6 amp., **67/-**; 24 v. 2 amp. **29 6**. Small space H.T. rectifiers, selenium, 250 v. 60 m.a., **7 6**; 110 v./135 v. 60 m.a. **6 6**; 250 v. 100 m.a. bridge **14 6**. All 6d. extra postage. 230 v. 200 m.a. bridge or half-wave (4 units) **22 6**.

"RENEWBAT" battery desulphator and conditioner **1 9**, post 3d. Car size, 3, post 4d.

CHAMPION PRODUCTS
43 Uplands Way, London, N 21. Phone LAB 4467

JOHN FARMER

236. CIRCUIT TESTING OHMMETERS, by Evershed & Vignoles. Scales 0-1,000 and 100-200,000 ohms and inf. Test leads and prods. Leather case, **£5,** post 1/6. **1003. TIME DELAY MOTOR DRIVEN RELAYS,** 110-115 v., 60 cycles continuous 1-pole, make contacts, 5 amps. Time delay adjustable 30 secs. to 1 min., re-cycling time 2 secs., **25/-** each, post 8d. Spare motors for these, fitted reduction gear box, totally enclosed, final drive 1 r.p.m., size 2¼in. x 2in. x 1¼in., **17/6** each, post 6d. **13. RADIO TRANSFORMERS,** pri. 200-220-240 v., sec. 350-0-350 v. at 80 m.a., 6.3 v. tapped at 4 v. at 5 a., 5 v. tapped at 4 v. at 2 a., screen, with slots for chassis mounting, new, boxed, with termination data, **20/-** each, post 1/3. **18. MULTIPLE L.T. TRANSFORMERS,** pri. 200-220-240 v., sec. 30 v. at 2 amps., tapped at 3-4-5-6-8-9-10-12-15-18-20-24 v. Brand new, boxed, **22/6** each, post 1/3. **19. WESTINGHOUSE RECTIFIERS,** selenium full wave bridge, D.C. output 12 v. at 2 amps. from input of 15 v. A.C. An ideal small battery charger used with item 18 above. New, unused, with fixing brackets **15/-** each, post 8d. **22. MODULATOR UNITS, TYPE 169,** complete with CV67 Klystron, 5U4G, EF50, 3 neon stabilizers and B4101. Brand new condition, a real bargain at **40/-** each, carr. 8/-. **100. CAMERA MOTORS,** 24 v., A.C. D.C., fitted overload clutch, takes approx. 1 amp. off-load and 2 amps. on-load at 24 v. A.C. Another item suitable for use with our multiple L.T. transformers listed above. Size, excluding shaft, 4¼in. long, 3¼in. dia., std. base mounting. These are one of the finest ex-Govt. motors, new, boxed, **20/-** each, post 1/3. **138. 45 MC/S. I.F. STRIPS,** "Pye," complete with six EF50's and one EA50. New, **60/-** each, post 1/6. **271. POWER TRANSFORMERS,** 1 phase 50 cycles, input tapped for 200-220-240 v. plus 10 v., bakelite panel attached with secondary leads to U17 and RZ1/150 valve bases, also negative, 700 v. pos. D.C. terminations. New, in wood cases, **35/-** each, carr. 4/-. **285. SIEMENS HIGH SPEED RELAYS,** micrometer blade and gap adjustments, sp. change-over, platinum contacts, size 3in. x 1¼in. x 1in. Three types : (a) twin coil each 1,000 ohms ; (b) twin coil each 500 ohms ; (c) single coil 145 ohms. All new unused, **10/-** each, post 4d. **266. MUIRHEAD VERNIER DRIVES,** type D. The popular slow motion drive, ratio 40-1, marked 0-180 deg., illuminated cursor. New, boxed, **8/6** each, post 6d. **150. MICROPHONES :** (a) carbon differential, bullet shaped, fitted switch, **1/9** each, post 4d. ; (b) m/c. type, in bakelite case, hand type, fitted switch, **3/6** each, post 8d. **90. TOGGLE SWITCHES,** panel mounting, 250 v., 2 amps., single pole change-over or on-off. Brand new, **9d.** each, post 3d. ; **7/6** per doz., post 6d. **24. AMMETERS,** 0-9 amps., A.C. D.C., hot wire. 3¼in. dia., 2¼in. scale, to fit 2¼in. dia. hole, flush panel mounting. Brand new, boxed, **10/-** each, post 6d. **17. H.T. UNITS,** No. 1 Mk. II. Input 12 v. D.C., output 230 v., 30 m/a. D.C. Contain a motor generator and several misc. items such as chokes, condensers, filter units, etc. These originally cost £18, our price brand new, **12/6,** carr. 3/-. **270. CIRCUIT BREAKERS 10P 500 MAGNETIC OVERLOAD,** 6½in. x 3¼in. x 2¼in. on-off switch, 1.75 and 2 amp., A.C. markings, 2 terminals, **12/6,** post 1/-. **VOLTMETERS,** 0-100 volts A.C., moving coil, internal rectifier, 1 m/a. Scaled 0-20-40-60-80-100 with 1/10th sub-divisions, 2¼in. scale, flush panel mounting. New, **20/-** each, post 6d. **223. "ZENITH" VARIABLE RHEOSTATS,** 0.4 ohms, 25 amps., helical screw traverse, laminated contacts, wire wound on vitreous steel former. Base mountings and brackets, unused condition, **7/6** each, post 1/6.

Our 1952 Catalogue is now available free with order, or price 6d. on application.

JOHN FARMER (DEPT. A.1.),
194 HARBORNE PARK RD.,
HARBORNE, B'HAM, 17

Tel : HARborne 1309

NEW GRAMOPHONE AND SOUND EQUIPMENT

TAPE recorder motors, 250v a.c., powerful, quiet, brand new, 13.11; post, etc., 1/.—K. W. Logan, Westalley, Hitchin, Herts. [6469

LP records by post, order with confidence, each record individually inspected and carefully packed, orders over £2 post free, under £2 please add 1/-; LP Record catalogue, 1/6 post free.—ROGERS DEVELOPMENTS, Co. (M.O. Dept.), 116, Blackheath Rd., Greenwich, S.E.10. [8104

9Kcs whistle can be attenuated with a high Q toroidal coil fitted as series or parallel resonant ort; easily adjusted aurally, coil only, 35/-; can be used also as inductance standard, accuracy 2%.—BEL SOUND PRODUCTS, Co., Marlborough Yard, London, Archway, N.19. [0187

THREE speed record players, walnut finish (with 1.d) fitted B.S.R. MU.14 motor at £11/5; complete with Chancery dual cartridge crystal pick-up £15.9/6; with Decca X.M.S. magnetic pick-up £18/5; any make fitted to order; MU14 motor at new reduced price of £6/8/6 post free.—RECORD filing cabinets for the Connoisseur in hand French polished oak, walnut or mahogany from £15.15; sizes to hold 500 or 500 discs; specials to order.—SAND-FILLED corner speaker enclosures, non-resonant (as described by G. A. Briggs in his book "Sound Production") in walnut finish, from £15.—BASS-REFLEX cabinets suitable for any size speaker, soldly constructed from hardwoods, plywood and Weyroc; any type of cabinet made to customer's own specification.—DETAILS for 2½d stamp from—"Phase-In" Speakers, 99, Ash Bank, Bucknall, Stoke-on-Trent. [8005

CINE VOX disc recording equipments, type C/C70 for high-quality recordings from existing microphone equipment, price from 28gns; also available as a complete channel inclusive of mic., amplifier and playback equipment, at 70gns; type C7 for highest quality professional requirements—recorder mechanism at 48gns, or complete channel at 110gns; demonstrations arranged in London.—PLEASE write for details to R.T.S., Ltd., 60, Aylward Rd., London, S.W.20. (Liberty 2426.) Callers by appointment only. [0209

GRAMOPHONE AND SOUND EQUIPMENT —SURPLUS AND SECONDHAND

WEARITE tape deck, 3 reels Durex tape, all unused, £35.—Box 6702. [8157

NEW 5in M88 discs, D.S., 6/- dozen.—Crampin, 33, Aosey Rd., Grimsby. [8159

TWO only "Connoisseur" brand new boxed, 2-speed motors at old price; £19/14/2 each. TWO only "Telefunzen" portable disc recorders with in-built power amplifiers, 78 r.p.m., 90 g.p.i., cut in-out, spare lead screws for out-in 15in turntable, amplifier 600 ohms input 15 ohms or 250 ohms output, valves MH4, PX4, U14, cases dirty but mechanically and electrically perfect including a host of spares; £50 the two. "SOUNDMIRROR" tape recorder, portable model, complete with microphone and tape, demonstration model, shop soiled only; £75. "SOUNDMIRROR" tape recorder table model, complete with microphone and tape, demonstration model, shop soiled only; £65.—SNELL & HAINES, Ltd., 133, Western St., Swansea. Phone 2848 [8158

BSR. D.R.33 recorder, amp., ribbon mike, all accessories, perfect, ready to record, £115 or offer.—Proprietor, Hare Arms, King's Lynn. [8033

MSS disc recorders converted to 33⅓, £17/10. Utah wire recorder, £45, 16in. recording discs, Presto, 4/9.—Matthews, Bentworth Priors, Tower Hill, Tel. Dorking 3426. [8060

25 watt P.A. amplifier, mike and mag. inputs, tone control, push-pull, 6L6 output, first-class job, 2 available; £13/15 each; also Williamson, £19/10.—Box 6097 [7988

SIMPHONIC magnetic tape recorder complete with microphone and spare tape; new condition, £40.—E. 8, Littler, Royal National, T.N. & E. Hospital, Golden Square, W.1. [8126

WIRE recorder constructional details, 1/6; S.S. recording wire, 5,600ft reels, 5/6; larger quantities available at reduced prices.—12, Rossendale Ave., Blackley, Manchester 9. [8142

SUPER recording amplifier, Consolette style, 5 channels, 11 inputs, main amplifier output 40 watts, triodes, separate monitor amp., talk back, bass and treble equalisers, etc., cost £350, hardly used; £140.—82, East St., Epsom, Surrey. [8056

BARGAIN superb reproducer consisting Lowther D.T.4 tuner, A.15.F amplifier, treble and bass correctors, whistle and scratch filter, Voigt P.M.1. speaker, extras, all as new; £65, quick sale.—36, Whitby Terrace, Cemetery Rd., York. [8055

NEW COMPONENTS

CRYSTAL microphone inserts (Cosmocord C/mic-6), guaranteed brand new; 15/6, post free.—RADIO-AID, Ltd. (Retail Dept.), 29, Market St., Watford. [0056

SUPACOILS famous range of coils are now obtainable from your local radio dealers. If you have any difficulty in getting supplies write to our office for complete catalogue or send 2/6 for our new constructor's handbook of circuits, gen. formulae, etc.—SUPACOILS, OFFICE 98, Greenway Avenue, London, E.17. [0155

Armstrong

THE CHASSIS PEOPLE

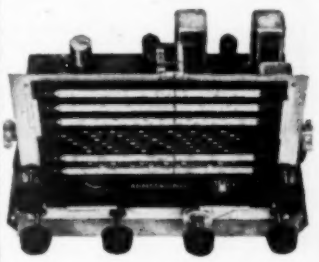

The prestige of Armstrong chassis is firmly based upon many years of constant endeavour to produce reliable and efficient receivers at an economical price. Our present range of chassis will even further advance the already high reputation enjoyed by our receivers. We are delighted to give demonstrations in our showroom and our illustrated catalogue will be sent on request.

MODEL EXP 125 3 14-VALVE ALL-WAVE RADIOGRAM CHASSIS

5 Wave Bands covering from 10.9 to 550m and 800 to 2,000m. R.F. Pre-Amplifier. Two I.F. Stages with Variable Selectivity. Bass and Treble Controls. 15-Watt Push-Pull Output. For A.C. Mains. **£36.15.0,** plus P.T.

MODEL RF 104 10-VALVE ALL-WAVE RADIO CHASSIS

4 Wave Bands. R.F. Pre-Amplifier. Two I.F. Stages with Variable Selectivity. 10-Watt Push-Pull Output. For A.C. Mains. **£24.0.0,** plus P.T.

MODEL EXP 73 8-STAGE ALL-WAVE RADIO CHASSIS

3 Wave Bands. Variable Selectivity. Fly-Wheel Tuning. 8-Watt Push-Pull Output with Negative Feed Back. For A.C. Mains. **£17.15.0,** plus P.T.

TELEVISION
The new ARMSTRONG TELEVISION CHASSIS, model TV.15, incorporating a 12" C.R.T., is now available for distribution.

PRICE: 53 GUINEAS
TAX PAID

Unfortunately, owing to the limited supply of material, the Chassis is at present available only for the London Service Area. Please send for full details.

ARMSTRONG WIRELESS & TELEVISION **CO. LTD.**
WARLTERS ROAD, HOLLOWAY, LONDON, N.7
Telephone : NORth 3213

THE MODERN BOOK CO.

The Magnetron. By Latham, King and Rushforth. Price 18s. Postage 6d.

Television Receiving Equipment. By W. T. Cocking. Price 18s. Postage 9d.

Principles of Radar. MIT Radar School. Price 21s. Postage 1s.

Handbook of Line Communication. Volume One by The Royal Signals. Price 20s. Postage 1s.

Magnetic Tape Recording. By P. A. Tarry. Price 6s. 6d. Postage 4d.

Radio Servicing. By A. Marcus. Price 35s. Postage 1s.

Vacuum Tubes. By Spangenberg. Price 60s. Postage 1s.

The Electronic Musical Instrument Manual. By A. Douglas. Price 18s. Postage 6d.

Amplifiers. By N. H. Crowhurst. Price 3s. 6d. Postage 3d.

Sound Reproduction. By G. A. Briggs. Price 10s. 6d. Postage 6d.

Radio Engineering. By R. Norris (editor). Price 15s. Postage 9d.

Elements of Sound Recording. By J. Frayne and H. Wolfe. Price 60s. Postage 1s.

World Radio Valve Handbook. By O. Lund Johansen. Price 11s. 6d. Postage 6d.

Radio Valve Data. Compiled by "Wireless World." Price 3s. 6d. Postage 3d.

Osram Valve Manual. Part One. Price 5s. Postage 6d.

We have the finest selection of British and American radio books in the country. Complete lists on application.

19-23 PRAED STREET
(Dept. W.3.)
LONDON, W.2
PADdington 4185

NEW S.T.C. SELENIUM RECTIFIERS. Largest L.T. range in Great Britain. Current products. NOT SURPLUS. E.H.T. N2 100 17-; for "W.W." Televisor, for VR97 N2 50, 12-; post 6d. PRIORITY ORDERS ONLY.

PLUS 15% ON ALL THESE PRICES

HALF WAVE HEAVY DUTY 7½in. SQUARE COOLING FINS, 16 v. 5 a., 26-; 10 a., 29-; 16 a. 53-; 30 v. 5 a., 41 6; 8 a., 47-; 48 v. 2.5 a., 31-; 5 a. 56-; 8 a. 65-; all post 1/-.

BRIDGE CONNECTED FULL WAVE. 17 v., 1.25 a., 14 2; 1.7 a., 22 9; 2.5 a., 25-; 3 a., 26-; 4 a., 30-; 5 a., 32 6; all post free. 33 v. 0.7 a., 21/-; 1 a., 24 3; 1.5 a., 39-; 2 a., 44-; 3 a., 45-; 4 a., 54-; 5 a., 58-; all post 11d. 54 v. 1 a., 33 6; 1.5 a., 54-; 2 a., 60-; 3 a., 61-; 5 a., 81-; 72 v. 1.5 a., 68-; 2 a., 79-; 3 a., 80-; 5 a., 106-; 100 v. 1.5 a., 97-; 2 a., 112-; 5 a., 152-; all post 1/1.

BRIDGE CONNECTED HEAVY DUTY 7½in. SQUARE COOLING FINS. 17 v., 6 a., 43-; 10 a., 49-; post 1/6.

BRIDGE CONNECTED HEAVY DUTY Funnel Cooled, also **7½in. SQUARE COOLING FINS.** Revised price, same both types. 17 v. 12 a., 80-; 20 a., 102-; 30 a., 142-; 50 a., £11; 33 v. 6 a., 79-; 10 a., 91-; 12 a., 146-; 20 a., 164-; 54 v. 6 a., 104-; 10 a., 124-; 72 v. 6a., 134-; 10 a. 154-; 100 v. 6 a., 192-; 10 a., £11; all post 1/8.

SOME G.E.C. & "WESTINGHOUSE" RECTS. NOW STOCKED.

VERY SLOW DELIVERY OF MANY RECTS. WILL DO OUR BEST! HOSPITALS, RESEARCH LABS. AND GOVERNMENT CONTRACTS GIVEN PRIORITY.

Wholesale & Retail

T. W. PEARCE (Est. 20 Yrs.)
60 GREAT PERCY STREET, LONDON, W.C.1
Off Pentonville Rd. Between King's Cross and Angel

NEW COMPONENTS

EVERYTHING for home constructor, chassis, condensers, coils, valves, resistors, gram units, speakers, test gear, Viewmaster kits, etc., cash or H.P.; stamp for lists; quick service, no Govt. surplus offered.—James H. Martin & Co., BCM/EDHWA, London, W.C.1. [7694

FOR really good results you can do no better than use Osmor coils and coilpacks, and anyone of experience! Send 5d (stamps) today for beautifully-drawn free circuits, our new coil-data leaflet, and latest lists of matched radio components. A speedy mail order department is at your service, and remember, all Osmor lines are guaranteed. (Trade enquiries invited). Dept. C.W.1.
OSMOR RADIO PRODUCTS, Ltd., Bridge View Works, Borough Hill, Croydon. Tel. Croydon 5148/9. [10046

TELEVISION-coilsets, all with video chokes: Viewmaster, Prac' Wless, E.Engr.; London 16/6, Midland 19/6, H. Moss 21/-, Scotland 25/-; ¾in canned coiled tagged screened TV formers, as used W.W. P.U. Rs 2- ea.; Viewmaster total cost abt £55, mostly 14-day delivery. Wireless World sensitive superhet, coilsets 62/6, RF strips 62/6, defn. coils 45/-, line trans. 65/6, blocking trans. (frame) 15/-, remainder from 60 days' delivery. Williamson high Q TRF feeder coils, on ¾in poly formers, MW or LW 5/6 pair, ½in, ¾in TV formers, 7d and 10d, add 2d tax/panel; material supply position may preclude immediate dispatch in some cases; trade inquiries invited.
BEL SOUND PRODUCTS, Co., Marlborough Yard, London, Archway, N.19. Arc. 5078. [10185

COMPONENTS SURPLUS AND SECONDHAND

C. J. EMMS, Ltd.

RECTIFIERS, full wave bridge type, as follows: 1amp. 12 or 6v. 5/6; 3 amp. 12 or 6v. 12/6; 4 amp. 12 or 6v. 15/-; 5 amp. 12 or 6v. 17/6; 7 amp. 6 or 12v. 22/6; 24v 1 amp. 11/-; 24v 3 amp. 25/-; 24v 4 amp. 30/-.
NEW sliding resistance sets from 1 to 4 amp 140 to 12 amp 10/7 in all. 30/- per carton.—26a, Coiherne Mews, London, S.W.10. Frenchmantle 4941. [0201

HALLICRAFTER Skyrider Model 25, perfect. 1154, transmitter, communication receivers in stock. Hammerlund Super Pro. H.R.O. Seniors, S.R.100, A.R.88D, A.R.88LF, etc., all in perfect order. R.1155 receivers in new condition; your enquiries are invited for rotary convertors and electric motors, most sizes and types available from stock, special clearance of F.H.P. electric motors, 55/- 110v-250v a.c.
UNIVERSAL a.c.-d.c. motors, suitable for sewing machines, 40/- each; 12v-15v a.c./d.c. motors with extended spindle, suitable for models, etc., 9/3; 20 watt P.A. rack mounting amplifier, new and complete, with heavy duty a.c. power pack, 200-250v, PX25 P.P. output, £5/10, less valves, new moving coil microphones, hand type, heavy duty and complete with 12yd screened cable, £3/15; 20ft telescopic tubular T.V. mast, 18/6 each; large selection of test equipment; multi-range meters, valve testers, signal generators, oscilloscopes, bridge meggers and meggers, etc., all at reasonable prices; hand bearing prismatic compasses, perfect, 45/- each; very large stocks of transmitting valves, Klystron, of all types, send us your requirements, special offer of new, not ex-W.D., mains transformer, semi-shrouded 200-250v tapped primary, 250-0-250, 100ma, 5v 3amp, 6v 4amp, 21/6 each; large stocks of L.T. transformers, special sizes and ratings wound to specification, auto-record changers in stock from £15.2.6 to £18.10; switchboard mounting voltmeters, ammeters, various ranges a.c. and d.c., available at cheap prices to clear; large stocks of resistances, 5 watts and 20 watts e.g., D.S.G. No. 15 U.X. base, American valves available. Special offer, H.R.O. coils, 48-96 m/s and 180-450 k/s, 45/- each, quantity of iitz and nickel chrome wire available, type 74 indicator units, complete with tube as new, £6 each. Hallicrafter Super Skyrider SX28 in stock. Eversheds bridge meager, 500v 1½kw, e.d.c. rotary converter, 220 d.c.-250 a.c., complete with Igranic starter, £28. Large selection of American Pyranch high-voltage working condensers, 0.5 m.a. meter rectifiers 6/3 ea.
HAMMERLUND B.C. 779B, perfect order, rack mounting, £42/10. G-Max, Q-5/10 receiver, new, £58; prices do not include postage.
SERVICE RADIO SPARES, 4, Lisle St., W.C.2. Gerrard 1754. [0188

V.H.F. receiver type 1481, complete with valves, £7/10.
BENDIX frequency meters, type BC221.
THROAT microphones, 3/6 each.
LORD antivibration mountings, 8lbs @ 10lbs, £8 per 1,000.
TELESCOPIC aerial for No. 19 set Mark II.
POWER unit for No. 19 set, U.S.A. and British Mark II, 25/-.
VOLTMETER MC DC 5,500 volts, 3½in projecting type, 45/- each.
EIMAC vacuum condensers 100pfd, 20,000 volts, 15/- each.
MICA condensers, American types, bulk quantities only, types X 41, Sangamo, Solar, A2, etc., 20kv to 5kv; vitreous enamelled resistors from 40 ohms to 50,000 ohms, wattages 25, 50, 75, 100, all at 4/- ea.
COMMAND receiver: Bendix drives from 5in to 25ft long, 5in 5/- each; from 2ft to 8ft, 8/6 ea.; from 10ft to 25ft, 16/- ea.
McELROY ADAMS MFG. GROUP, Ltd., 46, Greyhound Rd., Fulham, W.6. Tel. Fulham 1134-9. Cables: Hallicraft London. [0196

MAGSLIPS at 1/10 to 1/20 of list prices, huge stocks, please state requirements.—K. LOGAN Westaway Hitchin, Herts. [6569

SOUTHERN RADIO'S WIRELESS BARGAINS

WALKIE-TALKIE (TRANSMITTER-RECEIVER). Type 38 Mark II. Complete with 5 valves, Throat Microphone, Headphones and Aerial. 7 mc/s Amateur Band suitable for field use. Powerful Superhet Receiver. Modulated Transmitter. Guaranteed ready for the Air, less batteries, **£3/10/-.**

R.35IS TELEVISION UNITS. Complete with 21 valves. 6 Stage 14 mc/s I.F. Strip. Ideal for T.V. Conversion. Brand new in original wooden cases. **£3/10/-.**

G.E.C. "MINISCOPE" M861B. MINIATURE CATHODE RAY OSCILLOSCOPES 1½" Tube. Time Base etc., etc. Brand New in Makers Sealed Cartons with Leatherette Carrying Case—**£15/10/0** plus 5/- carriage.

LUFBRA HOLE CUTTERS. Adjustable from ⅛in. to 3½in. for use on Wood, Metal, Plastic, etc., **5/9. LUFBRA FLY CUTTERS, 14/6.**

LIONEL "BUG" KEYS. Genuine U.S.A. Automatic Morse Key, Type 136. Few only, **£3/7/6.**

THROAT MICROPHONES. Magnetic type complete with long lead and plug, **4/6.**

HAND GENERATORS. 6 volts at 5 amps. With Crank, **21/-.**

PLASTIC TRANSPARENT MAP CASES, 14 inches by 10½ inches. Ideal for Maps, Charts, Display, Photographs, etc., **5/6.**

STARIDENTIFIERS. With Hydrographic Office Modifications A-N Type V. Complete in case, **5/6.**

MOVING COIL D/C METERS. Brand new 2in. 0-2 mA., 0-5 mA., 0-30 mA., 0-20 volts, **9/6** ea.

WESTECTORS. Type WX6 and W112, 1/- ea., 11/- doz.

MARCONI AERIAL FILTER UNITS. Type "916" in conformity with P.O. Specification. Full instructions for fixing, **4/-.**

CONTACTOR TIME SWITCHES. 10-hour movement, 2 impulses per second. Thermostatic Control in soundproof Cases, **11/6.**

VISUAL INDICATOR UNIT Type 3 (10Q/4). Contains two Moving Coil movements, two Neons, etc. Easily convertible to very efficient M.C. Meters, **11/-.** Conversion fully described in "W.W." Sept. 1951.

Full list of Radio Publications, 2½d.

SOUTHERN RADIO SUPPLY LTD.,
11, LITTLE NEWPORT STREET, LONDON W.C.2. *GERrard 6653.*

Good Investments

SHORT WAVE TELEGRAPH-TELEPHONE RECEIVER. Type R.C.67 single bay self contained double detection Receiver 3-24 megacycles in three switched frequency ranges. Write for full spec.

WAVEMETERS. T.E.149 R.C.A. accuracy 0.005%, 200 K.C. to 30 Mc/s.

PANORAMIC RADIO ADAPTOR. Naval Model. Max. sweep width 100 kc.s., input frequency 5.25 Mc/s. 115/230 volts 50/70 cycles. Brand new. Send for special leaflet.

Rotary Convertors, Battery Chargers, Rectifiers, Pumps, Resistance, Meters, Condensers, Relays, etc., etc. Send us your enquiries.

MOTOR GENERATOR, 24-28 volts D.C. input 120 volts 7 amps. 800 cycles 8,000 r.p.m. output, enclosed, fan cooled **65-**, carr. 5/-.

ALTERNATORS. Inductor type totally enclosed 230 volts 2 amps. 460 watts 50 c/s. 3-ph, 3,000 r.p.m., **£8 10/-**, need exciter 6 volts 6 amps. Can also be wired for 230 volts 230 watts single phase 50 cycles.

LIGHTING PLANTS. Briggs & Stratton 350 watt 12 18 volts D.C. with 5 bd. and Fuel Tank **£30.** Norman Lyon 550 watt 12 18 volts with 5 bd. and Fuel Tank **£35.** Villiers 1,260 watt 36 volts 36 amp. **£40.** Homelite 1,500 watts 30 volts **£40.** Villiers 1 K.W. 50 volts 20 amps. **£35.** Carriage extra at cost. Send for leaflet.

RESISTANCES. Variable slider, 6 ohms 6 amps. **25-**; 14 ohms 5 amps. **32 6**; 5 ohms 10 amps. **27 6**; 152 ohms 2 amps. **30-**; 300 ohms ½ amp. **15/-.**

ROTARY CONVERTERS. D.C./A.C. 110 volts to 230 volts 100 watts **£10.** Starter **25-**, carr. extra. 230/230 volts 200 watts **£15.** Starter **30-**, carr. extra. 24 volts/230 volts 100 watts **75-**, carr. 5/-. Other sizes in stock to 3 K.W. Send for list.

BATTERY CHARGER. Mercury Vapour type, 365/440 volts 3-phase 50 c.s. input, 120 volts 18.5 amps. output. Rectifier Units and Battery chargers all sizes to your own requirements.

ELECTRADIX RADIOS

214 Queenstown Road, London, S.W.8
Telephone: MACauley 2159

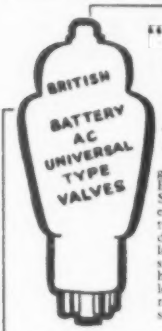

"DEMOBBED VALVES" MANUAL

2/9 post FREE

giving equivalents of British and American Service and Cross Reference of Commercial types, with an appendix of B.V.A. Equivalents and comprehensive Price List. We have still some valves left at PRE-BUDGET rates which actually sold at the old price.

—If yours is a (RARE) valve problem BULLS are the people most likely to solve it.

EXPORT

to all parts of the Commonwealth and beyond—safely packed, fully insured (no C.O.D.) and free of tax.

NEW :- COLOURED FILTERS FOR TELEVISION SCREENS. For viewing in 3 delightful colours graduating from blue at the top, red in centre to green at the bottom. Gives a 3 colour pastel shade picture on any black and white screen. 9in. and 10in., **10/9** ; 12in., **12/6** ; 15in., **19/6** ; Post 1/-.

CONDENSER TESTERS and Rectifier Units. Plugs straight into A.C. mains 200/240v. and is indispensable for examination of condensers. Very slight and intermittent leakages which cannot be discovered by conventional instruments can be traced by this unit. Complete **39/6**. Post 1/-.

TAYLOR ON EASY TERMS. EASY TERMS up to 10 months—and very near Cash Price on all TAYLOR METERS.

The New portable PLUS - a - GRAM

MODEL P.16

Portable model in Metal Case finished in Golden Brown Dimenso Super Enamel. Fitted with Garrard A.C. Rim Drive Motor and Magnetic Pick-up. For 110/250 Volts. 50 cycles. **£10 17 8.**

AERIALITE Indoor Flexible T/V Aerial, suitable Lounge, Loft, Attic (state which Transmitter). **13/6.**

"WYRE-JOINT" The Perfect Self-Insulating Wire Joint in a matter of seconds—makes a perfect insulated electrical joint with a lighted match. Packet of 12 **3/-**. Post free.

ELECTRIC HEATERS. Ex-Govt. with attachment for Wall or floor Mounting; Low Consumption. 300 watts, 200/250 v. A.C. D.C. Ideal for garages, greenhouses, cupboards, nursery etc. **27/6** only.

JUNEERO PATENT MULTI-PURPOSE TOOL REDUCED

It punches, bends, shears and threads. Specially designed for Model Making, Metal Working and Home Repairs. (Formerly 20/-) now **10/-**. With "Xakto" slide gauge, (formerly 27/6) now **17/6**. On APPROVAL one week. Refund Guaranteed. NOW **10/-** TAX FREE

Kindly Mark Envelope (WW3).

RADIO BULLS VALVES

246 HIGH ST. HARLESDEN NW10

COMPONENTS—SURPLUS AND SECONDHAND

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1.

SPECIAL offer of electrolytic condensers, capacity, voltage, size, type of mounting, price post paid, in final orders. 500+500, 6v, 1in×3in, cap. Dubilier. 2/9; 250+250, 6v, 1in×2in, cap. 2/9; 700+700, 6v, 1in×5in, lug, 2/9; 1,500, 6v, 1in×5in, clip, 3/-; 400, 6v, 1in×2in, lug, 2/6; 50+50, 150v, 1¼in×2in, clip, 3/6; 40+40, 150v, 1¼in×2in, cup, 3/6; 40, 150v, 1in×2in, clip, 2/9; 20+20, 275v, 1in×2in, lug, 4/3; 16+32, 275v, 1in×2in, lug, 4/3; 100+200, 275v, 1¼in×4½in, clip, 5/6; 64+120, 275v, 1¼in×4½in, clip, 5/6; 50, 350v, 1¼in×2in, clip, 3/6; 32+32, 350v, 1¾in×2in, clip 5/-; 10, 450v, ¾in×2in, tag, 2/9; 16, 450v, ¾in×2in, clip, 3/3; 20, 450v, 1in×2in, lug, 3/3; 32, 450v, 1¼in×2in, clip, 4/-; 16+8, 450v, 1¼in×2in, clip, 5/3; 16+16, 450v, 1in×3in, lug, 5/3; 24+12, 450v, 1¼in×2in, clip, 5/3; 40, 450v, 1in×3in, lug, 4/-; all are all. cons. some with cardboard sleeves all voltages are wkg., all new stock, some limited quantities.

TELEVISION! Set of 3 components, comprising line output trans., with E.H.T. winding to give 7 kV, using EY51 (heater winding for EY51 also included), and fitted with width control scanning coils, low impedance line and frame, focus coil (res. 10,000Ω, current approx. 20 mA); the set of 3 for 42/-, plus 1/6 post, diagram of line trans. supplied.

PERSONAL receivers, 3 valve T.R.F. using 1T4s, contained in handsome bakelite case with lift-up lid, size 7×6½×5in with lid closed, plastic carrying handle, fram AE in lid, these receivers cover the medium waveband and operate from self-contained dry batts., standard types W1485 and U2, output to a pair of lightweight 'phones (H.R.) controls, SM tuning and reaction, opening lid switches on, supplied brand new, with valves, batteries, 'phones, an ideal set for invalids, hosp. patients, etc., these receivers are not Govt. surplus and are offered ready to play, carr. paid £4/4.

CHASSIS steel, 15½×15½in drilled 5 button base holes, 1/9, 5×9×1½ drilled 5 button base holes, 2/3, a.l., 17·9½×2¾, drilled 7 int. octal and square, open ends 3/-, all. 14½×10×2¾ drilled 10-B6A, 5 int. octal, res. T.V. 4/3, primary 0-110-210-240v, 50c/s, secs 500-0-500v 80ma, 4v 2a, 6.3v, 2.5a, 15/6; smoothing chokes 8H 250ma 50Ω size 4×5×5 potted 10/6 post paid; electrolytics 32mf 350v card 2/-, 32-350v can 2/6; 16-450v can 2/6; 8+4 275v 2/-, 2-450v 1/6; superhet coils 1½×15, formers M. wave H.F. AE, Osc. L. wave H.F., AE, Osc., 1/9 per coil; I.F. trans. 465kc/s 1½×1½×4in iron cored 8/- pair; meters 2in square bakelite case, 0-5ma 6/6, 50ma 7/6, 0-500v d.c. with series res. 7/6; Rotary power units, type 104, p.m. rotary mounted on chassis with supp. input 12v d.c. output, 250v 60ma, 6.5v 2.5a, d.c. 7/-, type 87 24v input, outputs as 104, 6/6 post paid; plugs and sockets, bakelite with keyway, 5, 7, 1/6 pair; extension speaker controls, 10Ω wire wound, ¼in spindle, 9d; "Pye Strips," the well known 45mc/s crystal strips, brand new, from EF50s, with EA50, perfect condition, 59/6, plus 1/6 post; focus coils, low res., 200Ω, standard TV, 8/6, can be had as alternative with kit if required; 6½in loudspeakers, p.m., less trans., boxed, 12/6 post paid; Mansbridge conds., 4mf 1,000v wkg., 3/-; v.c. with sp switch, long spindle 25k+50k+100k+2m, 4/-.

OUTPUT trans., 5,000/3,750, 2/11; valveholders, Amphenol, int. octal 7d.

10IN loudspeakers with trans. (4,5000), 35/-, small size 4P 3w switches, 1in spindle, 2/9.

RADIO CLEARANCE, Ltd., 27, Tottenham Court Rd., London, W.1. Tel. Museum 9188. [0015

SUPREME RADIO, 746b, Romford Rd., Manor Park, London, E.12. Tel. Ilf. 1260. Est. 17 years.

LOOK! 1952 bargains.—New stocks of vol. controls, just arrived, standard size, with long spindle and s/pole switch, 2 meg, 250K ohms, 100K ohms, 25K ohms, 10K ohms and 5K ohms, 2/6 ea.; also the following values less switch: 2 meg, 250K ohms, 100K ohms and 10K ohms, 1/6 ea.

WESTINGHOUSE type metal rectifiers, 250v R.M.S., 65ma, 5/6; standard size I.F.Ts., 465kc/s, 8/6 pair; flat type mains dropper, tapped 200-250v, 630 ohms at 0.2 amp, 1/6 ea.

VALVE holders, moulded B7G, 10d ea.; int. octal, Amphinol type 7d ea.; B9G (EF50) slate type, 6d ea.; 3-pole 3-way small spindle rotary switches, 1/3 ea.; 4-pole 3-way small rotary switches, with medium spindle, 2/11 ea.

ELECTROLYTIC cond., 32+32mfd 350v, can type, 5/9 ea., 16+32mfd 350v small can cond., 4/9 ea.; 32mfd 500v tub. cardboard wire-end cond., 5/6 ea.; bias cond., 50mfd 50v cardboard or 50mfd 12v metal tag end cond., 1/- ea.

MAINS trans., drop through type, primary 0-250v tapped on voltage panel, sec. 275-0-275v 80ma, 6.3v 3amp, 5v 2amp, with screen, 15/11 ea.; 4B.A. brass n/plated terminals, 2/3 doz.; 28 way tag strips (break if as required, 1/- ea.

MANY other bargain lines in stock; terms c.w.o., no c.o.d.; send 6d extra for postage orders under £5; 2½d s.a.e. all enquiries and list. [0021

FREE bargain list, send s.a.e.; multi-ratio output transformers, 5/-; metal rectifiers, 250v 60m.a., 6/-; chokes, 10h 100m.a., 6/6; volume controls with switch, 4/-; I.F. transformers, 1.6m/cs, 4/-; slow motion dials and drives, 5/6; adjustable table mikes, 7/6; Eddystone 6-pin coils, 2/6; condensers, 100pf and 1,000pf, 3/6 doz.; Aladdin coil formers, 2/- doz.; cathode ray tubes, VCR139A, 25/-; photo electric cells, GS16, 25/-; stabilisers, 150/30, three for 24/-; all goods new and guaranteed; please add 9d postage on orders under £1.—Electrad Radio, 69, High St., Belfast, N.I. [8167

REPEAT THE DOSE

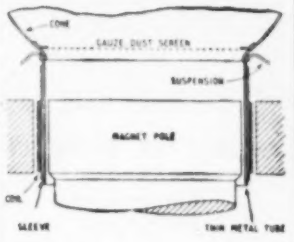

A friend in Yorkshire, where as many Barker sound units can be found per square mile as anywhere else in Great Britain, has just told us that at least six more units have been sold directly from the results given by his own. And he adds the hope that in their turn these others will bring further friends to share the great pleasure and constant joy he himself gets from his own equipment.

As another owner puts it, he is sure that his Barker unit is his best buy in many years of looking for his ideal loudspeaker.

And to-day a letter from New York comes along to order more units and says "We have made tests against some of the best units over here, switching directly from one to another many times. Because of the wonderful transients and smooth frequency response we consider Barker superior to any other of comparable cost. We intend to demonstrate this in our showroom and hope to sell many more for you.

This "chain sale" reaction is and has always been the greatest factor in the steady advance of our business. The Barker patent dual drive and cone is a source of lasting satisfaction which makes people proud of showing their friends what good sound really is, and brings us so many "repeats."

Last month we described the drive illustrated above, and briefly touched on the cone. This is made of special fabric, cut out, ironed, formed, coated with special dope, moulded to final shape under pressure and heat—the whole taking over two hours and much skill. Not cheap, but how well worth while! The 148a and 150 cones differ, the latter giving a flatter overall output and the former a little more upper middle, which many people prefer.

Well, here is the end of our space again. There is one more item we must mention—you can buy Barker units via any good dealer, or direct from us. We supply for cash or on fair H.P. terms.

Why not send a note or card now?

BARKER NATURAL REPRODUCERS

3 Newman Yard, London, W.1

CABINETS & CHASSIS

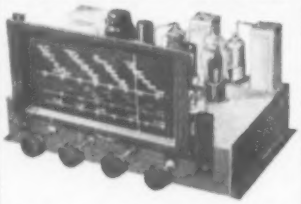

A.C. 5 valve 3 W.B Superhet Radiogram chassis. Absolutely complete kit of parts including detailed wiring diagram £10 15 0
Or fully wired and tested £12 10 0

CABINETS OF DISTINCTION

Send 6d. for our new illustrated cabinet catalogue.

AMPLIFIERS:
4 to 15 watts ... from £3 19 6

Full details from —

LEWIS RADIO CO.
(Dept. 152)
322 HIGH RD., WOOD GREEN, LONDON, N.22.

Callers to —
120 GREEN LANES, PALMERS GREEN LONDON, N.13
(near Bowes Road)
Phone: Bowes Park 6064

PITMAN *Books*

Cathode Ray Oscillographs

By J. H. Reyner, B.Sc. (Hons.), A.C.G.I., D.I.C., etc. A comprehensive account of the practical applications of cathode ray tubes and the theory underlying them. Fourth Edition 15/- net.

"Anyone desiring an understanding of the cathode ray oscillograph cannot do better than purchase this book."
ELECTRICAL TIMES

The Practical Engineer Pocket Book

Edited by N. P. W. Moore, B.Sc., A.C.G.I., D.I.C., A.M.Inst.F. A famous pocket book, now in its 64th year, containing technical data, up-to-date articles on practical aspects of engineering, mathematical tables and formulae, and Technical Dictionaries in German, French and Spanish. Revised edition. Over 750 pages, illustrated. 12/6 net.

"A wealth of useful information."
ENGINEERING AND BOILER HOUSE REVIEW

From booksellers. Published by

PITMAN
Parker St., Kingsway, London, W.C.2

COMPONENTS SURPLUS AND SECONDHAND

SOUTHERN RADIO SUPPLY, Ltd., 11, Little Newport Street, London, W.C.2. See our displayed advertisement page 100. [0016

1,250 push buttons, UX5, 3d; 25K potms, 1,555 IFT, 1/-; 5-pin sockets, 1,800 blocks, 2d. grammets, 9d. doz.; feedthrus, 6d. doz.; 1,500 5d.; .01 5kv. 9d; post extra; s.a.e. lists. ANNAKIN, 25, Ashfield Place, Otley, Yorks. [8157

ELECTROLYTIC conds. (not Govt. surplus) tub. wire end 500vw, 8mf 2/6, 16mf 3/6, 8mf 3/-, 25v 25mf 20/- doz. Al. can 500vw 16-16mf 5/6, mica conds., moulded case, 0.1mf 1,500v dew. 20/- doz.—Ward, 9, West Cliff, Dawlish, Devon. [0214

SPOTLESS surplus, not ex-Govt.: I.f. trans., gen 465, 10/6 pair; fresh stock condensers, 450vw 8mf 2/6, 16mf 3/-, 8+8 4/-, 16mf 4/-; special 52×52×16-350vw, 6/6; 1,550v, 6/- doz.; mains trans., 300-0-300, 6v, 5v, 100m.a., 23/-; speakers, 10in p.m., 1 weight, 19/6; semi-midget v. controls, 1 sp. 500K and 2meg, 3/-; standard size, all values, 3/-; s.w. 4/6; new lists, stamp.—Radio Unlimited, Elm Rd., London, E.17. [0062

EDE'S STUDIOS, Chelsea.—H.M.V. speakers, 6in brand new and boxed, 9in mains energised with heavy duty pentode trans., 1,500 ohm field, 17/6 plus 2/6 post; 6½in heavy duty magnet and trans., 1,500 ohm field, 17/6 plus 2/6 post; 8in 1,500 field less trans., 12/6; 8in P.M. with trans., 12/6; less trans., 10/-; EMI autochangers, 8in and 10in records, new and boxed but less spindle, £9 ea.; H.M.V. push-button units, mechanical type, 6 buttons, complete with 2 gang condenser, 25/- ea.; H.M.V. motor tuning units, complete with 5 gang, £2/5; 12+12 mfd small can 350 wkg, 2/9 ea.; metal rects, 125v 60ma, 5/6 ea.; Metalair electric clocks, 4½in dial, brand new and box, listed at £5, 18/9, our price 35/-; post 2/6. [8117

SPECIAL offers.—Reconditioned AC-DC Ekco chassis, complete with valves, speaker, is mounted on the chassis and tested, £5/10 plus 6/- carr.; Philco cathedral model AC-DC 5 valves, reconditioned, including cabinets repolished, £5/5 plus 6/- carr.; note, the Ekco components advertised in previous issues are still available. [8117

EDE'S STUDIOS, 255, Fulham Rd., Chelsea, S.W.3. Tel. Flaxman 5567. [8117

G. A. RYALL, "Utopia," Mayfield Rd., Herne Bay, Kent, offers post free bargains at reduced prices to clear: all new and unused: Paxolin panels, ½in, 12×9, 5/9 each or 55/6 doz. 4 new resistance panels with 50 ¼-½-1-2 watt colour coded best make carbon resistors, 5/-; condensers, mica, 0.01 350v, 6 1/6; 0.004mf 1,200v wkg, 6 1/6; 4mf mansbridge, 400v wkg, upright, terminals, feet, 2/3; 1mf ditto 500v wkg, 2 1/6; 250pf silver mica, 6 1/6; special note, insulation of all condensers perfect; 18mf, that is 11×7mf 250v wkg non-inductive mansbridge type, large construction, heavy terminals each side, 8/6 each; high resistance headphones with good type carbon microphone, padded double bands, sponge earpads, all wired into large 4-cleft plug ex R.A.F., good condition as new, 6/9 set; meters, 2in voltmeters, 0-500v with separate series (5ma) resistance, 6/9; best make open scale 2in 0-5ma, 6/9; good make 0-50ma 2½in, 6/9; and 2in circular 0-50ma, best make, 6/9; first two meters are square front; all front flange fixing, one type plug in meter, 2in circular, full scale deflection 1.5ma, scaled 0-5 in 50 divisions, 12/6 each; 5 high stability vitreous resistors, 2in on Govt. grade paxolin panel with insert sockets and bolts for mtg, 2-25,000 ohms and 1-150 ohms, 1/5 per panel; miniature red panel mtg. lamp holders in brass with 12v bulb and cap, 5 yards of best quality twin flex, 1/9; electrolytics, 1/9; over 2 yards screened twin cable 1/3, 3 yards light twin circular 1/3, 3 yards light triple circular 1/3, 2-way plug and socket 1/3, triple plug and socket 1/3, Bakelite toggle, 250v 2p ST 1/3, and 2p DT changeover, 1/9, 4-gang 0.0004 condensers, straight type, 5/10; 5-gang bar type 0.0004, 5/10; switches, miniature instrument, 8B 2p 6-way 1/3, standard Yaxley type, 2p 3P 6-way, 1/3; smaller type 3b 2p 6-way, total 5 poles, 2/-; one type soldered tags, 5 poles 4-way, 1/3; all single hole fixing; standard Yaxley type 8B 3P 9-way, 1/3 each; special offer control boxes, size 6×5×5 approx., contains Yaxley type switch, 5-pole 4-way, well finished 2½in pointer, knob, Bakelite switch 2p ST and ditto 2p DT CO, both 250v, 5 die-cast pegs, 5-18p, 5/6 each post free, new and boxed; radio mains filters, four divisions, fully screened in metal cases with fixing feet, 5/9 each; metal boxes, black finish, 9½×7½, abt. 3¼in depth, with 1¼in paxolin lid, feet for wall or bench, new, 6/9 complete. [0205

WORK WANTED

HOT press and transfer printing, long or short runs.—Wiltshear's, 9, Liverpool Gardens, Worthing, Sussex. [8092

CAPACITY and labour available light assembly of control, repetition work, long runs, own transport.—Box 6694. [8141

PRECISION wave-winding.: Govt. sub-contract work welcomed.—A. P. Creston, 549, Copnor Rd., Portsmouth. Tel. No. 21775. [7762

ASSEMBLY, wiring, conversions carried out, one or quantity, trade or private.—Radiovizier, 377 High Rd., London, N.22. [8107

DRAUGHTING, tracing and photoprinting services; estimates free; contractors to the Ministry of Supply and the Admiralty for drawing and tracing work to their requirements and specifications; sub-contracting work of this nature undertaken.
DRAWING & TRACING Ltd., 456a, Ewell Rd., Tolworth, Surbiton. Tel. Elmbridge 7406. [5975

SURPLUS BARGAINS

MANUFACTURERS' & BANKRUPT STOCKS
LIMITED SUPPLIES ONLY

We can offer for immediate delivery

JUST PURCHASED!

LARGE CONSIGNMENT OF RESISTORS
ALL VALUES: ¼, ½, 1, 2, and 3 WATT.

Low and High Resistance Headphones

EX. W.D. AERIALS—BRAND NEW—CAN ALSO BE USED AS FISHING RODS.

12 ft. Light Steel Aerials in 3—4 ft. sections, screw-in or plug-in type

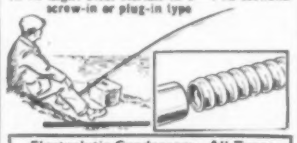

Electrolytic Condensers—All Types

Yaxley Type Switches, Mansbridge Condensers (Oil filled and Jelly), Burgoyne Solder Guns, Tannoy Handmikes, Dinghy Transmitter Sets, Adhesive Tape, Coaxial Cable, Magnifying Lenses, Rubber Masks, Speakers, Coaxial Plugs and Sockets, etc., etc.

Your enquiries are invited.

WHOLESALE AND EXPORT ONLY

For further bargains call at our Counter or write for NEW bulletin.

RADIO MERCHANDISE
COMPANY LIMITED
65, Farringdon Road, London, E.C.1
Telephone: HOLborn 8377. Quote Dept. W.W.

DUKE & CO.

SALVAGE RADIO CHASSIS. Prices from £9/17/6 for a 1952 All-Wave 8/9 with latest pin-type Midget Valves. Satisfaction guaranteed or money returned. These chassis were made to sell at three times this price. Many satisfied customers. Write for leaflet giving full particulars, with valve line-up and chassis sizes of all models.

PERSONAL RADIO. Price £5/19/6 for a 4 valve TRF Kit with complete instructions for assembly, our popular Midget receiver for A.C. or Universal, with choice of ivory or fawn plastic cabinet. Assembled ready for use—35/- extra. Point-to-point wiring instructions enable any amateur with the minimum of set-building experience to build it.

TRANSFORMERS. Standard O.P. Trans. 3/9 each. Post 1/-. Salvage Mains Trans. 200-0-200, 6.3 v. 2 a., 7/9 each. Post 1/3. All tested and guaranteed.

METAL RECTIFIERS. Price 7/9 each. Post 1/6. Made by Westinghouse. 4 wave type. As used in TV circuits. With suitable condensers will give a supply of 250 v. an output of 330 v. at 220 m.A. A real Bargain.

TELEVISION PRE-AMPLIFIERS. Price 7/6. Complete with valves. In excellent condition. Postage 1/-. A few only.

WIRE WOUND RESISTANCES. Price 1/9 each. Postage 3d. A precision wound job on a ceramic former giving 1 meg. 1 watt at 1% accuracy. Made by The International Resistance Co. Philadelphia. In brand new condition. Size 1¼in. by ⅝in. dia.

EARPHONES. Price 8/9 per set. Post 1/-. Type DLR2 and DLR3. A super-balanced sound powered phone, which is so sensitive that it can be used as a telephone without batteries. A very limited stock of these ex-W.D. units, in excellent condition.

COLOURED FILTERS FOR TELEVISION SCREENS. Price 10/9 for a 15in. screen, 12/6 for 12in. screen and 19/6 for a 14in. screen. A Colour filter can treble your viewing pleasure. Gives beautiful natural colour tints to the picture. Blue at the top, pink centre, and green at the bottom. Ideal for all open air scenes. Simply attach it to the outer screen.

VALVES. Send a stamp for our new valve list. We are one of London's largest new valve stockists. Also ask for our latest catalogue of Radio and Electrical bargains.

BARGAINS IN WIRE. Nickel Chrome and Spring steel wire. Sizes 0.14in. and 0.32in. in 50 yd. and 25 yd. reels respectively. Spring Steel wire, 1/- per reel, 3 reels for 4/-; postage 1/-. Nickel Chrome wire, 4/6 per reel, postage 6d. per reel. This wire is unobtainable today at these prices.

Mail orders: 621 Romford Road, Manor Park, London, E.12. GRA. 6677
Retail Sales: 219 ILFORD LANE, ILFORD, ESSEX. ILF. 0295

ALEC Davis SUPPLIES Ltd.

DEPT. W.W. 18 TOTTENHAM CT. RD.
LONDON, W.1 MUSeum 4539 2353

LANE TAPE TABLE complete with heavy duty motor erase and playback heads. **£16 10** - plus 10/- carriage and packing.

OC 2 OSCILLATOR COIL. For use with high or low impedance heads **10** - plus 6d. post.

SCOTCH BOY MC-1-111 MAGNETIC TAPE. 1,200ft. coil **£1 15** -.

LUSTRAPHONE DYNAMIC M.C MICROPHONES.
Low impedance type **£5** - -.
High impedance type **£5 12 6** plus 1/- post.

5-VALVE 3-WAVE BAND SUPERHET CHASSIS. In kit form, complete with 5in. speaker. A really first class kit. All new components. **£9 19 6** plus 2/6 carriage.

2-VALVE PLUS METAL RECTIFIER. 2-wave band T.R.F. kit, complete with speaker and cabinet. Nothing else to buy. **£6 15** - plus 2/6 carriage.

A.D.S. 4W. QUALITY AMPLIFIER incorporating a pre-amplifier stage with bass boost. Also suitable for use with a radio feeder unit. Complete set of components for above amplifier including cabinet. **£7 15** -. Complete amplifier constructed and fully tested **£9 17 6**.

A.D.S. 10W PUSH-PULL AMPLIFIER. Low and high level inputs. 3, 5, 7 or 15 ohms output. Details on request. **£12 17 6** plus 2/6 carriage.

A.D.S. MEDIUM-WAVE RADIO FEEDER UNIT. EF36 R.F. Amplifier, EF36 Triode connected detector. This unit is ideal for quality reproduction of local transmissions. Power required 250 v. 15 mA, 6.3 v. 3 a. Complete in Black Crackle Cabinet **£6 12 6** plus 1/6 carriage.

SPEAKERS.

3in. 3 ohms W.B Stentorian	19 6
5in. 3 ohms ELAC	15 -
8in. 3 ohms Manufacturers surplus	17 6
10in. 3 ohms Manufacturers surplus	39 6

All plus 1/- Post.

"DENCO" ALIGNMENT OSCILLATOR D.A.C.1. This unit provides a modulated signal for the alignment of I.F. Amplifiers, etc. The two standard frequencies of 465 kc/s and 1.6 mc/s are selected by the turn of a switch. Price **49 6**, plus 1/- post.

MAINS TRANSFORMERS (all upright mounting). Pri. 200-240 v., sec. 350-0-350 v. 80 mA., 0-4 v. 5 a., 6.3 v. 4 a., 0-4-5 v. 2 a. Price **21** -, plus 1/- post. Pri. 200-240 v., Sec. 3 v., 4 v., 5 v., 6 v., 8 v., 9 v., 10 v., 12 v., 15 v., 18 v., 20 v., 24 v., 30 v., 2 a. Price **19 6**, plus 1/- post.
Pri. 200-240 v., Sec. 250-0-250 v. 60 mA., 6.3 v. 3 a., 5 v. 2 a. Price **21**/-, plus 1/- post.
Pri. 200-240 v., Sec. 350-0-350 v. 80 mA., 6.3 v. 3 a., 5 v. 2 a. Price **27 6**, plus 1/- post.
Pri. 200-240 v., Sec. 250-0-250 v. 120 mA., 6.3 v. 7 a., 5 v. 3 a. Price **28 6** plus 1/- post.
*Pri. 200-240 v., Sec. 350-0-350 v. 120 mA., 6.3 v. 5 a., 5 v. 3 a. Price **37 6**, plus 1/- post.
Pri. 200-240 v. sec. 425-0-425 v. 150 mA. 6.3 v. 4 a. 5 v. 3 a., **52 6** plus 1/- post.
Pri. 200-230 v., 6.3 v. 1.5 a. Price **7 6**, plus 6d. post.
Pri. 200-240 v., sec. 12 v. tapped 6.3 v. 2 a., **21 9** plus 1/- post.
Pri. 200-230 v., 4 v. 2 a. Price **7 6**, plus 6d. post.
Brand New VCR97 Tubes, 39 6, plus 5/- carriage.
250 v. 60 mA H Wave Metal Rectifier, 10 - plus 9d. post.
3,000 ohm Colvern Type 901 Pots, 3/9 each.
10,000 ohm Colvern Type 901 Pots, 3/9 each.
9in. White TV Masks, 3/6 each, plus 6d. post.

CHOKES: 20 Hy. 10 mA. 1,000 ohms **5 6**
30 Hy. 20 mA. 1,000 ohms **6 6**
50 Hy. 30 mA. 1,000 ohms **6 6**
10 Hy. 75 mA. 750 ohms ..... **6** -
20 Hy. 60 mA. 500 ohms **9 6**
10 Hy. 100 mA. 300 ohms ..... **14** -
10 Hy. 120 mA. 200 ohms ..... **15** -
13 Hy. 120 mA. 170 ohms **17 9**

Postage and packing, 9d. extra.

Prices subject to change without notice.

FULL MAIL ORDER FACILITIES

Shop Hours: Monday-Friday 9-5.30 p.m. Sats. 9-1.

WANTED, EXCHANGE, ETC

RG cabinet for Peerless chassis 1148; reasonable.—Box 6696. [8147

TV Baird portable wanted; open inspection.—Hartshorn, 35, Mansfield Rd., Ilford, Essex. [8160

WANTED, dynamometer, a.c. test set, also oscilloscope type 559A, also L050A oscillator.
LESLIE DIXON & Co., 214, Queenstown Rd., Battersea, S.W.8. Macaulay 2159. [0176

ALDIS signalling lamps.—Large quantities of A genuine Aldis pattern lamps required.—Box 6689. [8154

KLYSTRONS 725 A/B and E.E.8 telephones, any condition.—Harris & Gillow, 93, Wardour St., London, W.1. [8145

DECCA (pre-war) portable all-wave radiogram (one which requires repair considered).—Payton, 7a, St. Giles Sq., Northampton. [8136

WANTED, laboratory test equipment including standard signal generator, watt meter, oscilloscope, bridges, recorders; send price and details to
HATFIELD INSTRUMENTS, 175, Uxbridge Rd., Hanwell, W.7. Tel. Ealing 0779. [0057

WANTED, HRO coils, Rxs, etc., A.R.88s, BC348s, S27s, etc.—Details to R.T. & I. Service, 254, Grove Green Rd., London, E.11. Ley. 4986. [0165

WANTED, BC348, AR88, R1155, R107 or similar receiver, BC221 frequency meters, test equipment, condensers, amplifiers.—Quotation to Box 6728. [8169

WANTED, set manufacturers' or ex-Government radio equipment, large or small quantities of valves, electrolytics, speakers, meters, also components.
LOWE BROS., 199, Mile End Rd., London, E.1. Ste. 2579.

COPPER wire and transformer laminations urgently wanted; top prices paid, or similar goods in exchange.—Porchester Electrical, 15-16, Gerrard St., London, W.1. [0212

WANTED.—Valve tester, must be modern design and in perfect condition; cash waiting.—N. R. S., 16, Kings College Rd., London, N.W.3. Primrose 8514. [8131

TRANSFORMER laminations and copper wire urgently wanted; top prices paid, or similar goods in exchange.—Porchester Electrical, 15-16, Gerrard St., London, W.1. [0211

VALVES, type 805, 807, 815, 852, 100th and 250th, urgently required; good prices paid.—Details, Pype-Hayes Radio, 606, Kingsbury Rd., Birmingham, 24. Tel. Erdington 4942. [8025

WANTED, RCA speech amplifiers type MI-11220 J or K and Ariel tuning units BC 939 A; offers, stating quantity and price to—PCA Radio, The Arches, Cambridge Grove, W.6. [0080

WE pay highest price in the trade, modern test equipment, tape recorders, modern radio and television receivers, car radios, amplifiers, record-changers, etc., etc.; call, write or send.
MILLER'S RADIO, 58a, Newport Court, Charing Cross Rd., near Leicester Sq. Tube. Ger. 4658. [7905

WE purchase all types of domestic or ex-Government radio receivers and equipment; send full details or call and collect cash, large or small quantities.—Wm's Wireless Stores, 48, Stafford St., Wolverhampton. [0146

WANTED, BC-610 Hallicrafters, RCA ET-4336 transmitters, SX-28, AR-88, S-27, HRO receiver and spare parts for above; best price.—Write Box 864, c/o Spiers, Service, 62, Centurion Road, Brighton, Sussex. [0061

WANTED AN/APR-4 receiver, any units; any other good quality U.S. surplus radio and radar tubes, test sets, laboratory equipments, etc.; give condition and price in first letter.—Littell, Farhills, Box 26, Dayton, 9, Ohio, U.S.A. [6346

URGENTLY wanted.—VHF test equipment, TS47AP, TS174U, TS69AP, TS34, TS124, BC221s and any other types; valves, klystrons, magnetrons, 723/AB; receivers, RCA AR88s, S27s, SX28s, 827GA and any late types; microwave equipment or spares; highest prices given; please write, call or telephone Gerrard 8410; prompt attention assured.—Universal Electronics, 27, Lisle St., Leicester Square, London, W.C.2. [0219

NOTICES

BRITISH SOUND RECORDING ASSOCIATION MEMBERSHIP of the Association is essential to all actively engaged or keenly interested in high quality sound recording and reproduction; the annual fee is most reasonable and within the reach of all; the 1951-2 lecture season is, as usual, very successful, and arrangements are also in progress to further increase our activities in the provinces; the publications of the association are extensive and include the journal, "Sound Recording and Reproduction"; full information is given on list P.104, this also includes particulars and prices of our special and exclusive test records; membership of the association is world-wide and growing rapidly; particulars are given in the new brochure and this, with a membership application form and P.104, may be obtained from the membership secretary—Harrie J. King, 48, Mount View Rd., North Chingford, London, E.4, England. [0119

REPAIRS AND SERVICE

TELEVISION, trade servicing by highly skilled engineers.—F. H. Hellyar, Ltd., Riv. 5484-5. [9003

COIL PACK

Model 320

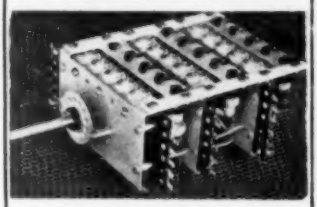

5-waveband coil unit

A comprehensive pre-aligned assembly consisting of switch, complete set of aerial, H.F. and oscillator coils and all associated trimming and padding condensers for 5-waveband operation with tuned H.F. stage on all bands. All coils have dust iron cores for inductance adjustment. A six position switch is used with provision for pick up connections and H.F. muting on the sixth position. For use with any of the standard frequency changer valves (6K8, ECH35, etc.) and an I.F. frequency of 470 Kc.

Ranges: 1, 13—40. 2, 30—100. 3, 80—200. 4, 200—550. 5, 900—2000 metres.

Price £5.5.0 plus tax.

All parts for the above can be supplied separately if required (tax free).

Circuit diagram of this pack is available free.

Send S.A.E.

Circuit diagrams for complete receivers are in course of preparation together with calibrated glass scale and scale plan.

TELEVISION COMPONENTS

"Electronic Engineering"—
Focus Coil
Deflector Coils
Line Output Transformer

Deflector Coils and Line Output Transformers suitable for Viewmaster are also available.

I.F. TRANSFORMERS Iron Core Tuned 472 Kc. Per pair, **15**/-

ALLEN
COMPONENTS LTD

CROWN WORKS,
197, LOWER RICHMOND ROAD,
RICHMOND, SURREY

'Phone: Prospect 4463

THE
BRITISH NATIONAL
RADIO SCHOOL
ESTD. 1940

NOW IN OUR THIRTEENTH YEAR AND STILL

NO B.N.R.S. STUDENT HAS EVER FAILED

to pass his examination(s) after completing our appropriate study course.

NOTHING SUCCEEDS LIKE SUCCESS

and we have every reason to believe that we can help YOU to increase your PRODUCTIVITY, i.e. your EARNING POWER!

A.M.Brit.I.R.E. and
CITY and GUILDS Radio and Telecommunications Exams, etc., etc.

Please mention this advert. and send for free booklet to :—

STUDIES DIRECTOR
BRITISH NATIONAL RADIO SCHOOL
86, ADDISCOMBE ROAD, CROYDON
Phone : Addiscombe 3341

L.S. QUESTIONS

Which to Choose. Those we list are each well known, picked for value and quality in their price and size.

Technicalities. Have you read C. S. Briggs' books? Informative but easy reading.

Supply. We have stocks of those types listed, but find increasing difficulty in getting fresh supplies. If you want one of these models order now! Other makes available from time to time. Send enquiries.

Goodmans Audiom 12in., £8/12/6; **W.B.** Duplex 10in., £6/6/0; **W.B.** 10in., 3Ω, *also newly available* 15Ω, £2/4/6; 9in., £1/16/9.

* Sound Reproduction " 2nd Edit. 11/-, post free.
* Loud-Speakers " 3rd Edit. 7/8.

AMPLIFIER ECONOMY

THE GRAMOPHONE Amplifier gives a high fidelity performance over 30-20,000 c.p.s.; 8 watts output with only 0.15 per cent. harmonic! Such performance is only usually attainable at a cost of over £30. Yet you can make this amplifier together with a pre-amp. giving flexible tone control for under £19, or buy both ready-made for 22 gns.

Full specification on request. Constructional details with diagrams, 1/6 post paid.

GRAMOPHONE EQUIPMENT

Collaro 3-speed changer, the most advanced of its type. Wonderful value in this new form mounted on rexine covered plinth ready for use. Microcell head, dual purpose sapphire, £15.11.6. Two Hi-fi magnetic heads, £17.16.8.

Chancery GPX Microcell Pick-up. With one head, 53/6; two heads, 84/6.

Pick-ups, motors and playing units of other makes available. Details on request.

QUALITY MART

Mail Orders Only. Note New Address :
8 Dartmouth Park Avenue, London, N.W.5

REPAIRS AND SERVICE

A SCOTCH unit winding service.—ALL types of transformers, chokes, field coils, etc., rewound and manufactured to highest standards, write for details.—WILFLO PRODUCTS, 250-254, Brand St., Glasgow, S.W.1. Tel. No. Ibrox 0140. [7947

MAINS transformers rewound, new transformers to any specification.—MOTOR rewinds and complete overhauls, first-class workmanship, fully guaranteed.—F.M. ELECTRIC Co., Ltd., Potters Bldgs., Warser Gate, Nottingham. Est. 1917. Tel. 5855.

LOUDSPEAKERS repaired promptly.—Model Loudspeaker Service, 54a, Bullingdon Rd., Oxford. [6919

MULLARD & Philips neg. feedback output trans., special rewind service, delivery by return, 1 year guarantee.—A. McLuckie, 141, Lowther St., Carlisle. [7944

MAINS transformers rewound or constructed to any specification; prompt delivery.—Bede Transformer Co., Ltd., Bedeswar, Bede Trading Estate, Jarrow. [5196

REPAIRS.—E.H.T., mains and O.P. transformers, field coils and chokes; also armatures and motors; new transformers designed to any specification, all work fully guaranteed.—WILLESDEN TRANSFORMER Co., Ltd., 20a, Church Lane, Church Rd., N.W.10. Tel. Willesden 7093. [0076

ELECTRICAL measuring instruments of every make, multi or single range, repaired and standardised, prompt attention.—The Electrical Instrument Repair Service, 329, Kilburn Lane, London, W.9. Tel. Lad 4166. [5715

REWINDS and conversions to mains and output trans., clock coils, fields, pick ups, etc., from 4/6; pp equipment a speciality; all work guaranteed.—N. L. Rewinds, 32, Blackbird Hill, N.W.9. Tel. Wordsworth 7791. [8156

BERNARD J. BROWN can supply individual designs and constructional data for radio/television amplifiers kits assembled or built to order; callers only by appointment.—55, Goldhawk Rd., Shepherds Bush, London, W.12. Tel. Riverside 3519. [0217

A 12 months' guarantee with all our rewinds, vacs, drills, gram armatures, transformers, conversions, to specifications, etc.; also special vac. motor service with 2 years' guarantee; price lists, etc.—H. G. Millett & Co., 60a, Gladstone Rd., Boscombe. [4108

24-HOUR service, 6 months' guarantee, any transformer rewind, mains outputs and t.f.s., etc., all types of new transf. etc., supplied to specification; business heading or service card for trade prices.—Majestic Winding Co., 180, Windham Rd., Bournemouth. [6520

L. COTTENHAM still at your service for your loudspeaker repairs and transformer rewinds; vacuum cleaner motors rewound and repaired, including new commutators fitted; trade service, guaranteed workmanship, quick delivery.—Send to Loudspeaker Repair Factory, Whetley Lane, Bradford, Yorks. [7859

A SERVICE with a smile, by F.R.I., great repair and winding service all speakers, osc., r.f., h.f., coils, etc., mains, special, trans and tele, rewinds all armature, fields, electric motor rewinds up 1hp, engineering, electrical work, send it to F.R.I., they will help, outside television service, London and near, electrical contracting, experimental work.—79, Church Hill Rd., East Barnet. [0112

MISCELLANEOUS

W. WORLDS, '46 to '50, complete and in good order, offers.—Box 6612. [8047

METALWORK, all types cabinets, chassis, racks, etc., to your own specifications.—PHILPOTT'S METAL WORKS, Ltd., (G4BI), Chapman St., Loughborough. [0208

WALNUT radiogram cabinets, stamp leaflets.—Cabinetware, Ltd., 8, St., Blackburn.

WALNUT radiogram cabinets, stamp details.—E. Wisker, 501, Hale End Rd., Highams Park, E.4. [6942

MANGANIN (Mn Cu/Ni) wire, 48 s.w.g. and upwards.—Philips Electrical, Ltd., Mitcham 5471 (extension 32). [8171

TV. cabinets, baffles, consoles, etc., to your own design measurements and finish, no enquiry too small or too large.—Write or 'phone, Ashdown, 98, Hertford Rd., N.9. Tot. 2621. [7934

SIGNAL lamps, ex-U.S., ammo and battery boxes (wood and metal), folding spades and covers, entrenching tools, etc., wanted.—H. Pordes, 19, Nettleden Avenue, Wembley, Middx. Wem. 0632. [8100

PANEL, insulating material, ¼in thick, very stiff, rectangular pieces, at least 50 sq. in. sample 3d, 6/6 per doz, 31/6 per ½ gross, £3 per gross, black or brown.—K. R. Whiston, New Mills, Stockport. [8173

ALLSCREWS, Ltd. for B.A. screws, nuts, washers, studding, grub-screws, bolts, soldering tags, woodscrews, etc., plain or nickel or cadmium plated, one-gross packets or large quantities; stamp for lists.—270a, King St., Hammersmith, W.6. Riv. 7762. [5426

COPPER wires enamelled, tinned, Litz, cotton, silk covered all gauges; B.A. screws, nuts, washers, soldering tags, eyelets, ebonite and laminated bakelite panels, tubes, coil formers, Tufnol rod; headphones, flexes, etc.; latest radio publications, full range available; list, s.a.e.; trade supplied.—Post Radio Supplies, 55, Bourne Gardens, London E.4. [0159

TV-ITIS, a complaint suffered by many who have no black screen; our conversion kit will change your ordinary television set into a black screen set; price 9/6, post free; will fit any size of set from 12in tube downwards, no stickers, no screws, no glue, and can be removed and replaced at any time; trade enquiries invited.—Unit Light Manufacturing Co., 19, Queen Street, Blackpool. [0221

The House for Quick Delivery

The following Goods Ex-Stock.

Cash with Order or C.O.D.

PLESSEY Multi-Speed Auto Record Changer. 10in.-12in. at 78 r.p.m. 10in.-12in. at 33⅓ r.p.m. 7in. at 33⅓ r.p.m. 7in. at 45 r.p.m. Virtually no needle changing. Simple design and construction, extremely easy to operate. Price including Tax, £23/13/-.

B.S.R. G.U.4. Three Speed Gramophone Unit complete with lightweight Pick Up, and High Fidelity crystal Head. Price including Tax, £9/19/11.

Limited number of G.E.C. Multi-Beam Loudspeakers. List Price £35. My Price £10/10/-. New, in original packing. Carriage extra.

ACOS G.P. 20, complete with either Standard or L.P. Heads, £3/11/5.

ACOS Heads, Standard or L.P., £2/3/4.

GARRARD Standard Playing Unit with Pick-Up, £6/3/2.

COLLARO Standard Playing Unit with Pick-Up, £6/10/6.

LEAK TL/12 Watt "Point One" Feedback Amplifier, £28/7/-.

LEAK RC/PA/U. Remote Control Pre-Amplifier, £9/9/-.

LEAK V.S. Superhet Tuner Unit complete with Valves, £37/2/4.

Send me your order for all your : Wharfedale Speakers.

A. ERNEST BUCHAN
(M.O. Dept.), 28 Belmont Street,
Aberdeen. Phone 23579

SOLONS FOR ESSENTIAL JOBS!

Use SOLONS for the jobs that matter—this modern precision tool makes soldering speedier, simpler and more reliable. 5 models: 65 watt with oval tapered and round pencil bit; 125 watt with oval tapered and round pencil bit; 240 watt with oval tapered bit; each with 6 feet 3-core Henley flexible. Voltage ranges from 100 to 250.

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD.
51-53 Hatton Garden, London, E.C.1

Write for Folder Y.10.

HENLEY SOLON ELECTRIC SOLDERING IRONS
FOR INDUSTRIAL USE

GALPINS

ELECTRICAL STORES

408 HIGH ST., LEWISHAM, LONDON, S.E.13

Tel.: Lee Green 0309 *Near Lewisham Hospital*

TERMS: CASH WITH ORDER NO C.O.D.

All goods sent on 7 days' approval against cash.

EARLY CLOSING DAY THURSDAY

MAINS TRANSFORMERS (NEW). Input 200/250 volts in steps of 10 volts, outputs 350-0-350 volts 100 m amps 6.3 volts 8 amps twice, 4 volts 4 amps, 5 volts 4 amps **65**/- each, carriage 3/6, ditto, 450-0-450 volts 250 m amps 6.3 volts 8 amps twice 4 volts 4 amps, 5 volts 4 amps **68**/- each, carriage 3/6, another input as above, output, 500-0-500 volts 250 m amps 6.3 volts 8 amps twice 6.3 volts 4 amps, 4 volts 4 amps, 5 volts 4 amps, **70**/-, carriage 3/6. Another, wound to (electronic) specifications, 350-0-350 volts 200 m amps 4 volts 8 amps, 4 volts 4 amps 6.3 volts 5 amps, 0/2/6.3 volts 2 amps **63**/6 each, carriage paid, another input as above output 500-350/0-350-500 volts 250 m amps 6.3 volts 6 amps 0-2-6.3 volts 2 amps, 0-4.5 volts 4 amps twice, **67**/6 each, carriage 3/6.

MAINS TRANSFORMERS (NEW). Input 200/250 volts in steps of 10 volts, outputs 350-0-350 volts 180 m amps 4 volts 4 amps 5 volts 3 amps, 6.3 volts 4 amps, **39**/6 exc. post 1/6, another 350-0-350 volts 150 m amps 6.3 volts 8 amps, 0/4.5 volts 4 amps, **39**/6 each, post 1/6, another 500-0-500 volts 150 m.a. 4 volts 4 amps C.T., 6.3 volts 4 amps, C.T., 5 volts 3 amps, **42**/6 each, post 1/6, another 425-0-425 volts 160 m amps 6.3 volts 4 amps, C.T. twice 5 volts 3 amps, **42**/6 each, post 1/6.

SWITCHBOARD. 4in. scale 4mp. meters, moving coil meters, 100 to 250 amps., complete with shunt, **30**/- each, post 1/6.

EX RADAR MAINS TRANSFORMERS 250 volts input 50 cycles 1 phase, output 4500-5500 volts approx. 30 m/amps 6.3 volts 2 amps, 4 volts 1½ amps 2 volts 2 amps, these transformers are new immersed in oil, can be taken out of the oil and used as television transformers giving output of 10 m amps, overall size of transformers separately 3½in. × 4½in. × 4in. and 3in. × 3in. × 2½in., price **£3 10**/- each, carriage paid.

ROTARY CONVERTERS. 24-28 volts D.C. input, 1,200 volts 70 m.amps D.C. output, **10**/- each, P.P.

TYPE 101 R.F. UNITS (NEW) containing 6 valves including grounded grid triode V.H.F. 24 volt Universal motor, numerous resistances and condensers, etc., **35**/- each, carriage 3/6.

RECTIFIERS (NEW) D.C. output 36 volts 50 amp., complete with mains transformer 230 volts A.C. input 50 cycles 1 phase output to match the required voltage for the rectifier, **£15**/-/- per set, carriage 10/-.

EX-NAVAL ROTARY CONVERTERS. 110 volts D.C. input, output 230 volts A.C. 50 cycles, 1 phase, 250 watts capable of 50% overload, weight 100 lbs, price **£10 10**/- each, carriage forward.

AUTO WOUND VOLTAGE CHANGER TRANSFORMERS, tapped 0/110/200/230 volts 350 watts, **48**/6 each, post 1/6, as above but 500 watts **62**/6 each, carriage 2/6, as above 200 watts, **35**/- each, post 1/6.

MAINS TRANSFORMERS (NEW) suitable for spot welding, input 200/250 volts, in steps of 10 volts, output suitably tapped 1 for a combination of either 2-4-6-8-10 or 12 volts 50-70 amps, **87**/6 each, carriage 7/6.

ELECTRIC LIGHT QUARTERLY TYPE CHECK METERS, all for 200/250 volts A.C. 50 cycles 1 phase, 5 amp load, **17**/6 each, post 1/6, 10 amp **21**/- each, post 1/6, 20 amp load, **25**/- each, post 1/6.

MAINS TRANSFORMERS (NEW). 200/250 volts input, in steps of 10 volts, outputs, 0, 6, 12, 24 volts 6 amps, **37**/6 each, post 1/6. Another as above but 10-12 amps, **48**/6 each, post 1/6, another as above but 25-30 amps, **70**/- each, carriage 3/6, another input as above, outputs 18-30-36 volts, 6 amps, **42**/6 each, post 1/6.

EX-R.A.F. ROTARY CONVERTERS. 24 volts D.C., input 50 volts, 50 cycles, 1 phase at 450 watts output, complete with step-up transformer 50 to 230 volts, **£9 10**/- each, carriage 10/-.

EX-U.S.A. W.D. ROTARY TRANSFORMERS. 12 volts D.C. input, 500 volts, 50 m amps, 275 volts 100 m amps D.C. output. Complete with smoothing switches, fuses, etc., as new, **17**/6 each, carriage 2/6, can be run on 6 volts giving half the stated output.

EX-W.D. ROTARY CONVERTERS. 24 volts D.C. input, 100 volts, 500 cycles, 1 phase at 300 watts output, **£4 10**/- each, carriage 10/-.

PREPAYMENT 1/- SLOT METERS, all calibrated at either ½d. or 1d. per unit 200/250 volts, 50 cycles, A.C. mains, 2 amp. load, **45**/- each, carriage 2/6, 10 amp. load, **57**/6 each carriage 2/6, 20 amp. load, **75**/- each, carriage 2/6.

BOOSTER TRANSFORMERS. 1,500 watts (auto wound), tapped 0/6/10/12/15/200/225/240/250 volts, **£6 5**/- each, carriage 5/-.

MAINS TRANSFORMER. 200/250 volts in steps of 10 volts output 400-0-400 volts, 200 m amps., 6.3 v., 5 a., 2 v. 3 a., 5 v., 2 a., 4 v. 2 a. twice at H.P., **75**/- each, carriage 3/6.

MAINS TRANSFORMERS. 230 volts input, tapped output 0/6/12/18 volts at 4 amps, **32**/6 each, post 1/6. Another auto wound, 230 volts input, output 0/14/17 volts at 30 amps, **45**/- each, carriage 3/6. Another 230 volts input 4 volts 20 amps twice (auto wound), **25**/- each, carriage 2/6.

MISCELLANEOUS

WALNUT radiogram and television cabinets soundly constructed, stamp details.—R. Shaw, 69, Fairlop Rd., Leytonstone, E.11. [0049

ENGRAVING.—On all metals and plastics. Name plates, panels, dials, instruction panels, advertising novelties, etc., etc.; trade enquiries invited.—E. S. Reddish, 17, Standard St., New Kent Rd., S.E.1. Hop. 0505. [7949

ENGRAVING, amateurs and trade could take the opportunity of engraving problems in the future by getting in touch with A. G. Engraving, 19a, Windmill Rd., London, S.W.18. Brass, bronze, ermold, Perspex dials, one knob or repetition really entertained. [0034

FLUORESCENT control ballast, wired, tested, ready for 5ft. 80w tube, 250v a.c., 49/3. 80w brick choke, 22/6. Glow starter lamps, 5/5. battery chargers, 230v. will charge 6v battery at 3 amps, meter, leads, 57/6; metal rects., 12v 2amp full-wave, 8/9; dry battery chargers, 250 a.c., all types up to 3v and 2v accumulators, 16/6.—Maiden Transformer Supplies, 202, Cambridge Rd., Kingston-on-Thames. [0058

SITUATIONS VACANT

ADMIRALTY.

APPLICATIONS are invited from engineering electrical and ship draughtsmen for temporary service in Admiralty Departments at Bath. CANDIDATES must be British subjects of 21 years of age and upwards, who have had practical workshop and drawing office experience. SALARY will be assessed according to age qualifications and experience within the range £320-£545 per annum.

APPLICATIONS, giving age and details of technical qualifications, apprenticeship (or equivalents), workshop and drawing office experience, should be sent to Admiralty (C.E. II, Room 88), Empire Hotel, Bath. Candidates required for interview will be advised within two weeks of receipt of application. [6952

RADIO Engineers.

WE have vacancies for several good class radio engineers; must be able to drive car; permanent posts and good wages for the right men. APPLICANTS should apply in own handwriting, stating age and giving full particulars of training and experience, to JAMES McKENZIE Ltd., 28, Oxton Rd., Birkenhead. [7942

TECHNICAL Assistants.

APPLICATIONS are invited from radar and electronic technicians for appointment as civilian technical assistants, Grade III, in Anti-Aircraft Command units situated throughout Great Britain. Applicants must have experience of the repair and maintenance of radar and electronic equipment and hold the Ordinary National Certificate in Electrical Engineering or its equivalent. Salary range is £460–£575 (in the London area). Starting salary will be fixed according to age, qualifications and experience. Annual increases are payable subject to satisfactory service. Excellent opportunities for promotion to higher grades exist in all areas. Candidates should submit their applications in writing, stating age, qualifications, experience and area preferred, to: Ministry of Labour and National Service, Milton Rd., Weadstone, Middlesex, quoting Order No. 14. [8086

UNIVERSITY of London.

POST-GRADUATE Medical School. ELECTRONICS engineer required to develop biophysics equipment for medical research; applicant should hold the Higher National Certificate or equivalent; salary depending on qualifications up to £580 with superannuation.—Applications, age and details, to the Secretary, Post-graduate Medical School, Du Cane Rd., W.12, by March 8. [8124

GOLD Coast and Nigeria.

SERVICE/SALES engineer required for West Africa by British company selling radio receivers, domestic refrigerators and office equipment. Sound radio and electrical experience essential, refrigeration experience desirable; selected man will be required complete technical training course in our products before proceeding West Africa; good salary and prospects; first-class passage, free furnished quarters, pension scheme. Apply in own handwriting, stating age (preferably between 21 and 26), whether married or single, full details education, qualifications, national service and business experience, original references should not be sent.—Box 6617. [9074

CROWN AGENTS FOR THE COLONIES.

WIRELESS station superintendent (temporary) required by the Gold Cast Government Posts and Telegraphs Department for two tours of 18 to 24 months in the first instance. Commencing salary (including overseas pay and temporary allowance) according to qualifications and experience in the scale £834 rising to £920 a year with gratuity of £25 for each completed period of three months' service. Outfit allowance £60. Free passages. Candidates must possess a Higher National Certificate in Electrical Engineering or equivalent, and have had practical experience in two or more of the following fields: V.H.F. link systems, H.F. communication network, frequency shift keying and teleprinter maintenance, V.H.F. and H.F. direction finding systems, aeronautical navigation aids (ground), manufacture of light engineering equipment. Apply at once by letter, stating age, full names in block letters, and full particulars of qualifications and experience, and mentioning this paper, to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting on letter M.29100.B. The Crown Agents cannot undertake to acknowledge all applications and will communicate only with applicants selected for further consideration. [8144

Come to Classic for

"The Classic Service"

We will ship to any part of the British Isles or Abroad.

All goods advertised are available from Stock at time of going to Press.

AMPLIFIERS AND HI-FI EQUIPMENT

Leak T.12 with Control Unit	**£37**	**16**	**0**
Williamson (Goodsell)	**£40**	**15**	**0**
Quad with Control Unit	**£35**	**0**	**0**
Sound Sales A.Z.	**£32**	**10**	**0**
Quad Radio Feeder Unit	**£26**	**10**	**0**
Leak Radio Feeder Unit	**£37**	**2**	**4**
Chapman Radio Feeder Unit	**£17**	**12**	**6**

PICKUPS AND PICKUP HEADS

Acos GP.20 Standard Head	**£3**	**11**	**5**
Acos Heads, Standard or L.P.	**£2**	**3**	**4**
Brierley pickup and diamond stylus	**£8**	**12**	**0**
Collaro pickup arm	**£1**	**7**	**6**
Collaro crystal dual purpose head	**£3**	**3**	**3**
Collaro Magnetic head	**£2**	**4**	**0**
Decca pickup arm	**£1**	**7**	**6**
Decca Magnetic head	**£2**	**19**	**2**
Garrard pickup with magnetic head	**£3**	**8**	**1**
Leak pickup with ruby stylus	**£11**	**17**	**6**
Leak pickup with diamond stylus	**£18**	**19**	**6**
Connoisseur Super Lightweight P/up	**£7**	**9**	**0**

MOTORS AND AUTO CHANGERS

Connoisseur 2-speed motor	**£22**	**18**	**8**
Connoisseur 2-sp. motor with pickup	**£29**	**7**	**8**
Plessey Auto changer 8-rcd. 3-spd.	**£23**	**13**	**0**
Collaro 3-speed 8 record	**£13**	**10**	**0**
Collaro Single speed S.P.	**£6**	**16**	**6**
Decca 2-speed Motor and pickup	**£9**	**19**	**6**
Decca Deccalian	**£37**	**10**	**0**
Trix Autogram (Garrard RC80)	**£44**	**0**	**0**
Chancery Long Playing attachment	**£3**	**12**	**6**

SPEAKERS AND UNITS

Goodmans Audiom 60, 12in. unit	**£8**	**12**	**6**
Goodmans Axiom 150, 12in. unit	**£10**	**5**	**6**
Decca Corner 3 or 15 ohm	**£21**	**10**	**0**
W.B. 10in. or 12in. units, from	**£7**	**7**	**6**
Wharfedale Units from	**£4**	**14**	**7**
Acoustical Corner Ribbon	**£83**	**0**	**0**
Decca Hi-fi Cabinet Speakers	**£105**	**0**	**0**

TAPE RECORDING EQUIPMENT

Simon Simphonic Model 2B	**£69**	**10**	**0**
Sound Mirror, table	**£69**	**10**	**0**
Sound Mirror, Portable	**£79**	**10**	**0**
R.G.D. Portable	**£99**	**0**	**0**
Bradmaster Tape Desks	**£42**	**10**	**0**
Microphones, Acos, from	**£6**	**16**	**4**
Tapes, Scotch Boy, GEC, EMI, from	**£1**	**5**	**0**
Bradmatic Heads 6RP	**£3**	**15**	**0**
Bradmatic Heads 5RP	**£3**	**5**	**0**

COMPONENTS AND PARTS

Viewmaster television receiver	**£37**	**10**	**0**

Mullard C.R. Tubes, 9in., 12in., 17in. from stock.

Mullard Valves, full range available.

Northern and Scottish Readers send for details of our special H.P. facilities. Wenvoe supplies soon available.

All Prices quoted are Retail Prices including Tax.

Goods despatched by Post or Passenger train. Please include carriage.

EXPORT ENQUIRIES WELCOMED. Goods for shipment free of Purchase Tax. Packing and Insurance extra. Send Stamps for List.

The Classic Electrical Co. Ltd.

"THE HI-FI TELEVISION SPECIALISTS"

352 354 Lower Addiscombe Road, Croydon, Surrey. *Telephone: Addiscombe 6061/2.*

FIDELIA *Plus*

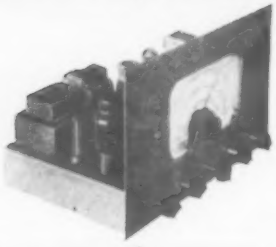

The whole range of Fidelia receivers has variable selectivity, wide-range tone control circuit with separate Bass and Treble controls, audio response of 20-20,000 c/s, triode-operated output stages. The range includes:—Fidelia Standard 7 valve model, £21 15 -.; Fidelia Plus illustrated above has been particularly successful in difficult reception areas, and has a very lively short wave performance. Price £24 5 -.; Fidelia De Luxe 9 valve model, with 7-watt push-pull output stage, £25 5 -.; Fidelia Major 10 valve model, £31 10 -. Data sheets free on request.

Our new "home" faces the main Brighton-Newhaven road. We shall be very pleased to demonstrate any of our equipment by appointment. This includes week-ends, should you be visiting the coast, provided you let us know in advance.

ELECTRO-*Acoustic*-DEVELOPMENTS

2 Amherst Road, Telscombe Cliffs, Sussex.

THE "FLUXITE" QUINS AT WORK

"There'll be no more sitting in night,
We're diddled clean out of the light!
So much for our letters,
At least it's a pleasure,
To know it'll mend with FLUXITE!"

See that **FLUXITE** is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all Ironmongers—in tins from 1/- upwards.

TO CYCLISTS! For stronger wheels that will remain round and true, here's a time tested tip. Tie the spokes where they cross with fine wire AND SOLDER. It's simple—with FLUXITE—but IMPORTANT.

The **FLUXITE GUN** puts **FLUXITE** where you want it by simple pressure. Price 2/6, or filled 3/6.

FLUXITE

SIMPLIFIES *ALL* SOLDERING

Write for Book on the Art of "SOFT" soldering and for leaflet on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1½d. ea.

FLUXITE LTD. (Dept. WW), BERMONDSEY STREET, LONDON, S.E.1.

SITUATIONS VACANT

PHYSICISTS, Radio Engineers, Electronic Engineers.

POSITIONS for Senior and Junior Staff are available for Research and Development work on TV, Electronics and Vacuum Physics. This Company is one of the Pioneers in the development of Television and is still in the forefront of Research and Development in this field. Our organisation is built up primarily to undertake Research and Development work, and we have a large Scientific and Technical Staff engaged on an increasing Government and Commercial programme. Excellent opportunities exist for progressive work on new and interesting developments.

REQUIREMENTS for Senior posts. A British University Degree or its equivalent, in Physics, Electrical Engineering, or Communications Engineering. At least 5 years' Post-Graduate work on Research or Development. Successful applicants will be placed in charge of Research or Development projects being carried out by the Company.

REQUIREMENTS for certain Junior posts. A British University Degree, or its equivalent, in Physics, Electrical Engineering or Communications Engineering. Practical experience not essential, but an advantage.

REQUIREMENTS for other Junior posts. Ordinary National Certificate, or equivalent, in Physics, Electrical Engineering or Communications Engineering. Three to five years' experience on Research, Development or Design of Radio, Electronic or TV Equipment. Successful applicants for Junior posts will join groups working on Research or Development projects being carried out by the Company.

SALARY and facilities offered by the Company: Senior Engineers in range of £650–£1,000 p.a.; Junior Engineers in range of £350–£650 p.a.; depending on age, qualifications and experience. Pensions Scheme. 5-day week. Canteen facilities.

WRITE, giving all particulars of experience, qualifications, age, etc., to Personnel Department, Cinema-Television, Ltd., Worsley Bridge Rd., Lower Sydenham, London, S.E.26. [8149

RUSH RADIO, Ltd., have vacancies for engineers as follows:—

CHISWICK Laboratory.—for television development and telecommunications development.

PLYMOUTH Laboratory.—A senior development engineer for telecommunications work; also a transformer designer for development of small power transformers, pulse transformers, etc., and power supplies.—Write, giving full details of qualifications, experience and salary required, to Chief Engineer, Rush Radio, Ltd., Power Rd., Chiswick, W.4. [8113

MANAGER for March shop, must be good T.V. engineer/salesman.—Box 6421. [8060

A LARGE engineering firm in the London area has a number of vacancies for:—
(1) Senior engineers. Ref. S.E.
(2) Junior engineers. Ref. J.E.
(3) Draughtsmen of all grades. Ref. D.
THE posts are in connection with both important defence projects and long term private venture development work and are permanent and pensionable; these are first-class opportunities and very adequate salaries are available.—Write, quoting the reference "T.E." and the category for which you wish to apply, to the Personnel Manager, Box 6476. [8115

A PROGRESSIVE firm of control instrument manufacturers has a vacancy for:—
APPLICATION Engineer for scientific (Electrical) instruments and vacuum pumping equipment. Will be required to advise customers on application and sell the company's products, negotiate and secure sales. Must have had similar experience with an important manufacturer and possess good commercial background. Corporate membership of I.E.E. or equivalent essential.
WRITE, giving experience (in chronological order), age, qualifications, to Box 6628. [8202

TECHNICAL engineer, to take charge of layout and planning of special electronic products.
TECHNICAL manager to control transformer production.—Write details of experience to All-Power Transformers, Ltd., Chertsey Rd., Byfleet, Surrey. [7965

TELEVISION RADIO repair and installation engineers, learners, salesmen.—Godfrey Radio Television, Norwich. [8091

TRANSFORMER designer for design and quality control of transformers for electronic apparatus.—Box 6095. [7969

REQUIRED, television fault finders, production line work, and television engineers; must be fully experienced.—Write Box 6030. [8106

ELECTRICAL and radio draughtsmen required.—Apply Employment Manager, Vickers-Armstrongs, Ltd. (Aircraft Section), Weybridge, Surrey. [7875

RADIO Engineer required, television experience essential, able to drive.—Barnes & Avis, Ltd., H.M.V., Murphy, etc., 140-141, Friar St., Reading. [8098

RADIO service technician required by motor distributors in Salisbury, thorough technical knowledge of radio and servicing experience essential.
PERSONALITY and appearance important as successful applicant will be responsible for developing the department and its contact with traders and private customers.
FULL details on application by letter for interview by appointment in Salisbury to Managing Director, Avon Motors (Salisbury), Ltd., Rampart Rd., Salisbury. [8048

OPPORTUNITIES IN RADIO

Get this FREE Book!

'ENGINEERING OPPORTUNITIES' reveals how you can become technically qualified at home for a highly paid key appointment in the vast Radio and Television Industry. In 144 pages of intensely interesting matter, it includes full details of our up-to-the-minute home study courses in all branches of **TELEVISION and RADIO, A.M. Brit. I.R.E., City & Guilds, Special Television, Servicing, Sound Film Projection, Short Wave, High Frequency, and General Wireless Courses.**

We definitely Guarantee

"NO PASS—NO FEE"

If you're earning less than £14 a week this enlightening book is for you. Write for your copy today. It will be sent **FREE** and without obligation.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY
388b SHAKESPEARE HOUSE,
17-19 STRATFORD PLACE, LONDON, W.1

BIET

EX GOVERNMENT BARGAINS

H.F. Amplifiers Admiralty Pattern, containing 4 v. 4 a. heater transformer, variable resistance, indicator light, condensers, valve holder, etc., in steel case 12 × 4 × 3in., 15 6, postage 2/6.

Bomb Release Controls, containing relays, toggle switch, indicator lamp, selenium rectifier, 32 mf. condenser, Yaxley switch, thermal switch and various small condensers and resistances, all contained in metal box, black crackle finish, a good experimenter's lot, also useful as a power tuner, will give 20 different speeds, 16 6, post 1/9.

Camera Control Units, containing 2 P.O. 3000 type relays (one relay with 4 ohm winding is suitable as current relay for model railways), press switch, toggle switch, indicator light, condenser, etc., all contained in grey metal box 8in. × 5in. × 3in., 10 6, postage 1/9.

Uniselectors P.O. Type three banks of 25 contacts. Solled 7 6 and 12 6. 1600 as new 25 -, postage 1/6.

Relays American Miniature Type, 250 ohm, 2 6, postage 6d. Ideal for model railway control, etc. Ditto 650 ohm D.P.D.C.O., 3 -, postage 6d.

Receivers 1125. Complete with 2 valves, 10 6, postage 2/-.

Remote Contactors, 12 v. stepping mechanism, 120 impulses for 1 rev. of pointer, glass front, resetting control, on-off switch, flex, etc., will make an ideal 0-120 magnetic counter for coil winding, etc., brand new 5 6, postage 1/-. Has sound possibilities as electric pendulum clock.

Microphones. Electro-magnetic microphone fitted switch, 3 6, postage 6d. M.C. type 5 6, postage 6d. Tannoy sound power metal handle, 9 6, postage 1/-. Tannoy Bakelite with handle, 3 9, postage 6d.

Cathode Ray Tubes. VCR97, 45 -, postage 3/6. VCR139A, 25 -, postage 2/6. VCR138A, 25 6, postage 2/6. VCR517 23 6, postage 2/6. 3BP1, 25 -, postage 2/6.

Chassis. 8in. × 5in. × 11in. with cover, 5in. × 5in. × 11in., ideal for power packs, amplifiers, etc., 4 6, postage 2/-.

A. T. SALLIS
93, North Road, Brighton, Sussex
Phone: Brighton 25806

ALPHA OFFERS

WAX CARTON CONDENSERS. All 500 v. D.C. with flexible leads. 4 mfd., **1 8** ; 4·4 mfd., **3 4** ; 8 mfd., **3** - ; 8·4 mfd., **3 9** ; 8·8 mfd., **4 6**.

TUBULAR CONDENSERS — WIRE ENDS. Metal case, cardboard or P.V.C. covered. 16 mfd. 500 v. D.C., **4 6** ; 8 mfd. 500 v. D.C., **3** - ; 8 mfd. 450 v. D.C., **2 11**.

WEARITE "P" COILS. Types available PA2, PHF2, etc., **3** - each.

CONDENSERS. .1 mfd. 350 v., .02 mfd. 750 v., .01 mfd. 1,000 v., **7** - doz. ; .001 mfd. 1,000 v., **4** - doz. Midget .01 mfd. 600 v., **7** - doz.

MOULDED MICA CONDENSERS. .0001, .0002, .0003, .00027, .0004, .0005, .0008, .01, .001, .002, .003, .005. All by well known makers, mixed wire and tag ends. All **5 6** doz.

DIAL BULBS. 6.3 v., 15 a., 15 mm., Ball Type, M.E.S., **6 6** doz. 6.3 v., 3 a., 10 mm. Tubular Type M.E.S., **8 6** doz.

METAL RECTIFIERS. 300 v. 80 mA., **5 9** each ; 2 v. 1 amp., **5** - each ; 250 v. 80 mA., **5 9** each ; 12 v. 3 amp., **18 6** each. 12 v. ½ amp., **1** - each.

COOKER SWITCH. Heavy duty type, four positions, 30 amp., **4** - each, post and packing 1 6.

SPEAKERS. All 2 to 3 ohms unless otherwise stated. Midget 3in. Speaker for personal sets, **12 9** ea. 2½in. P.M. Lightweight, 15 ohms, **12 6** ea. 3½in. P.M. Lightweight, **13 6** ea. 5in. P.M. Lightweight, **13 9** ea. 5in. P.M. Lightweight, **13 9** ea. 5in. Standard, **14** - ea. 8in. P.M. Lightweight, **13 6** ea. 10in. P.M. Lightweight, **34 6** ea. 10in. P.M. Standard, **32 6** ea. Truvox 12in. P.M. Lightweight, **70** - ea. 6½in. P.M. Standard, **13 6**. ea.

PLUGS AND SOCKETS. Co-axial Plug and Socket, Pye Type, complete. Suitable for ¼in. or ⅜in. cable, **7 6** doz. Bulgin Mains Plug and Socket, with flexible socket and chassis mounting plug, **2 6** ea. 2 pin Plug and Socket, non-reversible. Ex Ministry. Black bakelite, **1 3** ea. Belling-Lee 5 Pin Chassis mounting socket with flexible plug, **2** - ea. Belling-Lee 7 Pin Chassis mounting plug with flexible socket, **2** - ea. Bulgin Heavy Duty Mains Plug and Socket, non-reversible, **3 9** ea.

CAR HEADLAMP AND SPOT BULBS, 6 7 volts, 18 watts (a great bargain), **1 6** ea.

PUSH BACK WIRE, 7/0076 size, colours Yellow, White, Blue, **2d.** yd.

TAG BOARD, 2 Tag Type, **1 6** each.

FLUORESCENT STARTER LAMPS, S.B.C., **2 6** ea.

VOLTAGE SELECTOR PANELS with Shorting Plug, **6d.** ea.

100 P.F. AIR SPACED TRIMMERS, 1 - ea.

2½ mm. HIGH VOLTAGE SLEEVING, per yard length, **3d.** yd.

BRASS SPINDLE COUPLINGS, Two Grub Screws, **6d.** each.

PAXOLIN SHEET, 6in. x 6in. x 1·32in., **1 3** ea.

OUTPUT TRANSFORMERS. Fully shrouded output transformers, 2 ratios, at **1 11** each. A.W.F. power pentode type, **4 6** each.

CO-AXIAL CABLE, Etc. Standard 75Ω, **1 2** yd. ; twin feeder ribbon type, 300Ω, **7½d.** yd. Any length cut.

G.P.O. TYPE PRESS SWITCH, **1 3** ea.

H.F. CHOKES. Pile wound, **1** - ea.

VIBRATOR TRANSFORMERS. 12 v., **11 6** ea.

SPADE TERMINALS. Red and Black, **3** - doz.

VOLUME CONTROLS. 100K. Ohms, ¼ Meg., ½ Meg., 1 Meg., 2 Meg., all with Single Pole Switch, **4 3** ea. ¼ Meg., ½ Meg., 1 Meg., less Switch, **2 6** ea. 50K Ohms ¼ Meg., 1 Meg. Midget Type, **1 9** ea. 1 Meg. Log. S.P.S., **4 9** ea.

EX EQUIPMENT, 5K(Ω, 50K(Ω, 20K, 25K(Ω, 10K(Ω, Carbon **1** - ea.

5(Ω, 200(Ω Wire Wound, **1 6** ea.

Post orders only. C.W.O., C.O.D. Postage extra under £2. Send **3d.** stamp for full list.

ALPHA RADIO SUPPLY CO.
5 6 Vincis Chas., Victoria Square, LEEDS 1

SITUATIONS VACANT

TRANSFORMER winding foreman to take complete charge of small shop.—Write details of experience to All-Power Transformers, Ltd., Chertsey Rd., Byfleet, Surrey. [7966

SENIOR Draughtsmen experienced in work on electronic equipment. Salary according to age and experience.—Apply Mullard Equipment Ltd., Brathway Rd., Wandsworth, S.W.18. [8111

RATEFIXERS required, experienced in assembly and wiring, batch production of radio instruments.—Apply Mullard Equipment Ltd., Brathway Rd., Wandsworth, S.W.18. [8110

MURPHY RADIO, Ltd., offer the following vacancies in an expanding programme covering the field of domestic equipment and many branches of electronic development:—
(1) SENIOR development engineers having degrees in engineering or physics with post-graduate experience of equipment design who would be capable of leading a development team.
(2) DEVELOPMENT engineers with similar academic qualifications having less or no industrial experience.
(3) A SPECIALIST engineer with good academic qualifications having a sound knowledge of components and raw materials used in the radio industry; this vacancy is only suitable for an applicant who is experienced in electrical measurements and life testing of components.
THESE posts are permanent and pensionable and offer good opportunities for advancement.—Applications giving full details of experience and qualifications should be forwarded to the Personnel Manager, Murphy Radio, Ltd., Welwyn Garden City. [8050

LEADING London radio and television dealer urgently requires fully experienced service engineers; must be able to drive; good permanent positions for the right men.—Box 6626. [8092

PILOT RADIO, Ltd., require immediately fault finders and testers for radio and television alignment; five-day week with good rates of pay; call or write to—Park Royal Rd., N.W.10. [8041

MANUFACTURERS of radios, televisions and records require immediately a technical writer for the compilation of service notes and the handling of some correspondence.—Box 6616. [8072

TELEVISION service engineer (manager) for service department of retail shop in N.15; must be top grade, permanent position; £10 week plus bonus for qualified man.—Box 6638. [8140

TESTERS and calibrators required, previous electrical testing knowledge and experience, or radio testing experience.—Apply Electrofo Meters Co., Ltd., Abbey Rd., Park Royal, N.W.10. [8040

TEST Service Engineer with experience of audio amplifiers, experience of magnetic tape recorders preferred but not essential; write giving details of experience and salary required to—Box 6782. [8175

E. K. COLE, Ltd. (Malmesbury Division), invite applications from electronic engineers for permanent posts in development laboratories engaged on long-term projects involving the following techniques:—
1. Pulse Generations & Transmission.
2. Servo Mechanisms.
3. Centimetric & V.H.F. Systems.
4. Video & Feedback Amplifiers.
5. V.H.F. Transmission & Reception.
6. Electronics as applied to Atomic Physics.
THERE are vacancies in the senior engineer, engineer and junior grades. Candidates should have had at least three years' industrial experience in the above types of work together with educational qualifications equivalent to A.M.I.E.E. examination standard. Commencing salary and status will be commensurate with qualifications and experience. Excellent opportunities for advancement are offered with entry into Pension Scheme after a period of service. Forms of application may be obtained from Personnel Manager, Ekco Works, Malmesbury, Wilts. [7822

MULLARD Research Laboratory in Surrey has a number of vacancies suitable for honours graduates in Physics, Electrical Engineering, Mathematics, or persons with other but similar qualifications for work on:—
1. LINE Communications.
2. RADIO Communications.
3. RADAR.
4. COMPUTORS.
5. ELECTRONIC Measurement and Control Devices.
6. METAL Physics.
7. ELECTRON Accelerators.
8. TELEVISION.
9. ULTRASONICS.
PREVIOUS experience in one or more of these fields is an advantage, but is not essential, and equal significence is attached to the candidate's potential ability to apply himself to such work. IN addition to these posts there are a number for which several years' experience in addition to academic qualifications is essential:—
1. DEVELOPMENT of carrier systems and filter design.
2. COMMUNICATION receiver and transmitter design.
3. RESEARCH and development associated with television reception.
RATES of pay are proportional to qualifications, experience and age. Publication of original work wherever possible is desirable and is encouraged. Successful candidates are eligible for the superannuation scheme.
APPLICATIONS should be made in the first case to the Personnel Officer, Mullard Research Laboratory, Redhill, Surrey. [8148

OUTSTANDING VALUE IN BRAND NEW EQUIPMENT

COLLARO AUTOCHANGERS, model RC511, new single speed model with interchangeable plug-in pick-up head, plays nine records, reject mechanism, beautifully finished unit plate, A.C. operation. Price with magnetic head **£11 16 9**, or with Acos GP27 crystal head, **£13 2 6**, carr. 5/-.

COLLARO 3-SPEED AUTOCHANGERS, model 3RC511, as above but for 33⅓, 45 and 78 r.p.m. Price with one dual purpose Acos GP27 head, **£15 10 6**, or with two separate GP27 heads for Std. and L.P. **£18 15** -, carr. and pack. 5/-.

COLLARO 3-SPEED GRAM. UNIT, model ACJ 514, with pick-up and autostop. Price with dual-purpose GP27 plug-in head, **£11 9 9** ; with two sep. GP27's, **£14 8 9**, carriage and pack. 3 6.

DECCA GRAM MOTORS, adjustable for 78 or 33⅓ r.p.m., **£3 17 6**. Ditto with switch giving instantly 33⅓, 45 and 78, **£6 8 6**.

DECCA XMS PICK-UPS, with Std. and L.P. hi-fi magnetic heads, **£7**, post 1 6. Ditto fitted with Acos crystal cartridges, **£4 4 6**.

G.P.20 PICK-UPS with standard or L.P. head, **£3 11 5**, post 1 6, separate heads (Std. or L.P.), **£2 3 4**, post 8d.

GARRARD GRAM MOTORS. Model AC6, centre-drive, variable speed with full 12in. turntable, **£6 7 6**.

RECORD PLAYER CASES, well made, measure 15¼in. x 13¼in. x 7in., beautifully covered in brown rexine, fitted hinged lid, clasps and sprung carrying handle. Price complete with uncut motorboard, **57 6**. Post 2 6.

MICROGRAM CABINETS, ex ENSA, very robust, measure 17¼in. wide x 15¼in. back to front x 8¼in. high overall with uncut motorboard and speaker grill at front, reinforced corners, two locked clasps and carrying handle, finished blue rexine. Price **52 6**. Post paid.

SYMPHONY No. 1 (AMPLIFIER) by N.R.S. The most versatile domestic Audio Amplifier on the market to-day. Independent control of Bass, Middle and Top, separate Scratch Cut, negative feedback. For A.C. 200-250 v., input for magnetic, crystal and hi-fi pick-ups and Tuner. 5-watts output. Price : 3 ohm model, **9¼ gns.** ; 15 ohm model, **£10 7 6**, carriage 5/-.

SYMPHONY No. 2 MARK II. New model with 10 watts push-pull triode output, breathtaking realism, hum level negligible—90 db down. Woden main transformer, choke and output transformer for 3, 7.5 and 15 ohms. Input for ordinary and hi-fidelity pick-ups. Tone control system same as No. 1. A truly magnificent instrument for only **15 gns.**, carriage 5/-.

ABOVE, but fitted with remote control panel on flyin; cable, **£17**.

No. 2 PUBLIC ADDRESS AMPLIFIER Same chassis and power parts as No. 1 Symphony but simple one knob tone control. 15 watts push-pull output, 2 inputs with separate volume controls for fading mike and gram. Complete kit **10 gns.** Ready built, **£11 19 6**.

BASS-REFLEX CABINET KITS give superb bass response and top (¼in. patent timber). Full instructions supplied. Bin. speaker model 2/6. 6in. high x 1ft. 3in. x 1ft. deep. Price **85** - ; 10in. speaker model, 30in. x 16in. x 13½in., **97 6** ; 12in. speaker model, 30in. x 17½in. x 16in., **107 6**. Any of above ready built for 7 6 extra. Carr. in any case, 7/6.

FOR CALLERS ONLY. Above B.R. Cabinets also now available, finished in high-class veneers to match customers' individual furnishing schemes. Examples on view.

WODEN OUTPUT TRANSFORMERS, high-grade, input to match two 6V6's or two 6L6's, output tapped 3, 7.5 and 15 ohms, **25 6**, post paid.

NORTHERN RADIO SERVICES

16 Kings College Road, London, N.W.3
Phone: PRImrose 8314

POTENTIOMETERS

Wire-wound and Composition types. Single, Ganged, Tandem Units. Characteristics: linear, log., semi-log., non-inductive, etc. Full details on request.

RELIANCE

RELIANCE MNFG., CO. (SOUTHWARK), LTD.
SUTHERLAND ROAD, HIGHAM HILL,
WALTHAMSTOW, E.17
Telephone: Larkswood 1165

SITUATIONS VACANT

EXPERIENCED radio/television engineer required; top wages paid, bonus scheme, etc., good prospects for right man.—Apply Lasky's R.T.C. Ltd., 116-118, Roman Rd., Bethnal Green, E.2. Tel. Adv. 2025. [8075

SHOP Foreman required for line assembly of communications receivers and transmitters; must have had several years' experience of this type of work; salary according to qualifications.—Rees Mace Marine, Ltd., Oulton Works, Lowestoft. [8174

£500 to £800 per annum offered to experienced electronic engineers in expanding section of modern factory near Cardiff; pension scheme.—Full details to Personnel Manager, Simmonds Aerocessories, Ltd., Treforest, Glamorgan. [8196

ADMIRALTY.—Vacancies exist for electrical and/or mechanical engineering draughtsmen in Admiralty Research and Development Establishments located in the vicinity of Weymouth, Portsmouth, Teddington (Middlesex) and Baldock, Herts.

DRAUGHTSMEN experienced in light current electro-mechanical, precision mechanical and electronic equipment are particularly needed.

CANDIDATES must be British subjects of 21 years of age and upwards, who have had practical workshop experience (preferably an apprenticeship) together with Drawing Office experience.

APPOINTMENTS will be in an unestablished capacity, but opportunities will occur for qualified staff to compete for established posts.

THE salaries offered, depending on age, experience, ability and place of duty, will be within the range £320-£575 p.a.

HOSTEL accommodation is available at some establishments.

APPLICATIONS, stating age and details of technical qualifications, apprenticeship (or equivalents) workshop and drawing office experience, should be sent to Admiralty (C.E.11), Room 951, Empire Hotel, Bath, quoting DM.R.D. Original testimonials should not be forwarded with application. Candidates required for interview will be advised within two weeks of receipt of application. [7958

DRAUGHTSMEN, senior and junior, required; experience in electronics and light electrical engineering an advantage.—Apply by letter, stating age, nationality and experience, to E.M.I. Engineering Development, Ltd., Pentelow Works, Wells, Somerset. [8125

ENGINEER with good knowledge of radio components and design experience in this field required for interesting liaison post.—Applications should be sent to Personnel Department (ED/70), E.M.I. Engineering Development, Ltd., Hayes, Middlesex. [8054

SENIOR design draughtsman required by manufacturers of electrical and electronic equipment; a thorough knowledge of materials and production methods is essential; the salary will be commensurate with qualifications and experience.—Box 6652. [8109

DESIGN engineer required to take charge of audio frequency section of development department of large wire broadcasting company; work would be in South-West London.—Write, giving particulars of qualifications, experience and salary required, to Box 6690. [8135

DRAUGHTSMEN.—Senior and junior electro mechanical and circuit draughtsmen required for work on electronic computing apparatus; pension scheme operates.—Apply Head of Communications Laboratory, Redifon, Ltd., Broomhill Rd., Wandsworth, S.W.18. [8061

AN electrical engineer required for investigation and quality control work in radio valves and other electronic devices. Inter B.Sc. standard or equivalent.—Apply Personnel Superintendent, The Edison Swan Electric Co., Ltd., Cosmos Works, Brimsdown, Enfield, Middlesex. [8119

INSTRUMENT makers and laboratory technicians required by firm of instrument makers in the Guildford area, for work on prototype instruments and electrical equipment; varied and interesting work; canteen; 5-day week.—Write, stating age and experience, to Box 6618. [8076

TELEVISION engineers required by E. London firm with all leading agencies; applicants should have extensive experience and initiative, and will work with 1st class team of engineers; salary according to ability.—Apply to "LB," Leytonia Radio, 828, High Rd., Leyton, E.10. [8022

EXPERIENCED radio service engineer with some television experience required; first-class rates and excellent working conditions.—Write, stating age, qualifications, experience and salary required, to British Relay Wireless Ltd., Services Department, 397, Albany Rd., S.E.5. [7951

ELECTRONIC Engineers are required for development of instruments in an engineering research establishment on Tyneside. Applicants should possess a degree or equivalent and have experience on similar work. Salary according to qualifications.—Write Box 6700. [8099

VACANCIES exist for men with qualifications in electronic engineering or physics for interesting development work of national importance. These posts are permanent and pensionable.—Apply Personnel Department (Ref. 2571), Standard Telephones & Cables, Ltd., North Woolwich, E.16. [8062

TELEVISION engineers wanted at once by important retail house, 12 miles S.E. of Manchester; single men, car drivers preferred; only first-class men should apply for these vacancies; salary £500 p.a. plus optional overtime; prospect of management.—Apply, in confidence, to Box 6619. [8077

WILCO ELECTRONICS

TWIN P.A. LOUDSPEAKERS. Reflex re-entrant type, very sensitive and directional, 8in. diam., 16in. overall. Brand new with matching transformers 4.5 to 1 and 6 to 1 Ratios. Voice coil 7 ohms. Only **75/-**, Cge. & Pkg. 5/-.
POWER MICROPHONE INSERTS. Tannoy self-energising, carbon, which can be used directly with a microphone transformer requiring no external voltage. Diam. 2¼in. x 1in. **5/-** each. Post 6d.
THROAT MICROPHONES. American twin button type with strap lead and plug. **5/-** each. Post 6d.
HEAD SET ADAPTOR. MC38S. High to low impedance. **2/6** each. Post 6d.
RESISTANCE MATS.—Make ideal heating mats for Aquariums, Photographic solutions, Print dryers, etc. Mains voltage. Black Heat, size 10in. x 6in. Price **2/6**, post free.
B.T.H. 16 mm. TALKIE PROJECTORS. Complete. Model S.R.B. also spares.
ACCUMULATOR CHARGERS in black crackle case with fuses and meter. 6 and 12 volts at 4 amps. Bargain Price, **£4 19 6**. Pkg. and carr., **5/-**.
SLOW-MOTION DIALS, 6in. Scaled 0-100, reduction 200 to 1 or direct, ideal for wavemeters, signal generators, etc. Our price, while they last, **5/6** each, post 1/-.
"ELF" CIRCUIT BREAKER, 220 volts 2 amps., size 3 inches round, **10/6**, post 1/-.
CUTTER HEADS. "Recording" high impedance. Amazing bargain, **55/-** ea. Post 1/-.
CUTTERS STYLII, 6/- per dot., large quantity available at special rates.
ACFIL PUMPS. These pumps enable you to fill all accumulators on the bench with the carboy at floor level. Brand new, only **30/-**, post 1/6.
VOLTMETERS. 0-300 M.I. 3½in. flush or surface type, **22/6**. Post 1/6.
HAND MICROPHONES. No. 3 with switch, flex and plug, **5/6**. Post 1/-.
AERIAL RODS. 12in. long, ¼in. diameter. Any number of sections can be fitted together **2/6** dozen; **6/-** for 3 dozen; **11/-** half gross; **20/-** gross.

204 LOWER ADDISCOMBE ROAD, CROYDON.

LOCKWOOD
makers of
Fine Cabinets
and woodwork of every description for the Radio and allied trades
LOCKWOOD & COMPANY
Lowlands Rd., Harrow, Middlesex. Byron 3704

SAMSONS
SURPLUS STORES

26 AERIAL MAST. R.A.F. Type 30. Complete kit consists of 9 Tubular Steel Sections. Length 8ft. Diameter 2in. Set of Pickets, Top Plate, Guys and all fittings. Brand new in Canvas Carrying Bags. Ideal for T.V. Aerial Masts **£8 10/-**, carr. 7/6.
BRAND NEW HOOVER INDUCTION MOTORS 1/6 h.p. 220-240 v. A.C. Single Phase. 1,425 r.p.m. Double Ended Spindle. **£4 17 6**, carr. 6/-. A few available for 110 v.
THERMOSTATS. Adjustable type 37-85° F. approx. **5/6**. Post 6d.
WILLARD BATTERIES. 12 v. 85 A.H., in solid vulcanised rubber. Size 17½in. × 7in. × 10½in. Brand new **£6 10/-**. Callers only.
HEAVY DUTY TRANSFORMERS. Prim. 200-240 v. 50 cy. Sec. 6.3 13 amps. **19/6**, carr. 1/6. Prim. 200-240 v. 50 cy. Sec. 43 v. 5 amps. **25/-**, carr. 1/6. Prim. 200-240 v. 50 cy. Sec. 4.2-4.2 v. 10 amps. **25/-**, carr. 2/-.
SIEMENS INERT CELLS. 1½ v. Size 3in. × 2½in. × 2in. **2/9**. Post 6d.
50-0-50 MICROAMMETERS. Centre Zero Black Scale. 3½in. Panel mounting **25/-**, post 1/-.
300ft. LENGTHS COILS COAXIAL CABLE, with Pye Sockets on each end. **8/6**, post 1/-.
VARIOMETER INDUCTANCES, as used in the No. 19 Set Variometer. **3/6**, post 9d.

169-171 Edgware Road
London, W.2. Tel. Pad. 7851
125 Tottenham Court Road, W.1
Tel. EUS. 4982

All orders and enquiries to our Edgware Road branch, please. Open all day Saturday at the Edgware Road Branch.

"NEO"-MAINTEST

THE PERFECT FAULT FINDER
NEO ELECTRICAL INDUSTRIES LTD.
MANCHESTER 4

Convert that old Gramophone OR OBSOLETE RADIOGRAM into a MODERN All-WAVE RADIO GRAM OR POWERFUL RECORD PLAYER

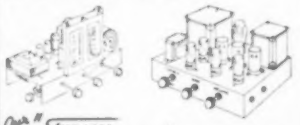

Our "Skyway" DESIGNS" Book gives full details on how to build FOUR first-class Amplifiers and Radiogram chassis. No radio experience is required to understand the clear circuit diagrams and stage by stage wiring plans.

2/6 POST FREE

All parts and materials are easily obtainable, mostly without purchase tax. Performance equal to radiograms costing over £100

only from

Firth RADIOCRAFT Ltd
PHONE 58971
89-91 CHURCH GATE LEICESTER

What's our line?

High Fidelity Equipment by,

LEAK. T12 Amplifier with T.C. Unit	£37	16	0
V.S. Radio Tuner Unit	£37	2	4
SOUND SALES. A.Z Amplifier and Tone Colour Unit	£32	10	0
Tonemaster Amplifier and T.C. Unit	£25	0	0
D.X. Plus One Radio Tuner Unit	£22	14	7
ACOUSTICAL. Q.U.A.D. Amplifier and T.C. Unit	£35	0	0
Pre-set Radio Tuner	£26	0	0
ROGERS DEVELOPMENTS. Williamson Amplifier	£29	0	0
Baby de Luxe Amplifier with T.C. Unit	£25	10	0
R.D. Junior De Luxe with T.C. Unit	£17	10	0
GOODSELL. S.A.8. Amplifier	£15	15	0
Tone Control Unit	£6	10	0
V.S. Radio Tuner	£19	10	0
ARMSTRONG. 7-valve Radiogram Chassis	£25	12	4
10-valve All-wave Radiogram Chassis	£34	12	10
GOODMANS. Axiom 150 12in. Speaker Units	£10	5	6
Audiom 60, 12in. Units	£8	12	6
WHARFEDALE. W12C.S. Speaker Units	£9	0	0
Super 12 C.S.A.L. Speaker Units	£15	0	0
TANNOY. 12in. Dual Concentric Speaker Unit	£27	10	0
BARKER. 150. 12in. Loudspeaker Unit	£18	18	0
VOIGT. Domestic Corner Horn (in white)	£47	10	0
P.M. Unit with 23 k. line gap flux	£40	0	0
LEAK. Moving Coil Pick-up	£14	10	0
DECCA. X.M.S. Pick-up with 78 and L.P. Heads	£7	0	0
CONNOISSEUR. Super Lightweight pick-up	£6	9	0
ACOS. G.P.20 Super lightweight Crystal P.U.	£3	11	5
CONNOISSEUR. 2-speed A.C. Motors	£22	18	8
COLLARO. 3-speed Autochangers, from	£11	16	9
RADIOGRAM CABINETS, from	£12	12	0
CORNER SPEAKER CABINETS, from	£7	10	0
DECCA. G.U.4 Transcription type Player Units	£12	5	6
GOLDRING. Three-way Lightweight Pickup.			

Daily demonstrations of above equipment, hours 9.30 a.m.—6 p.m.; 9.30—1 p.m. Thursday at :—

HOLLEY'S RADIO STORES,

285 CAMBERWELL ROAD, S.E.5.

Open all day Saturday. Callers only.

Phone : RODney 4988

SITUATIONS VACANT

RADIO and television engineers, fully experienced men required at Luton and Bedford; liberal wage and bonus on output permanent and progressive situation; good working conditions with up to date equipment David Robinson, Ltd., Radio Service Dept., 47, St. Peter's St., Bedford. [6085

TELEVISION engineers, with clean driving licence, urgently needed in Holme Moss and Sutton Coldfield T.V areas for outside service; would consider training of first-class radio engineers; if you are a skilled man and are looking for a permanent well-paid position,—Write to Box 6606. [8058

SENIOR and junior electronic development engineers required. H.N.C and degree standard experience in U.H.F. and centimetric work an advantage.—Apply by letter, stating experience, nationality and salary required, to E.M.I. Engineering Development, Ltd., Pemleigh Works, Wells, Somerset. [8126

ADMIRALTY—Technical Class Grade III vacancies exist in the Naval Ordnance Inspection Department for staff with knowledge of electronics. The posts are mainly in the London area and the duties involve acceptance tests and inspection of electronic equipment at manufacturers' works.
CANDIDATES must be British subjects at least 25 years' of age and should have served an apprenticeship or had equivalent workshop training, followed by experience in the manufacture of electric and electronic equipment. Possession of Ordinary National Certificate, preferably in telecommunications, or an equivalent City and Guilds Certificate, is desirable.
APPOINTMENTS will be temporary and unestablished. Opportunities may occur at a later date for qualified staff to secure established appointments which would carry possibilities of promotion to grades with higher salary scales.
THE Technical Class Grade III salary scale for the London Area is £460 × £20—£575 per annum and the point at which applicants will be entered within this range will depend on age, experience and ability.
APPLICATIONS, stating age and details of technical qualifications, apprenticeship (or equivalent) and experience should be sent to the Inspector of Naval Ordnance, Middlesex House, Royal Arsenal, Woolwich, London, S.E.18. Original testimonials should not be forwarded with application. Candidates required for interview will be advised within two weeks of receipt of application. [8046

TECHNICAL assistant required for interesting work in connection with high frequency cable testing; previous experience not essential, but applicants should hold national certificate or equivalent qualifications.—Apply in writing to Siemens Brothers & Co., Ltd., Ref. 425, Woolwich, London, S.E.18. [8164

ELECTRICAL draughtsmen required for electrical, radar and radio installation design work on aircraft; aircraft experience not necessary provided applicant has a sound electrical engineering training.—Apply in first instance to Personnel Manager, Scottish Aviation, Ltd., Prestwick Airport, Ayrshire. [8058

ACOUSTICS.—Research and development engineers with good theoretical knowledge of acoustics. Design of high fidelity loudspeakers desirable but not essential. Good salaries for right men; state age, qualifications, past experience and salary required.—Goodmans Industries, Ltd., Axiom Works, Wembley 1200. [8068

A NEW defence project of National importance being undertaken by a well-known aircraft company located in the northern outskirts of London, offers highly progressive and interesting posts for suitably qualified applicants; vacancies exist in senior (salaried grades) and for junior engineers in various categories :—
(a) PHYSICISTS with experience in electronic problems.
(b) PHYSICISTS with experience in optical work.
(c) ELECTRONIC engineers with Servo-mechanism experience.
(d) ELECTRONIC engineers with experience of low frequency work and measuring systems.
(e) ELECTRICAL engineers with experience in small motor design and development.
APPLICANTS for senior posts should possess a good University degree and preferably should have some industrial experience.
APPLICANTS for junior posts should have a good industrial experience, be qualified either by City & Guilds Certificate or by Inter B.Sc.
WRITE full details, qualifications, experience, age, salary sought, to—Box A.C 65488, Samson Clarks, 57/61, Mortimer St., W.1. [7405

RADIO television salesman, single, car driver, wanted by busy retailers near Manchester, really good salary and prospects for a keen, energetic man 25-40 years, who thoroughly understands his profession. If you are a "customer server" please do not apply.—John Shinn & Sons, Ltd., Leigh, Lancs. (Pop. 50,000.) [8078

DRAUGHTSMEN (senior and junior) required in research department for design and detail work on special radar and electro-mechanical equipment; West London area.—Write, giving full particulars of experience, age and salary required to Box A.E. 694, Central News, Ltd., 17, Moorgate, London, E.C.2. [7959

RADIO engineer required for the development of switches and similar components for high frequency and tropical use; good prospects for man having right kind of training and experience, and house available if married; salary according to experience.—Address applications to General Manager, A.B. Metal Products, Ltd., Abercynon, Glam. [8116

A WINDOW WORTH LOOKING INTO

Television Coil Formers. With iron dust cores. Polystyrene, 1in. x ¼in. with single hole fixing, 6 BA, **6d.** each, **5/6** per dozen.
Television. 1 mfd. high-voltage condensers "Mansbridge" type, 5000 volt. "No Trouble," very limited number left. **2/-** each
Television. EF50 (VR91) Boxed, brand new, **7/6** each.
Television. Diode Holders. **3d.** each; Cradle type, **6d.** each; Ditto, Polystrene, **8d.** each.
Television. Wire-Wound Pots 10k, 20k, 25k, 50k. All at **2/-** each.
Television Dural Aerial Masts. Telescopic from 15in.—7ft. 6in. long, ideal for making your own Television Aerial, **4/6** each.
Wavemeters. Ex-W.D. Type W1185a, crystal controlled 4 switched bands 20-30 Megs. 30-45 Megs. 45-68 Megs. 68-100 Megs., A.C. mains operated, 200-250 volt 50 cycle, complete with valves and crystal. **£14** each.
Micro-Amp Meters, Brand New and Boxed. 0-100. 2½in. Scale. **39/6** each.
Special Offer. Condensers 16 x 16 x 16 Mfd. 450 working, brand new, **3/6** each.
Micro Switches. Several types available. Large stocks, please let us have your enquiries.
Switch. Suitable for the Williamson Amplifier. Single pole 6 way 5 bank, **3/6** each.
Ex-W.D. 2-Valve Battery Amplifiers. Complete with 2-volt driver and Q.P.P. output valve. Brand new. Ideal for mic. or gramophone, **12/6** each, valves alone are worth this.
Bendix Command. 12/14-volt input plug-in type Rotary Transformers, output 250 volts 60 M.a. Very limited number only, **29/6** each.
Moving Coil Headphone Microphone Sets. Ex-W.D., **10/6** per set. Limited number only available.
Rotary Convertors. 24 volt D.C. input, 230 volts A.C. 50 cycle output at 100 watts. **92/6** each.
Welding Transformers. Input 230 volt A.C., output 15 volts 80 amps. **82/6** each.
Midget Wire-Wound Volume Controls. 20 ohm centre tapped. ¼in. diameter, ¼in. spindle, large number available **2/-** each.
Chokes. Ex-W.D. 30 Henry 100 M.a., will pass up to 150 M.a., wonderful bargain, **12/6** each.
Chokes. Ex-W.D. 5 Henry 200 M.a., resistance 100 ohms. **5/6** each.
87G Button Base Holders. With bottom screen, large stocks available, **1/2** each.
Bendix Command Receivers, 6-9 Meg., brand new in sealed boxes, with valves and rotary transformer, absolute 100 per cent condition, **99/6** each.
Callers Only. No Post. 8 x 8 x 8 Mfd. electrolytic condensers, 450 volt. Special temptation price, **1/-** each.

Don't forget your postage.

Open all day Saturday.

G. W. SMITH & CO.

(RADIO) LTD.

3, LISLE STREET, LONDON, W.C.2.

Telephone : GERrard 8204/9155.

ODDIE FASTENERS

PAT. 507249

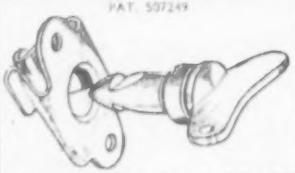

THE FASTENER WITH ENDLESS APPLICATIONS—SIMPLE—POSITIVE SELF-LOCKING. MADE IN A VARIETY OF TYPES AND SIZES.

SPECIAL FASTENERS TO SUIT CUSTOMERS REQUIREMENTS.

WIDELY USED IN THE RADIO INDUSTRY.

Illustrated brochures and other information will be gladly sent on request.

DEPT. "W.W."

Oddie, Bradbury & Cull Ltd., Southampton

Tel.: 55883 Cables: Fasteners, Southampton

TOROIDAL WINDING CAPACITY AVAILABLE

BEL SOUND PRODUCTS CO.
Marlborough Yard, London, N.19
Tel: ARChway 5078

J. C. LADD, WHOLESALE

NEW BOXED VALVES. ALL GUARANTEED. LISTS FREE.

1R5	6B6G	6Q7	5U4	EBC33	8D8
1S5	6J6	6SN7	807	EF39	KT66
1T4	6P19	6V6	866	EF50	MU14
2D4	6J5	7A5	DK91	EF55	ut7150
5U4	6J7	7B7	DAF91	EF91	SP61
6J4	6K7	12K7	DF91	PW4/500	U50
6AG5	6K8	12K8	DL91		X61
6AM6	6L6	5U4	DL94	HVR2	Y63

Some types available in manufacturer's quantities. THO J. C. LADD, 67 DAGNALL PARK, LONDON, S.E.25. 1685

QUARTZ CRYSTAL UNITS

For—

***AIRCRAFT, MARINE AND COMMERCIAL USE* are available in the complete range from 35 kilocycles to 15 megacycles.**

Alternative mountings in standard two-pin A.M. pattern 10X, International octal, and miniature type FT243, can be supplied for most frequencies.

Prices are fully competitive, and we specialise in prompt deliveries for urgent requirements.

WE WELCOME YOUR ENQUIRIES.

THE QUARTZ CRYSTAL Co., Ltd.
63-71 Kingston Road,
NEW MALDEN, SURREY
Telephone: MALden 0334

SITUATIONS VACANT

ILFORD, Ltd., require mechanical draughtsmen with experience mainly concerned with process machinery, particularly of the automatic type; 5-day working week, canteen facilities and staff pension scheme.—Reply in writing, giving age and full particulars of experience and qualifications, to Ilford, Ltd., P.O. Box No. 10, Romford. [8049

TECHNICAL representative required for the Midlands by light electrical engineers, age 25-35, education to G.I.E.E. standard, able to drive car, presentable appearance; salary £500-£600 according to qualifications, plus expenses with prospects; previous selling experience not so important as sound basic electrical knowledge. Write Box 6727. [8146

MURPHY RADIO require engineers with knowledge of magnetic amplifiers and servo-mechanisms; applicants should have the mathematical and engineering knowledge necessary to design systems and undertake original development work in this field.—Apply, giving full details, to Personnel Manager, Murphy Radio, Ltd., Welwyn Garden City. [8146

A FEW vacancies exist for electronic engineers in a highly technical company. The appointments are to be not older than 35 years of age, must have a physical and experimental outlook, and be confident of designing and testing modern pulse circuits. A very good salary for age will be paid, and there are prospects of rapid promotion in an expanding laboratory.—APPLY in writing to Cottage Laboratories, Ltd., Portsmouth Rd., Cobham, Surrey. [8101

MICHAEL RADIO, Ltd., require qualified draughtsman with experience in the mechanical design of radio and electronic instruments for the Government services; salary will be commensurate with ability.—Write, stating age, training, experience and salary required, to the Chief Engineer, Equipment Division, Michael Radio, Ltd., Slough, Bucks. [8069

SENIOR Engineer required to undertake development work on low frequency iron cored components. Previous experience in this subject is essential, and a degree or equivalent would be an advantage. The salary will be in accordance with qualifications and experience. Apply in writing to Advance Components, Ltd., Back Rd., Shernhall St., Walthamstow, E.17. [8097

E.M.I. ENGINEERING DEVELOPMENT, Ltd., have a number of vacancies for engineers and senior engineers on interesting development work in various electronic engineering projects. The posts are for permanent pensionable staff and offer good prospects. Qualification: a degree in Physics or Engineering or equivalent, together with several years' design or specialised experience in the following fields:—

(a) L.F. Equipment.
(b) Television Equipment.
(c) Microwave Techniques.
(d) Pulse Techniques.
(e) Servo Mechanisms.
(f) Test Gear Designs.
(g) Inspection.

Applicants should write, giving full details of experience and type of work required, and quote ED.53, to Personnel Department, E.M.I. Engineering Development, Ltd., Hayes, Middlesex. [8095

A VACANCY exists for a chief electrical and mechanical inspector for progressive electrical manufacturing concern in Wiltshire; preference will be given to applicants who have had several years' experience of similar work, and particularly small transformer and coil winding manufacture; permanent position in expanding organisation engaged on defence work; salary according to experience and ability.—Box 6699. [8150

B.B.C. requires engineers (minimum age 21) of British nationality for duty at transmitter, studio, recording and television centres anywhere in U.K. Essential qualification include degree, Higher National Certificate, or equivalent, in Electrical Engineering. Promotion prospects. Salary £500 with annual increments to maximum £683.—Applications to Engineering Establishment Officer, Broadcasting House, London, W.1, within 7 days. [8095

BELLING & LEE, Ltd., Cambridge Arterial Rd., Enfield, Middlesex, require research assistants in connection with work on electronic components, fuses, interference suppressors and television aerials; applicants must be graduates of the I.E.E. or possess equivalent qualifications together with similar laboratory experience; salary will be commensurate with experience; applications must be detailed and concise, and will be treated as confidential.

ENGLISH ELECTRIC VALVE Co., Ltd., Chelmsford, have vacancies for young engineers to work on radio valve design and development; applicants should be of degree standard; whilst experience of this type of work is desirable, it is not essential and otherwise suitable candidates will be considered.—Write, giving full details, quoting ref. 497, to Central Personnel Services, English Electric Co., Ltd., 24-30, Gillingham St., London, S.W.1. [8165

EXPERIENCED electronic engineers required for interesting development work on a number of projects; applicants should have a sound theoretical background with several years' experience in the design and engineering of prototype electronic equipment; the posts are for permanent staff and offer good salaries and prospects.—Please write, giving full details and quoting ED.65, to Personnel Department, E.M.I. Engineering Development, Ltd., Hayes, Middx. [8051

This UNIQUE BENDER

Quickly and Accurately Forms

Angles, Channels, Sections, Boxes, Lids, Trays, Tanks, Chassis Brackets, Clamps, Clips, Shrouds, Chemical, Electronic and Electric Medical apparatus. Used by leading Radio Manufacturers. Invaluable to Servicing Engineers, Hospitals, Universities and Research Workers.

For 6 page Folder write to:—

A. A. TOOLS (W)
197a Whiteacre Rd., Ashton-u-Lyne

QUALITY TELEVISION COMPONENTS

Scanning and Focus Coils
P.M. Focus Units
5.10 Kv. R.F. E.H.T. Units
E.H.T. and Output Transformers
Line fly-back E.H.T. Units
"TELEVISION CIRCUITS"
3rd Edition, 2/6

HAYNES RADIO Ltd.
Queensway : Enfield : Middlesex

Special offer of **Electric Meters**, 2½in. scale, navy, flu., 3½in. **Milliammeters**, moving coil, 0-500 mA. **Avometer** 0-600 mA., panel mounting. **Thermocouple R.F Meters**, 0-6 amps. **Hot Wire Ammeters**, 0-9 amps. All the above price 7/6, post 9d.

D.C. Ammeters, moving iron, smaller, centre zero, 25-0-25 amps., bar mounting, suitable cars, chargers, etc., 7/6, post 9d.

A.C. Voltmeters (will read D.C.), moving iron, 0-15 volts. Price 9/6, post 9d.

L. C. NORTHALL
16 Holly Road, Quinton, Birmingham, 32
Retail: 416 High Street, Smethwick. Phone: WOO 2166

THE *HAYES RG/135* RADIOGRAM CHASSIS

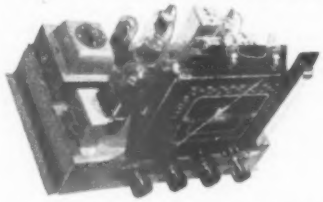

Combining advanced design with a high standard of construction, the RG.135 7-valve circuit includes a 6 watt output stage with negative feedback, and a new tone control system. Price £19.10.- complete. Write for full details of this chassis and also of our popular RG.120 5-valve model, price £14 complete. Demonstrations on Saturdays from 10 a.m. to 6 p.m., or on other days by appointment.

THE *HAYES* COMPANY
1 Alcester Road, Birmingham 13
Telephone South 0202

HAVE YOU GOT

SUPACOILS

NEW CONSTRUCTOR'S HANDBOOK ?

Costs 2'6 only!

1000's already sold

Contents include:—

(a) Circuits of these sets
(1) 2-wave plus Gram. Superhet.
(2) Fixed Station T.R.F. Transportable.
(3) 2-wave plus Gram. T.R.F. Set.
(4) 3-wave Superhet Feeder Unit.
(5) 3-wave Superhet Feeder Unit with H.F. Stage and incorporating Gram. and Quality switching.
(6) 5 v. A.C. all-wave Superhet.
(7) 5 v. A.C./D.C. all-wave Superhet.
(8) Feeder Unit Amplifier and Power Pack.
(9) 6 v. A.C. all-wave Superhet.
(10) 6 v. A.C./D.C. all-wave Superhet.
(11) Signal Tracer.
(12) 4 v. Battery Superhet.
(13) 5-watt Amplifier.
(14) 10-watt Quality Amplifier.

(b) Full constructional details of our very popular 2-wave plus gram. Superhet Coil Pack (extremely simple point-to-point wiring given in detail).

(c) Illustrations of many Receivers you can build with no previous experience.

(d) Complete Technical and Descriptive details of all our products.

(e) Pages of Constructional and Servicing hints.

(f) Many simple formulae in constant use.

(g) Complete Resistance Colour Code.

(h) Catalogue of our extensive Radio Stock forwarded with each Handbook.

A HANDBOOK YOU CANNOT AFFORD TO BE WITHOUT.

It will save you pounds.

Send 2/6 **now** for your copy to :—

SUPACOILS MAIL ORDER OFFICE

98, Greenway Ave., London, E.17

THE W.A.S.P. LONG RANGE INDOOR T.V. AERIAL

We have always been convinced that the largest demand is for a really good indoor T.V. Aerial and, after extensive research, we are proud to announce that we have developed an entirely new type which is highly efficient, simple and inexpensive and when erected indoors it will give comparative results to the standard 'H' type outdoor aerial.

It is in the form of a circle, approximately 5 feet in diameter, and comprises a special type of dipole with reflector and has a front to back ratio of 7 to 1, ensuring high signal to noise ratio. Installation is extremely simple and full instructions are supplied with each aerial.

This is, without doubt, the finest indoor T.V. aerial on the market, irrespective of cost, and can be obtained through all bona-fide dealers at **38/6** or in case of any difficulty, write direct to the manufacturers and patentees.

W.A.S.P. Engineering Co. Ltd.,
Mowbray Drive, Layton, Blackpool

SITUATIONS VACANT

REPRESENTATIVE required by small but well-known and rapidly expanding Surrey firm of radio coil and component manufacturers, to call on manufacturers and wholesalers; own car and knowledge of radio essential; please write, giving details of age, exp., etc.—Box 6695. [8145

CHIEF Inspector required by leading London telecommunications company. In addition to sound knowledge of modern line transmission and carrier practice, applicants must have had wide experience of the testing of components and electronic equipments by the latest methods. Initiative and the ability to lead and reorganise a fairly large department are other essential qualifications.—Write giving fullest details of theoretical training, experience, age and salary required to Box 6651. [8108

AN instrument mechanic is required for duties in the Electronics Section of the Research and Experimental Department; applicants should possess a high degree of mechanical skill, and be able to participate intelligently in both design and manufacture of small electro-mechanical devices; experience in a similar capacity, whilst desirable, is not essential.—Write, stating age, experience, and salary expected to the Personnel Officer, Saunders-Roe, Ltd., East Cowes, I.O.W. [7821

ASSISTANT transformer designer and planning engineer, with specialised experience in line and input transformers and power transformers up to 500 v.a., required for progressive electrical manufacturing concern in Wiltshire; applicant should have experience of planning for production quantities, and sound knowledge of fundamentals and latest techniques is essential; permanent position in expanding organisation engaged on Defence work; salary according to experience and ability.—Box 6700. [8151

PHYSICISTS and electrical engineers interesting and varied work is available in a West London research department, for versatile qualified physicists and electrical engineers on applied measurements—electrical, acoustic and mechanical; good salaries are offered.—Applicants, who should have several years industrial experience of this type of work, are asked to forward full details of education, qualifications, experience, salary required, to Box A.E.781, Central News, Ltd., 17, Moorgate, E.C.2. [8127

McMICHAEL RADIO, Ltd., require senior project engineers in their equipment division development laboratory at Slough. Training and experience in the field of applied electronics (including communications) and experience of working with Government departments are the chief qualifications required; salary will be commensurate with ability.—Write, stating age and full details of training, qualifications and experience, to the Chief Engineer, Equipment Division, McMichael Radio, Ltd., Slough, Bucks. [8070

TELECOMMUNICATIONS draughtsmen in a newly formed and quickly expanding division of the Plessey Co., Ltd.; applicants should have experience of line communications or radio communications equipment and should be capable of undertaking work on own responsibility; the positions give the right of entry to the company's pension fund and life assurance scheme and offer excellent long-term opportunities of promotion; state full particulars to—Personnel Manager, The Plessey Co., Ltd., Ilford, Essex. [8057

TECHNICAL Assistant.—A large light electrical engineering company, in the West London area, require a technical assistant for their engineering laboratory; applicants should have a good working knowledge of domestic electrical and mechanical appliances, including radio, television and industrial electronics; minimum qualification Higher National Certificate (Electrical); special knowledge of electronics an advantage; good conditions and pay; write giving details of age, qualifications and experience to Box 6611. [8044

ENGINEERS or physicists are invited to apply for positions in the following fields of work: (a) electronic circuitry; (b) servo-mechanisms, (c) D.C. amplifiers, (d) micro-wave and transmitters, and (e) test gear for field trials; work will be in experimental research and development teams at Stanmore (Middx); preference will be given to men with some experience and good qualifications.—Apply to the Staff Manager (Ref. GBLC/414), Research Laboratories of The General Electric Co., Ltd., North Wembley, Middlesex, giving age and record. [8057

H.F. heating engineers are required by the English Electric Company for their industrial electronics department; these vacancies are for junior and senior engineers with good experience of valve-type H.F. heaters; these are permanent and progressive appointments offering excellent opportunities for qualified engineers or those with sound practical experience of this class of work; interviews can be arranged for Saturday mornings.—Write, giving full details and quoting Ref. 557c, to Central Personnel Services, English Electric Co., 24/30, Gillingham St., London, S.W.1. [7971

RADAR research and development laboratories in London area require senior engineers and physicists at all grades up to that of project leaders at salary scales of up to £1,500 per annum. Applications are invited from men with sound qualifications and extensive experience in the design of microwave radar systems and associated electronic apparatus. Assistance will be given in obtaining satisfactory local housing; removal expenses from any part of the United Kingdom will be met.—Please write in first instance full details of experience, qualifications, age and salary required, to Rev. GX G.C., Box 6614. [8063

ADCOLA

(Regd. Trade Mark)

SOLDERING INSTRUMENTS *means* SOUND JOINTS *for* SOUND EQUIPMENT

★

***Reduce your* H.R. JOINTING FAULTS**

Any volt range supplied 6.7 to 230/250

Designed for Telecommunications Radar - Wireless Assembly - Maintenance, etc.

MADE IN ENGLAND

- 1/4" dia. bit Standard Model
- 1/2" dia. bit Standard Model
- 1/4" Detachable Bit Type (Factory Bench Line)
- Heating time : 90 seconds
- Consumption : 25 watts
- Weight : 4 ozs.
- Total length of instruments : 9 inches
- High temperature
- Good temperature control
- Handle unaffected by element temperature

Registered Design
(British, U.S.A. & Foreign Patents)

Sole Manufacturers and Distributors :

ADCOLA PRODUCTS LTD.

Gen. Offices & Works : Cranmer Court, Clapham High Street, London, S.W.4. *MACaulay 4272*

CHANGE OF ADDRESS

GENERAL LAMINATION PRODUCTS LTD.

Makers of :—

The Sound Magnet Tape Recorder
Tape heads, motors, parts, etc.,
Portable Sound Equipment,
Gramophone Amplifiers.
Transformers.

Removed to :—

" Sound Magnet " Works,
62, High Street, Plumstead,
London, S.E.18.

(Send S.A.E. for new lists)

—TUNERS—

Our Type 84 is the ideal Quality Tuner for your high quality amplifier. This four-stage Super Het T/set has a lively performance with very low distortion. Fitted variable selectivity 15K.C. and 10K.C. Wave-band coverage 16-50m., 190-550m., 900-2,000m. Using latest Mullard valves EC.H42, EF41, EBF80, 6J7, 6 × 5 tax paid.

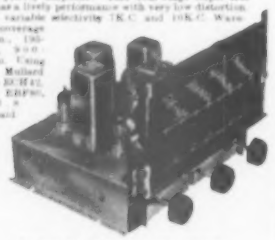

Type 85 with B.F. stage also available.

Manufacturers of Ventex Products

C. T. CHAPMAN (Reproducers) LTD.

RILEY WKS., RILEY ST., CHELSEA, S.W.10

FLAxman 4577-8

Demonstration at **Webb's Radio**, London.

Distributors for S. Wales —

Snell & Haines, Ltd., 132, Western St., Swansea.

The business of

COULPHONE RADIO

has closed down

Any communications to :

SEA VIEW HOUSE, ST. BEES, CUMBERLAND.

Quixo RADIO Cell Tester

Accurate tests
High, Low and Grid
Bias Batteries.
Write for leaflet 30M

RUNBAKEN MANCHESTER 1

G.E.C. GERMANIUM CRYSTAL DIODES

Midget Size, 5/16in. x 3/16in.
Wire Ends for Easy Fixing.
4/6 each, postage 2½d.
Technical Details and Selected Types available.

B.T.H. GERMANIUM CRYSTAL DIODES

Moulded in thermo-setting plastic.
4/6 each, postage 2½d.

SILICON DIODES, 3/6. Postage 2½d.
Fixing Brackets, 3d. pair.

COPPER INSTRUMENT WIRE
ENAMELLED, TINNED, LITZ.
COTTON and SILK COVERED
Most gauges available.

B.A. SCREWS, NUTS, WASHERS, soldering tags, eyelets and rivets.
EBONITE AND BAKELITE PANELS.
TURNOL ROD. PAKOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS.
ERIE AND DUBILIER RESISTORS.
Latest Radio Publications.

SEND STAMP FOR LIST. TRADE SUPPLIED

POST RADIO SUPPLIES

33 Bourne Gardens, London, E.4

SITUATIONS VACANT

TECHNICAL Assistant required for the Commutator Laboratory of a large engineering factory in the West London area; applicants should have served an apprenticeship and should possess Higher National Certificate and Draw ing Office experience if possible; salary at 25 years of age approximately £10 10s per week; write giving details of age, qualifications and experience to Box 6785. [8176

APPLICATIONS are invited for positions in the radio section of the design office of the G.E.C. research laboratories for work at Stanmore (Middx); candidates must be capable of making first-class engineering drawings of sub-assemblies and fully dimensioned details of airborne radio and radar equipments for quantity production; knowledge of inter-services specifications and standards would be an advantage; special starting salaries will be given for outstanding ability.—Write to the Staff Manager (Ref. GBLC/415), Research Laboratories of The General Electric Co., Ltd., North Wembley, Middlesex, giving age, qualifications and experience. [8056

SCUNTHORPE Hospital Management Committee.—Immediate vacancy for technician in Physics Department of Radiotherapy Centre to assist in instrument making, laboratory work, darkroom work and X-ray plant maintenance particularly; applicants with knowledge of building and servicing electronic equipment preferred; electrical engineering qualifications and experience in other aspects of the work advantageous; some radiation work will have to be undertaken; Whitley Council terms and conditions of service present salary scale £410×£15(5) and £20(1) to £475; N.H.S. superannuation scheme. Apply, stating two referees, to Secretary, The War Memorial Hospital, Scunthorpe, Lincs. [8170

TELEPHONE MANUFACTURING Co., Ltd., Sevenoaks Way, St. Mary Cray, Kent, require several men for vacancies in the Engineering Laboratories; the company is engaged in the development, design and manufacture of Telecommunications Line Transmission Equipment including multichannel carrier and associated apparatus; minimum qualifications Higher National Certificate (Telecoms and/or Radio); salaries according to qualifications and experience plus after a qualifying period the benefit of a participating bonus scheme; engineers interested to visit the works in connection with these vacancies should telephone or write the Personnel Manager, for an appointment.—Orpington 6611. [8177

WAYNE KERR require several engineers for design and development work on electronic equipment; the development programme is varied and ranges from S-band oscillators and Q meters to H.F. signal generators. Audio frequency sources, and precision D.C. measuring equipment; there is a particular need for a senior engineer with a good degree and a background of practical achievement, who will take a leading part in the laboratory and who will qualify for a salary in the range £900-£1,250; the salaries for the remaining posts are in the range £600-£950 depending on qualifications and experience.—Write to The Technical Director, Wayne Kerr Laboratories, Ltd., Sycamore Grove, New Malden, Surrey. [8039

B.B.C. requires two technical assistants for maintenance work on communications equipment, including carrier systems and teleprinters. Essential qualifications: good fundamental knowledge of electricity and magnetism, acquaintance with principles of amplifiers and oscillators. Desirable qualifications: knowledge and experience of equipment associated with communications work, such as carrier systems, switchboards and teleprinters, ability to carry out tests on lines and associated apparatus. The vacancies are in Glasgow and Leeds but would be preceded by an extended training period in London. Salary £415 with annual increments to maximum £575.—Applications to Engineering Establishment Officer, Broadcasting House, London, W.1, within 7 days. [8094

TECHNICAL writers (male or female) required to edit reports and prepare handbooks for publication. Qualifications: a good general training in electronics with wide practical experience of electronic equipment, preferably including design experience, and with the ability to write clear English; a marked critical faculty for English composition and technical accuracy is required; several posts are available in all aspects of the following fields: Radar, A.M. and F.M. communication equipment, including sound and television, receivers, gramophone reproduction and C.R.T. and valve manufacture; experience in more than one of these fields is preferred.—Applicants should write, stating age, salary required, etc., to Personnel Department (ED.67), E.M.I. Engineering Development, Ltd., Hayes, Middlesex. [8052

A WELL-KNOWN progressive company has a vacancy in a rapidly expanding commercial department for a technical sales executive for radio and radar apparatus; candidates should have a good university degree together with industrial and/or Government experience, a methodical nature with a flair for organization, and a genuine interest in the varied types of work undertaken by sales engineers; importance will be attached to the adaptability of applicants and to their suitability to handle both technically and commercially a variety of equipments and to deal with customers at all levels; the post is permanent and has very good prospects for advancement; applications will be treated in strict confidence.—Please forward detailed personal information and salary required to Box 6005. [7974

RANSOM
FOR RADIO VALVES

10,000 Valves in stock. If the valve you want is not listed here, send us your requirement; we probably have it.

B.V.A. valves new and boxed at pre-increased prices C.O.D. or C.W.O., plus 1/- postage.

VALVES. HL23, 5/10; EB34, DDL4, DD41, DD91, 6/9; PM2A, LP2, 7/6P, 7/4; 6L6, 6D13C, 41MTL, HL1320, HL91DD, 9/2; 6/30, 10/-; 4D1, 10/9; KL35, UY41, Z22, 2/6SG, UU7, 11/-; 2A5, 7/A, DL74M, HL133DD, 11/7; 1A4P, 12/-; TT4, 12/2; 4s, EB91, 12/7; 6K8, 7A7, 37, 42, 77, 8P4, 5/P, PEN 4VA, 8P13, KT74, KTW62M, MS PEN B, MS PEN TP22, 12/10; 31, 13/3; 7D3, 13/11; 2B7, EF9, EL3, X71, 4THA, 14/-; 6C6, 9A1, 1W4, 500, MKT4/7P, 15/1; 13D2, QP21, H30, 2402P, QP25, 6B8, 6SP7, 15/3; 1s, 15/10; MP PEN, 16/6; 164V, 17/-; 1D5, PM24M, 17/3; 5Z3, 18/3; PC2A, 19/6; EL37, 19/11; DCP, DC8G, 20/-; CBL1, 21/4.

Send stamped envelope for our competitive price list of radio components.

CONDENSERS. 750pF MICA, 2d.; 02 400 v. tub, 3d.; 1 mfd. 600 v. card tub, 1/-; 2 mfd. 150 v. tub, 6d.; 4 mfd. 600 v. oil filled, 4/6; 8 mfd. 500 v. tub can BI, 3/9; 25 mfd. 25 v. solar can, 1/6; 25 mfd. 50 v. card tub, 2/-.

VALVE HOLDERS. 4-pin B.V.A. Pax, 2d.; 5-pin B.V.A. pax, 2d.; 7-pin B.V.A. pax, 6d.; inter octal pax, 3d.; inter octal amp., 9d.; 4-pin U.X. pax, 3d.; 5-pin U.X. pax, 3d.

KNOBS. Walnut hex 1¼in., black 1¼in. dia., black 2in. dia., all ¼in. spindle fixing, 4d.

TOGGLE SWITCHES. SPDT, 2a. bake, 1/-; SPST 4 a., 1/-; DPST 3 a., 2/9.

Above items C.O.D. or C.W.O., plus postage.

34, BOND STREET, BRIGHTON.

TELECRAFT
AERIALS ENSURE THE
BEST TELEVISION
TRY ONE AND SEE FOR YOURSELF

MAGNETIC TAPE RECORDERS and COMPONENTS
from
WILL DAY, LIMITED
19 L'sle Street, London, W.C.2.
GERrard 7105 and 4476
SEND 1½d. STAMP FOR LIST — SENT BY RETURN

"SENSITIVE TRF RECEIVER"
(Amos & Johnstone, November Issue)

SMITH'S
OF
EDGWARE ROAD
The Component Specialists
can supply ALL the parts, as used by the designers, for this amazing receiver.
Total cost about £7.

Send for complete, priced, list of parts.

H. L. SMITH & CO. LTD.
287/9, EDGWARE ROAD, LONDON, W.2.
Tel. Paddington 5891. Hours 9 to 6 (Thursdays 1 o'clock)
Near Edgware Road Stations, Metropolitan and Bakerloo.

NUSOUND PRODUCTS

136 WARDOUR STREET, LONDON, W.1

(Oxford Street End)

Tel : GERrard 8845

NUSOUND FIDELITY-TEN. The latest super quality Amplifier. All Triode line up P-Pull PX4 output. Frequency response 20-25 kcs. + .6 d.b. and continuing up to 50 kcs. + 9 d.b. Sensitivity 120 mv for max 10 w output. Total harmonic distortion 1 per cent. at 1,000 c.p.s. at 6 watts. 20 d.b. neg. feedback. Independent Treble and Bass controls. Chassis size : 14 x 9 x 7½in. high. A.C. model only, **£36.**

A NEW FEEDER UNIT. This is our latest addition to our range, and employs a s.het c.c.t. with two I.F. stages and variable selectivity controls giving bandwidths of 7-10 and 14 kcs. The unit covers the medium-long and short wavebands and has a large illuminated dial. Price **17 gns.** inc.

RETAIL TRADE ENQ. ON ABOVE ITEMS. PLEASE SEND STAMP FOR LEAFLETS.

NUSOUND QUALITY AMPLIFIERS. 8½-WATT OUTPUT.—PP 6V6s—independent bass and treble boost and cut—switch for L.P. records—neg. feedback—provision for radio feeder unit—freq. response 25 to 20,000 c.p.s. + ½ d.b.—hum 80 d.b. down at 6.5 watts—feedback 14 d.b.—sensitivity .05 volt. Price only **£15/17/6.** Also available with remote control unit. Price **£17/10/-.**

NUSOUND REFLEX CABINETS.—For Wharfedale speakers—10in., **£9/9/-**; 12in., **£10/10/-.** Veneered polish finish mahogany, oak or walnut.

Please send stamp for list of all our products. Our other products inc. 4½ watt Amp.—A.C. Model **£11/10/-**; A.C./D.C. **£12**; T.R.F. Pre-set Feeder, 3 station, **£7/12/6**; 3 station Pre-set S/Het, **£8/10/-**; two-band variably tuned S/Het, **£11/5/-.**

Remote control pre-amp. Unit, inc. tone controls, **£5/7/6.**

GRAMOPHONE EQUIPMENT

Decca 33 or 78 r.p.m. motor, **£3/14/4**, inc. Connoisseur Plups. Stnd. L.weight, **£4/11/8.** Trans. 13/-. Super L.weight, one head, **£6/9/-.** LP Head **71/8.** Trans. 15/-. Fibre P/up **£4/3/2.** Trans. 25/-. Two-speed Stroboscope **3/11.** Garrard Heads : Standard **25/3.** Miniature **50/11.** HiFi **56/-.** Type A Adaptor **7/7.** Decca Mag. Heads **59/2.** Decca XMS P/up **£7** complete. Chancery Attachment **72/6.** Decca 3-speed motor **£7/3/4.** Connoisseur 2-speed motor **£22/18/8.** Chancery Xtal P/up (LP20 insert) **53/-.** Spare insert, LP **31/6.** Garrard AC6 motor, speed controlled, 12in. table **£6/15/10.** Collaro A.C. 514MB motor and P/up **£6/10/5.** Collaro A.C./D.C. motor, 12in table **£12/2/7.**

(We stock a full range of Wharfedale & Goodmans speakers and accessories.) TV and Gram. list 4d. (Please Add Postage.)

ENGINEERS!

Whatever your age or experience, you must read "**ENGINEERING OPPORTUNITIES.**" Full details of the easiest way to pass **A.M.I.Mech.E., A.M.I.C.E., C. & G. (Electrical, etc.) General Cert., etc.**, on "**NO PASS—NO FEE**" terms and details of Courses in all branches of Engineering — **Mechanical, Electrical, Civil, Auto., Aero., Radio, etc., Building, etc.** If you're earning less than £14 a week, tell us what interests you and write for your copy of "**ENGINEERING OPPORTUNITIES**" today—**FREE**

144 PAGES

Free!

B.I.E.T.

387 Shakespeare Inc. 17-19 Stratford Place, London, W.1

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

SITUATIONS VACANT

RADAR mechanics, ex-R.E.M.E. or others with experience of service radar.—Write details of experience to All-Power Transformers, Ltd., Chertsey Rd., Byfleet, Surrey. [7967

ELECTRONIC testers, for test and repair of special electronic equipments.—Write details of experience to All-Power Transformers, Ltd., Chertsey Rd., Byfleet, Surrey. [7968

TELEVISION and radio engineer required in Epsom, Ewell district, good wages and working conditions, able to drive; write full details of experience, etc., to—Box 5858. [7946

TECHNICAL Assistant required to study the performance of Geiger counter tubes and cathode ray tubes, etc. Applicants should be of Intermediate standard. The post is open to young people of either sex and offers good opportunities on the technical side of an expanding organisation in S.E. London. Staff pension scheme. Applicants should give age, experience and salary required.—Box 6625. [8105

TECHNICAL Grade II required by Ministry of Supply in London. Qualifications: British of British parentage; regular apprenticeship in light engineering, preferably in motion picture or allied industries; sound experience of modern workshop methods; Ordinary National Certificate or equivalent qualification. Knowledge of electronics as applied to sound engineering an advantage. Duties: Assist in planning and progressing the production and repair of motion picture and still projection equipment, spare parts and ancillary apparatus. Salary: £570 (linked to age 30)—£675 p.a. Rates for women slightly lower. Not established, opportunities for established pensionable posts may arise. Written applications giving date of birth and education, full details of qualifications and experience of posts held (including dates) should be addressed to Appointments Officer, Ministry of Labour and National Service, 1-6, Tavistock Square, W.C.1, quoting reference number K.1.10. In no circumstances should original testimonials be forwarded. Only candidates selected for interview will be advised. [8112

ENGINEER, technical grades II and III, required by Ministry of Supply establishment in Farnoorough, Hants; qualifications, British, of British parentage; recognised engineering apprenticeship or equivalent training, followed by few years' workshop and drawing office experience on radio or allied equipments, ability to interpret engineering drawings, specifications and circuit diagrams essential; possession of Ordinary National Certificate or equivalent qualification and/or knowledge of component standardisation and R.A.F. equipment servicing requirements is desirable; duties, one of the following: (i) Preparation of schedules of R.A.F. telecommunications' main equipments, involving breaking down to sub-assemblies and components for provisioning action; preparation of spares lists; (ii) Examine and report on contractors' drawings of R.A.F. telecommunications' equipment; preparation of drawing lists; (iii) Preparation of schedules of connectors for aircraft installations of R.A.F. telecommunications' equipments; salaries, Grade II £540 (linked to age 30) to £645 p.a., Grade III £457 (linked to age 26) to £545 p.a.; not established; opportunities for establishment may arise.—Written applications, giving date of birth and education, full details of qualifications and experience of posts held (including dates) should be addressed to Appointments Officer, Ministry of Labour and National Service, 1-6, Tavistock Square, W.C.1, quoting reference No. K.1.24. In no circumstances should original testimonials be forwarded. Only candidates selected for interview will be advised. [8152

SITUATIONS WANTED

SALES manager executive seeks position, Surrey area preferred.—Box 6607. [8054

EX-R. Sigs. Offr., 27, own 1952 Bedford van, some service exp., reqs. posn. in South, alt. small business with accom. considered.—Box 6622. [8084

SENIOR R.A.F. Officer, Assoc. I.E.E., many years pre-war business experience in radio industry, expecting release shortly, requires position where tact, initiative, organizing ability, and power to handle staff, would be advantageous.—Box 6691. [8158

ENGINEER (40), considerable previous experience radio, television field and depot service and production, trouble-shoot, war service on radar; employed since in technical advisory and administrative capacities; requires responsible post in South or West England with minimum salary £625.—Box 6687. [8150

AMBITIOUS electronic engineer (36) with wide executive experience in small businesses, ideas, and a capacity for hard work, wishes to join manufacturer where these qualifications would be of value, might suit owner-manager wishing to be relieved of some responsibility; London area preferred, but all propositions considered.—Box 6625. [8090

BUSINESSES FOR SALE AND WANTED

RADIO, television, electrical, sales and service, s.f. shop, l.u. large service room, batt. charging rooms, semi-main road, W. Middx., low rent, lease available, £570.—Box 6615. [8066

RETAIL radio, television and furniture business for sale, including double-fronted premises in main shopping centre of North Derbyshire town; the premises are centrally heated, in an excellent state of repair and contain well-equipped showrooms and workshop, auxiliary lighting plant, garage accommodation, main agencies, annual turnover £25,000 audited accounts available; principals only.—For full particulars write Box 6615. [8062

L·R·S

Est. 1925

FOR

PROMPT & EFFICIENT SERVICE

CASH or EASY TERMS

We have a limited stock of the following quality equipment available for cash or on our Revised Easy Terms.

ARMSTRONG ALL WAVE CHASSIS

(See Makers Advertisement page 99)

MODEL EXP. 73. Cash £25/12/4 or £8/11/- with order and 10 monthly instalments of 40/-.

MODEL RF. 104. Cash £34/12/10 or £12 with order and 12 monthly instalments of 40/-.

Passenger carriage 10/- extra payable with deposit.

LOUDSPEAKERS

GOODMANS AUDIUM 60. Cash £8/12/6 or £3/-/- with order and 6 monthly instalments of 20/-.

GOODMANS AXIOM 150. Cash £10/5/6 or £3/15/- with order and 7 monthly instalments of 20/-.

10in. W.B. CONCENTRIC-DUPLEX. Cash £7/15/- or £2/12/- with order and 6 monthly instalments of 20/-.

CONNOISSEUR

(See Makers Advertisement page 20)

SUPER L.W PICK-UPS. Complete with one Green Spot and one Red Spot interchangeable Heads for Standard and Microgroove recordings. **Cash £10/0/8** or £3/15/- with order and 7 monthly instalments of 20/-.

DUAL SPEED GRAMOPHONE MOTORS. 33⅓ and 78 r.p.m. Full 12in. turntable. Synchronous type motor, dynamically balanced—virtually vibration less. Cash price **£20/19/3** or £7/-/- with order and 8 monthly instalments of 40/-. Delivery from stock.

The L.R. SUPPLY CO. Ltd.

(LONDON RADIO SUPPLY CO)

BALCOMBE - - SUSSEX

Telephone : Balcombe 254

CRYSTALS

of OUTSTANDING QUALITY

TYPE "S"

Frequency range : 100 Kc/s to 15 Mc/s. Black bakelite case, 1⅛" high, 1⅛" wide, ⅝" thick, with two ¼" diameter pins spaced ⅝" apart.

BROOKES CRYSTALS LTD.

10 Stockwell St., Greenwich, London, S.E.10

Phone : GREenwich 1828. Cables : Xtals London. Grams : Xtals Green London

When it's

Tenawire

it's **TROUBLE FREE**

Science brings a new high standard wiring in Tenawire. A high quality wire with outside covering which will not harden, split or crack. Really flexible yet tough, Tenawire is absolutely resistant to corrosion. Let our technical representative call and show you this important and unrivalled development.

TENAPLAS
(SALES) LIMITED
Southern Sales & Export
24 Zb, Manchester Sq., London, W.1.
Tel.: Welbeck 7041.
Midland & Northern Sales Office:
181, Wollaton St., Nottingham.
Tel.: 45514.

BRASS, COPPER, DURAL, ALUMINIUM, BRONZE
ROD, BAR, SHEET, TUBE, STRIP, WIRE.
3,000 STANDARD STOCK SIZES
No Quantity too Small. List on application.
London: H. ROLLET & Co. Ltd. Liverp'l:
6, Chesham Place, S.W.1. Kirby Estate.
SLOane 3463 SIMONSWOOD 3271/3

EXCEL SOUND SERVICES LTD.
are pleased to announce that they are now accepting orders for their Tape Recorders.
Trade enquiries invited
40, BRADFORD ROAD, SHIPLEY, YORKS.
Telephone: Shipley 55779 & 51291

ELECTRONICS
DUPLEY
LTD.
CRANMER AV, EALING, W 13.
Transformer and Coil Manufacturers to the Trade
Telephone: EALing 2899

TRANSFORMERS
FOR ALL PURPOSES
SINGLY OR IN QUANTITIES
FROM OUR STANDARD RANGE
OR TO YOUR SPECIFICATIONS
GOOD DELIVERIES
REASONABLE PRICES
We have also a department for rewinds giving you a 24-hour service and a better job. Please label all burnt-outs with your name and address when despatching.
P. HOWORTH
51 POLLARD LANE · BRADFORD
Tel.: 37030

BUSINESSES FOR SALE AND WANTED

WELL-established wireless, television, electrical contracting business in Herts town; living accommodation over shop, also workshop; price including freehold, goodwill, £5,500.—A.B.V.—Box 6701. [8155

AGENCIES

STOCKHOLM wholesalers with first-class connection and selling organisation throughout Sweden require agencies for all kinds of radio and accessories.—ERIK GRANSTEDT & Co., Radmansgatan 56, Stockholm. [8083

PATENTS

THE proprietor of British Patent No. 575513, entitled "Multiple Section Electronic Tube and Method of Making it," offers same for license or otherwise to ensure practical working in Great Britain.—Inquiries to Singer, Stern & Carlberg, 14, East Jackson Boulevard, Chicago 4, Illinois, U.S.A. [7950

THE proprietor of British Patents Nos. 615624, entitled "Improvements in transmitter-receiver combination," and No. 613217, entitled "Improvements in Radio Transmitting Receiving System," offers same for license or otherwise to ensure their practical working in Great Britain.—Inquiries to Singer, Stern & Carlberg, Chrysler Building, New York 17, N.Y., U.S.A. [8011

PAINTS, CELLULOSE, ETC.

PAINT spraying handbook 5/6, post free; cellulose and synthetic paints and all spraying requisites supplied; catalogue free.—Leonard Brooks, 55, Harold Wood, Romford. [0207

TECHNICAL TRAINING

CITY & Guilds (Electrical, etc.) on "no pass —no fee" terms; over 95% successes; for full details of modern courses in all branches of electrical technology send for our 144-page handbook—free and post free.—B.I.E.T. (Dept. 586A), 17, Stratford Place, London, W.1. [0117

INDUSTRY needs trained men, send for free brochure giving details of our Home Study Courses in radio, television and all branches of electronics; we prepare students for the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the college backed by Britain's largest electronic industry.—Write to E.M.I. Institutes, Postal Division, Dept. WW55, 43, Grove Park Rd., London, W.4, Chiswick 4417 (Associated with H.M.V.). [0179

TUITION

UNIVERSITY COLLEGE, Southampton.

DEPARTMENT of Electronics.
THE Department of Electronics (Professor E. E. Zepler) gives an advanced course at Honours Degree standard in Electronics. The course is full-time for one academic year and the College grants a Diploma by examination to students who successfully complete the course. Entry qualification is a University degree in Physics or Electrical Engineering, or its equivalent. The sixth of these courses will commence in October, 1952, and application for admission should be made now to the Academic Registrar, from whom further details may be obtained. [8123

RADIO training.—P.M.G. exams and I.E.E. Diploma; prospectus free.—Technical College, Hull. [0111

WIRELESS operating; attendance and postal courses.—Stamp for reply to Manager, The Wireless School, Manor Gdns., London, N.7.

NOTHING succeeds like success! What we have done a thousand times we can do again, for you.—See the B.N.R.S. advt., page 104.

SEE the world, 600 Radio Officers required, send 2d stamp for prospectus to Britain's leading college; we train most in shortest period at lowest cost.—Wireless College, Colwyn Bay.

A.M.I.Mech.E., A.M.Brit.I.R.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes; for details of exams. and courses in all branches of engineering, building, etc., write for 144-page handbook—free.—B.I.E.T. (Dept. 587B), 17, Stratford Place, London, W.1. [0118

WIRELESS Telegraphy.—Merchant Navy offers to youth, 15½ upwards when qualified, lucrative positions as radio officers.—Apply British School of Telegraphy, Ltd., 179, Clapham Rd., London, S.W.9. Also postal courses in theory of wireless for P.M.G. Certificates and Amateur Transmitting Licence. [0124

THE Institute of Practical Radio Engineers have available home study courses in every phase of radio and television engineering, specialising in the practical training of apprentices in the retail trade; enrolments limited, fees moderate.—The Syllabus of Instructional Text may be obtained post free from the Secretary, I.P.R.E., Fairfield House, 20, Fairfield Rd., Crouch End, London, N.8. [0088

FREE! Brochure giving details of home study training in radio, television and all branches of electronics; courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations; train with the college operated by Britain's largest electronic organization; moderate fees.—Write to E.M.I. Institutes, Postal Division, Dept. WW28, 43, Grove Park Rd., London, W.4. Chiswick 4417. (Associated with H.M.V.). [0001

PERSONAL

OPPORTUNITY to invest with active directorship in established radio component manufacturing company; applicant must be practical with ability to design coils and electronic components.—Box 6668. [8132

TAMSA
TAPE & WIRE RECORDING
We supply ALL RECORDING COMPONENTS. Write for Latest Price List of :—
TAPE MECHANISMS, TAPES, WIRES and SPOOLS, HEADS, AMPLIFIERS, OSCILLATOR COILS and UNITS.
NOW AVAILABLE—HIGH COERCIVITY TYPE H60 EMITAPE.
TOPHET M, High Quality Recording Wire.
Constructors' Envelopes. Books on Tape Rec'd'g.
Manufactured by
AUDIGRAPH LTD.
Dept. MRJ, 74 Great Hampton Street, HOCKLEY, BIRMINGHAM, 18.

AUTOMATIC SWITCHES
(RECONDITIONED)
ELECTRIC 1 to 100 AMPS. **CLOCKWORK** 7 to 35 DAYS
From **35/-** EACH
All guaranteed for a year.
Write for illustrated lists:
DONOHOE'S (Timers), 6, GEORGE ST., NORTH SHIELDS, NORTHUMBERLAND.

BRADMATIC
HIGH CLASS
TAPE RECORDING EQUIPMENT
HEADS, DESKS, TAPE, ETC.
Send for lists
BRADMATIC LTD.
STATION ROAD, ASTON, BIRMINGHAM, 6
Telephone: East 0574

TANNOY
PRODUCTS
SOUND EQUIPMENT
clearly the best for all occasions

WEST NORWOOD S.E. 27 Tel. GIPsy Hill 1131 (7 lines)

The VOIGT Loudspeaker is still ahead of all others.
P.M. Unit with 23,000 line gap flux £40 ex. works.
Corner Horns (in the white) £19.10.0 or £47.10.0 ex works.
Demonstrations in Toronto, Canada, by arrangement with Mr. Voigt.
VOIGT PATENTS LTD.
Sydenham, S.E.26 SYD 6666
Sole makers of VOIGT Products

YOUR METER DAMAGED?

Leading Electrical Instrument Repairers to the Industry
Contractors to The Ministry of Supply.
Repairs by skilled craftsmen of all makes and types of Voltmeters, Ammeters, Microammeters, Multirange Testmeters, Electrical Thermometers, Recording Instruments, Synchronous Clocks, etc. Quick deliveries—for speedy estimate send defective instrument by registered post to:—
L. GLASER
Electrical Instrument Repairers
341 CITY ROAD, E.C.1
Tel. Terminus 2489

REOSOUND

DE LUXE INSTRUMENT CASE

12in. x 8in. x 5in. in 18G. Steel with Radiused Top Corners, Louvred Back and fitted with Chromium Plated Handle, and four P.V.C. feet. Finished in Black, Grey, or Brown Wrinkle Enamel. 18G. Steel front panel, **£1 6 3**
With front panel in 16G. Aluminium, **£1 7 6**
Small steel chassis with angle brackets to fit, Black **5 8**
Ditto, in 16G. Aluminium, self-colour ... **7 6**

Postage and Packing 2/-.
Carriage Paid on Orders over £5.
Illustrated Lists on request.
All List Prices now plus 25%.
Trade Terms on application.

REOSOUND ENGINEERING & ELECTRICAL COMPANY, "Reosound Works," Coleshill Road, Sutton Coldfield.
Grams: Reosound, Sutton Coldfield. Tel. SUT. 4685.

BOOKS, INSTRUCTIONS, ETC.

I.P.R.E. technical publications' 5,500 Alignment Peaks for Superheterodynes, 5/9, post free; data for constructing TV aerial strength meter, 7/6; sample copy "The Practical Radio Engineer," quarterly publication of the Institute, 2/-; membership and examination data, 1/-.—Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8. 17909

ELEMENTS OF RADIO, by A. & W. Marcus. Beginning with a simple crystal set the authors gradually introduce every improvement so that the final chapter deals with the most complicated modern radio, astonishingly easy to follow; ask your bookseller to get you a copy, 13/- (post free), or write to Allen & Unwin 40 Museum St., W.C.1. 17905

★

'Radiospares' Quality Parts

The Service Engineer's First Choice

★

"You can rely on us"

FOR CLEAN COMPONENTS AT COMPETITIVE PRICES

MIDGET I.F. TRANSFORMERS.
465 K.cs. Wearite M-900 1.3/16" square 1 13/16" high 10/6 each. Super midget, 13/16" square 1¾" high 10/6 each.
QUALITY OUTPUT P.P. FULL TRANSFORMERS.
MR 7, 10 watts, 12 ratios, fitted with Terminal Panel, 18/9.
MR 15, 18 watts, 11 ratios, secondary 1 to 30 ohms, primary 2,000 to 16,000 ohms. **41/6.**
MR 30, 30 watts, 11 ratios. Max. Current 170 m/s., Primary and Sec., as MR 15. **49/6.**
PA50L, 15 watts, 6L6 Class A, 4 ratio. Primary 5,000. **42/-.**
PA24L, 10 watts PX4, 4 ratio. **33/-.**
All new Unbalanced. NOT surplus.
EXPERIMENTAL TRANSFORMERS.
Standard Primary 200/250 v., Secondary 3 v. to 30 v. at 2 a. **24/-.**
COILS.
Wearite "P" Coils all ranges, **3/-** each. Weymouth "H" coils **3/6**. "K" coils **4/9**. T.R.F. pair with reaction, MW/LW **7/6**.
COILPACKS MW/LW/SW.
Bargain offer. Superhet pack for 465 K.cs I.F., **25/-** each.
LOUDSPEAKERS.
WB 24" **17/3**. Plessey 5" T.V. Type **14/9**. 6" TV Type, **15/-**.
HIGH VOLTAGE CONDENSERS.
T.C.C. .001 mfd. 8 Kv. **4/6**, .002 mfd. 12.5 Kv. **7/6**, .01 mfd. 5 Kv. **4/6**, 1 mfd. 5 kv. **13/6**. All new stock.
MISCELLANEOUS.
Full range of Morganite Type "I" Miniature resistors, max. rating ½ watt 6d. each. 3-piece polished aluminium Int. Octal Valve cans **1/6**. Miniature Vol. Controls, with s. w. **5/-**, less **3/6**. Aladdin Formers and Cores ¾" **10d.**, ½" **7d.** New High Resistance Lightweight Headphones **12/6** pair. Rotary toggles, SP ST **2/6**, DP ST **4/3**. B.Lee Co-Ax. Plugs **1/6**. Sockets **1/6**.

Stockists of :—
HAYNES, WEARITE, WEYMOUTH, VIEW-MASTER, B.V.A. Valves, ELSTONE Products.
Our 32-page Catalogue No. 10 **6d.**

RADIO SERVICING Co.
444 Wandsworth Road, London, S.W.8
Phone: MACaulay 4155.
77, 77A Bus. 28 Tram. Wandsworth Rd. S.R. Station.
Open till 6.30 p.m.

YOU READ MUSIC?

Then how about making yourself an electronic organ? Constructional data available—full circuits, drawings and notes. It has 5 octaves, 2 manuals and pedals with 24 stops—uses 43 valves. With its variable attack you can play Classics and Swing.

Write now for free booklet to : **C. S. Co., 10 Duke Street, Darlington, Durham.**

A REMARKABLE ACHIEVEMENT IN FILTER DESIGN

Pat. Applied For

E.M.G. STEEP-CUTTING INFINITELY VARIABLE FILTER

- Cuts at any selected frequency between 4,000 and 5,000 c.p.s.
- Average steepness of cut 30 db. per octave.
- Connects between secondary of output transformer and speaker (15 ohms, rated impedance).
- Specially valuable for use with new microgroove records.
- Greatly reduces needle-hiss on ordinary records with minimum high note loss and suppresses high pitched interferences on radio.
- No distortion, and no appreciable loss of volume.
- Leaflet available from the manufacturers.
- *Send circuit, patents pending.*

£4 - 10 - 0

Trade Enquiries Invited

E.M.G. HANDMADE GRAMOPHONES LTD
Newman St., Oxford St., W.1
Telephone: Museum 9971-2-3

Easco **RECTOSTAT**

HOME BATTERY CHARGERS
1-6 Amp., 2-6-12 Volt. A.C. Mains

EASCO ELECTRICAL LTD.
6/8 BRIGHTON TERRACE, LONDON, S.W.9
Telephone: BRIxton 4961-2-3

HIGH QUALITY CABINETS

Radiogram Cabinets from	£13.10.0
T.V. Console (Suit Viewmaster, etc.)	£11.10.0
10" Reflex (Suit Wharfedale, etc.)	£7.10.0
12" " " "	£8.5.0
12" Corner Reflex, from ... ... "	£12.10.0

Special designs quoted for

THE CHAFFEY CABINET CO.
50A, CHELTENHAM ROAD, LONDON, S.E. 15
Telephone: Orpington 3559

RADIO G200 OFFERS

Govt. Surplus Components, Transmitting, Obsolete Receiving, Special Purpose and Industrial Type Valves. NGT1, IB24, HK304H, 35T, HK24G, FG27A, 878a, 725a, 2V36, WL2J32 magnetron, CV2, etc., available from stock.

EXPORT—IMPORT Enquiries invited.

ARTHUR HOILE 50 UNION STREET, MAIDSTONE, KENT
Telephone 2812

R. C. S.

Send stamp for new Catalogue giving range of "proprietary makers' components" including

Coils, air spaced, all ranges. Coils, dust cored, all ranges. Coil Packs, I.F.'s, T.R.F. Coils, Chokes, Transformers, Speakers, Condensers, Resistors, Chassis, Dials etc. to

RADIO COMPONENT SERVICE,
68 Chesterfield Road, Leyton, E.10.

Dits and Dahs!!

THIS IS THE LANGUAGE OF THE AIR THAT EVERY RADIO AMATEUR, PILOT, SHIP'S OPERATOR, ETC., MUST BE ABLE TO READ AND SEND. IT IS EASILY AND QUICKLY LEARNED BY THOSE WHO TAKE UP A

CANDLER CODE COURSE

THE CANDLER SYSTEM not only teaches you the **right way** to *send* but the **right way** to *read* code sound just as easily as you read print by sight.

The Special Course covers all the Code training necessary to pass the G.P.O. test for an **Amateur Transmitting Licence.**

The Junior Course is a complete Code Course for the **Beginner** who desires to secure the G.P.O. Certificate in which he is interested.

The Advanced Course is for those with a consistent sending and receiving speed of not less than 15 w.p.m.

Touch-Typing Course. A series of interesting and easily followed lessons which enable one to record messages at high speeds.

Courses supplied on Cash or Monthly Payment terms.

You are invited to send for a copy of the CANDLER "BOOK OF FACTS," it gives full details of the above training.

THE CANDLER SYSTEM CO.,
(55W) 52b, ABINGDON RD., LONDON, W.8
Candler System Company, Denver, Colorado, U.S.A.

INDEX TO ADVERTISERS

	PAGE
A.A. Tools	110
Acoustical Mfg. Co., Ltd.	57
Acru Electric Tool Mfg. Co., Ltd., The	116
Adcola Products, Ltd.	111
Aerialite, Ltd.	22
Allan, Richard, Radio, Ltd.	12
Allen Components, Ltd.	105
Alpha Radio Supply Co., The	107
Altham Radio Co.	92
Ambassador Radio	46
Amplex Appliances (Kent), Ltd.	56
Amplivox, Ltd.	60
Ander's Radio, Ltd.	92
Antiference, Ltd.	49
Armstrong Wireless & Television Co., Ltd.	99
Ashdown, H.	58
Ashworth, H.	12
Audigraph, Ltd.	114
Audix, B. B., Ltd.	76
Automatic Coil Winder & Electrical Equipt. Co., Ltd., The	1
Automatic Telephone & Electric Co., Ltd.	53
A.W.F. Radio Products	92
B. & H. Radio	96
Bakers "Selhurst" Radio	18
Barker Natural Reproducers	101
Belling & Lee, Ltd.	69
Bel Sound Products Co.	110
Bennett College, Ltd., The	88
Berry's (Short Wave), Ltd.	52
Birmingham Sound Reproducers, Ltd.	64
Bradmatic, Ltd.	114
Brierley, J. H. (Gramophone & Recordings, Ltd.	42
Britain, Chas. (Radio), Ltd.	95
British Communications Corpn., Ltd.	28
British Institute of Engineering Technology	106, 115
British National Radio School	104
British Physical Laboratories	58, 47
British Sarosal, Ltd.	96
Broadcaster Radio Supplies, Ltd.	57
Brookes, Crystals, Ltd.	115
Brown, S. G., Ltd.	52
Buchan, A. E.	104
Bulgin, A. F., & Co., Ltd.	56, Edit. 125
Bull, J. & Sons	101
Bullers, Ltd.	51
Candler System Co.	115
Chaffey Cabinet Co., The	115
Champion Products	96
Chapman, C. T. (Reproducers), Ltd.	112
Cinema-Television, Ltd.	21
City Sale & Exchange, Ltd.	50
Classic Electrical Co., Ltd.	105
Clydesdale Supply Co., Ltd.	91
Cohen, D.	93
Cook's, Chas., Furnishing Stores, Ltd.	62
Cosmocords, Ltd.	66
Cossor, A. C., Ltd.	75
Coulphone Radio	112
Coventry Radio	96
C.S. Company	115
Davis, Alec, Supplies, Ltd.	50, 105
Davis, Jack (Relays), Ltd.	54
Day, W., Ltd.	112
Dewitt, V. L., Ltd.	96
Donohoe's (Tuners)	114
Drayton Regulator & Instrument Co., Ltd.	28
Dubilier Condenser Co. (1925), Ltd.	9
Duke & Co.	102
Dupley Electronics, Ltd.	114
Easco Electrical, Ltd.	115
Edison Swan Electric Co., Ltd.	19
Electradix Radios	100
Electro Acoustic Industries, Ltd.	62
Electro Acoustic Developments	106
Electro Technical Assemblies	14
Electronic Instruments, Ltd.	56
Electronic Precision Equipment	78, 79, 80, 81
Electronic Service (Hallamshire), Ltd.	65
Elm Electric Co.	58
E.M.G. Handmade Gramophones, Ltd.	115
E.M.I. Institutes	20, 54, 76
Erie Resistor, Ltd.	Cover ii
Eta Tool Co. (Leicester), Ltd.	48
Excel Sound Services, Ltd.	114
Factice & Chemical Supplies, Ltd.	62
Farmer, John	99
Fluxite, Ltd.	106
Foyle, W. & G., Ltd.	56
Frith Radiocraft, Ltd.	26, 109
Furzehill Laboratories, Ltd.	56
Galpins	105
Garland Bros.	62
General Electric Co., Ltd.	8
General Lamination Products, Ltd.	111
Glaser, L.	114
Goodmans Industries, Ltd.	4, 5
Goodsell, Ltd.	53
Grampian Reproducers, Ltd.	28
Gray, Arthur, Ltd.	54
Hallam, Sleigh & Cheston, Ltd.	16
Hall Electric, Ltd.	59
Hanney, L. F.	24
Hartley, H. A., & Co., Ltd.	98
Haves Co., The	110
Haynes Radio, Ltd.	110
Heney's, W. T., Telegraph Works Co., Ltd.	104
Henry's	50
Hivac, Ltd.	49
Hifi, Ltd.	96
Hoile, Arthur	115
Holley's Radio Stores	109
Homelab Instruments	54
Howorth, P.	114
H.P. Radio Services, Ltd.	88
Hyde, J. B., & Co., Ltd.	20
Industrial Electronics	44
International Correspondence School, Ltd.	24
Jackson Bros. (London), Ltd.	26
Ladd, J. C., Wholesale	110
Lasky's Radio	83, 84, 85
Leak, H. J., & Co., Ltd.	77
Lewis Radio Co.	108
Lockwood & Co.	106
London Central Radio Stores	45
Lowther Mfg. Co.	48
L.R. Supply Company, Ltd.	115
Lyons Radio	94
Mail Order Supply Co.	6, 7
Marconi Instruments, Ltd.	25
Marconi's Wireless Telegraph Co., Ltd.	72, 73
Masteradio, Ltd.	44
Mayco Electric	94
McElroy-Adams Mfg. Group, Ltd.	50
McMurdo Instrument Co., The	47
Measuring Instruments (Pullin), Ltd.	52
Metro Pex, Ltd.	26
Metropolitan-Vickers Electrical Co., Ltd.	15
Minnesota Mining & Mfg. Co., Ltd.	29
Modern Book Co.	100
Modern Electrics, Ltd.	40
M.R. Supplies, Ltd.	46
Mullard, Ltd.	3, 46, 55, 66
Multicore Solders, Ltd.	Cover iv
Neo Electrical Industries, Ltd.	108
Newman, J. & S., Ltd.	56
Northall, L. C.	110
Northern Radio Services	107
N.S.F., Ltd.	41
Nusound Products	113
Nu-Swift, Ltd.	96
Oddie Bradbury & Cull, Ltd.	110
Olympic Radio Components	94
Osmor Radio Products, Ltd.	18
Painton & Co., Ltd.	35
Pamphonic Reproducers, Ltd.	62
Panrex	60
Park Radio, Ltd.	56
Parmeko, Ltd.	53
Partridge Transformers, Ltd.	97
P.C.A. Radio	94
Pearce, T. W.	100
Phildelity Magnetic Products, Ltd.	30
Pitman, Sir Isaac, & Sons, Ltd.	102
Post Office Supplies	38, 112
Pratts Radio	58
Premier Radio Co.	15, 16, 17
Price, Norman (Publishers), Ltd.	22
Quality Mart	104
Quartz Crystal Co., Ltd.	110
Radio & Electrical Mart, The	99
Radio Component Service	115
Radio Exchange Co.	94
Radiomenders, Ltd.	60
Radio Merchandise Co., Ltd.	103
Radio servicing Co.	115
Radiospares, Ltd.	115
Radio Supply Co.	50
Radio Traders, Ltd.	54
Ranson, H.	113
Redifon, Ltd.	59
Reliance Mfg. Co. (Southwark), Ltd.	108
Reosound Engineering & Electrical Co.	115
Reproducers & Amplifiers, Ltd.	14
Robinson, F. C. & Partners, Ltd.	18
Roding Laboratories	52
Rogers Developments Co.	44
Rola Celestion, Ltd.	24
Rolet, H. & Co., Ltd.	114
Rose, A.	22
Royal Air Force, The	27
Rudman, Darlington & Co., Ltd.	53
Runbaken Electrical Products	112
Salford Electrical Instruments, Ltd.	11
Sallis, A. T.	106
Salway Morgan Co., Ltd.	48
Samsons Surplus Stores	106
Sangamo Weston, Ltd.	76
Savage Transformers, Ltd.	98
Savage, W. Bryan, Ltd.	52
Scharf, Erwin	12
Sifam Electrical Instrument Co., Ltd.	40
Simon Sound Service	55
Smith, G. W. (Radio), Ltd.	109
Smith, H. L., & Co., Ltd.	112
Sound Sales, Ltd.	74
Southern Radio Supply, Ltd.	100
Spencer West	54
Stability Radio Components, Ltd.	59
Standard Telephones & Cables, Ltd.	67, 70
Steatite & Porcelain Products, Ltd.	31
Stern Radio, Ltd.	86, 87
Sugden, A. R., & Co. (Engineers), Ltd.	20
Supacoils	111
Szymanski, S.	10
Tannoy Rentals, Ltd.	114
Taylor Electrical Instruments, Ltd.	2
Taylor, Tunnicliff & Co., Ltd.	23
Telecraft, Ltd.	50, 112
Telegraph Condenser Co., Ltd.	Cover iii
Telegraph Construction & Maintenance Co., Ltd., The	43
Telekit Supply Co.	96
Telemechanics, Ltd.	10
Teleonics (Communications), Ltd.	58
Tele-Radio (1943), Ltd.	52
Tenaplas (Sales), Ltd.	114
Thermionic Products, Ltd.	42
Transradio, Ltd.	40
Trix Electrical Co., Ltd.	Edit. 123
Ultra Electric, Ltd.	61
United Insulator Co., Ltd.	61
Universal Electrical Instruments Corpn.	95
Universal Electronics	90
University Radio, Ltd.	89
Valradio, Ltd.	14
V.E.S. Wholesale Services, Ltd.	88, 92
Vitavox, Ltd.	57
Voigt Patents, Ltd.	114
Vortexion, Ltd.	71
Walton's Wireless Stores	92
W.A.S.P. Engineering Co., Ltd.	111
Westinghouse Brake & Signal Co., Ltd.	63
Weymouth Radio Mfg. Co., Ltd., The	10
Wharfedale Wireless Works	42
Wilco Electronics	108
Wilkinson, Ltd.	94
Woden Transformer Co., Ltd.	54
Wright & Weaire, Ltd.	74
Young, C. H.	96

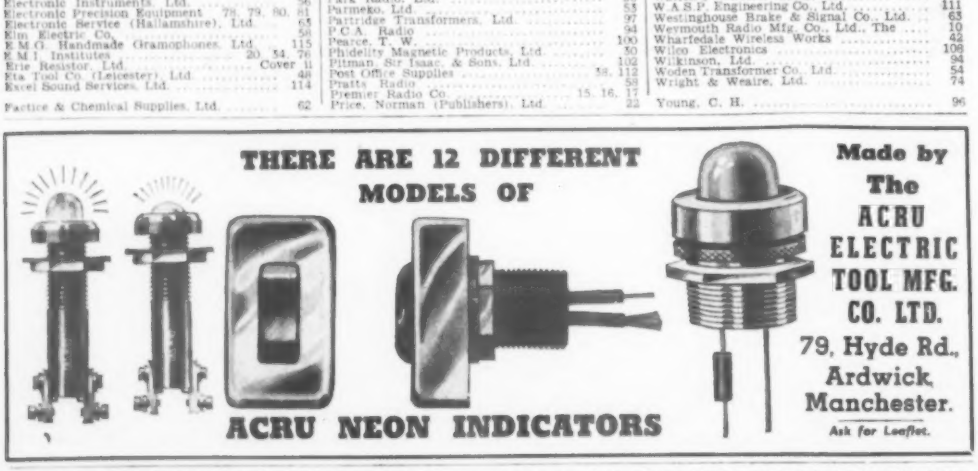

Printed in Great Britain for the Publishers, ILIFFE & SONS LTD., Dorset House, Stamford St., London, S.E.1, by CORNWALL PRESS LTD., Paris Garden, London, S.E.1. *Wireless World* can be obtained abroad from the following: AUSTRALIA AND NEW ZEALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service Ltd.; Gordon & Gotch, Ltd. SOUTH AFRICA: Central News Agency, Ltd., William Dawson & Sons (S.A.), Ltd. UNITED STATES: The International News Co.

LEADERSHIP from the inside

Quest and Test—symbols of Condenser Perfection

MANUFACTURING IN MILLIONS demands scientific planning, layout and lighting to ensure an uninterrupted flow of production. It demands more than this—skilled fingers, special machinery and rigorous checking at all stages. All these requirements are found at T.C.C.—the largest organisation in Europe solely devoted to condenser manufacture.

The illustration shows one of the multi-reel paper dielectric winding machines designed to simplify the winding of many ranges of condensers.

TCC

SPECIALISTS IN CONDENSERS SINCE 1906

THE TELEGRAPH CONDENSER CO. LTD · *RADIO DIVISION* · LONDON · W.3 · Tel: ACORN 0061 (9 lines

THESE *QUALITY* FEATURES

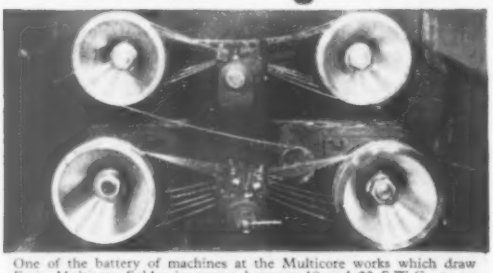

One of the battery of machines at the Multicore works which draw Ersin Multicore Solder in gauges between 10 and 22 S.W.G., to an accuracy of .002 in. By selecting the finest suitable gauge, the maximum economy of materials is obtained.

QUALITY MANUFACTURE

Only the purest tin and lead, alloyed in guaranteed proportions, are used in making Ersin Multicore Solder. Particular care is taken to ensure that the liquids used in the drawing machines, which reduce the solder to the required diameter, do not contaminate the wire. The solder wire is drawn to the correct gauges within very fine limits, so that every length produced has the same unvarying characteristics.

MAKE ERSIN MULTICORE

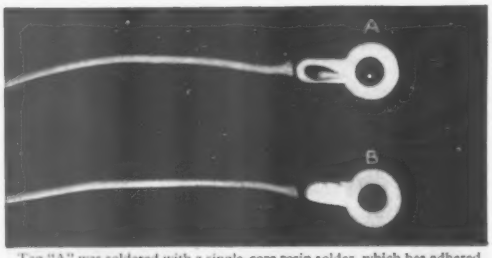

Tag "A" was soldered with a single-core rosin solder, which has adhered only to the copper wire. This is a typical "dry" joint. Tag "B" was soldered with Ersin Multicore, which has spread evenly over the wire and tag, making a sound electrical joint.

QUALITY FLUX

Ersin Multicore is the only solder containing three cores of Ersin Flux. Ersin is a high-grade rosin which has been subjected to a complex chemical process to increase its fluxing action, without impairing the well known non-corrosive properties of the original rosin. Ersin not only prevents oxidation during soldering, but actually cleans any oxides from the surface of the metal.

The Finest Cored Solder in the World

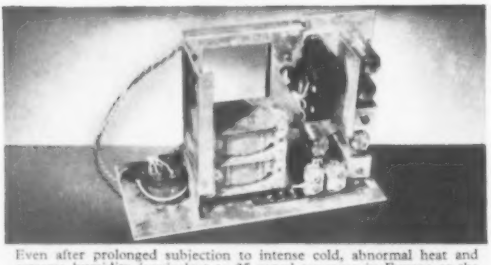

Even after prolonged subjection to intense cold, abnormal heat and extreme humidity (equivalent to 25 years' exposure in Europe or the U.S.A.), the Ersin Multicore soldered joints of this radio set were found to be absolutely sound.

QUALITY PERFORMANCE

The three-core construction of Ersin Multicore means thinner solder walls, instant melting and speedier soldering, without waste. The guaranteed continuity of the flux stream eliminates all risk of "dry" or H.R. joints. Tested under climatic conditions, soldered joints made with Ersin Multicore remained perfect electrical connections, completely free from corrosion or fungus growth.

7 lb. reel for factory use. Size 1 Carton for Service Engineers

SIZE 1 CARTONS 5/- RETAIL

Catalogue Ref. No.	Alloy Tin/Lead	S.W.G.	Approx. Length per carton
C 16014	60/40	14	13 feet
C 16018	60/40	18	37 feet
C 14013	40/60	13	13 feet
C 14016	40/60	16	26 feet

MULTICORE SOLDERS LTD., MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1 REGent 1411